
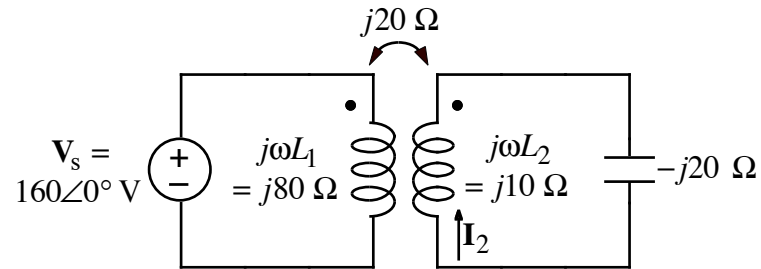


Ex:

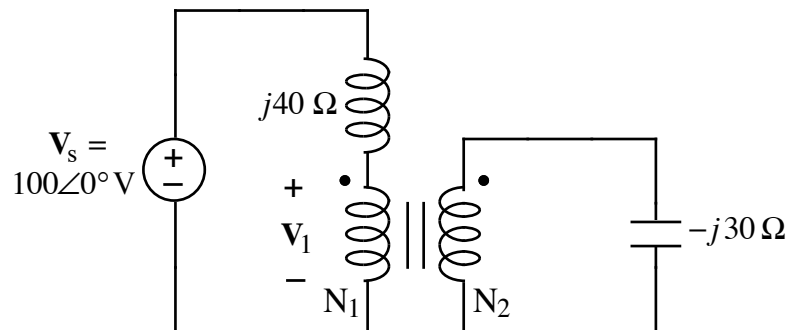

- a) Calculate the numerical value of phasor current, I_2 , flowing upward in the right coil of the transformer in the above circuit. Note: the transformer is linear.




- b) Given $V_1 = 150\angle 0^\circ \text{ V}$ find the turns ratio, N_1/N_2 , for the transformer in the above circuit. Note: the transformer is ideal.

sol'n: a) We first use reflected impedance to find I_1 (current in primary). Then we use the transformer eq'n's to find I_2 .

$$\text{Reflected } z: \quad z_r = \frac{(\omega M)^2}{z_{\text{sec tot}}} = \frac{20^2 \Omega^2}{j10 - j20 \Omega}$$

$$z_r = \frac{400}{-j10} = j40 \Omega$$

Model of primary:

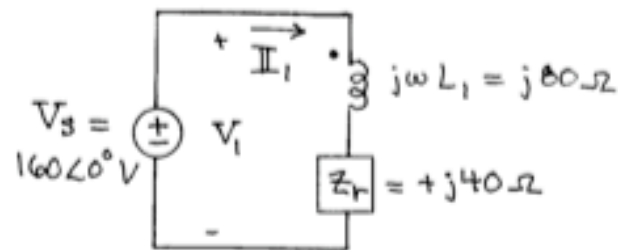

$$I_1 = \frac{V_s}{j\omega L_1 + z_r} = \frac{160 \angle 0^\circ \text{ V}}{j80 + j40 \Omega}$$

or

$$I_1 = -j \frac{4}{3} \text{ A} \quad \text{or} \quad \frac{4}{3} \angle -90^\circ \text{ A}$$

Transformer eq'n's:

$$V_1 = (R_1 + j\omega L_1)I_1 - j\omega M I_2$$

$$V_2 = +j\omega M I_1 - (R_2 + j\omega L_2)I_2$$

where $R_1 = 0 \Omega$, $R_2 = 0 \Omega$.

We observe that $V_1 = V_s$, and we can use the first transformer eq'n to find I_2 .

$$V_s = j\omega L_1 I_1 - j\omega M I_2$$

or

$$I_2 = \frac{j\omega L_1 I_1 - V_s}{j\omega M}$$

or

$$I_2 = \frac{j80\Omega \left(-j\frac{4}{3}\right) A - 160\angle 0^\circ V}{j20\Omega}$$

or


$$I_2 = \frac{\frac{320}{3} - \frac{480}{3} V}{j20\Omega}$$

or

$$I_2 = -\frac{160}{j60} A = j\frac{8}{3} A$$

b) We replace the transformer with the reflected impedance $z_r = \left(\frac{N_1}{N_2}\right)^2 z_L$

where $z_L = -j30\Omega$:

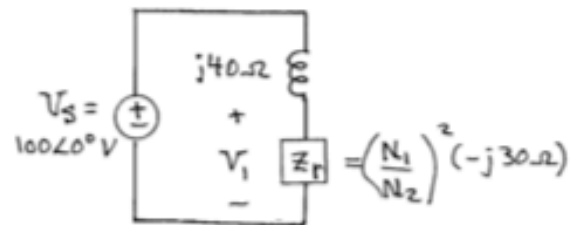

Using a voltage-divider, we have

$$V_1 = V_s \frac{z_r}{j40\Omega + z_r}$$

or

$$V_1 (j40\Omega + z_r) = V_s z_r$$

or

$$V_1 (j40\Omega) = (V_s - V_1) z_r$$

or

$$z_r = \frac{V_1 (j40\Omega)}{V_s - V_1} = \frac{150 (j40\Omega)}{100 - 150} = -j120\Omega$$

But $z_r = \left(\frac{N_1}{N_2}\right)^2 (-j30\Omega)$, so $\left(\frac{N_1}{N_2}\right)^2 = 4$, $\frac{N_1}{N_2} = 2$.