
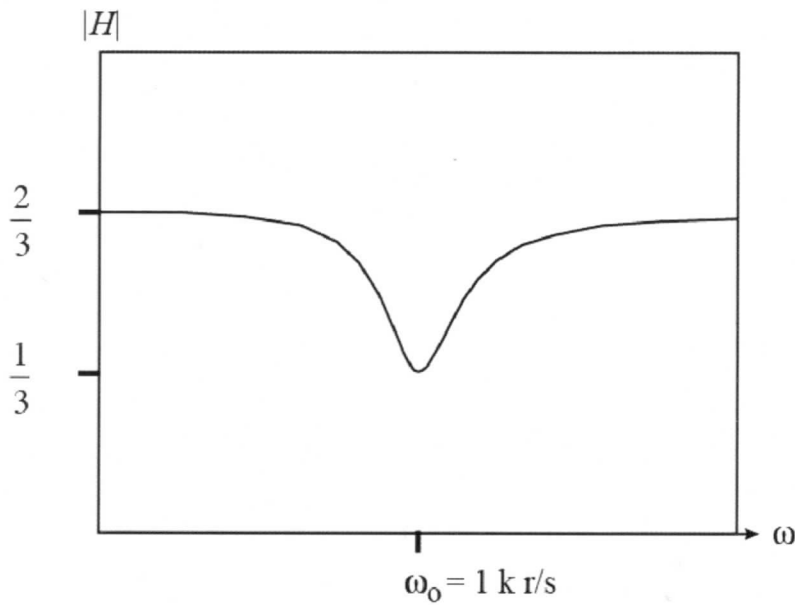


Ex:

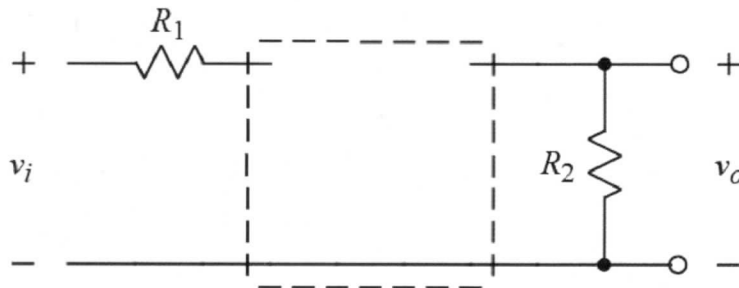

Given the resistors connected as shown with the following values,

$$R_1 = 1 \text{ k}\Omega$$


$$R_2 = 2 \text{ k}\Omega$$

and using not more than one each R , L , and C in the dashed-line box, design a circuit to go in the dashed-line box that will produce the **band-reject** $|H(j\omega)|$ vs. ω shown above. That is:


$$\min_{\omega} |H(j\omega)| = \frac{1}{3} \text{ and occurs at } \omega_0 = 1 \text{ k r/s}$$

$$|H(j\omega)| = \frac{2}{3} \text{ at } \omega = 0 \quad \text{and} \quad \lim_{\omega \rightarrow \infty} |H(j\omega)| = \frac{2}{3}$$

sol'n: To create the dip in $|H|$ at $\omega_0 = 1/kr/s$, we may use one of two methods: a vertical LC that shorts out at ω_0 , or a horizontal LC that becomes an open circuit at ω_0 . The vertical LC would be in series. The horizontal LC would be in parallel.

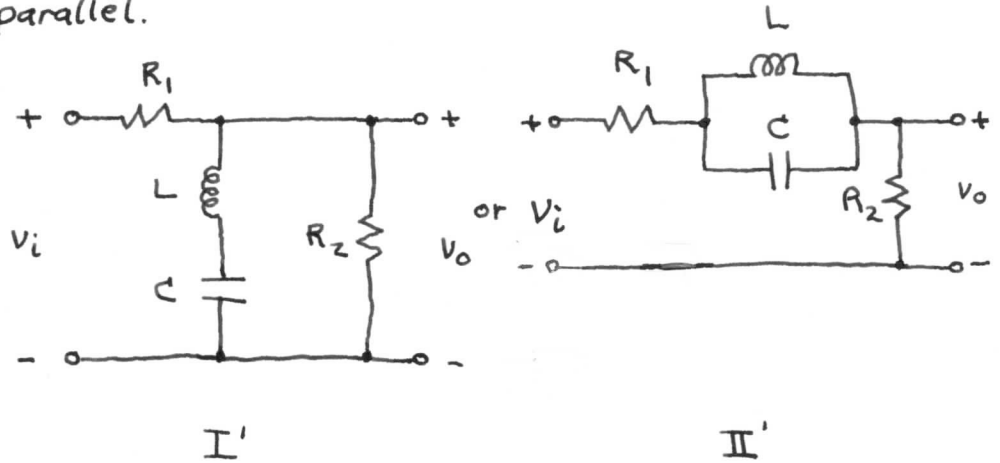


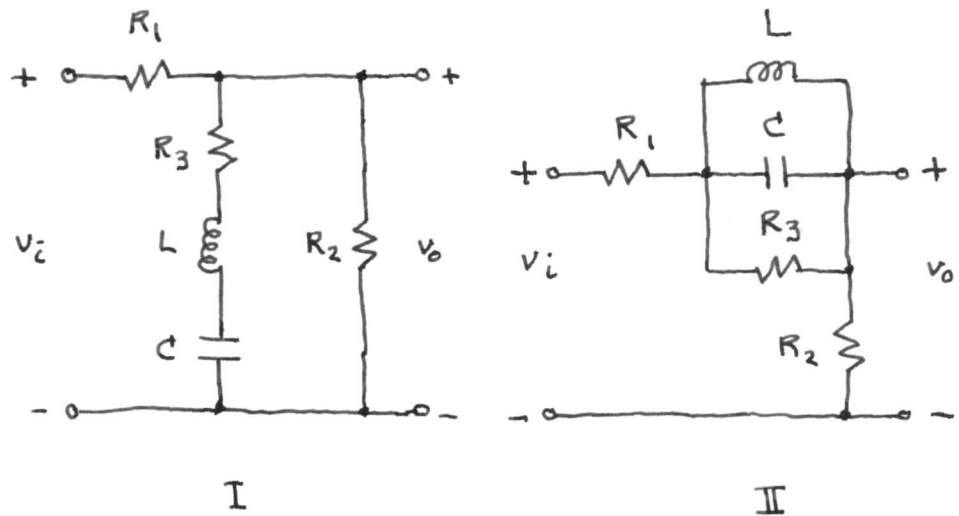Circuit I' would yield a gain of zero at ω_0 , so we need to add an R in series with L and C. Circuit II' would also yield a gain of zero at ω_0 , so we need to add an R in parallel with L and C. Thus, we have the two possible circuits shown below.




We now consider the behavior of each circuit at $\omega = 0$, $\omega = \omega_0$, and $\omega \rightarrow \infty$.

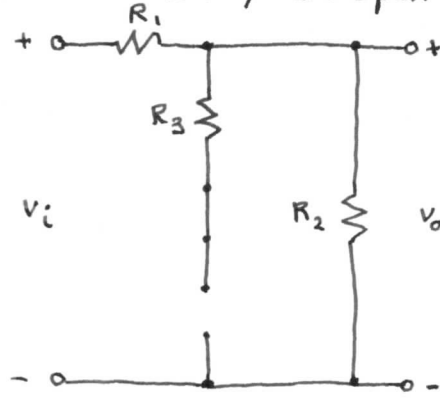$\omega = 0$: $L = \text{wire}$, $C = \text{open}$



I

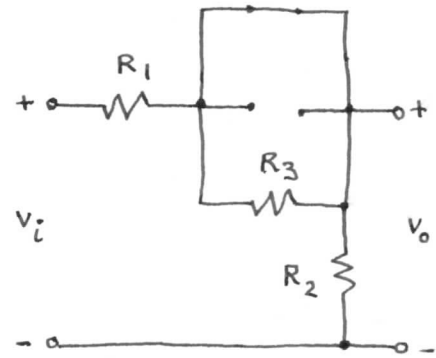


II


$$H(j0) = \frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2} = \frac{2k\Omega}{1k\Omega + 2k\Omega} = \frac{2}{3} \text{ for both circuits}$$

Note: R_3 is bypassed by L in circuit II.

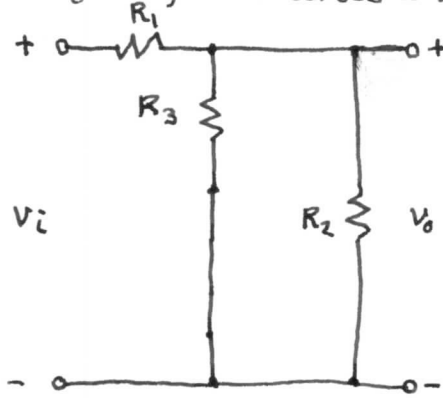$\omega = \omega_0$: L, C in series = wire, L, C in parallel = open



I

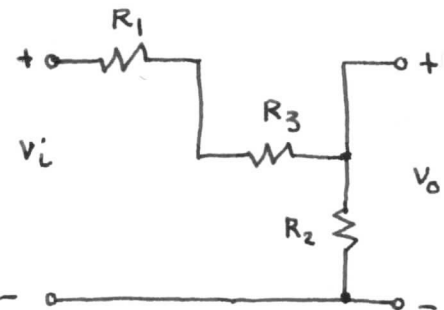

II

$$\text{I: } H(j\omega_0) = \frac{V_o}{V_i} = \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} \quad \text{II: } H(j\omega_0) = \frac{V_o}{V_i} = \frac{R_2}{R_1 + R_2 + R_3}$$

We want $|H(j\omega_0)| = \frac{1}{3}$ @ $\omega = \omega_0$.

$$\text{I: } \frac{R_2 \parallel R_3}{R_1 + R_2 \parallel R_3} = \frac{1}{3}$$

$$\text{II: } \frac{R_2}{R_1 + R_2 + R_3} = \frac{1}{3}$$

$$3(R_2 \parallel R_3) = R_1 + R_2 \parallel R_3$$

$$3R_2 = R_1 + R_2 + R_3$$

$$R_2 \parallel R_3 = \frac{R_1}{2} = \frac{1k\Omega}{2} = \frac{1}{2}k\Omega$$

$$R_3 = 2R_2 - R_1 = 3k\Omega$$

$\begin{matrix} 2k\Omega & 1k\Omega \end{matrix}$

An interesting way to calculate R_3 is to use the formula for parallel resistance in terms of conductance, $(1/R)$.

$$\frac{1}{\frac{1}{R_2} + \frac{1}{R_3}} = \frac{1 \text{ k}\Omega}{2}$$

or

$$\frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{\frac{1}{2} \text{ k}\Omega}$$

or

$$\frac{1}{R_3} = \frac{1}{\frac{1}{2} \text{ k}\Omega} - \frac{1}{R_2}$$

or

$$R_3 = \frac{1}{\frac{1}{\frac{1}{2} \text{ k}\Omega} + \frac{1}{-R_2}}$$

or

$$R_3 = \frac{1}{2} \text{ k}\Omega \parallel (-R_2) = \frac{1}{2} \text{ k}\Omega \parallel -2 \text{ k}\Omega$$

$$= 1 \text{ k}\Omega \cdot \frac{1}{2} \parallel -2$$

$$= 1 \text{ k}\Omega \cdot \frac{\frac{1}{2}(-2)}{\frac{1}{2} - 2}$$

$$= 1 \text{ k}\Omega \cdot \frac{-1}{-\frac{3}{2}}$$

$$R_3 = 1 \text{ k}\Omega \cdot \frac{2}{3} \approx 667 \Omega$$

For L and C , we have $\omega_0 = \frac{1}{\sqrt{LC}} = 1 \text{ kr/s}$.

Thus, $LC = \frac{1}{\omega_0^2} = \frac{1}{(1 \text{ kr/s})^2} = 1 \mu (\text{r/s})^2$.

Any $LC = 1 \mu$ will work.

For example $L = 10 \text{ mH}$ and $C = 100 \mu\text{F}$ is one practical solution.