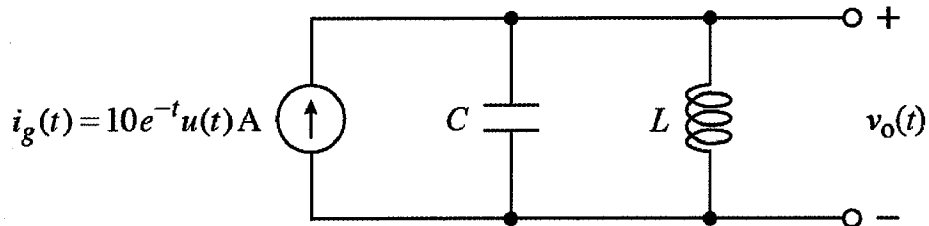


Ex:



Note: The initial conditions for C and L are zero.


$$C = 1 \text{ F}$$

$$L = 250 \text{ mH}$$

- Write the Laplace transform $I_g(s)$ of $i_g(t)$.
- Write the Laplace transform $V_o(s)$ of $v_o(t)$. Write your answer as a ratio of polynomials in s with numerical coefficients.
- Write a numerical time-domain expression for $v_o(t)$ where $t \geq 0$.

SOL'N: a) $\mathcal{L}\{i_g(t)\} = \mathcal{L}\{10e^{-t}u(t)\} \text{ A}$
 $\mathcal{L}\{i_g(t)\} = \frac{10}{s+1} \text{ A}$

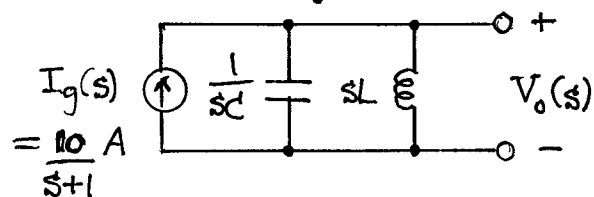- b) Since initial conditions are zero, we may proceed directly to the s -domain circuit diagram.



$$V_o(s) = I_g(s) \cdot \frac{1}{sC} \parallel sL$$

$$V_o(s) = \frac{10 \text{ A}}{s+1} \cdot \frac{1}{sC} \parallel sL$$

$$V_o(s) = \frac{10 \text{ A}}{s+1} \cdot \frac{L/C}{sL + 1/sC}$$

$$\begin{aligned}
 V_o(s) &= \frac{10}{s+1} \cdot \frac{250m/1}{s(250m) + \frac{1}{s}} \cdot \frac{s}{s} \\
 &= \frac{10}{s+1} \cdot \frac{s/4}{s^2/4 + 1} \cdot \frac{4}{4}
 \end{aligned}$$

$$V_o(s) = \frac{10s}{(s+1)(s^2+4)}$$

c) $v_o(t) = \mathcal{L}^{-1}\{V_o(s)\}$

Use partial fractions

$$\begin{aligned}
 V_o(s) &= \frac{A}{s+1} + \frac{Bs+C}{s^2+2^2} \\
 &= \frac{A(s^2+2^2) + (Bs+C)(s+1)}{(s+1)(s^2+2^2)} \\
 &= \frac{As^2 + 4A + Bs^2 + (B+C)s + C}{(s+1)(s^2+2^2)} \\
 &= \frac{(A+B)s^2 + (B+C)s + 4A+C}{(s+1)(s^2+2^2)} \\
 &= \frac{10s}{(s+1)(s^2+2^2)}
 \end{aligned}$$

Matching coefficients of powers of s ,
we have

$$\begin{aligned}
 A+B &= 0, & B+C &= 10, & 4A+C &= 0 \\
 A &= -B \Rightarrow -A+C &= 10, & 4A+C &= 0 \\
 C &= 10+A \Rightarrow 4A+(10+A) &= 0 \\
 & & 5A+10 &= 0
 \end{aligned}$$

$$A = -2, \quad B = 2, \quad C = 8$$

$$\text{So } V_o(s) = \frac{-2}{s+1} + \frac{2s+8}{s^2+2^2}$$

$$V_o(s) = \frac{-2}{s+1} + 2 \cdot \frac{s}{s^2+2^2} + 4 \cdot \frac{2}{s^2+2^2}$$

$$v_o(t) = \left[-2e^{-t} + 2 \cos(2t) + 4 \sin(2t) \right] u(t) \text{ V}$$