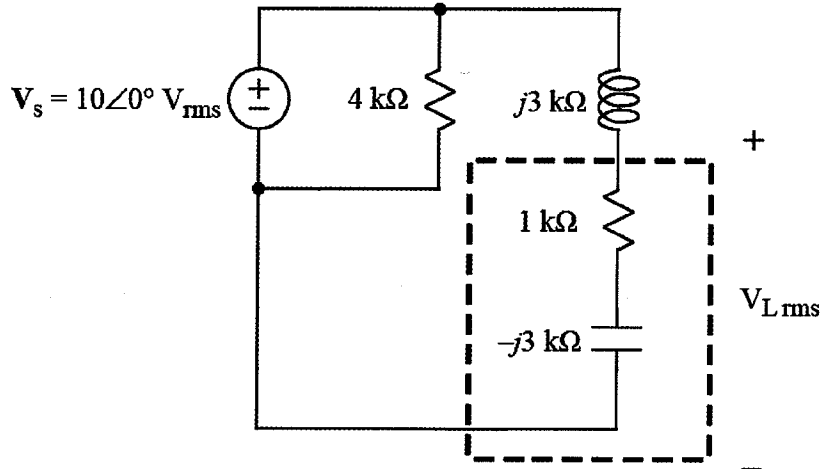


EX:



- Calculate the value of rms voltage,  $V_{L\text{rms}}$ , across the dashed box.
- Calculate the value of the average power,  $P$ , dissipated by the circuitry in the dashed box.

sol'n: a) We have two circuits in parallel across  $V_s$  - the  $4\text{k}\Omega$  and everything else. These circuits may be solved separately. Thus, the  $4\text{k}\Omega$  may be ignored.

We have a V-divider.

$$\begin{aligned} V_{L\text{rms}} &= V_s \cdot \frac{1\text{k}\Omega - j3\text{k}\Omega}{j3\text{k}\Omega + 1\text{k}\Omega - j3\text{k}\Omega} \\ &= 10\angle 0^\circ V_{\text{rms}} \frac{1\text{k}\Omega - j3\text{k}\Omega}{1\text{k}\Omega} \\ &= 10 \cdot (1 - j3) V_{\text{rms}} \end{aligned}$$

$$V_{L\text{rms}} = 10 - j30 V_{\text{rms}}$$

Note: Since our source is given in rms, the value of  $V_{L\text{rms}}$  will be rms.

b) Complex power is  $S = P + jQ = V_{rms} I_{rms}^*$

Using Ohm's Law, we find  $I_{Lrms}$  from

$$V_{Lrms}: \quad I_{Lrms} = \frac{V_{Lrms}}{Z_{box}} = \frac{V_{Lrms}}{1k\Omega - j3k\Omega}$$
$$" = \frac{10 - j30}{1k\Omega - j3k\Omega} V_{rms}$$

$$I_{Lrms} = 10 \text{ mA}_{rms}$$

Since  $I_{Lrms}$  is real,  $I_{Lrms}^* = I_{Lrms}$ .

$$\text{So } S = V_{Lrms} I_{Lrms}^* = (10 - j30) \cdot 10 \text{ m VA}$$

$$S = \frac{1}{10} - j\frac{3}{10} \text{ VA}$$

The average power,  $P$ , is the real part of  $S$ .

$$P = \frac{1}{10} \text{ W}$$

Note: The units for  $P$  are Watts, for  $Q$  are VAR, and for  $S$  are VA.