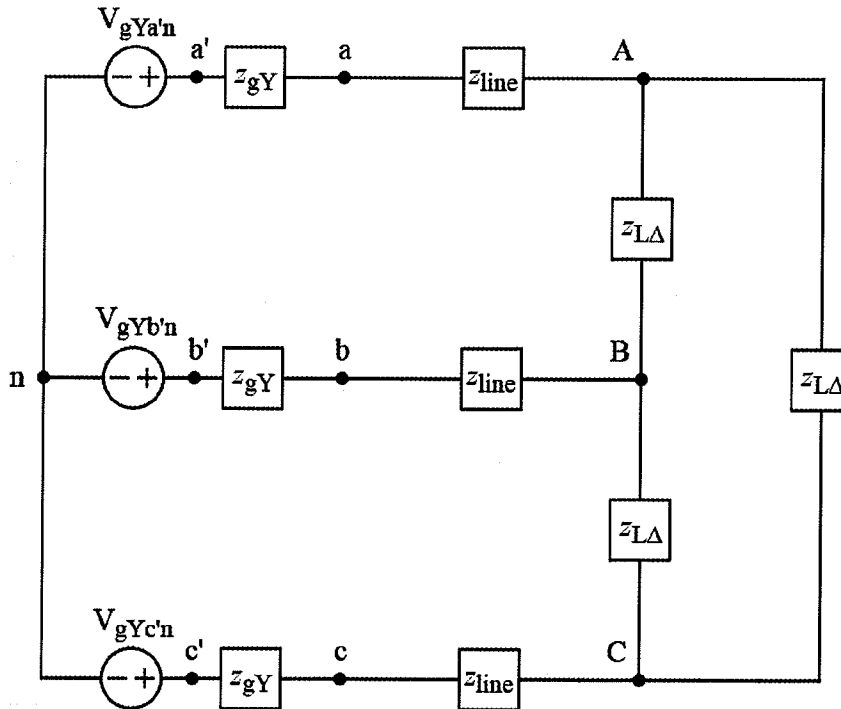



Ex:



$$\begin{aligned}
 V_{gYa'n} &= 172\angle 0^\circ \text{ V} & z_{gY} &= 1 + j3 \ \Omega \\
 V_{gYb'n} &= 172\angle -120^\circ \text{ V} & z_{line} &= j3 \ \Omega \\
 V_{gYc'n} &= 172\angle +120^\circ \text{ V} & z_{L\Delta} &= 3 \ \Omega
 \end{aligned}$$

- Draw a single-phase equivalent circuit.
- Calculate the voltage drop  $V_{ca}$  from  $c$  to  $a$ .

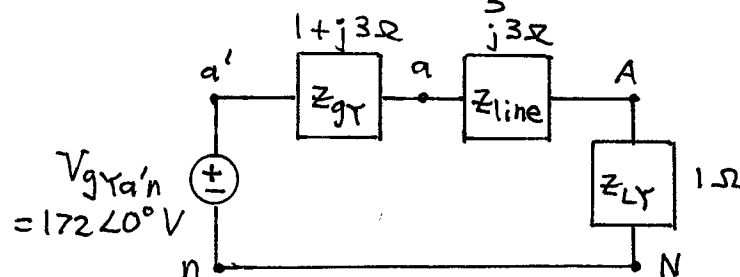sol'n: a) We convert from this Y-Δ to a Y-Y configuration. We need only divide  $z_{L\Delta}$  by 3:  $z_{LY} = \frac{3\ \Omega}{3} = 1\ \Omega$




b)  $V_{ca} = V_{ab}$  shifted by  $+120^\circ$

$$V_{ab} = V_{an} - V_{bn} \text{ and } V_{bn} = V_{an} \cdot 1 \angle -120^\circ$$

$$\text{So } V_{ab} = V_{an} (1 - 1 \angle -120^\circ)$$

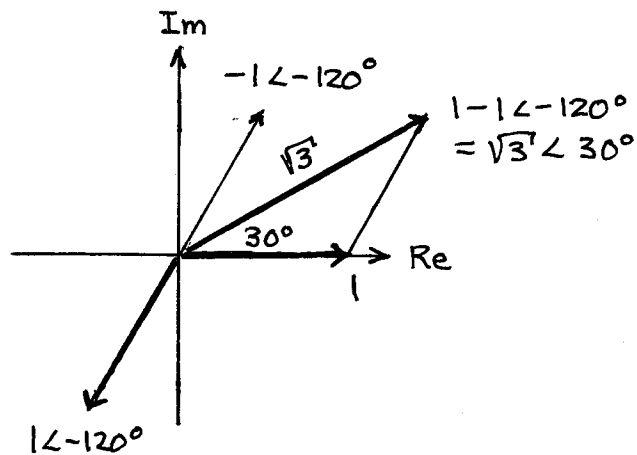We compute  $1 \angle -120^\circ$  graphically:



$$V_{ab} = V_{an} \cdot \sqrt{3} \angle 30^\circ$$

We use a voltage divider to find  $V_{an}$  from the single-phase model, and we observe that  $V_{an} = V_{aN}$ .

$$V_{aN} = V_{gYa'n} \frac{z_{line} + z_{LY}}{z_{gY} + z_{line} + z_{LY}}$$

$$" = 172 \angle 0^\circ \text{ V} \frac{j3 + 1 \Omega}{1 + j3 + j3 + 1 \Omega}$$

$$" = 172 \angle 0^\circ \text{ V} \cdot \frac{1}{2}$$

$$V_{aN} = 86 \angle 0^\circ \text{ V}$$

$$V_{ab} = V_{an} \cdot \sqrt{3} \angle 30^\circ$$

$$" \approx 86 \angle 0^\circ \cdot \sqrt{3} \angle 30^\circ \text{ V}$$

$$V_{ab} \doteq 149 \angle 30^\circ \text{ V}$$

$$V_{ca} \doteq V_{ab} \cdot 1 \angle 120^\circ$$

$$\doteq 149 \angle 30^\circ \text{ V} \cdot 1 \angle 120^\circ$$

$$V_{ca} \doteq 149 \angle 150^\circ \text{ V}$$