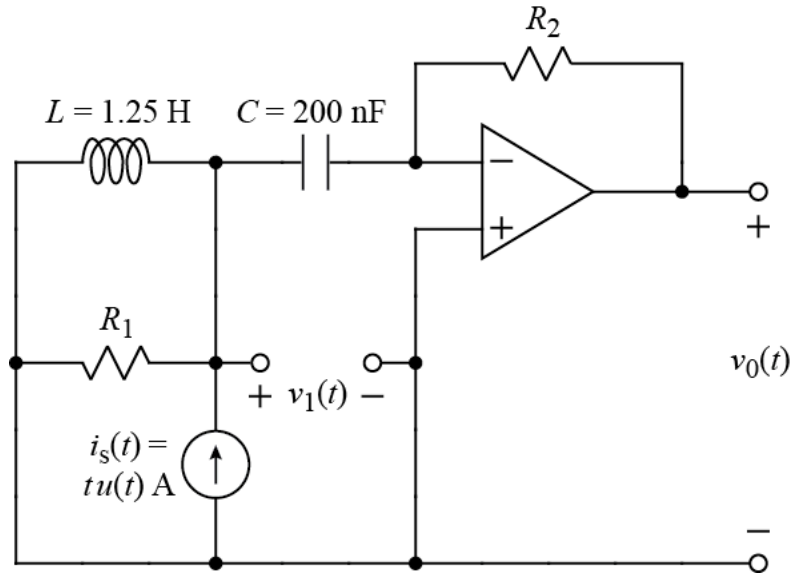




1.



The current source in the above circuit is off for $t < 0$.

Find a symbolic expression for the Laplace-transformed output, $\mathbf{V}_o(s)$, in terms of not more than R_1, R_2, L, C , and values of sources or constants.


2. Choose a numerical value for R_1 for the circuit in problem 1 to make

$$v_1(t) = v_m - v_m e^{-\alpha t} \left[\cos(\beta t) + \frac{1}{2} \sin(\beta t) \right]$$

where v_m, α , and β are real-valued constants.


Hint: C behaves as though it is in parallel with L and R_1 .

3.

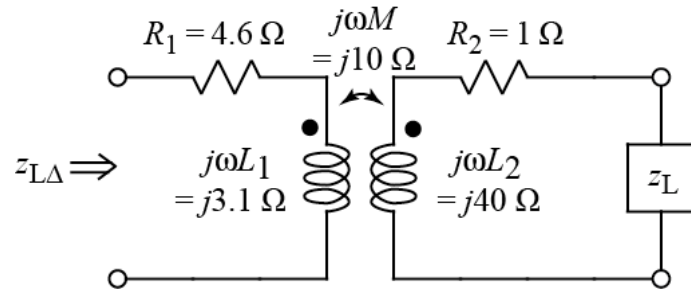

Find the value of load impedance, z_L , that makes $z_{L\Delta} = 24.6 - j36.9 \Omega$. Note that $z_{L\Delta}$ is the equivalent impedance of the entire circuit.

4.

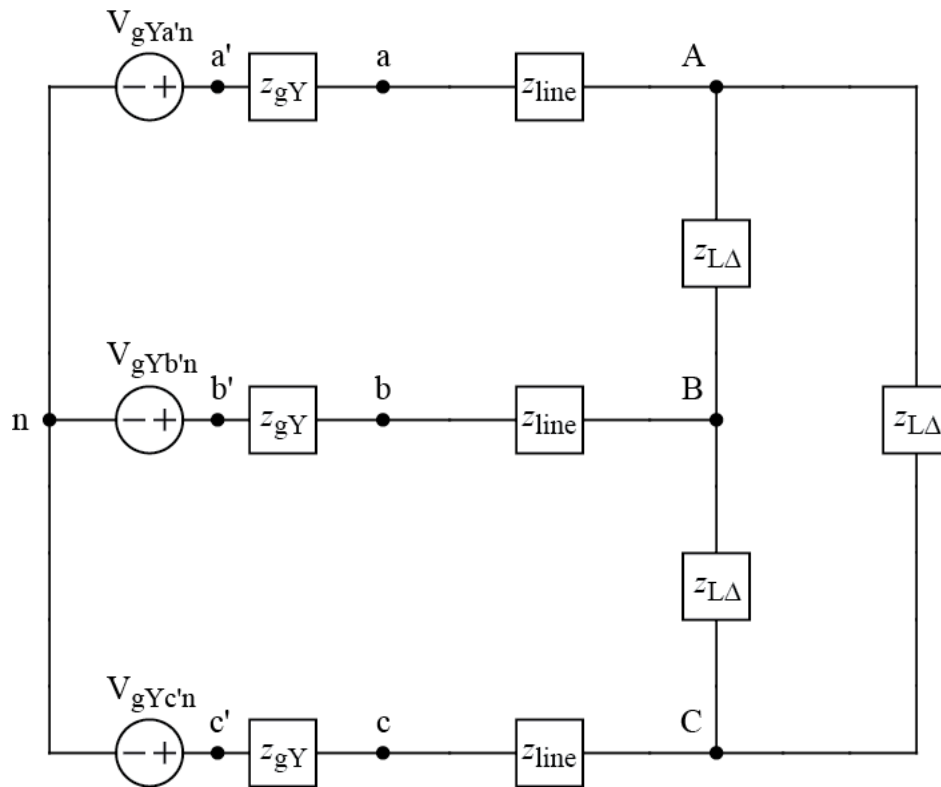

$$V_{gYa'n} = 67 \angle 0^\circ \text{ V}$$

$$z_{gY} = 11.9 + j19.7 \Omega$$

$$V_{gYb'n} = 67 \angle -120^\circ \text{ V}$$

$$z_{line} = j6 \Omega$$

$$V_{gYc'n} = 67 \angle +120^\circ \text{ V}$$

$$z_{L\Delta} = 24.6 - j36.9 \Omega$$

For the above 3-phase balanced circuit, find the numerical value of the phasor current I_{CA} .

5.

For the above 3-phase balanced circuit, find the numerical value of the phasor voltage $V_{b'a'}$.