
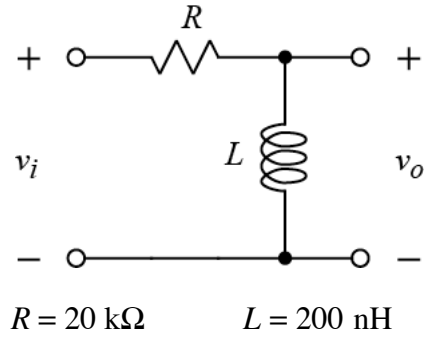


1.

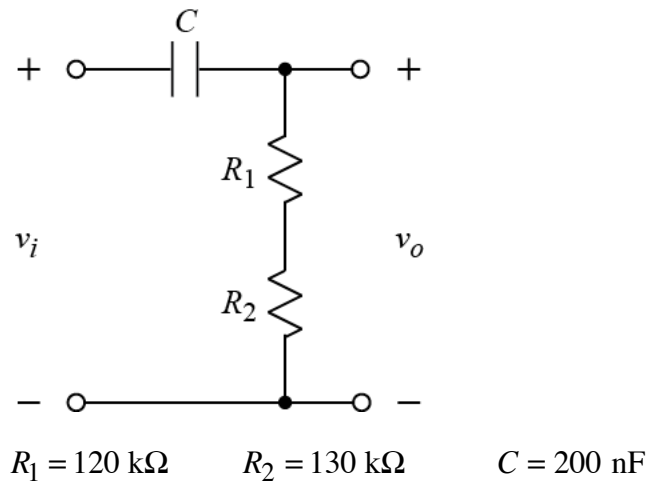


- a) Determine the transfer function  $V_o/V_i$ .
- b) Plot  $|H(j\omega)| \equiv |V_o/V_i|$  versus  $\omega$ .
- c) Find the value of  $\omega$  where  $|\text{Re}(H(j\omega))| = |\text{Im}(H(j\omega))|$ .

2.



- a) Determine the transfer function  $V_o/V_i$ .
- b) Find  $\omega$  such that  $|V_o/V_i| = 1/\sqrt{2}$ .
- c) Find  $\omega$  such that  $\angle V_o/V_i = 45^\circ$ .
- d) Is it true that  $\left| \frac{1}{j\omega C} \right| = |R_1 + R_2|$  at  $\omega = \omega_C$ ?


3.

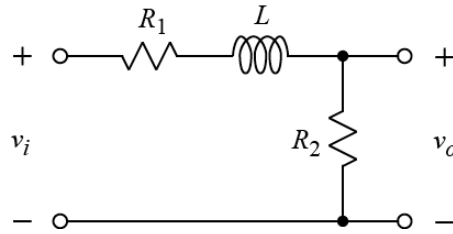

$$R_1 = 150 \Omega \quad R_2 = 750 \Omega \quad L = 1 \mu\text{H}$$

- Determine the transfer function  $V_o/V_i$ . **Hint:** switch the order of  $R_1$  and  $L$  and use a voltage divider.
- Express the maximum of  $|V_o/V_i|$  as a function of  $R_1$  and  $R_2$ .


4.

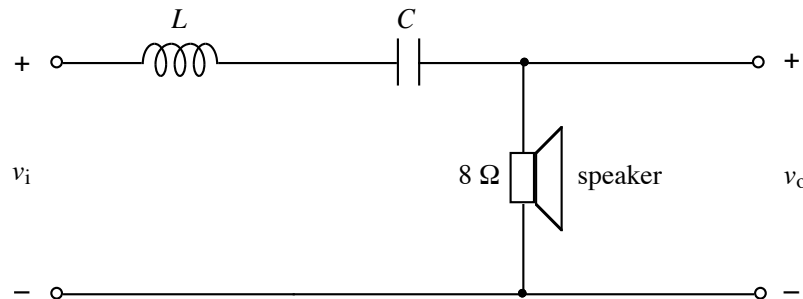

The above circuit is part of a simple crossover network for driving a midrange speaker having an impedance of  $8\Omega$ . The circuit is described at the following web site: <http://www.termpro.com/articles/xover2.html>. A more in-depth discussion of crossover networks may be found at <http://sound.westhost.com/lr-passive.htm>.

- The web site describing the above bandpass filter suggests using cutoff frequencies of  $f_{C1} = 130$  Hz and  $f_{C2} = 4$  kHz. Determine the  $L$  and  $C$  values that yield these cutoff frequencies.
- Plot  $|V_o/V_i|$  versus  $\omega$ .

5.

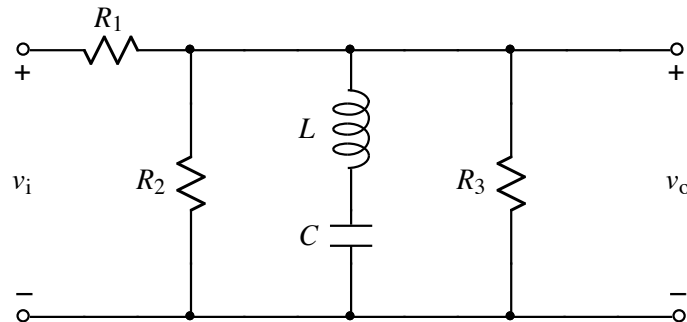

$$R_1 = 18 \Omega \quad R_2 = 48 \Omega \quad R_3 = 144 \Omega \quad C = 31.25 \mu\text{F} \quad L = 2 \text{ mH}$$

- What type of filter is the above circuit: a band-pass or a band-reject?  
**Hint:** Use a Thevenin equivalent to combine all the R's into one.

For the filter shown above, calculate the following quantities:

- $\omega_o$
- $\omega_{C1}$  and  $\omega_{C2}$
- $\beta$  and  $Q$