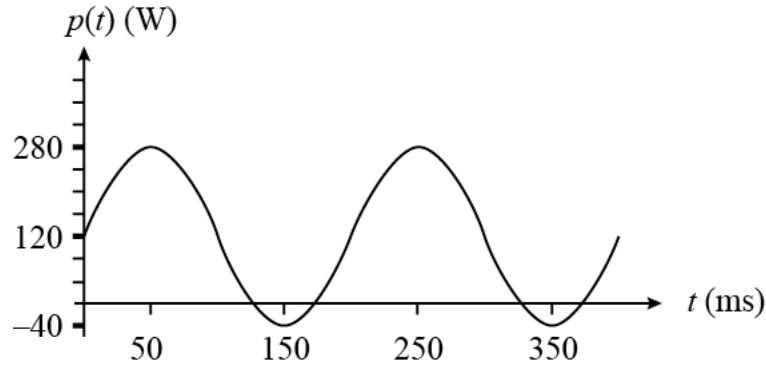



1.



Use the waveform of power versus time shown above to answer the following questions:

- Determine the value of  $\omega$ .
- Calculate complex power  $S = P + jQ$ .
- Can the phasor values of  $\mathbf{V}$  and  $\mathbf{I}$  be determined uniquely from the waveform? If so, find  $\mathbf{V}$  and  $\mathbf{I}$ .

2.

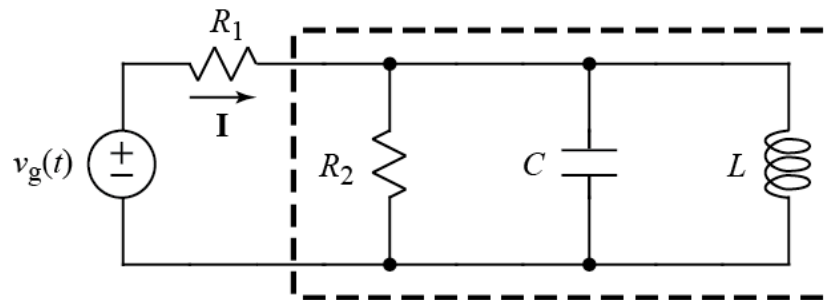


$$v_g(t) = 5 \cos(2Mt) \text{ V}$$

$$R_1 = 0.1 \, \Omega \quad R_2 = 1 \, \Omega$$

$$C = 1 \, \mu\text{F} \quad L = 125 \, \text{nH}$$

- Calculate  $\mathbf{I}$ .
- Calculate the complex power,  $S$ , for the components inside the box.


3.

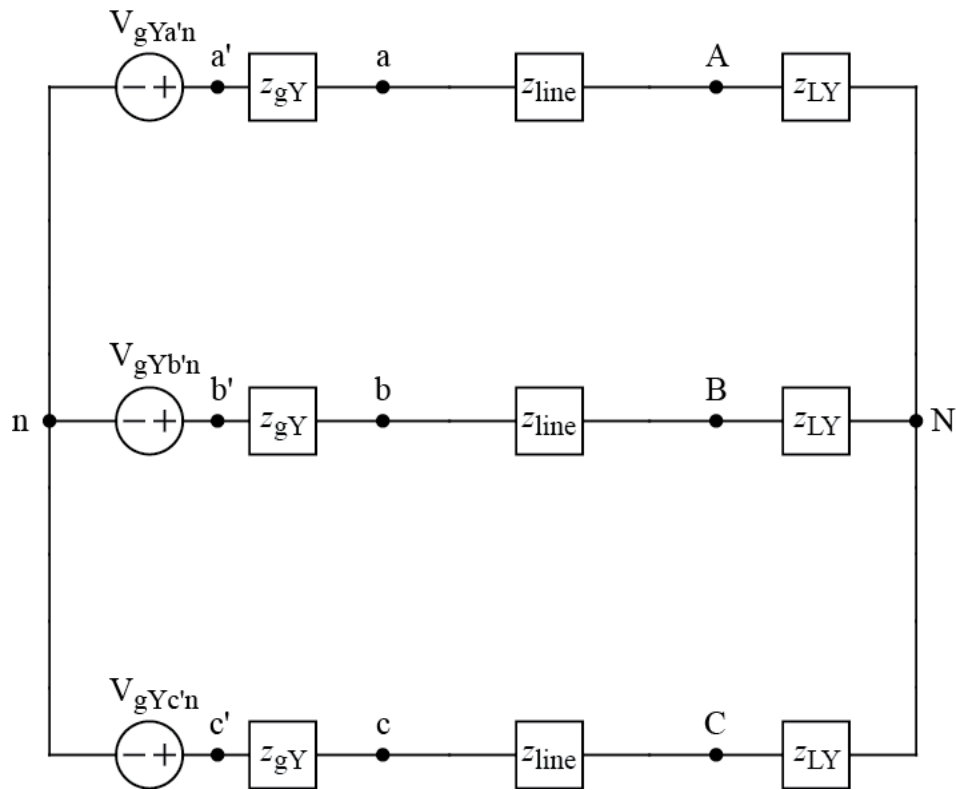

$$\begin{aligned}
 V_{gYa'n} &= 120 \angle 0^\circ \text{ V} & z_{gY} &= j0.3 \ \Omega \\
 V_{gYb'n} &= 120 \angle +120^\circ \text{ V} & z_{\text{line}} &= j0.6 \ \Omega \\
 V_{gYc'n} &= 120 \angle -120^\circ \text{ V} & z_{LY} &= 3 - j0.1 \ \Omega
 \end{aligned}$$

- a) Draw the single-phase equivalent circuit.
- b) Calculate  $V_{aA}$ .

4.

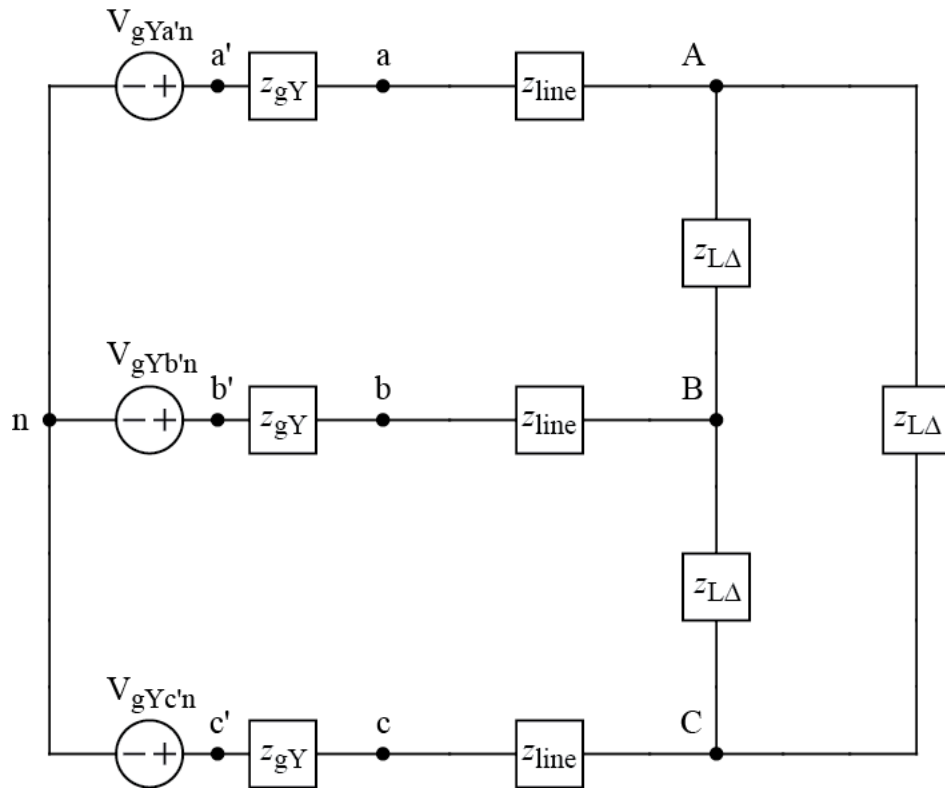

$$\begin{aligned}
 V_{gYa'b'} &= 2930\angle 0^\circ \text{ V} & z_{gY} &= j4\Omega \\
 V_{gYb'c'} &= 2930\angle +120^\circ \text{ V} & z_{line} &= j2\Omega \\
 V_{gYc'a'} &= 2930\angle -120^\circ \text{ V} & z_{L\Delta} &= 24\Omega
 \end{aligned}$$

- a) Draw the single-phase equivalent circuit.
- b) Calculate  $\mathbf{V}_{BC}$ .

5.

- a) Calculate  $\mathbf{I}_{AB}$ .
- b) Write a numerical time-domain expression for  $v_{BC}(t)$ .