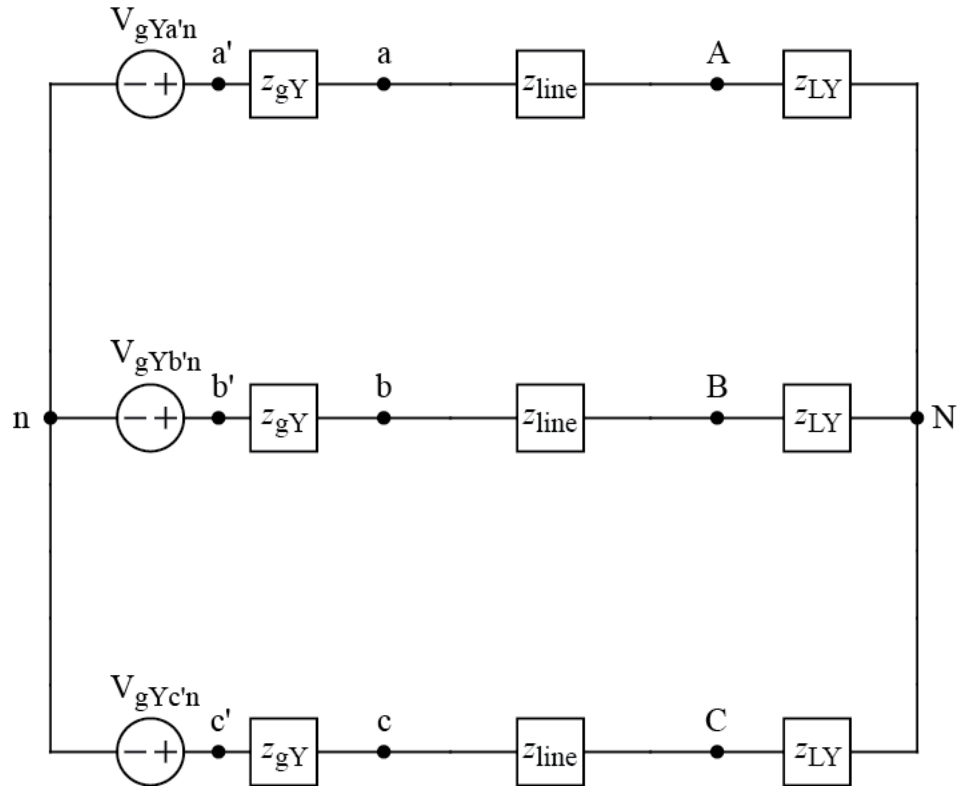



Ex:



$$\begin{aligned}
 V_{gYa'n} &= 120 \angle 0^\circ \text{ V} & z_{gY} &= j0.3 \ \Omega \\
 V_{gYb'n} &= 120 \angle +120^\circ \text{ V} & z_{line} &= j0.6 \ \Omega \\
 V_{gYc'n} &= 120 \angle -120^\circ \text{ V} & z_{LY} &= 3 - j0.1 \ \Omega
 \end{aligned}$$

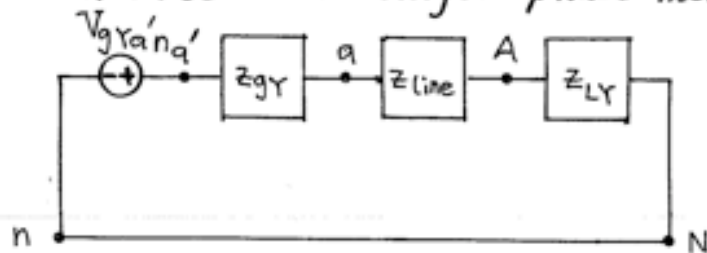- a) Draw the single-phase equivalent circuit.
- b) Calculate V_{aA} .

sol'n: a) This 3-phase circuit is already in a Y-Y configuration. Thus, the single phase model is obtained by adding a wire from n to N , (which has no effect on the circuit since the voltages and currents in a 3-phase circuit sum to zero). Then we use the added wire and the components in the a-phase to create the single-phase model.



$$V_{g_{Ya'n}} = 120 \angle 0^\circ \text{ V} \quad z_{gY} = j0.3 \Omega$$

$$z_{line} = j0.6 \Omega$$

$$z_{LY} = 3 - j0.1 \Omega$$

b) V_{aA} in the original circuit is outside of the generator and the load. Therefore V_{aA} is the same in the original circuit and in the single-phase model.

In the single-phase model, V_{aA} is given by a voltage-divider:

$$\begin{aligned} V_{aA} &= V_{g_{Ya'n}} \cdot \frac{z_{line}}{z_{gY} + z_{line} + z_{LY}} \\ &= \frac{120 \angle 0^\circ \text{ V} \cdot j0.6}{j0.3 + j0.6 + 3 - j0.1 \Omega} \end{aligned}$$

$$V_{qA} = 120 \angle 0^\circ \text{ V} \cdot \frac{0.6 \angle 90^\circ}{3 + j0.8}$$

$$= 120 \angle 0^\circ \text{ V} \cdot \frac{0.6 \angle 90^\circ}{3.1 \angle 14.9^\circ}$$

$$= \frac{120(0.6)}{3.1} \text{ V} \angle 0^\circ + 90^\circ - 14.9^\circ$$

$$V_{qA} = 23.2 \angle 75.1^\circ \text{ V}$$