
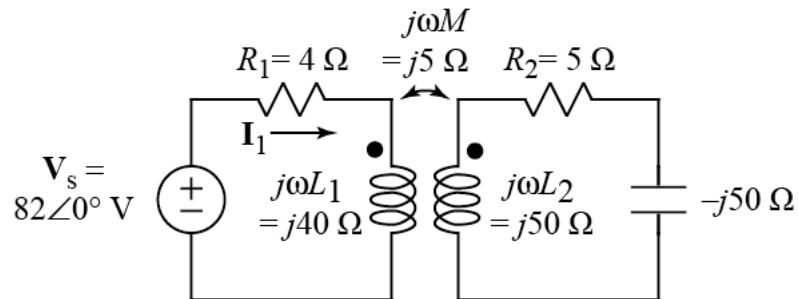


Ex:

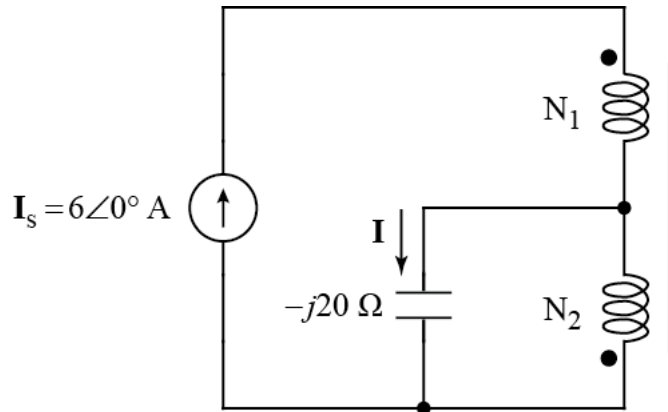


- a) Calculate the numerical value of phasor current,  $I_1$ , flowing into the primary side of the transformer. Note: the transformer is linear.



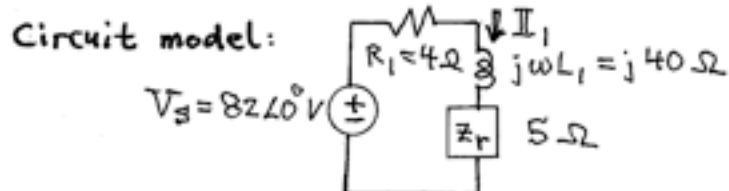- b) The turns ratio of the transformer is  $N_1/N_2 = 6$ . Calculate the numerical value of phasor current,  $I$ , flowing down through the capacitor. Note: the transformer is ideal.

sol'n: a) We account for the secondary of the transformer by using the reflected impedance,  $z_r$ :

$$z_r = \frac{(\omega M)^2}{z_{\text{secondary tot}}} = \frac{5^2}{j40 + 5 - j50} = 5 \Omega$$



$$\mathbb{I}_1 = \frac{V_s}{R_1 + j\omega L_1 + Z_r} = \frac{82 \angle 0^\circ \text{ V}}{4 \Omega + j40 \Omega + 5 \Omega}$$


$$= \frac{82 \angle 0^\circ \text{ V}}{9 + j40 \Omega} = \frac{82 \angle 0^\circ \text{ V}}{41 \angle 77.3^\circ \Omega}$$

$$\mathbb{I}_1 = 2 \angle -77.3^\circ \text{ A}$$

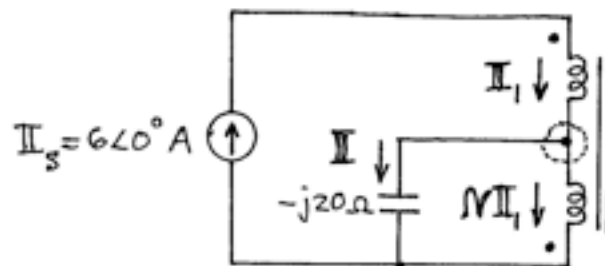b) We use the ideal transformer eq'ns:

$$\frac{V_1}{V_2} = \frac{N_1}{N_2} = N, \quad \frac{\mathbb{I}_1}{\mathbb{I}_2} = \frac{N_2}{N_1} = \frac{1}{N}$$

Applying these eq'ns to the circuit diagram reveals that we can solve the circuit by considering a current summation.



A current summation at the node with the dashed circuit, and the observation that  $\mathbb{I}_1 = \mathbb{I}_s$  yields the following equations:

$$\mathbb{I}_1 = \mathbb{I}_s, \quad N=6$$

$$-\mathbb{I}_1 + N\mathbb{I}_1 + \mathbb{I} = 0$$

$$\text{Thus, } \mathbb{I} = (1-N)\mathbb{I}_1 = -5\mathbb{I}_s = -30 \text{ A}$$

$$\text{or } \mathbb{I} = 30 \angle 180^\circ \text{ A}$$