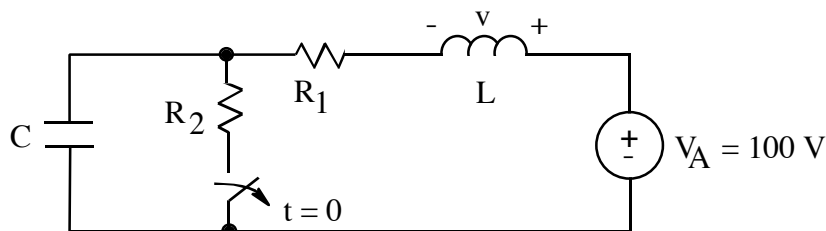


1. (50 points)



After having been open for a long time, the switch is closed at $t = 0$.


$$R_1 = 12.5\Omega$$

$$R_2 = 12.5\Omega$$

$$L = 6.25 \mu\text{H}$$

- Two capacitances are available: 2 nF and 250 nF. Specify the value of C that will make $v(t)$ overdamped.
- Using the value of C found in (a), write a time-domain expression for $v(t)$.

2. (50 points)

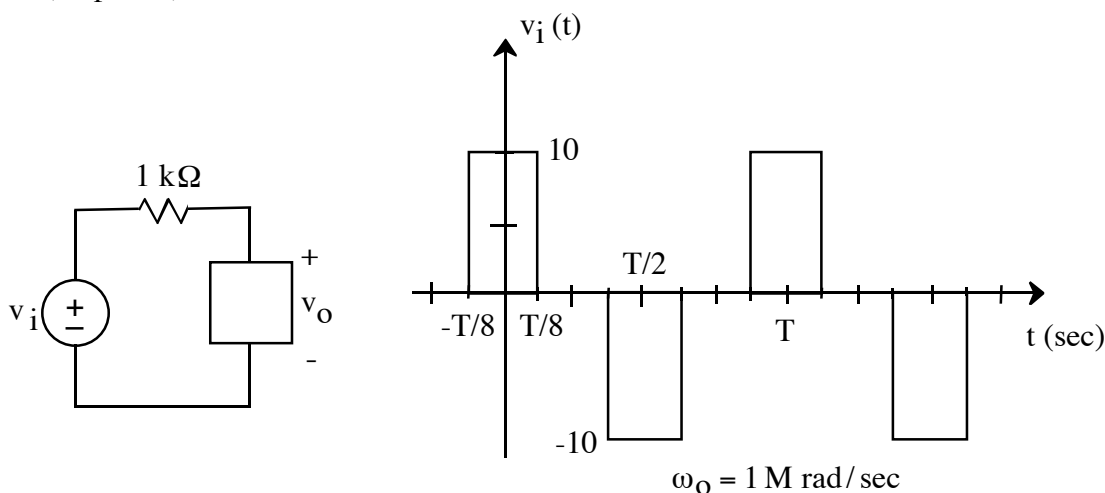


- Determine the coefficients of the Fourier series, a_v , a_n , and b_n , for the periodic waveform $v_i(t)$. Also, use these Fourier coefficients to find the coefficients of the first five terms of the Fourier series written in terms of inverse phasors:

$$v_1(t) = a_v + \sum_{n=1}^{\infty} A_n \cos(n\omega_0 t + \theta_n)$$

Note any symmetry properties of the waveform that you use to determine coefficients.

- The circuit on the left is a filter with output $v_o(t)$. Design a circuit to be placed in the box such that the filter rejects the fundamental frequency of $v_i(t)$ and has a bandwidth of 10,000 rad/sec. Specify the component values. Show how the components are connected in the circuit.

3. (50 points)

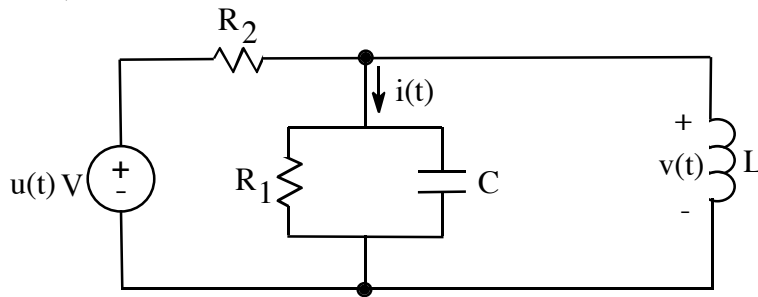

The initial energy stored in the circuit is zero.


$$R_2 = 500 \Omega \quad L = 200 \text{ mH}$$

a. Choose values of R_1 and C to accomplish the following:

- (1) $v(t)$ and $i(t)$ are decaying sinusoids 90° out of phase with each other.
- (2) $1/\alpha = T$, where α is the exponential decay constant and T is the period of oscillation of the decaying sinusoid.

b. With the component values you chose in the circuit, write numerical expressions for $v(t)$ and $i(t)$.


4. (50 points)

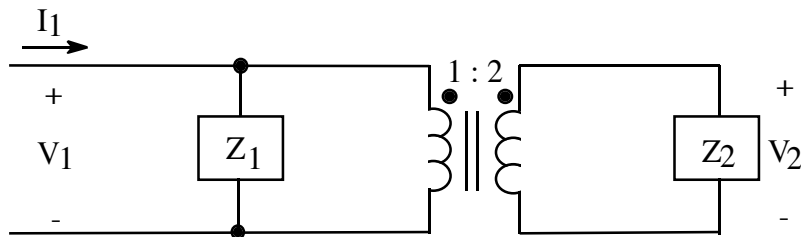

$$Z_1 = (5 - j5)\Omega \quad Z_2 = (20 + j20)\Omega$$

a. Find the input impedance, $z_{in} = V_1/I_1$, for the above circuit.

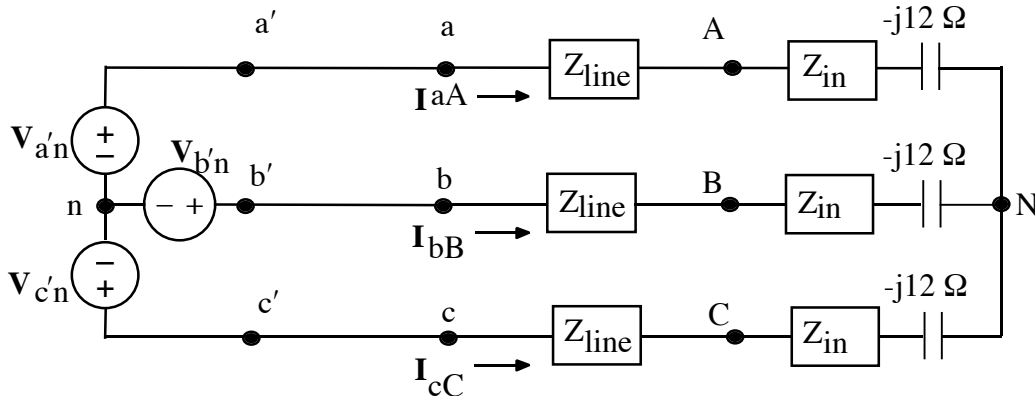b. Using z_{in} from (a), find a numerical expression for V_{AB} in the circuit below.



Balanced three-phase system.

$$V_{an} = 52 \angle 0^\circ \text{ V} \quad V_{bn} = 52 \angle -120^\circ \text{ V} \quad z_{line} = j12 \Omega$$