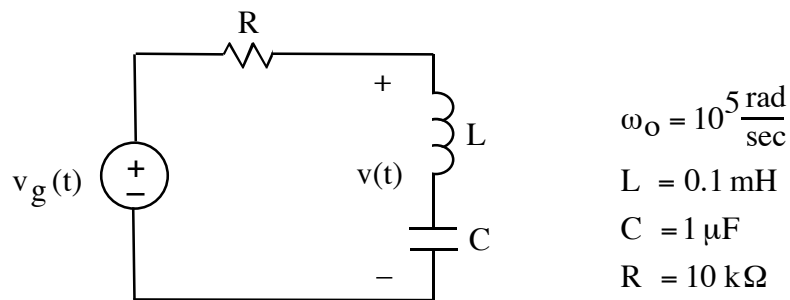


3. (30 points)



$$v_g(t) = \frac{16}{\pi} \sum_{n \text{ odd}}^{\infty} \frac{1}{n} \sin(n\omega_0 t)$$

Write the time-domain expression of $v(t)$ for the first through third harmonics.

Ans: $v(t) = 1.6 \cos(300k t - 69.4^\circ) \text{ V}$

Sol'n: Summary of steps expanded upon below:

1. We turn each frequency of $v_g(t)$ into a phasor.
2. We pass each frequency, $k\omega_0$, through the circuit by multiplying by the transfer function $H(jk\omega_0)$.
3. The result is the phasor for frequency $k\omega_0$ in the output signal.
4. We convert the output signal phasor back to the time domain, (through the 1st 3 harmonics).

Note: We only have 1st and 3rd harmonics to worry about since we only have odd harmonics in $v_g(t)$ and we were only asked to find the output signal's 1st through 3rd harmonics.

1. We turn each frequency of $v_g(t)$ into a phasor.

$$k = 1: \frac{16}{\pi} \sin(\omega_0 t) \xrightarrow{\text{P[]}} -j \frac{16}{\pi} \text{ or } \frac{16}{\pi} \angle -90^\circ$$

$$k = 3: \frac{16}{\pi} \frac{1}{3} \sin(3\omega_0 t) \xrightarrow{\text{P[]}} -j \frac{16}{3\pi} \text{ or } \frac{16}{3\pi} \angle -90^\circ$$

2. We pass each frequency, $k\omega_0$, through the circuit by multiplying by the transfer function $H(jk\omega_0)$.

$$H(j\omega) \equiv \frac{V}{V_g} = \frac{j\omega + \frac{1}{j\omega C}}{R + j\omega L + \frac{1}{j\omega C}} \quad (\text{V-divider})$$

k = 1:

$$H(j\omega_o) = \frac{(j\omega_o)^2 LC + 1}{j\omega_o RC + (j\omega_o)^2 LC + 1}$$

$$H(j\omega_o) = \frac{-(100k)^2 0.1m \mu + 1}{j100k 10k \mu - (100k)^2 0.1m \mu + 1}$$

$$H(j\omega_o) = \frac{-100^2 \cdot 0.1m + 1}{j1k - 100^2 0.1m + 1} = \frac{0}{j1k} = 0$$

In this case, the L and C together behave like a wire at frequency ω_o . The voltage drop across the wire is zero, as is the circuit output. Consequently, $H(j\omega_o) = 0$.

Note: In this case, the ω_o for the $v_g(t)$ Fourier series happens to be the same as the center (or resonant, or characteristic) frequency of the L and C:

$$\omega_o = \sqrt{\frac{1}{LC}}$$

Typically, the ω_o for the Fourier series is different from the ω_o for an L and C.

k = 3:

$$H(j3\omega_o) = \frac{-3^2 + 1}{j3k - 3^2 + 1} = \frac{-8}{j3k - 8}$$

Note: $(j3\omega_o)^2 LC$ is 3^2 since it was 1^2 for ω_o .

$$H(j3\omega_o) = \frac{8}{8 - j3k} = \frac{1}{1 - \frac{j3k}{8}} = \frac{1}{1 - j375} = 2.67 \text{ m} \angle 89.85^\circ$$

3. The result is the phasor for frequency $k\omega_o$ (where $k = 3$) in output signal.

Input phasor is

$$V_{i3} = -j \frac{16}{3\pi} \text{ V} = \frac{16}{3\pi} \angle -90^\circ \text{ V}.$$

Output phasor is

$$V_{o3} = V_{i3} H(j3\omega_o) = \frac{16}{3\pi} \angle -90^\circ \cdot 2.67 \angle 89.85 \text{ mV}.$$

$$V_{o3} = 4.53 \angle -0.15^\circ \text{ mV}$$

4. We convert the output signal phasor back to the time domain, (through the 1st 3 harmonics, of which only the third harmonic is nonzero).

$$v_{o3} = 4.53 \cos(300 kt - 0.15^\circ) \text{ mV}$$