

1. (25 points)

a. Find $f(t)$ if

$$F(s) = \frac{s + 2}{(s + 1)^2 (s + 4)}$$

b. Plot the poles and zeros of $G(s)$ in the s plane

$$G(s) = \frac{12 + 4s}{(s + 2)(s^2 + 25)(s^2 + 6s + 25)}$$

c. Find $\lim_{t \rightarrow 0^+} f(t)$ if


$$F(s) = \frac{3(s^3 + 7s^2 + 14s + 8)}{s^4 + 14s^3 + 98s^2 + 350s + 625}$$

d. Find $\lim_{t \rightarrow \infty} f(t)$ if


$$F(s) = \frac{2s^4 + 6s^3 + 30s^2 + 25s + 120}{s^6 + 14s^5 + 112s^4 + 448s^3 + 975s^2 + 625s}$$

(All poles of $F(s)$ are in the left-half plane.)

e. Write an expression for $H(s)$.

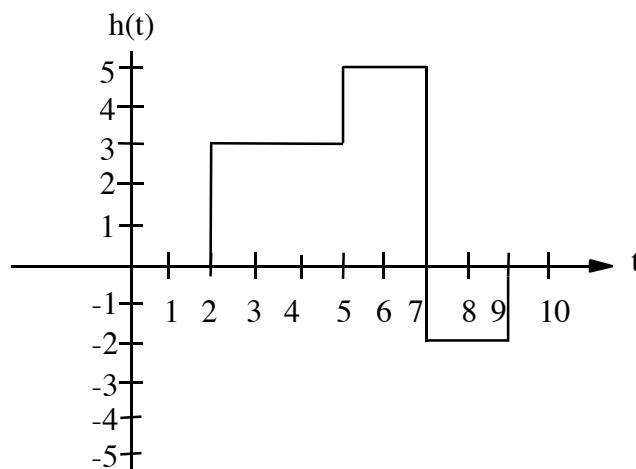


2. (45 points)

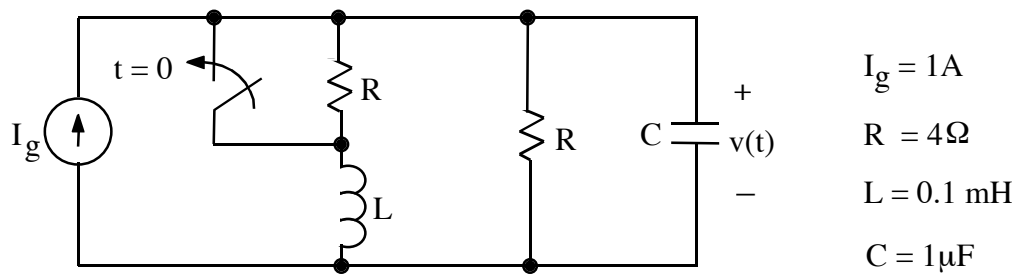

The current source is a dc current source. After being open for a long time, the switch is closed at $t = 0$.

- Write a numerical time-domain expression for $v(t)$.
- From the Laplace transform of $v(t)$, find the numerical values of $v(t)$ for $t = 0^+$ and $t \rightarrow \infty$.

3. (30 points)

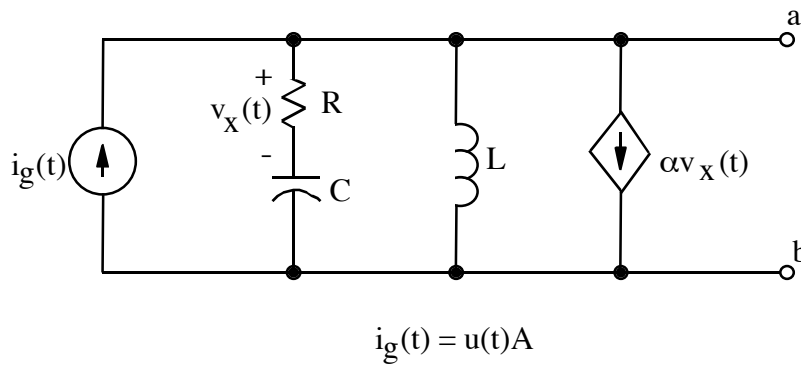

Construct an s-domain Thevenin's equivalent to the circuit at the terminals a-b. There is no initial energy stored in the circuit.