
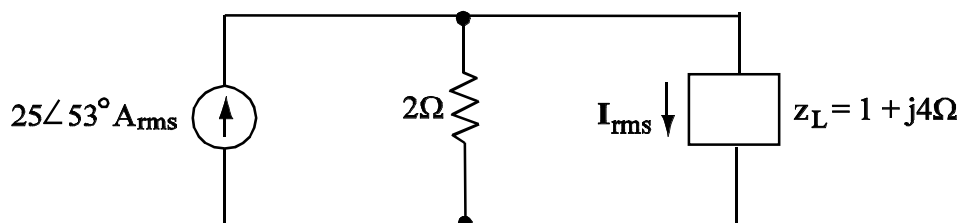


1. (30 points)

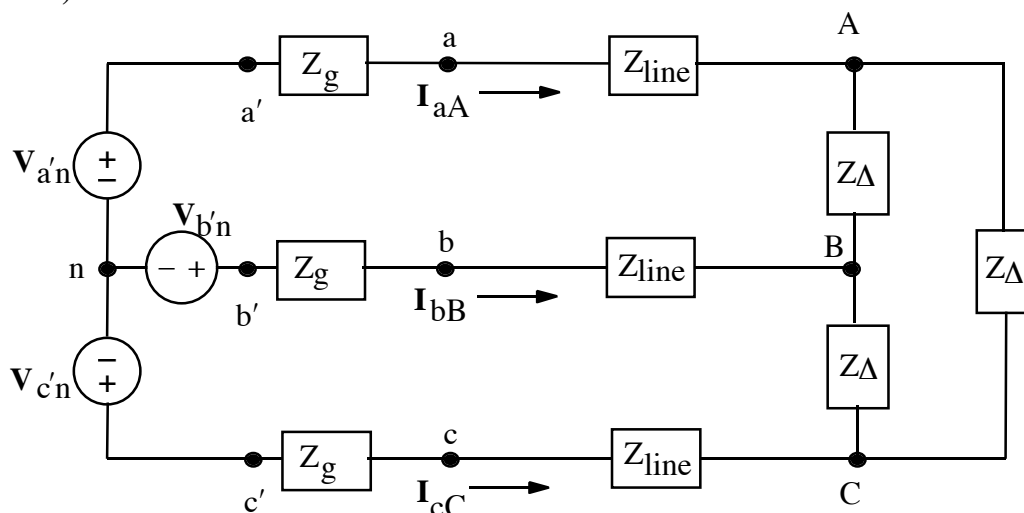

- Calculate the value of rms current,  $I_{\text{rms}}$ , flowing through  $z_L$ .
- Calculate the complex power,  $S$ , for  $z_L$ . Include appropriate units.


2. (30 points)




Balanced three-phase, positive-sequence system  
 $I_{aA} = 15 \angle 0^\circ \text{A}$        $Z_g = (0.2 + j0.2)\Omega$   
 $V_{aA} = 22.5 \angle 53.13^\circ \text{V}$        $Z_\Delta = (30 + j24)\Omega$

- Draw a single-phase equivalent circuit.
- Calculate  $I_{AB}$ .

3. (40 points)

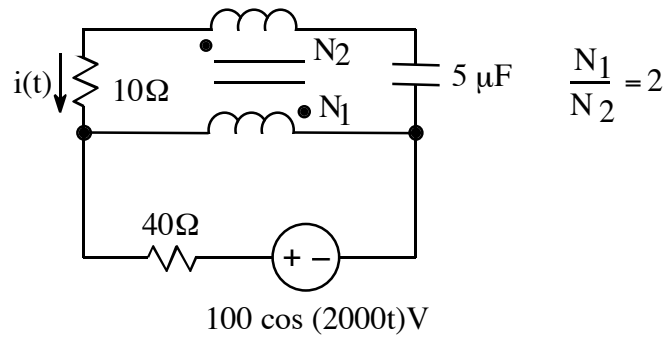

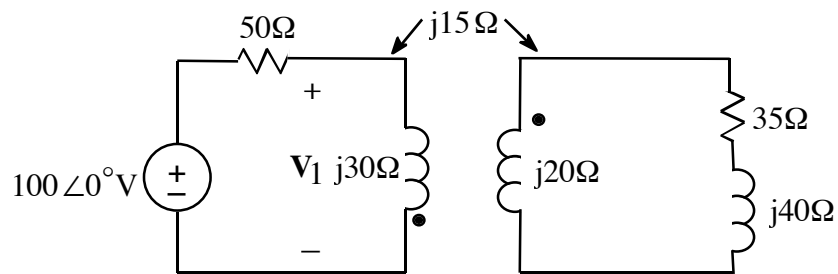a. Write a numerical time-domain expression for the current  $i(t)$ .



b. Calculate  $V_1$ .