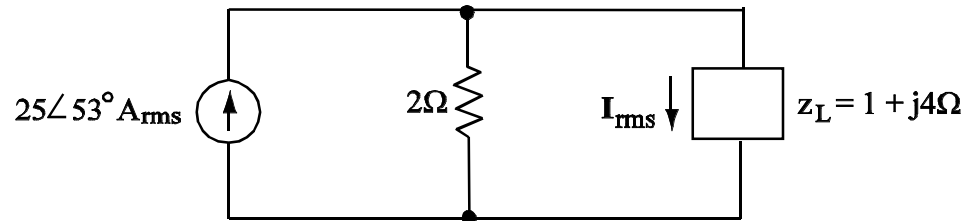


1. (30 points)



- Calculate the value of rms current, I_{rms} , flowing through z_L .
- Calculate the complex power, S , for z_L . Include appropriate units.

- ans: a)** $I_{\text{rms}} = 10 \text{ A}_{\text{rms}}$
b) $S = 100 + j400 \text{ VA}$

sol'n: (a) The circuit is a current divider:

$$I_{\text{rms}} = 25\angle 53^\circ \text{ A}_{\text{rms}} \cdot \frac{2\Omega}{2\Omega + 1 + j4\Omega}$$

$$I_{\text{rms}} = 25\angle 53^\circ \text{ A}_{\text{rms}} \cdot \frac{2\Omega}{3 + j4\Omega}$$

$$I_{\text{rms}} = 25\angle 53^\circ \text{ A}_{\text{rms}} \cdot \frac{2\Omega}{5\angle 53^\circ \Omega}$$

$$I_{\text{rms}} = \frac{25 \cdot 2}{5} \angle (53^\circ - 53^\circ) \frac{\text{A}_{\text{rms}} \Omega}{\Omega}$$

$$I_{\text{rms}} = 10\angle 0^\circ \text{ A}_{\text{rms}}$$

sol'n: (b) $S = |I_{\text{rms}}|^2 z_L = |10\text{A}|^2 (1 + j4\Omega)$

$$S = 100(1 + j4) \text{ VA}$$

$$S = 100 + j400 \text{ VA}$$