
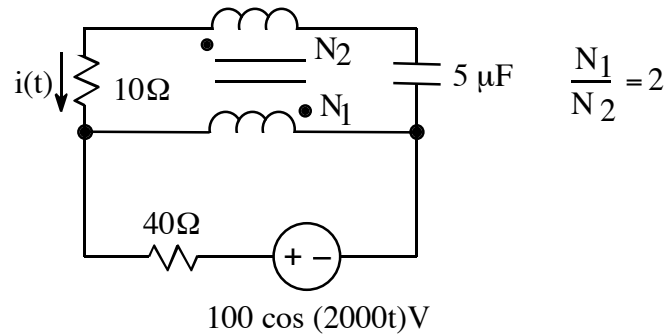


3. (40 points)

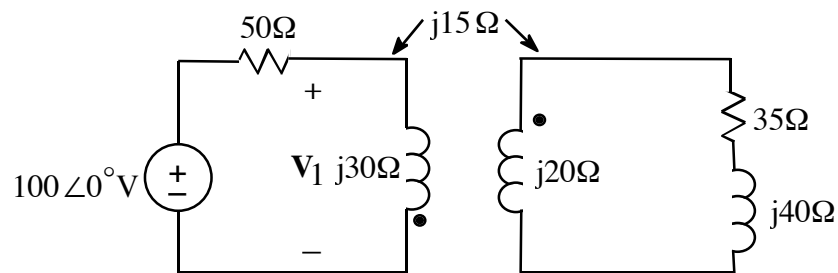

a. Write a numerical time-domain expression for the current $i(t)$.



b. Calculate V_1 .

ans: a)

$$i(t) = \frac{3}{4} \sqrt{2} \cos(2kt - 135^\circ) \text{ A}$$

b)


$$V_1 = 46.7 \angle 58.8^\circ \text{ V}$$

sol'n: (a) We assume an ideal transformer since we are only given the turns ratio N_1/N_2 . We want to draw the circuit in the s -domain with labels for \mathbf{I}_1 , \mathbf{I}_2 , \mathbf{V}_1 , and \mathbf{V}_2 .

$$\omega = 2k \quad \text{from} \quad V_s = 100 \cos(2k \cdot t) \text{V}$$

$$\frac{1}{j\omega C} = \frac{1}{j2k \cdot 5\mu} \Omega = -\frac{j}{10m} \Omega = -j100\Omega$$

Our circuit diagram in the s -domain:

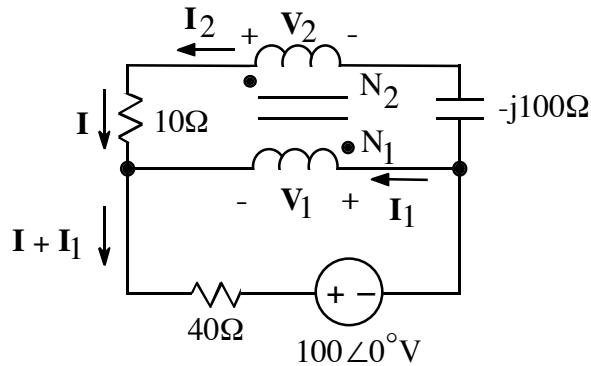

Note: We measure \mathbf{V}_1 and \mathbf{V}_2 with plus signs at dots on transformer.

\mathbf{I}_1 (primary side) flows into dotted terminal.

\mathbf{I}_2 (secondary side) flows out of dotted terminal.

For the above definitions of \mathbf{I}_1 , \mathbf{I}_2 , \mathbf{V}_1 , and \mathbf{V}_2 , we have ideal transformer equations without minus signs:

$$\frac{\mathbf{V}_1}{N_1} = \frac{\mathbf{V}_2}{N_2} \quad \mathbf{I}_1 N_1 = \mathbf{I}_2 N_2$$

Now we write equations for mesh (current) loops. (We could also use the node-voltage method.)

We observe that $\mathbf{I} = \mathbf{I}_2$ in the top loop, and since \mathbf{I}_2 is flowing on the outer edge of the circuit, (where there is no circuit on the other side to cause a summation of mesh currents through components), we see that \mathbf{I} is also the mesh current for the top loop.

The current mesh equation for the top loop is (the sum of V drops around the loop):

$$(1) \quad \mathbf{V}_2 - \mathbf{I} \cdot 10\Omega + \mathbf{V}_1 - \mathbf{I}(-j100\Omega) = 0\text{V}$$

Note: \mathbf{I} must also flow up through C. What \mathbf{I} goes down, must come up. (Otherwise, we would accumulate charge in the bottom half of the circuit.)

The mesh current for the bottom loop will be $\mathbf{I} + \mathbf{I}_1$. This current is flowing on the outside edge of the circuit in the bottom loop.

Our mesh loop equation for the bottom (i.e. sum of V drops around loop) is:

$$-V_1 - (\mathbf{I} + \mathbf{I}_1)40\Omega - 100\angle 0^\circ = 0V$$

or

$$(2) \quad -V_1 + (\mathbf{I} + \mathbf{I}_1)40\Omega + 100\angle 0^\circ = 0V$$

Now we use the ideal transformer equations to eliminate all but two unknowns:

$$\mathbf{V}_1 = \frac{N_1}{N_2} \mathbf{V}_2 = 2\mathbf{V}_2, \quad \mathbf{I}_1 = \frac{N_2}{N_1} \mathbf{I}_2 = \frac{N_2}{N_1} \mathbf{I} = \frac{\mathbf{I}}{2}$$

Substituting these into Eq. 1 and Eq. 2 gives two equations in two unknowns:

$$(1') \quad \mathbf{V}_2 - \mathbf{I} \cdot 10\Omega + 2\mathbf{V}_2 - \mathbf{I}(-j100\Omega) = 0V$$

$$(2') \quad 2\mathbf{V}_2 + \left(I + \frac{I}{2}\right) 40\Omega + 100\angle 0^\circ = 0V$$

Now we solve for \mathbf{I} . From Eq. 2':

$$\mathbf{V}_2 = -\left(\frac{\frac{3}{2}\mathbf{I} \cdot 40\Omega + 100}{2}\right) = -30 \cdot \mathbf{I} - 50V$$

Eq. 1' rearranged is

$$3\mathbf{V}_2 + (-10 + j100)\mathbf{I} = 0V.$$

By substituting for \mathbf{V}_2 , and doing the algebra, we find \mathbf{I} :

$$3(-30 \cdot \mathbf{I} - 50) + (-10 + j100)\mathbf{I} = 0V$$

$$(-100 + j100)\mathbf{I} - 150 = 0V$$

$$\mathbf{I} = \frac{150}{-100 + j100} A = \frac{3}{-2 + j2} A = -\frac{3}{2} \frac{1}{1 - j} A$$


$$\mathbf{I} = -\frac{3}{4} \sqrt{2} \angle 45^\circ A$$

$$\mathbf{I} = \frac{3}{4} \sqrt{2} \angle -180^\circ + 45^\circ A$$

$$\mathbf{I} = \frac{3}{4} \sqrt{2} \angle -135^\circ A$$

$$\therefore i(t) = \frac{3}{4} \sqrt{2} \cos(2kt - 135^\circ) A$$

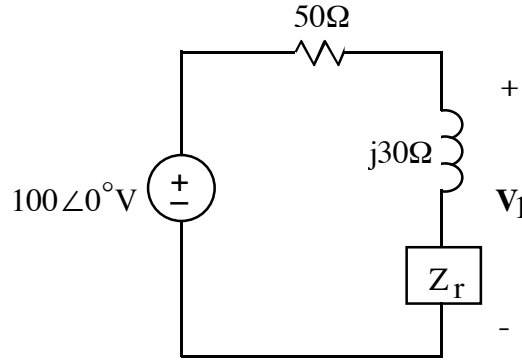sol'n: (b) We use the idea of reflected impedance for a linear transformer:



The formula for reflected impedance with a linear transformer is

$$Z_r = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

Here, we have $R_2 = 0\Omega$, $j\omega L_2 = j20\Omega$, and $Z_L = 35\Omega + j40\Omega$.

$j\omega M = j15\Omega$ is the mutual inductance. $\therefore \omega M = 15\Omega$

$$\therefore Z_r = \frac{225\Omega^2}{j20 + 35 + j40\Omega} = \frac{225}{35 + j60}\Omega = \frac{45}{7 + j12}\Omega$$

$$Z_r = \frac{45}{193}(7 - j12)\Omega$$

Using the equivalent model for primary side, as shown above, we have

$$V_1 = \frac{j30\Omega + Z_r}{50 + j30 + Z_r} \cdot 100\angle 0^\circ \text{V}$$

$$V_1 = \frac{j30 + \frac{45}{193}(7 - j12)}{50 + j30 + \frac{45}{193}(7 - j12)} \cdot 100\angle 0^\circ \text{V}$$

We can factor out a 5 from top and bottom:

$$V_1 = \frac{j(193)30 + 45(7 - j12)}{(193) \cdot \frac{50}{10} + j(193)\frac{30}{6} + \frac{45}{9}(7 - j12)} \cdot \frac{20}{100} = \frac{315 + j5250}{1993 + j1050} \cdot 20 \text{V}$$

Evaluating the expression and converting to polar form gives

$$V_1 = 46.7\angle 58.8^\circ \text{V}.$$