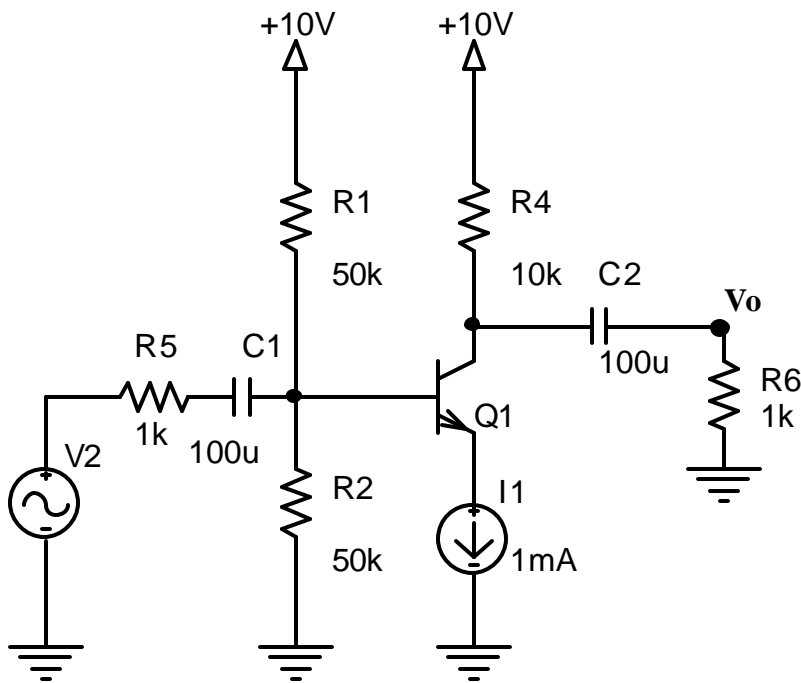


Problem 1 (10 points)


$V_2 = 0.1m \sin(\omega t)$ and β can vary from 20 to 200. The circuit shown below is suppose to amplify but does not. You expect the output at V_o to amplify V_2 . When you are testing the circuit, you find that it does not amplify. Explain why it does not and what exact resistor can be changed to allow it to amplify. I_1 is not an ideal current source and can have a voltage drop across it.



Problem 2 (35 points)

Use $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$ (V_2 is an ac source).

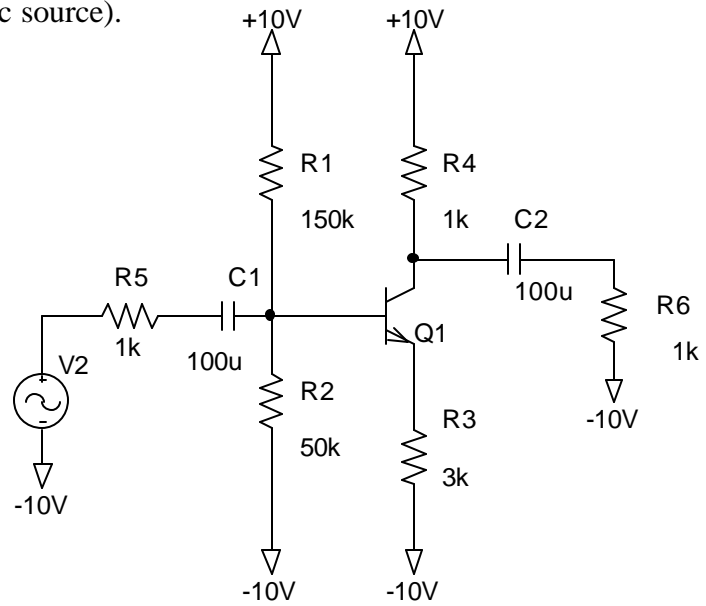- Find the DC values for the following
 - a. I_{E1} (15 points)
 - b. I_{C1} (3 points)
 - c. V_{E1} (6 points)
 - d. V_{C1} (6 points)
 - e. V_{B1} (5 points)




Problem 3 (55 points)

Use $|V_{BE}|=0.7$, $\beta=20$, $V_T=25\text{mV}$ (V_s is an ac source), ignore r_o .

This small-signal model circuit is drawn below. The original circuit is also shown below. It was found through a DC analysis that $I_{C1}=50\mu$ and $I_{C2}=25\mu$.

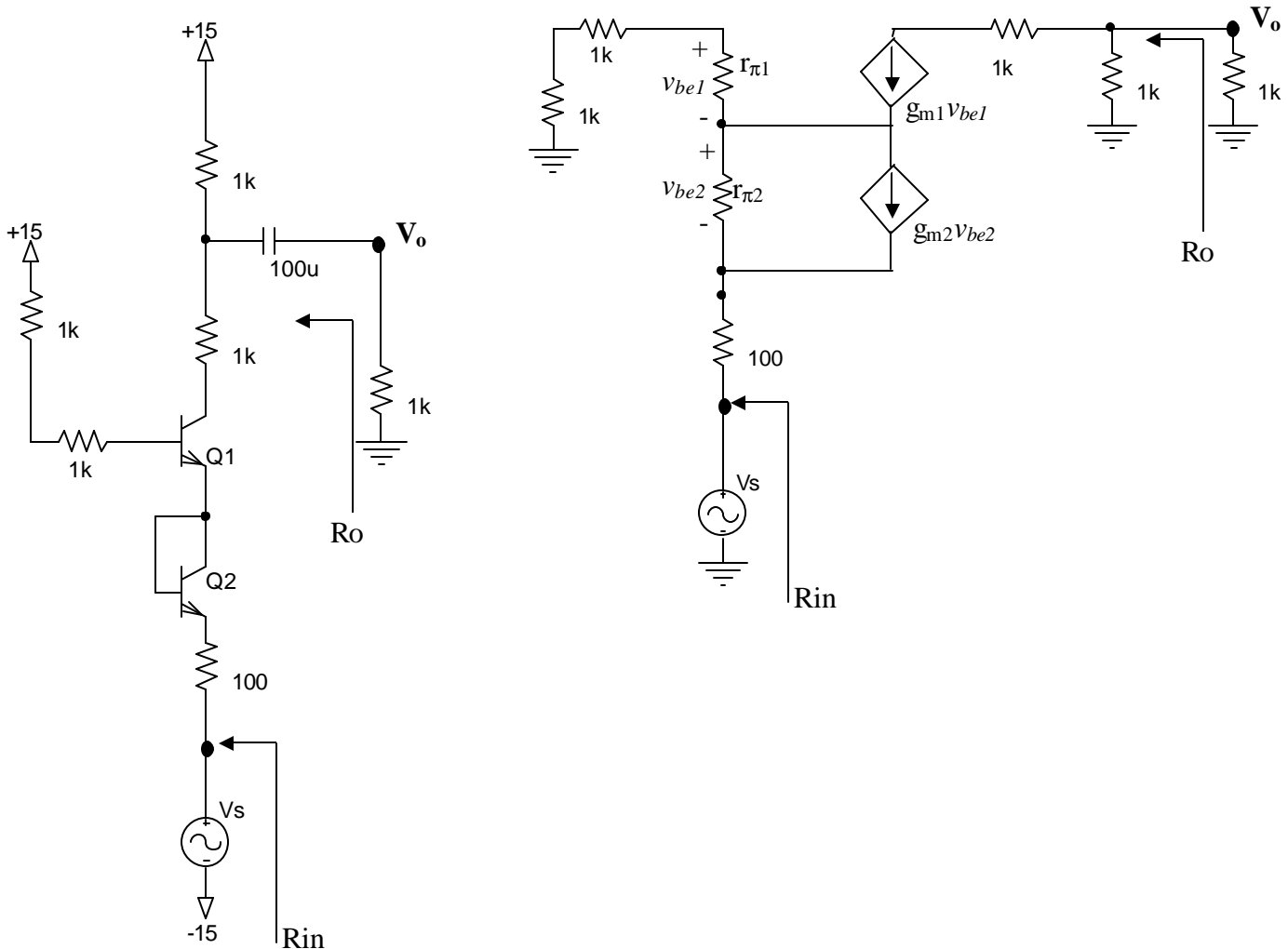- (a) Find the ac parameters
 - a. $r_{\pi 1}$ (3 points)
 - b. $r_{\pi 2}$ (3 points)
 - c. g_{m1} (3 points)
 - d. g_{m2} (3 points)
- (b) Find that input resistance, R_{in} . (Ignore the AC input source V_s , include the 100 ohm) (12 points)
- (c) Find the output resistance, R_o . (Ignore the load resistor of 1k to the right of arrow) (6 points)
- (d) Find the overall gain, V_o/V_s . (25 points)



There are 3 problems total – make sure to show all your work


Problem 1 – (48 points)

Use $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$ (V_s is an ac source).

(b) Find the DC values for the following (30 points)

- a. I_{E3} (12 points)
- b. I_{C4} (3 points)
- c. I_{B4} (5 points)
- d. V_{C4} (5 points)
- e. V_{B2} (5 points)

(c) Draw the small-signal model for the circuit below. (use hybrid- π or Model-T). Make sure to label all the nodes shown in the circuit and mark the difference between each transistor (i.e. use g_{m1} , g_{m2} , g_{m3} , etc.) DO NOT ignore r_o . (18 points)

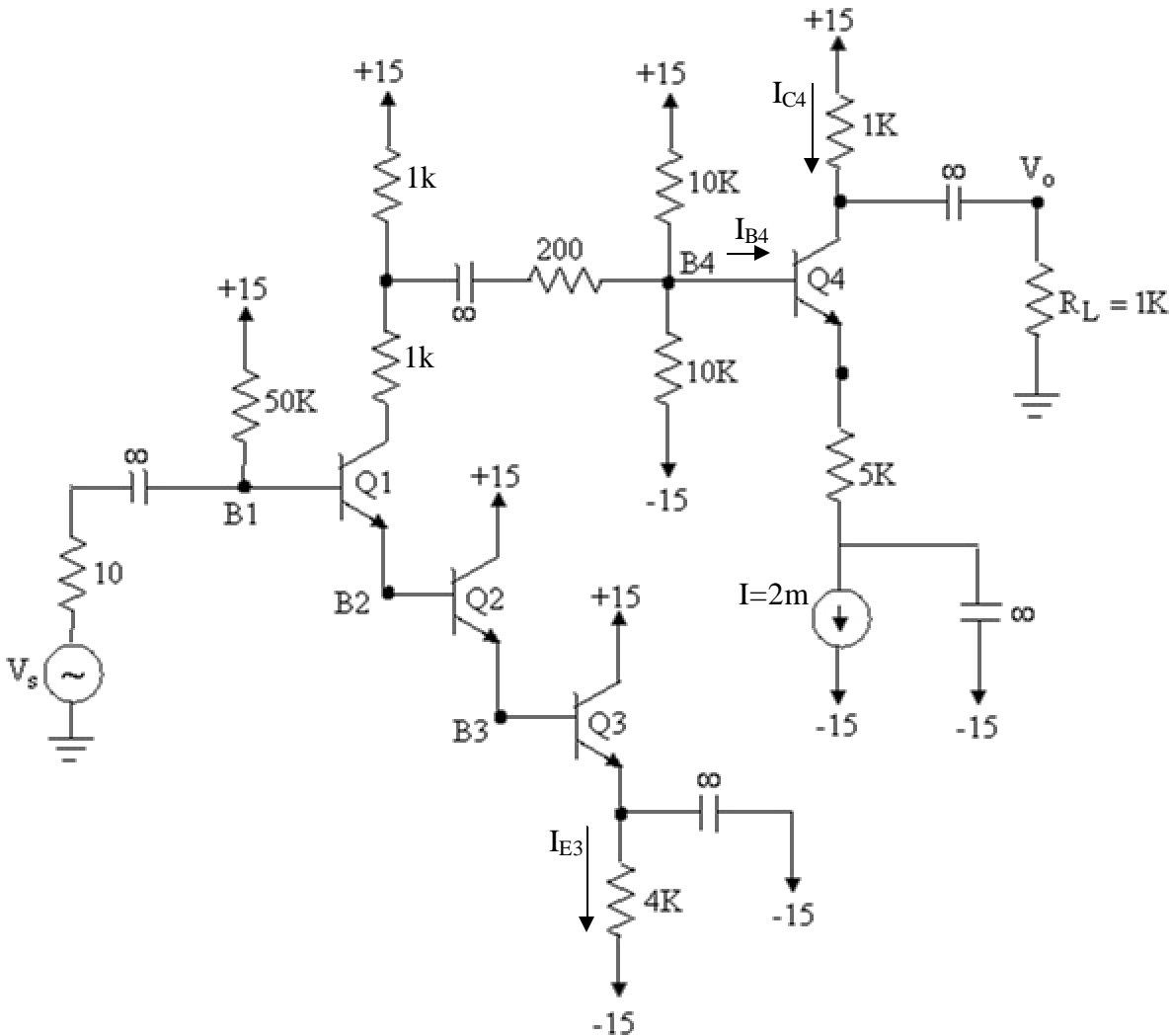


Problem 2 – (47 points)

Use $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$ (V_s is an ac source), ignore r_o .

This small-signal model comes from a circuit that has 2 transistors Q1 and Q2 denoted below as subscripts 1 and 2. It was found that $I_{E1}=2.525\text{m}$ and $I_{E2}=1.2625\text{m}$.

- (e) Find the ac parameters (12 points)
- $r_{\pi 1}$ (3 points)
 - $r_{\pi 2}$ (3 points)
 - g_{m1} (3 points)
 - g_{m2} (3 points)
- (f) Find R_{in} . (11 points)
- (g) Find R_{out} . (6 points)
- (h) Find the overall gain, V_o/V_s . (18 points)

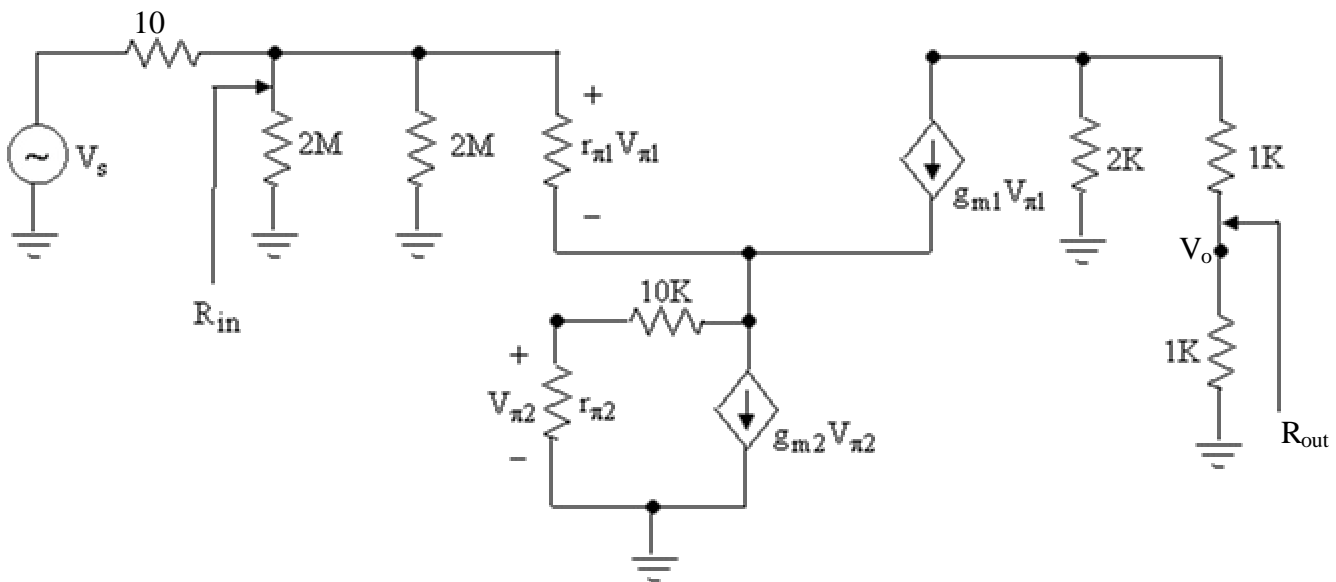

Problem 3 – (5 points)

Use $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$ (V_s is an ac source), ignore r_o .

Will this circuit work as an amplifier? Why or why not?

