

Problem Session #2

Problem 2 – (25 points)

- a) Sketch the Bode (both magnitude & phase) plot for: {label all critical values for both magnitude and phase and show all your work}

$$H(s) = \frac{-10(s^2)}{(s + 10k)^2}$$



- b) What is the estimated magnitude value at $\omega=50k$ rad/sec (in dB):

20dB

- c) What range of frequency will this circuit operate correctly:

$\omega \geq 10k$


$$H(s) = \frac{-10(s^2)}{(s+10k)^2} = \frac{-10s^2}{(10k)^2 \left(\frac{s}{10k} + 1\right)^2}$$

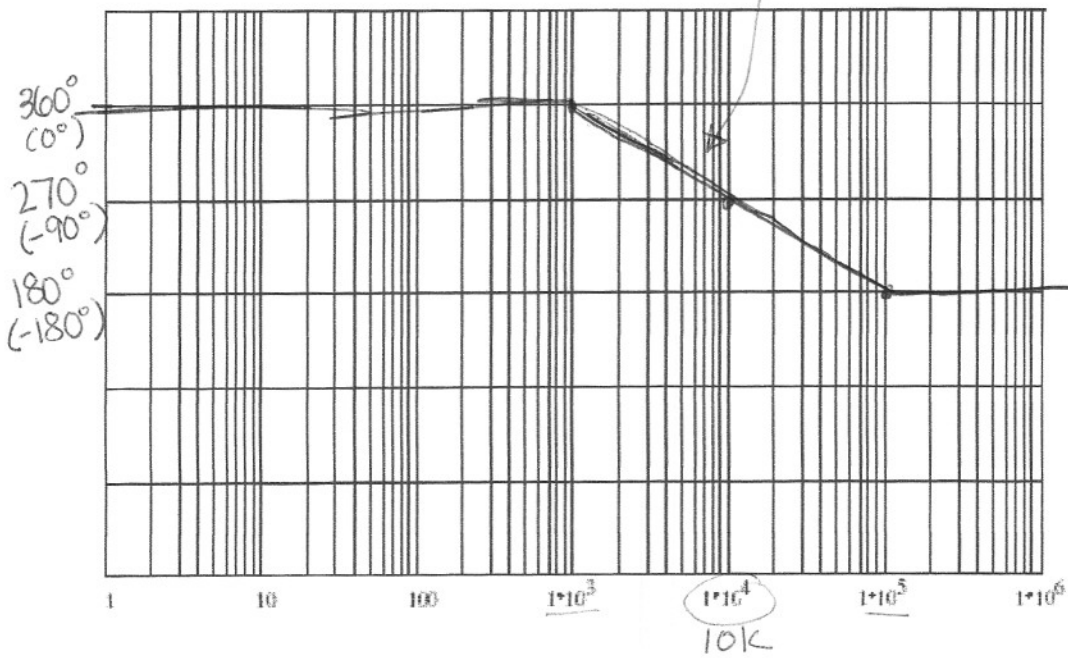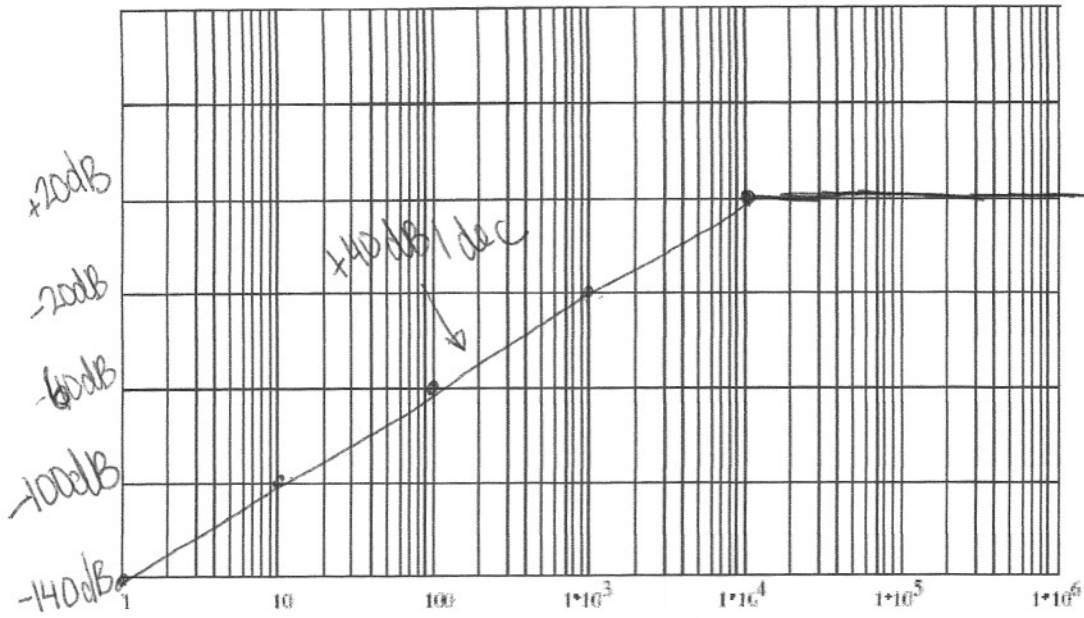

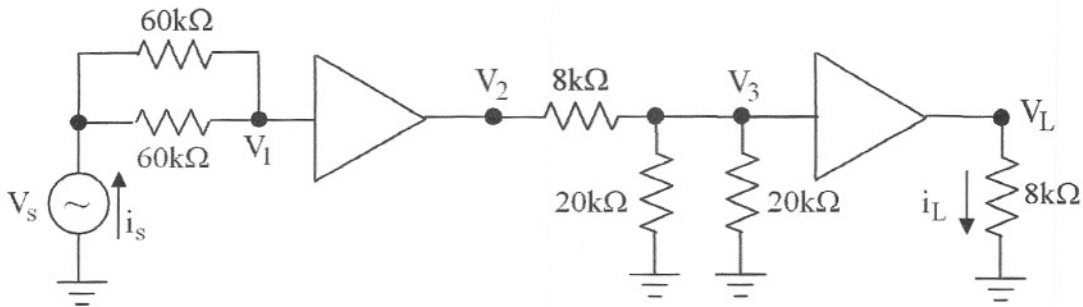
Problem 4 – (15 points)

v_s is an AC signal. Both amplifiers have the following characteristics:

$A_{vo}=20$, $R_i=10k\Omega$, $R_o=2k\Omega$, Clipping levels: $L=\pm 12V$ (unloaded)



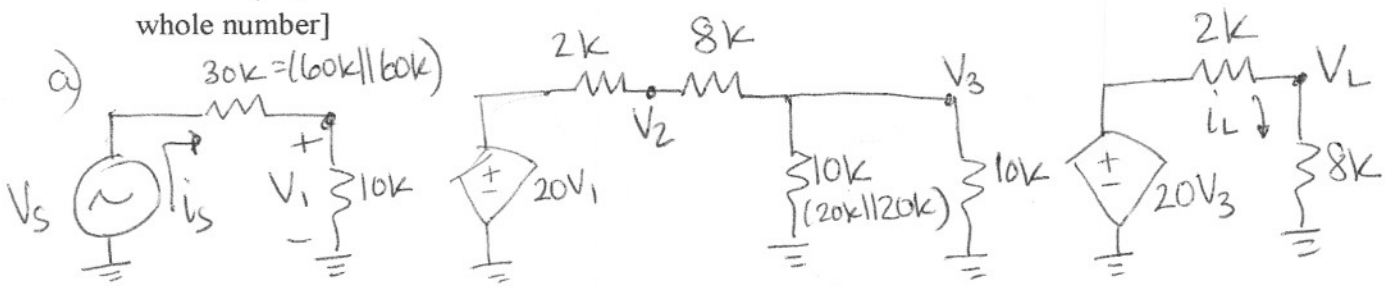- Redraw this 2 stage amplifier using the amplifier model. Make sure to label V_s , V_1 , V_2 , V_3 , and V_0 on the schematic.
- Find $A_v = \frac{v_L}{v_s}$. Express your answer as a ratio (V/V) and in dB. [Round answer to the nearest whole number]
- Find $A_i = \frac{i_L}{i_s}$. Express your answer as a ratio (A/A) and in dB. [Round the answer to the nearest whole number]



$$b) \quad V_L = \frac{8k \cdot 20V_3}{10k} = \frac{4}{5} \cdot 20V_3$$

$$V_3 = \frac{5k \cdot 20V_1}{5k + 10k} = \frac{1}{3} \cdot 20V_1$$

$$V_1 = \frac{V_s \cdot 10k}{40k} = \frac{1}{4} \cdot V_s$$

$$\frac{V_L}{V_s} = \left(\frac{4}{5}\right)(20)\left(\frac{1}{3}\right)(20)\left(\frac{1}{4}\right)$$


$$\frac{V_L}{V_s} = \frac{4}{3}(20) = \frac{80V}{3} \approx 29dB$$

$$c) \quad V_L = i_L \cdot 8k, \quad V_s = i_s \cdot (40k)$$

$$\therefore \frac{V_L}{V_s} = \frac{i_L \cdot 8k}{i_s \cdot 40k} = \frac{80}{3} \quad \therefore \frac{i_L}{i_s} = \frac{80}{3} \left(\frac{40}{8}\right) = \frac{400V}{3} \approx 43dB$$

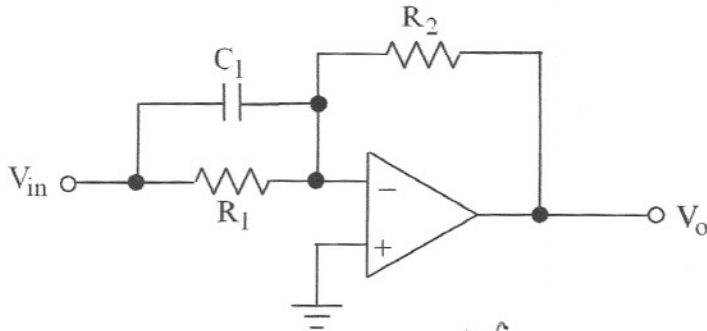Problem 5 – (10 points)

Analyze the circuit below to obtain the transfer function, V_o/V_{in} . Assume ideal opAmp.



Inverting amplifier \Rightarrow



$$\frac{V_o}{V_{in}} = - \frac{R_2}{R_1 \parallel \frac{1}{C_1 s}}$$

$$R_1 \parallel \frac{1}{C_1 s} = \left[\frac{R_1 \left(\frac{1}{C_1 s} \right)}{R_1 + \frac{1}{C_1 s}} \right] \frac{C_1 s}{C_1 s} = \frac{R_1}{(R_1 C_1 s + 1)}$$

$$\therefore \frac{V_o}{V_{in}} = - \frac{R_2 (R_1 C_1 s + 1)}{R_1}$$

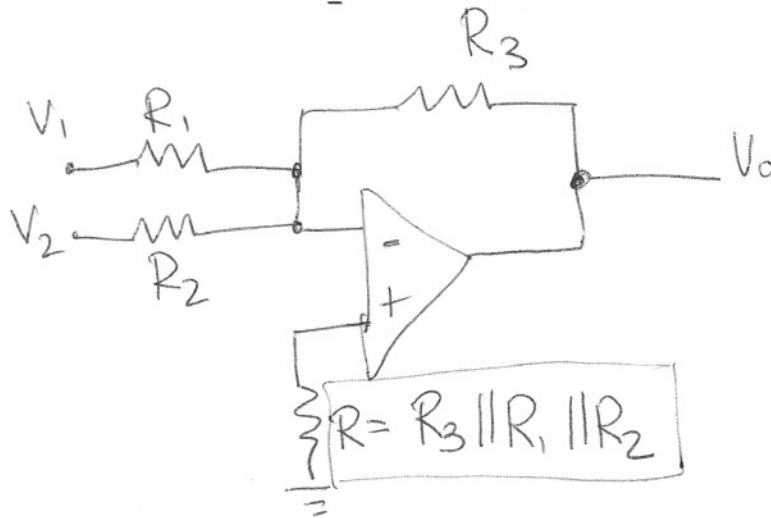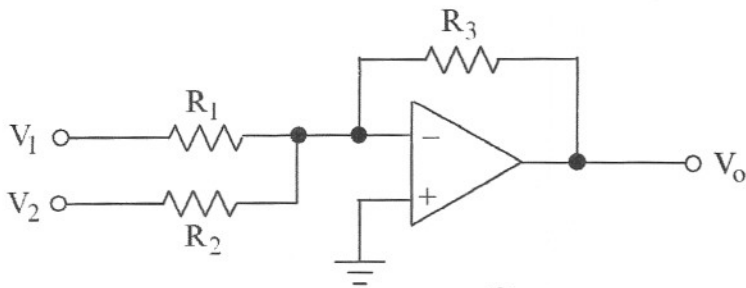
Problem 6 – (5 points)

Explain in detail, by giving exact values and drawing any schematics, the technique used to reduce the **input bias current** for the circuit below.



2
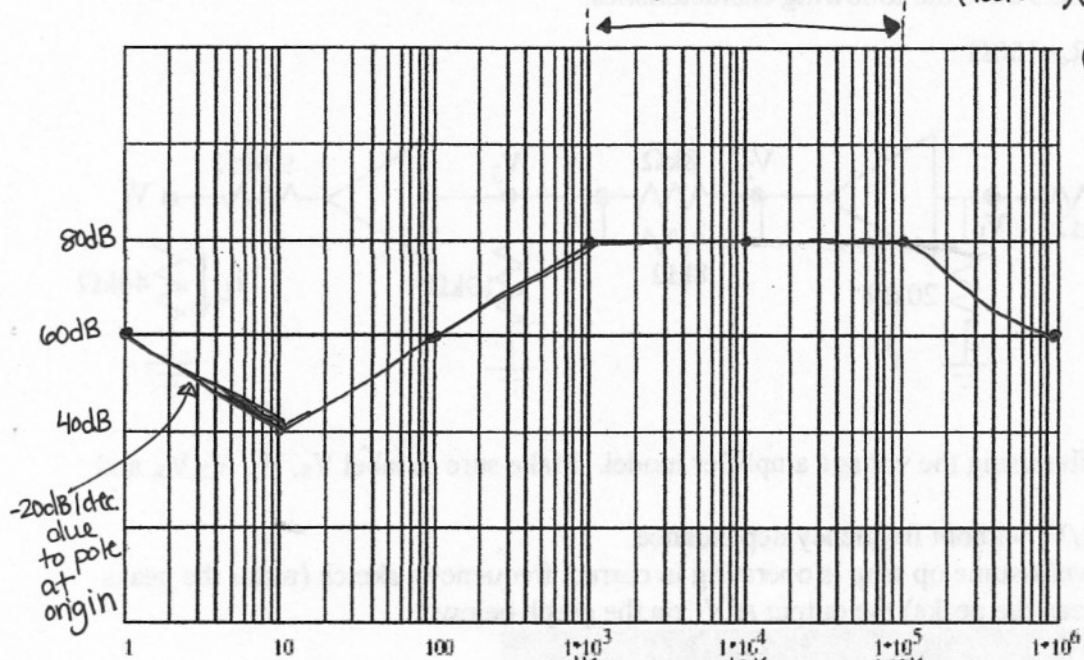
$$H(s) = \frac{1 \times 10^9 (s+10)^2}{s(s+100k)(s+1k)} = \frac{1 \times 10^9 (10)(10) \left(\frac{s}{10} + 1\right) \left(\frac{s}{10} + 1\right)}{s \cdot 100k \cdot 1k \left(\frac{s}{100k} + 1\right) \left(\frac{s}{1k} + 1\right)} = \frac{1,000 \left(\frac{s}{10} + 1\right) \left(\frac{s}{10} + 1\right)}{s \left(\frac{s}{100k} + 1\right) \left(\frac{s}{1k} + 1\right)}$$



① $10 \Rightarrow +20\text{dB/dec} \times 2$
 $+45^\circ \times 2$ between $\omega = 1$ to 100


$1k \Rightarrow -20\text{dB/dec}$
 -45° between $\omega = 100$ to $10k$

$100k \Rightarrow -20\text{dB/dec}$
 -45° between $\omega = 10k$ to 1Meg .

magnitude at $\omega = 1 \Rightarrow$
 $\frac{1,000 \left[\sqrt{\left(\frac{1}{10}\right)^2 + 1^2} \right]^2}{1 \cdot \sqrt{\left(\frac{1}{100k}\right)^2 + 1^2} \cdot \sqrt{\left(\frac{1}{1k}\right)^2 + 1^2}} = 1,000$
 60dB
 slope is -20dB/dec through $\omega = 1$ at 60dB

-20dB/dec due to pole at origin


at $\omega = 20k$, magnitude = $80\text{dB} = 100\text{V/V}$ circuit operates between $\omega = 1k$ to $\omega = 100k$

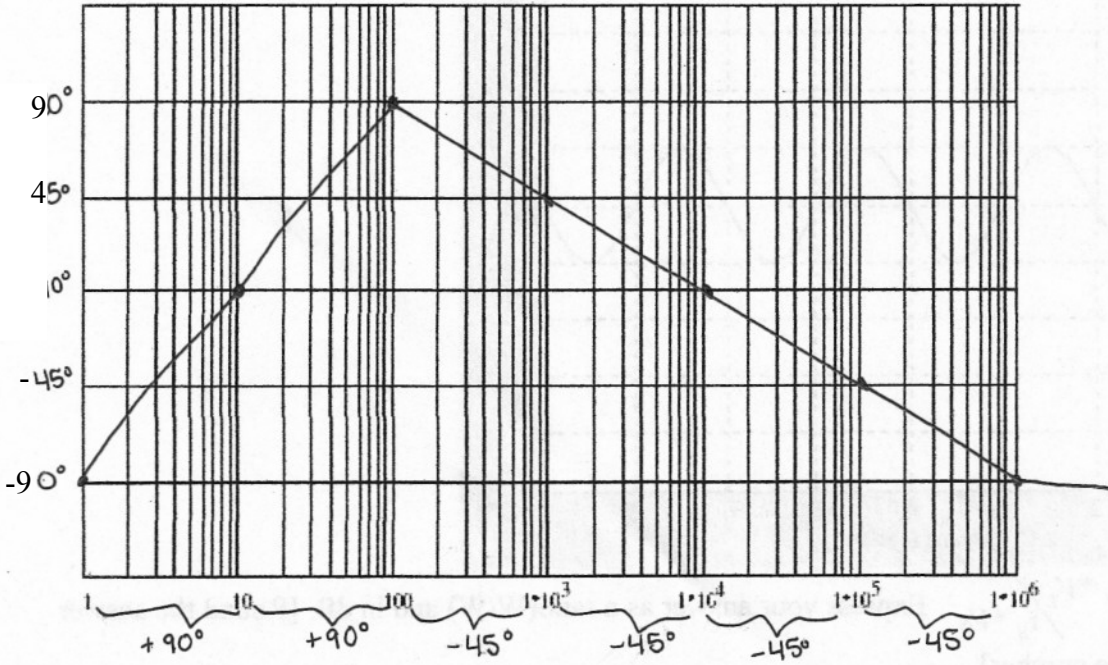

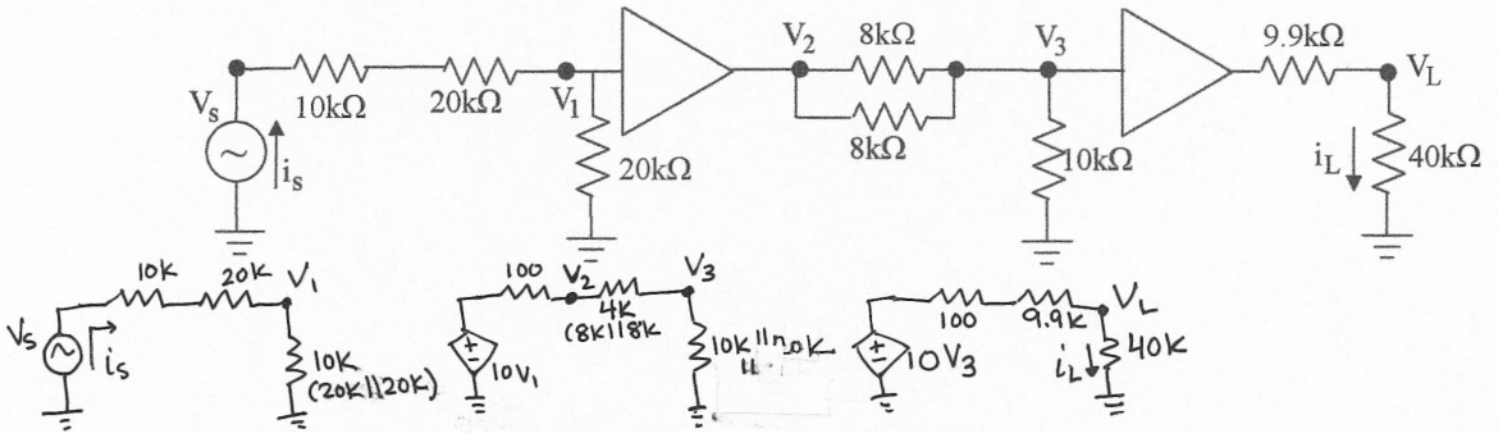Problem 3 – (20 points)

V_s is an AC signal. Both amplifiers have the following characteristics:

$$A_{vo}=10, \quad R_{in}=20k\Omega, \quad R_o=100\Omega$$



$$V_L = \frac{10V_3 (40k)}{50k} = 8V_3$$

$$\frac{V_L}{V_s} = 8 \cdot 6.2 \cdot \frac{1}{4} \approx \boxed{12.4 \text{ V/V}}$$

$$V_3 = \frac{10V_1 (6.7k)}{6.7k + 100 + 4k} \approx 6.2V_1$$

$$V_1 = \frac{V_s \cdot 10k}{10k + 30k} = \frac{1}{4} V_s$$


$$i_L = \frac{V_L}{40k}$$

$$i_s = \frac{V_s}{40k}$$

$$\therefore A_p = \frac{i_L \cdot V_L}{i_s \cdot V_s} = \frac{V_L}{40k} \cdot \frac{V_L}{V_s} \cdot \frac{40k}{V_s}$$

$$A_p = (12.4)^2 \approx \boxed{154 \text{ W/W}}$$
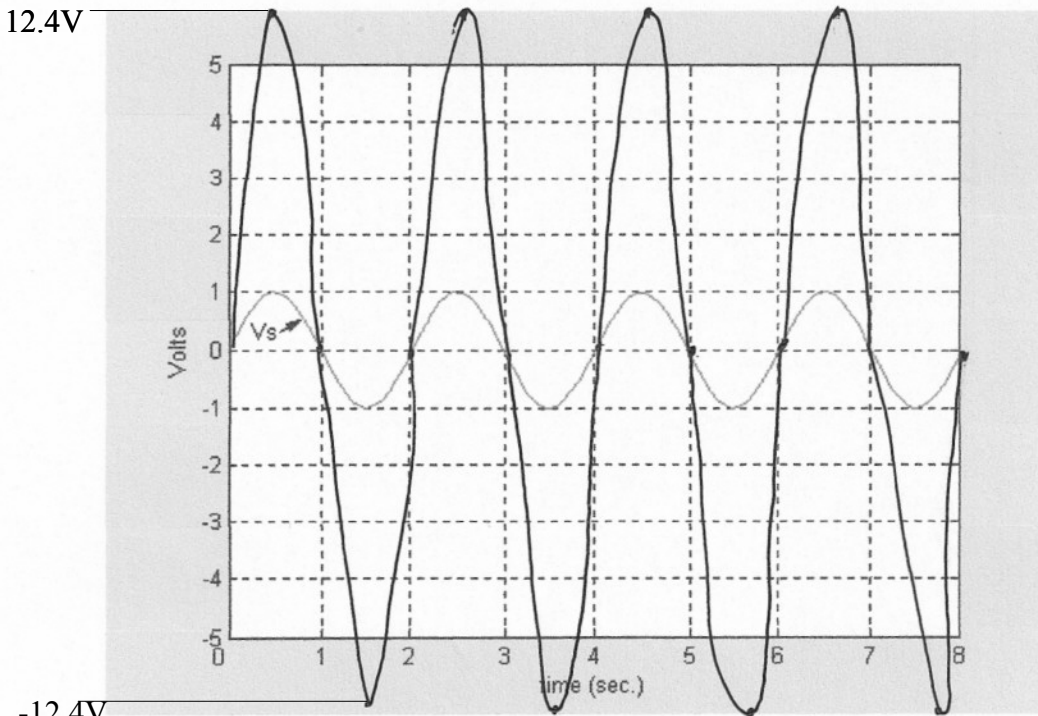
$$10 \log(154) \approx \boxed{22 \text{ dB}}$$




No clipping on output
 signal if power supply
 voltages are $> 12.5V$
 Otherwise, the output will
 clip.

- (a) Find $A_p = \frac{P_L}{P_s} = \frac{i_L \cdot V_L}{i_s \cdot V_s}$. Express your answer as a ratio(W/W) and in dB. [Round the answer to the nearest whole number]

Problem 4 – (15 points)

Use the circuit below:

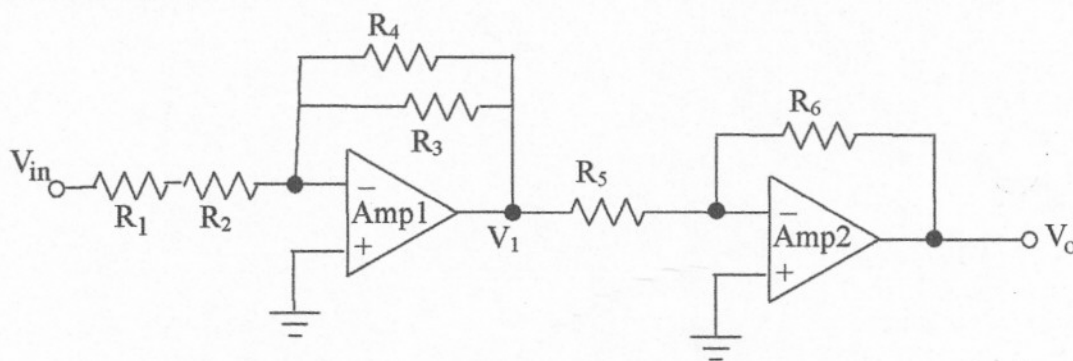

Use $f_T = 5\text{MHz}$ for both amplifiers.

State the overall transfer function (V_o/V_{in}) in terms of R_1 , R_2 , R_3 , R_4 , R_5 , and R_6 .

$$\frac{V_o}{V_{in}} = \frac{+ \frac{R_6}{R_5} \cdot \frac{(R_4 || R_3)}{R_1 + R_2}}{\left(1 + \frac{s}{\left(\frac{5\text{MHz}}{R_6/R_5}\right)}\right) \left(1 + \frac{s(R_4 || R_3)}{5\mu(R_1 + R_2)}\right)}$$

Problem 5 – (10 points)

Redraw or add to the schematic below to show how to reduce the effect of the **input bias current**. State the symbolic value(s) of any components added to the schematic. State the answer in terms of R_1 , R_2 , R_3 , and R_4 .

