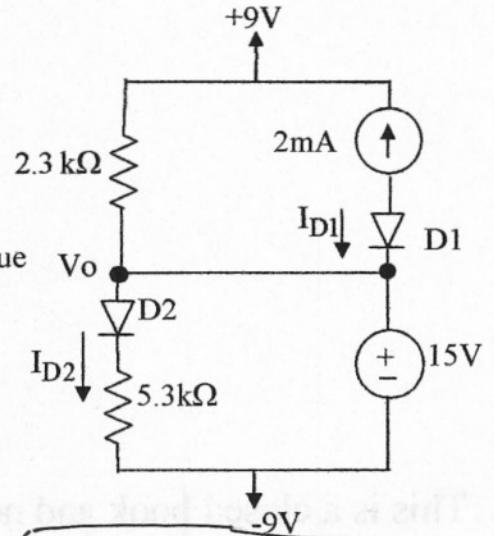



Problem 1 – (30 points)

Assume all diodes are identical and have $V_{DO}=0.7V$, $n=1$, and $V_T=25mV$. Use the constant voltage drop method. Verify that your assumption for the diode operation (i.e. on or off) are correct. Find the following making sure you find the correct operation of the diodes.

- State your assumptions (diode is on/off).
- The current I_{D1}
- The current I_{D2}
- The voltage V_o
- Your verification to prove your assumptions for the diodes are correct.
- If there is noise on the $-9V$ supply of $\pm 1V$, what is the total value for I_{D2} (the AC current through diode, D_2). {Hint: remember to use the AC model for the diode}



Assume D_1 off and D_2 on

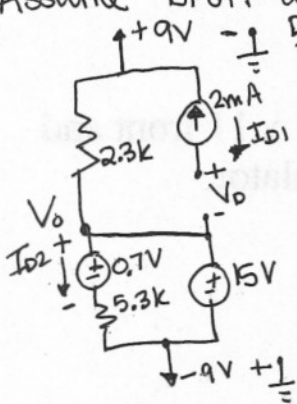

DC: $I_{D1} = -2mA$ \therefore NOT on $I_{D1} < 0$
 \rightarrow can not check V_o

$$+15 - 0.7 - I_{D2}(5.3k) = 0$$

$$I_{D2} = \frac{14.3}{5.3k} = 2.7m$$


$I_{D2} > 0 \therefore$ ON

$I_{D1} = 0$

$$-9 + 15 - V_o = 0$$

$V_o = +6V$

AC:

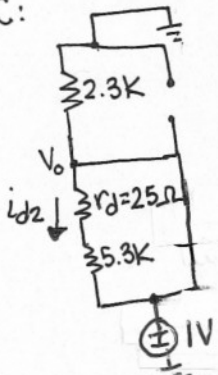


$$r_d = \frac{nV_T}{I_{D2}} = \frac{1(25m)}{2.7m} = 9.3ohm$$

$$i_{d2} = \frac{0}{5.3k + 9.3} = 0 A_{AC}$$

$I_{D2} = 2.7m$

\therefore no ac contribution

other case
 D_1 off, D_2 off

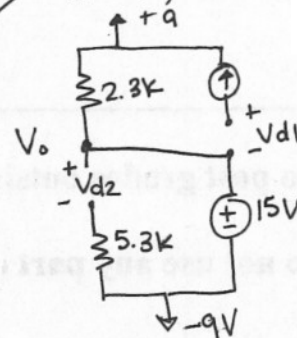

$$+15 - V_{d2} = 0$$


$$V_{d2} = +15V$$

$$V_{d2} > 0.7$$

\therefore Not off

2
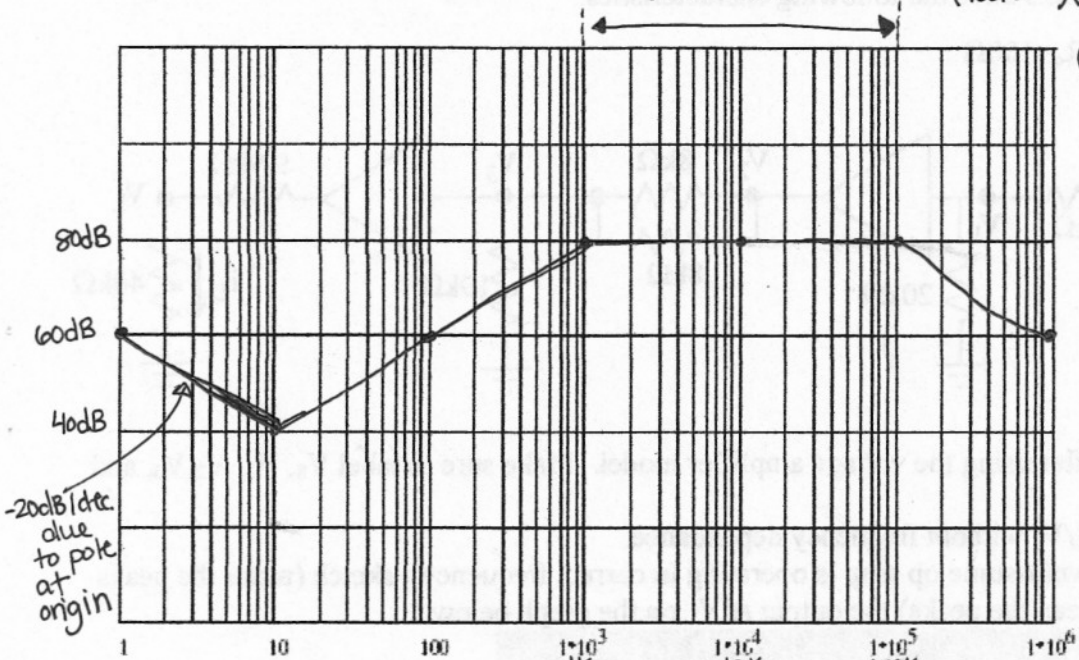
$$H(s) = \frac{1 \times 10^9 (s+10)^2}{s(s+100k)(s+1k)} = \frac{1 \times 10^9 (10)(10) \left(\frac{s}{10} + 1\right) \left(\frac{s}{10} + 1\right)}{s \cdot 100k \cdot 1k \left(\frac{s}{100k} + 1\right) \left(\frac{s}{1k} + 1\right)} = \frac{1,000 \left(\frac{s}{10} + 1\right) \left(\frac{s}{10} + 1\right)}{s \left(\frac{s}{100k} + 1\right) \left(\frac{s}{1k} + 1\right)}$$




10 ⇒ +20dB/dec * 2
+45° * 2 between
ω = 1 to 100

1k ⇒ -20dB/dec.
-45° between
ω = 100 to 10k

100k ⇒ -20dB/dec.
-45° between
ω = 10k to 1Meg.

magnitude at ω = 1 ⇒
 $1,000 \left[\sqrt{\left(\frac{1}{10}\right)^2 + 1^2} \right]^2 = 1,000$
 $1 \cdot \sqrt{\left(\frac{1}{100k}\right)^2 + 1^2} \cdot \sqrt{\left(\frac{1}{1k}\right)^2 + 1^2} = 60dB$
slope is -20dB/dec
through ω = 1 at 60dB


at ω = 20k, magnitude = $80dB = 100V/V$ circuit operates between ω = 1k to ω = 100k

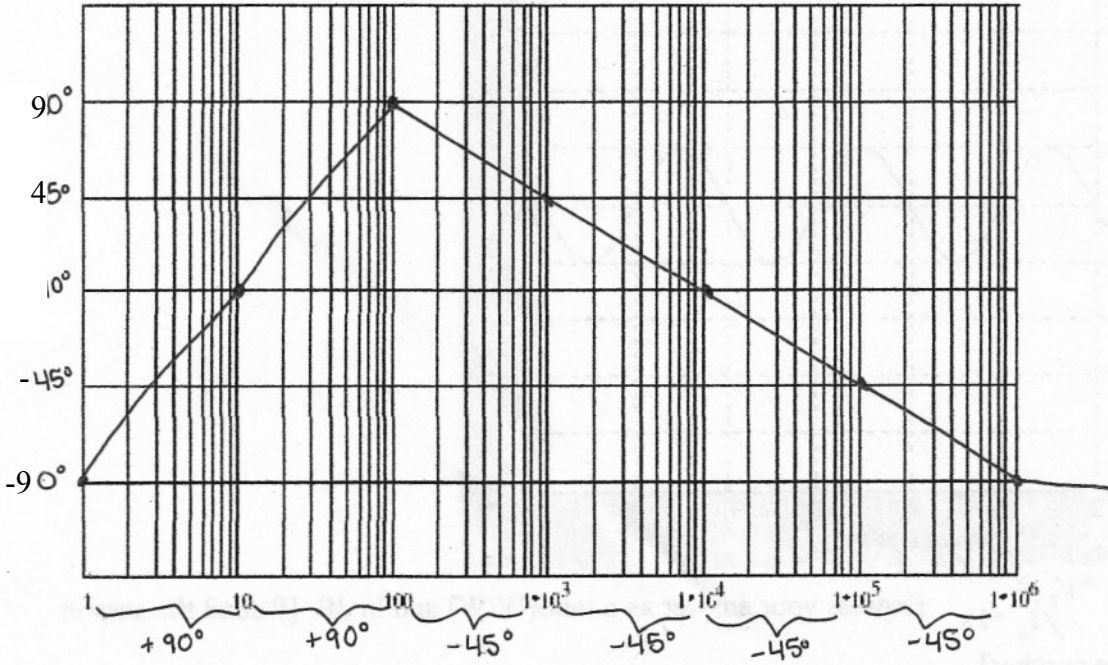

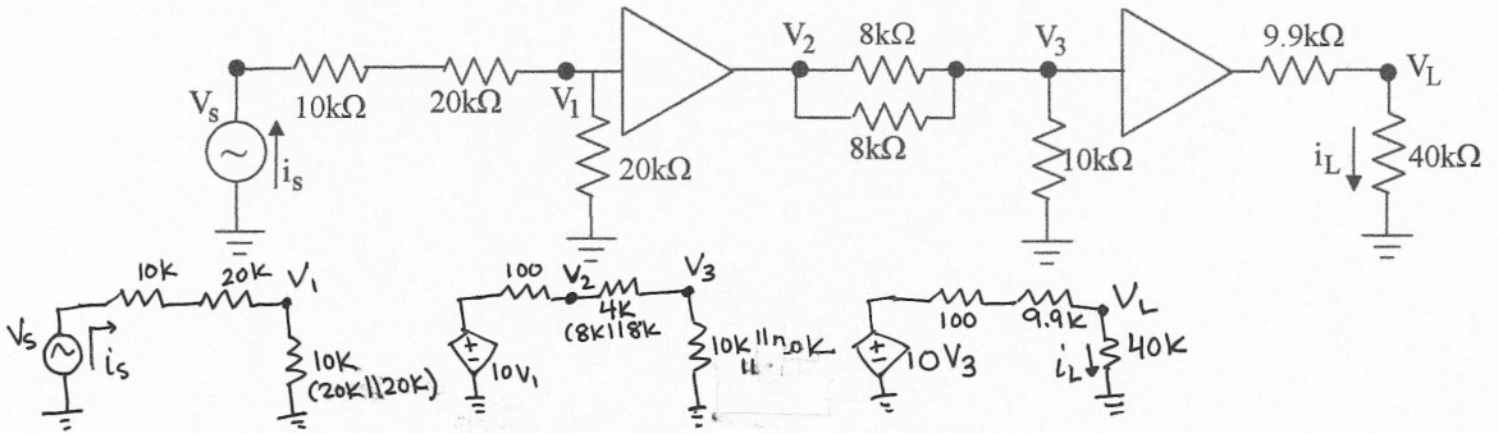Problem 3 – (20 points)

V_s is an AC signal. Both amplifiers have the following characteristics:

$$A_{vo}=10, \quad R_{in}=20k\Omega, \quad R_o=100\Omega$$



$$V_L = \frac{10V_3 (40k)}{50k} = 8V_3$$

$$\frac{V_L}{V_s} = 8 \cdot 6.2 \cdot \frac{1}{4} \approx \boxed{12.4 \text{ V/V}}$$

$$V_3 = \frac{10V_1 (6.7k)}{6.7k + 100 + 4k} \approx 6.2V_1$$

$$V_1 = \frac{V_s \cdot 10k}{10k + 30k} = \frac{1}{4} V_s$$


$$i_L = \frac{V_L}{40k}$$

$$i_s = \frac{V_s}{40k}$$

$$\therefore A_p = \frac{i_L \cdot V_L}{i_s \cdot V_s} = \frac{V_L}{40k} \cdot \frac{V_L}{V_s} \cdot \frac{40k}{V_s}$$

$$A_p = (12.4)^2 \approx \boxed{154 \text{ W/W}}$$
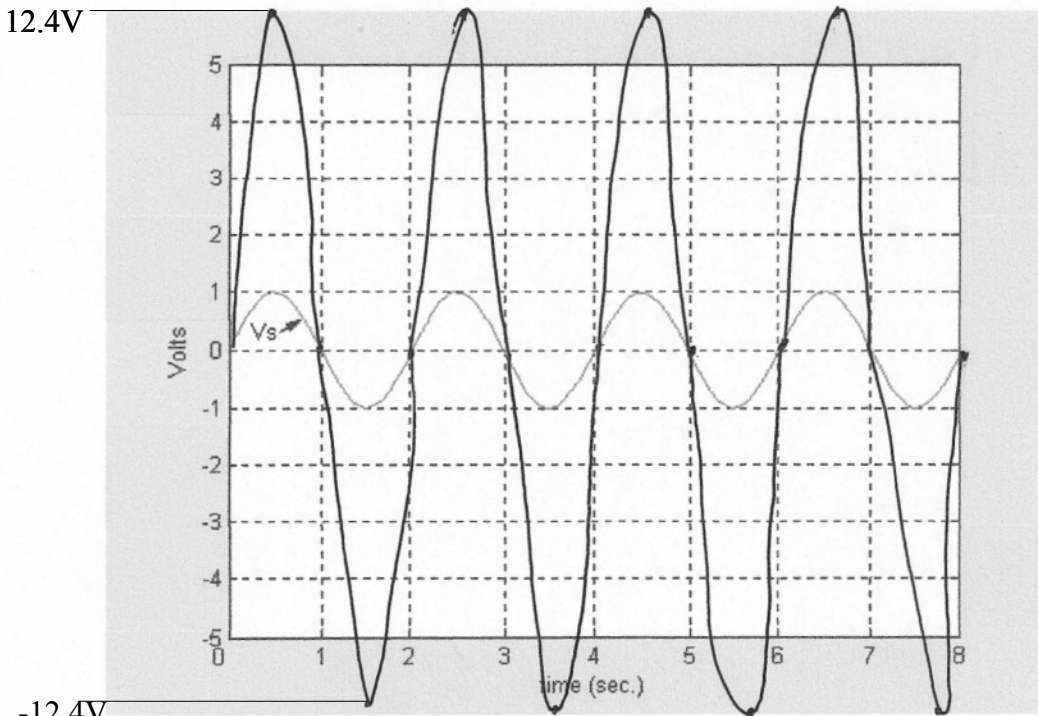
$$10 \log(154) \approx \boxed{22 \text{ dB}}$$




No clipping on output
 signal if power supply
 voltages are $> 12.5V$
 Otherwise, the output will
 clip.

- (a) Find $A_p = \frac{P_L}{P_s} = \frac{i_L \cdot V_L}{i_s \cdot V_s}$. Express your answer as a ratio(W/W) and in dB. [Round the answer to the nearest whole number]

Problem 4 – (15 points)

Use the circuit below:

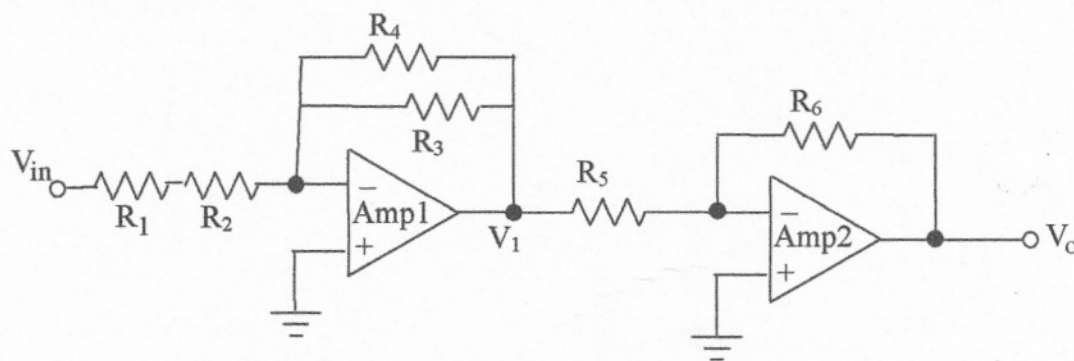

Use $f_T = 5\text{MHz}$ for both amplifiers.

State the overall transfer function (V_o/V_{in}) in terms of R_1 , R_2 , R_3 , R_4 , R_5 , and R_6 .

$$\frac{V_o}{V_{in}} = \frac{+ \frac{R_6}{R_5} \cdot \frac{(R_4 || R_3)}{R_1 + R_2}}{\left(1 + \frac{s}{\left(\frac{5\text{MHz}}{R_6/R_5}\right)}\right) \left(1 + \frac{s(R_4 || R_3)}{5\mu(R_1 + R_2)}\right)}$$

Problem 5 – (10 points)

Redraw or add to the schematic below to show how to reduce the effect of the **input bias current**. State the symbolic value(s) of any components added to the schematic. State the answer in terms of R_1 , R_2 , R_3 , and R_4 .

