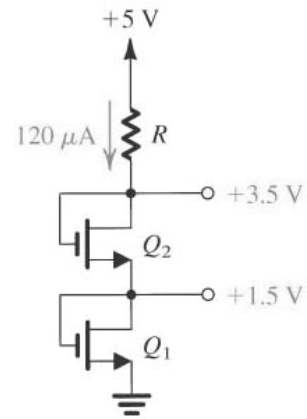


Problem Session 4

Problem 1:

The NMOS transistors in the circuit at right have $V_t=1V$, $\mu_n C_{ox}=120 \mu A/V^2$, $\lambda=0$, and $L_1=L_2=1\mu m$. Find the required values of gate width for each Q_1 and Q_2 , and the value of R , to obtain the voltage and current values indicated.



Solution:

$$V_{D2} = 3.5 \text{ V}$$

$$R = \frac{V_{DD} - V_{D2}}{I_D}$$

$$R = \frac{5 - 3.5}{120 \mu A}$$

$$R = 12.5 \text{ K}\Omega$$

Gate and drain Q_2 at same potential, hence Q_2 in saturation region

$$V_{G2} = V_{D2} = 3.5 \text{ V}$$

$$V_{GS2} = V_{G2} - V_{S2} = 3.5 - 1.5 \text{ V}$$

$$V_{GS2} = 2 \text{ V}$$

$$I_D = \frac{1}{2} \times \mu_n C_{ox} \frac{W_2}{L_2} (V_{GS2} - V_t)^2$$

$$120 = \frac{1}{2} \times 120 \times \frac{W_2}{1 \mu m} (2 - 1)^2$$

$$W_2 = 2 \mu m$$

Gate and drain of Q_1 at same potential, hence Q_1 in saturation region

$$V_{GS1} = 1.5 \text{ V}$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{GS1} - V_t)^2$$

$$120 = \frac{1}{2} \times 120 \times \frac{W_1}{1 \mu m} (1.5 - 1)^2$$

$$W_1 = 8 \mu m$$

Problem 2:

The PMOS transistor in the circuit shown at right have $k_p' = 8\mu\text{A}/\text{V}^2$, $W/L = 25$, and $|V_{tp}| = 1\text{V}$. For $I = 100\text{mA}$, find the voltages V_{SD} and V_{SG} for $R = 0$, $10\text{k}\Omega$, $30\text{k}\Omega$, and $100\text{k}\Omega$. What value of R is $V_{SD} = V_{SG}$?

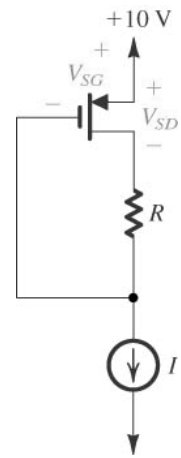

$$\text{Also, } V_{SD} + IR = V_{SG}$$

$$\Rightarrow V_{SD} = V_{SG} - IR$$

$$\Rightarrow IR \leq |V_t| \text{ For PMOS to be in saturation}$$

(A) $R = 0$

$$IR = 0 < |V_t|$$

Saturation :

$$I = 100 = \frac{1}{2} \times 8 \times 25 \times (V_{SG} - |V_t|)^2$$

$$V_{SG} - 1 = \pm 1$$

$$V_{SG} = 2\text{ V} = V_{SD}$$

(B) $R = 10\text{ K}\Omega$

$$IR = 10 \times 0.1 = 1\text{ V}$$

\Rightarrow Saturation

$$V_{SG} = 2\text{ V}$$

$$V_{SD} = 2 - 1 = 1\text{ V}$$

(C) $R = 30\text{ K}\Omega$

$$IR = 30 \times 0.1$$

$$= 3\text{ V}$$

\Rightarrow Triode region

$$100 = 8 \times 25 \left[(V_{SG} - |V_t|) V_{SD} - \frac{1}{2} V_{SD}^2 \right]$$

$$0.5 = \left[(V_{SG} - 1)(V_{SG} - 3) - \frac{1}{2} (V_{SG} - 3)^2 \right]$$

$$0.5 = 0.5 V_{SG}^2 - V_{SG} - 1.5$$

$$V_{SG}^2 - 2 V_{SG} - 4 = 0$$

$$V_{SG} = 3.24\text{ V}, -1.2\text{ V}$$

$$V_{SD} = 3.24 - 3 = 0.24\text{ V}$$


$$\begin{aligned}
 (D) \quad R &= 100 \text{ k}\Omega \\
 IR &= 100 \times 0.1 \\
 &= 10 \text{ V} \\
 &\Rightarrow \text{Triode region} \\
 100 &= 8 \times 25 \left[(V_{SG} - 1)(V_{SG} - 10) - \frac{1}{2}(V_{SG} - 10)^2 \right] \\
 0.5 &= 0.5 V_{SG}^2 - V_{SG} - 40 \\
 V_{SG}^2 - 2V_{SG} - 81 &= 0 \\
 V_{SG} &= 10.1 \text{ V} \\
 V_{SD} &= 0.1 \text{ V}
 \end{aligned}$$

$V_{SD} = V_{SG}$ when $R=0$

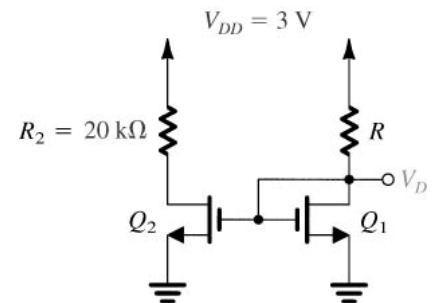Problem 3:

Let Q_1 and Q_2 have $V_t = 0.6 \text{ V}$, $\mu_n C_{ox} = 200 \mu\text{A/V}^2$, $\lambda = 0$, $L_1 = L_2 = 0.8 \mu\text{m}$, and $W_1 = 8 \mu\text{m}$.

- Establish a current 0.2 mA in Q_1 . Find R .
- Find W_2 and a new value for R_2 so that Q_2 operates in the saturation region with a current of 0.5 mA and drain voltage of 1 V .



(a)

$$\begin{aligned}
 i_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 \\
 \text{We know that } i_{D1} &= 0.2 \text{ mA} \\
 0.2 \times 10^{-3} &= \frac{1}{2} \times 200 \times 10^{-6} \times \frac{8}{0.8} (V_{GS1} - 0.6)^2 \\
 V_{GS1} - 0.6 &= \sqrt{0.2} \\
 V_{GS1} &= 1.047 \text{ V} \\
 V_{GS1} &= 1.05 \text{ V} \\
 \text{From the circuit the value of } R \text{ is} \\
 R &= \frac{3 - 1.05}{0.2 \times 10^{-3}} \\
 R &= 9750 \Omega \\
 \boxed{R = 9.75 \text{ k}\Omega}
 \end{aligned}$$

(b)

For Q_2 to conduct with 0.5 mA

$$\begin{aligned}
 R_2 &= \frac{3 - 1}{0.5 \times 10^{-3}} \\
 R_2 &= 4000 \Omega \\
 R_2 &= 4 \text{ k}\Omega
 \end{aligned}$$

Since the gates are connected together, both transistors have the same V_{GS} and hence same i_D . In order to conduct 0.5 mA or multiply i_D by 2.5.


$$\begin{aligned}
 \frac{W_2}{W_1} &= 2.5 \\
 W_2 &= 2.5 \times 8 \times 10^{-6} \\
 \boxed{W_2 = 20 \mu\text{m}}
 \end{aligned}$$

Problem 4:

Let $V_t=2\text{V}$, $\mu_n C_{ox}(W/L)=2\text{mA/V}^2$, and $\lambda=0$

(a) Find I_D and V_D .

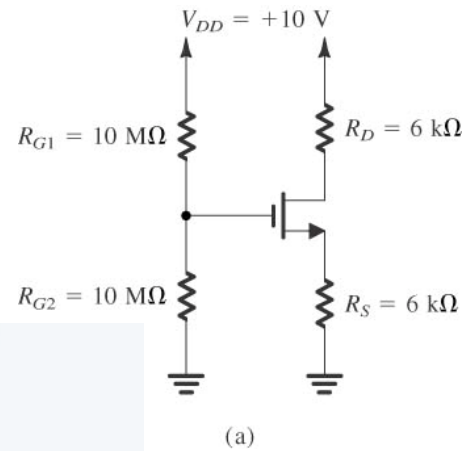(b) Compare these answers to the solution (Example 4.5) was found when $V_t=1\text{V}$, $\mu_n C_{ox}(W/L)=2\text{mA/V}^2$, and $\lambda=0$ that $I_D=0.5\text{mA}$ and $V_D=7\text{V}$. Comment on how tolerant (or intolerant) the circuit is to changes in device parameters.



Since the gate current is zero, the voltage at the gate is

$$V_G = V_{DD} \frac{R_{G2}}{R_{G1} + R_{G2}}$$

$$V_G = 10 \times \frac{10}{10 + 10}$$

$$V_G = +5 \text{ V}$$

$$V_S = 6I_D \text{ V}$$

$$V_{GS} = V_G - V_S = (5 - 6I_D) \text{ V}$$

Thus I_D , when transistor is replaced with another transistor

having $V_t = 2 \text{ V}$ and $K'_n \frac{W}{L} = 2 \text{ mA/V}^2$. Then I_D

$$I_D = \frac{1}{2} K'_n \frac{W}{L} (V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2} \times 2 \times (5 - 6I_D - 2)^2$$

$$36I_D^2 - 37I_D + 9 = 0$$

I_D has two values $I_D = 0.632$ not possible

Then

$$I_D = 0.4 \text{ mA}$$

$$V_D = V_{DD} - 6I_D$$

$$V_D = 10 - 6 \times 0.4$$

$$V_D = 7.6 \text{ V}$$