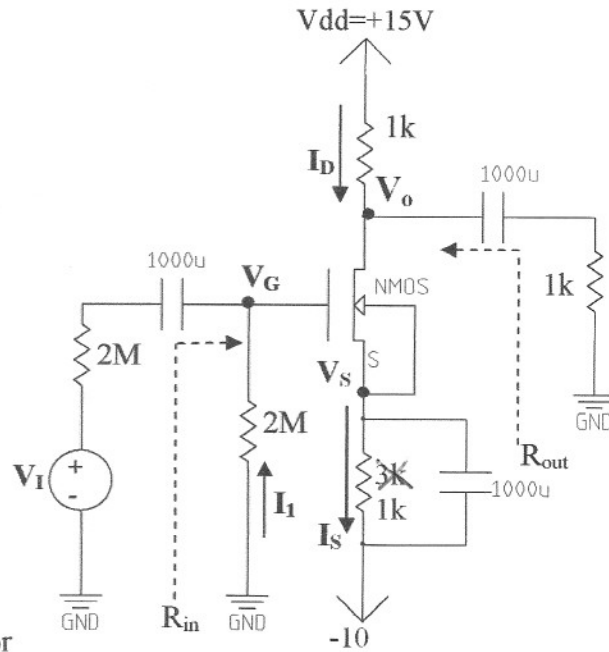


Problem 1 – (35 points)

Use: $V_t = 2V$
 $k_n'(W/L) = 50\mu A/V^2$
 $\lambda = 0$
 $V_I = 5 + 0.001\sin(10t)$

- (a) Solve for the DC currents:
- $I_1 = 0$
 - $I_D = 1.2m$
 - $I_S = I_D$
- (b) Solve for the DC voltages:
- $V_G = 0$
 - $V_S = -8.8V$
 - $V_o = 13.8V$
- (c) Verify that the transistor is saturated
- (d) State the operating point, bias point, or quiescent point for this amplifier



a. $\boxed{I_1 = 0}$ $I_D = I_S$

$$I_D = \frac{1}{2}(50\mu)(V_{GS} - V_t)^2 \quad (\text{SAT. EQ.})$$

$$V_{GS} = V_G - V_S$$

$$V_G = 0$$

$$V_S = I_D(1k) - 10$$

$$\therefore I_D = \frac{1}{2}(50\mu)(0 - I_D(1k) + 10 - 2)^2$$

$$I_D(40k) = (I_D^2(1k)^2 + 64 - 16(1k)I_D)$$

$$I_D = \frac{56k \pm \sqrt{(56k)^2 - 4(1k)^2(64)}}{2(1k)^2} = \boxed{1.2m}, 54.8m \rightarrow \text{Gives } V_{GS} \approx -45$$

$$V_S = \boxed{-8.8V}$$

d) $V_{GS} = \boxed{8.8V}$ which gives $\Rightarrow I_D = \boxed{1.2m}$

$$V_D = V_o = 15 - I_D(1k) = \boxed{13.8V}$$

$$\therefore \boxed{V_{DS} = 22.6 > (V_{GS} - V_t) = 6.8V}$$

Problem 2 – (35 points)


Use: $V_t = 1V$
 $k_n'(W/L) = 2mA/V^2$
 V_{sig} is an AC source
 Transistor 1 has DC values: $V_{GS1} = 2V$, $I_{D1} = 1mA$
 Transistor 2 has DC values: $V_{GS2} = 3V$, $I_{D2} = 4mA$
 $\lambda = 0$ (for all transistors)

For the following hybrid- π equivalent circuit, find the following values:

(a) R_i (input resistance – ignore the 10Ω and V_{sig})

(b) R_o (output resistance – ignore the $1k\Omega$ load)

(c) gain, $\frac{V_o}{V_{sig}}$

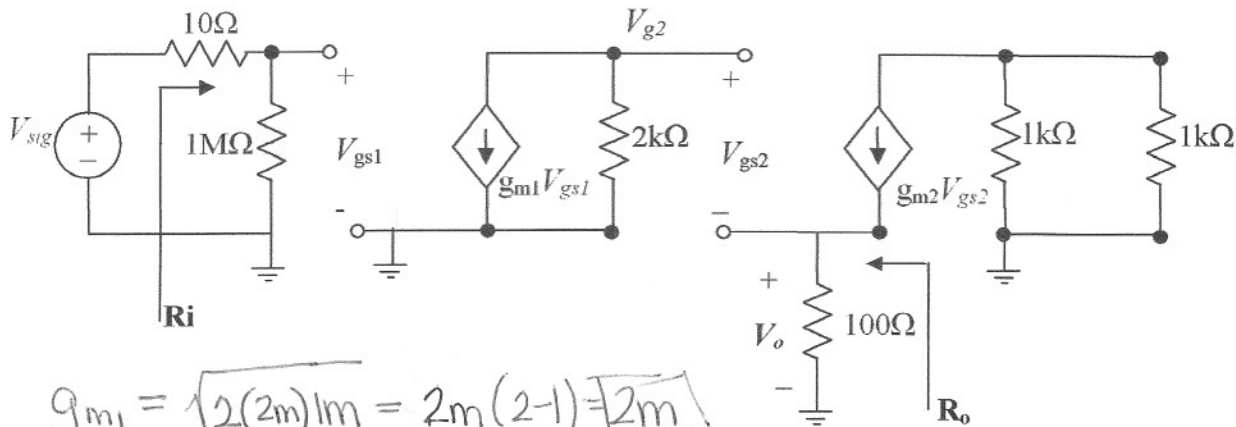

$$g_{m1} = \sqrt{2(2m)1m} = 2m(2-1) = \boxed{2m}$$

$$g_{m2} = \sqrt{2(2m)4m} = 2m(3-1) = \boxed{4m}$$

a) $\boxed{R_i = 1M}$

b) $R_o = 100\Omega \parallel \frac{1}{g_{m2}} = 100 \parallel 250 \approx \boxed{71\Omega}$

c) $V_o = +g_{m2} V_{gs2} (100)$

$$V_{gs2} = V_{g2} - V_o = -g_{m1} V_{gs1} (2k) - g_{m2} V_{gs2} (100)$$



$$V_{gs1} = \frac{V_{sig} (1M)}{1M + 10} \approx V_{sig}$$

$$V_{gs2} = \frac{-g_{m1} (2k) V_{sig}}{1 + g_{m2} (100)}$$

$$\frac{V_o}{V_{sig}} = \frac{g_{m2} (100) (-g_{m1}) (2k)}{1 + g_{m2} (100)} = \boxed{-1.14 V/V}$$

Problem 3 – (17 points)


For the circuit shown below, **draw** the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , v_{gs2} , etc.). $\lambda=0$ for all transistors. $v_{sig}=0.001\sin(10t)$ AC and $V_2=10V$ DC.

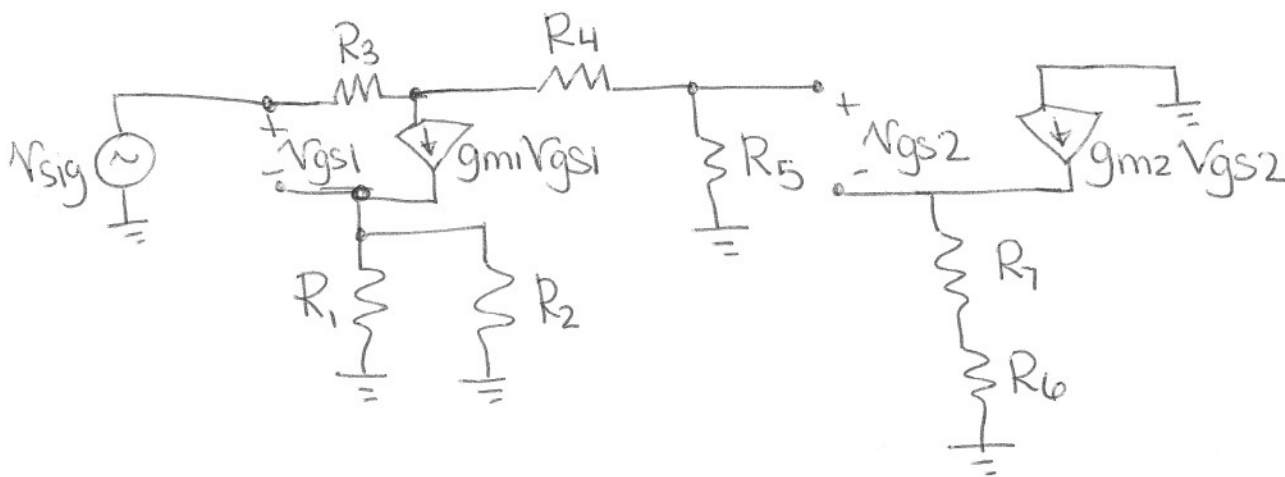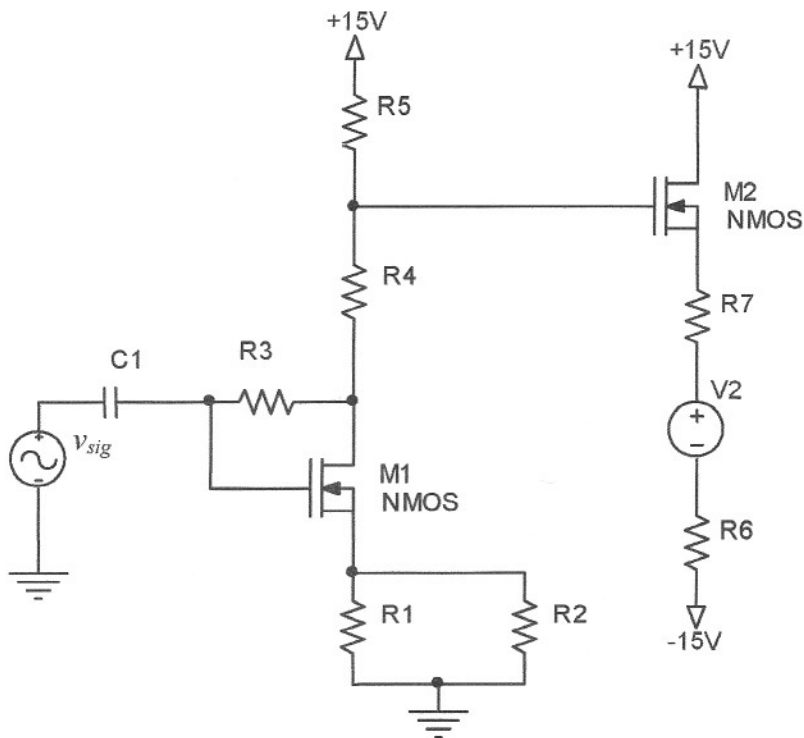

Problem 4 – (8 points)


Use: $V_t = 2V$
 $k_n'(W/L) = 1mA/V^2$

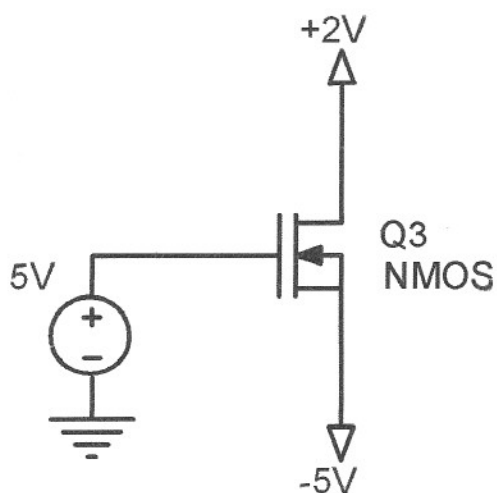- (a) What region of operation is the transistor below operating?
- (b) Draw a cross section of the transistor below making sure to label all voltages and show how the current is flowing.





$V_{GS} = +10V \therefore ON$
 $V_{GS} > V_t$
 $V_{DS} = 7$
 $(V_{GS} - V_t) = 10 - 2 = 8V$
 $\therefore V_{DS} < V_{GS} - V_t$

TRIODE Operation

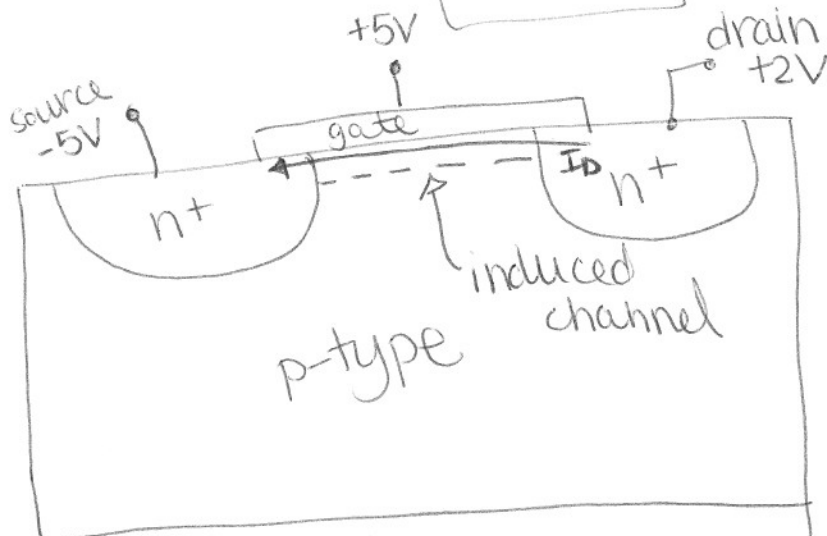

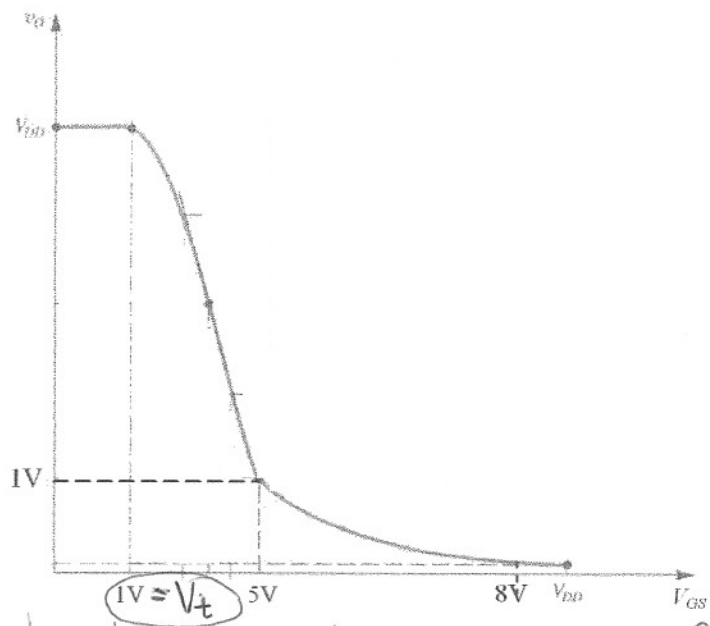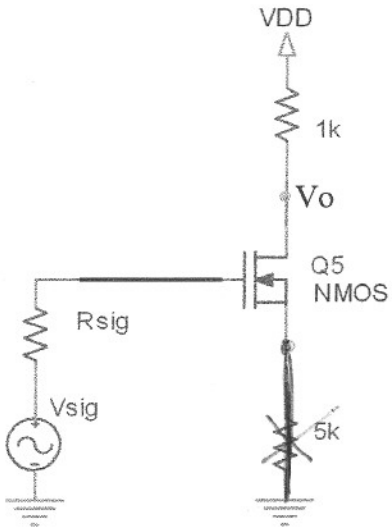Problem 5 – (5 points)

$v_{sig} = \{8 + 0.01 \sin(\omega t)\}$ Volts. Does this circuit operate as a **linear** AC amplifier? If so, what is the gain, $\frac{V_o}{V_{sig}}$, of the following circuit in terms of V_{DD} , V_{sig} , R_{sig} , $k'(W/L)$? If not, explain why. The graph below shows measurements taken for this circuit.



This mosfet is biased at a gate voltage of $V_G = 8V$ and $V_S = 0$.
 $\therefore V_{GS} = 8V$.

It looks like the transistor will be in triode \Rightarrow

$$V_{DS} \approx 0 < (V_{GS} - V_t) = 8 - 1 = 7V$$

\therefore TRIODE Region \rightarrow will not amplify linearly