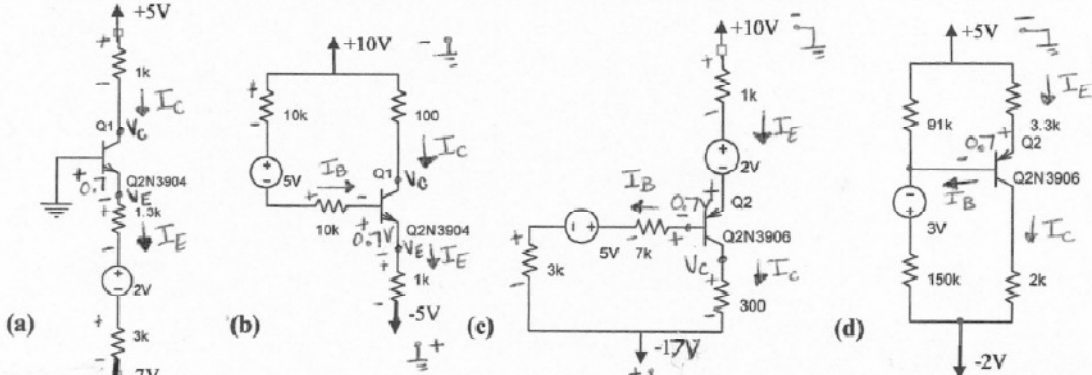


PROBLEM SESSION 6

1. Use $|V_{BE}|=0.7$, $\beta=100$. Find voltages at all nodes and currents through all branches. (worth 4 problems)



Assume Active

a. $+0.7 + 1.5k(I_E) + 2 + 3k(I_E) - 7 = 0$

$$I_E = \frac{5 - 0.7}{4.3k} = 1mA$$

$$-7 + I_E(3k) + 2 + I_E(1.5k) - V_E = 0$$

$$V_E = -5 + I_E(4.3k) = -0.7V$$

$$I_C = \alpha I_E = \frac{100}{101}(1m) = 0.99m$$

$$V_B = 0$$

$$5 - I_C(1k) - V_C = 0$$

$$V_C = 5 - I_C(1k) = 4V$$

$V_C > V_B > V_E \rightarrow$ Active mode ✓

b. $+10 - I_B(10k) - 5 - I_B(10k) - 0.7 - I_E(1k) + 5 = 0$

$$I_B = \frac{I_E}{\beta+1} \Rightarrow I_E = \frac{9.3}{\frac{20k}{101} + 1k} = 7.76mA$$

$$I_C = \beta \cdot I_B \Rightarrow I_C = 769\mu A$$

$$I_B = 76.9\mu A$$

$$V_B \approx 5 - I_B(20k) = 3.5V$$

$$V_E = -5 + 1k(I_E) = 2.8V$$

$$V_C = 10 - 100(I_C) = 9.2V$$

$V_C > V_B > V_E$ Active ✓

c. $+10 - I_E(1k) - 2 - 0.7 - I_B(7k) - 5 - 3k(I_B) + 17 = 0$

$$I_B = I_E/\beta+1 \Rightarrow I_E = \frac{19.3}{\frac{10k}{101} + 1k} = 17.6mA$$

$$I_C = \alpha I_E = 17.4mA$$

$$I_B = I_C/\beta = 174\mu A$$


$$-17 + 3k(I_B) + 5 + 7k(I_B) = V_B \Rightarrow V_B = -12 + 10k(I_B)$$

$$V_B = -10.26V$$

$$+10 - I_E(1k) - 2 - V_E = 0 \Rightarrow V_E = -9.6V$$

$$-17V + I_C(300) - V_C = 0 \Rightarrow V_C = -11.78V$$

$V_C < V_B < V_E$ ✓

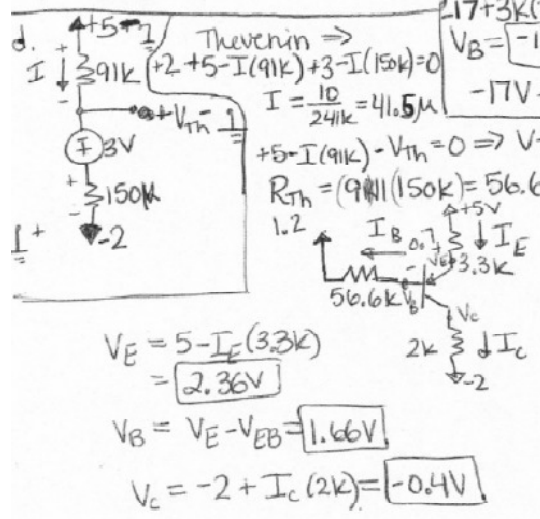

d. Thevenin \rightarrow

$$I = \frac{2 + 5 - I(91k) + 3 - I(150k)}{241k} = 41.5\mu A$$

$$+5 + I(91k) - V_{th} = 0 \Rightarrow V_{th} = 1.2V$$

$$R_{th} = (91k || 150k) = 56.6k$$

$$+5 - I_E(3.3k) - 0.7 - I_B(56.6k) - 1.2 = 0$$

$$I_B = \frac{I_E}{\beta+1} \Rightarrow I_E = \frac{3.1}{3.3k + \frac{56.6k}{101}} = 0.8mA$$

$$I_C = \alpha I_E = \frac{100}{101}(0.8m) = 0.8mA$$

$$I_B = \frac{I_E}{101} = 8\mu A$$


$$V_E = 5 - I_E(3.3k) = 2.36V$$

$$V_B = V_E - V_{EB} = 1.66V$$

$$V_C = -2 + I_C(2k) = -0.4V$$

$V_C < V_B < V_E$ ✓ Active

2. Use $|V_{BE}|=0.7$, $\beta=100$. Find voltages at all nodes and the currents through all branches. $V_{CE-SAT}=0.2V$

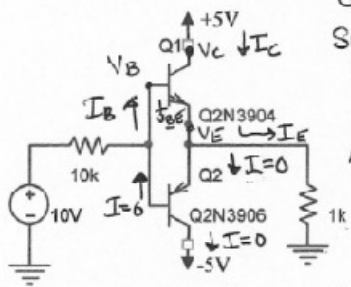

Q1 on, Q2 off: they can not both be on at the same time. (see Example 5.12 in the book).
 { Can not have current flow "into" the +10V supply.

Assume active: $+10 - I_B(10k) - 0.7 - I_E(1k) = 0$ $I_B = \frac{I_E}{\beta+1}$
 $\Rightarrow I_E = 8.5m$ $\therefore V_E = 8.5V, V_B = 9.2V$
 $\therefore V_C < V_B > V_E$!! NOT ACTIVE $V_C = +5V$

Assume SAT: $V_{CE} = 0.2V$
 $+5 - V_{CE-SAT} - \frac{I_E(1k)}{V_E} = 0$
 $V_E = 4.8V$

$V_B = 4.8 + 0.7 = 5.5V$ $I_E = \frac{V_E}{1k} = 4.8m$
 $V_C = 5V$ $I_B = \frac{(10 - 5.5)}{10k} = 0.45m$
 $5 < V_B > V_E$ ✓ SAT $I_C = I_E - I_B = 4.35m$
 For Q2: $V_{EB} = 4.8 - 5.5 = -0.7 < 0.7$ \therefore off

3. Assume active operation for all transistors. (V_{BE} is an average) \therefore off