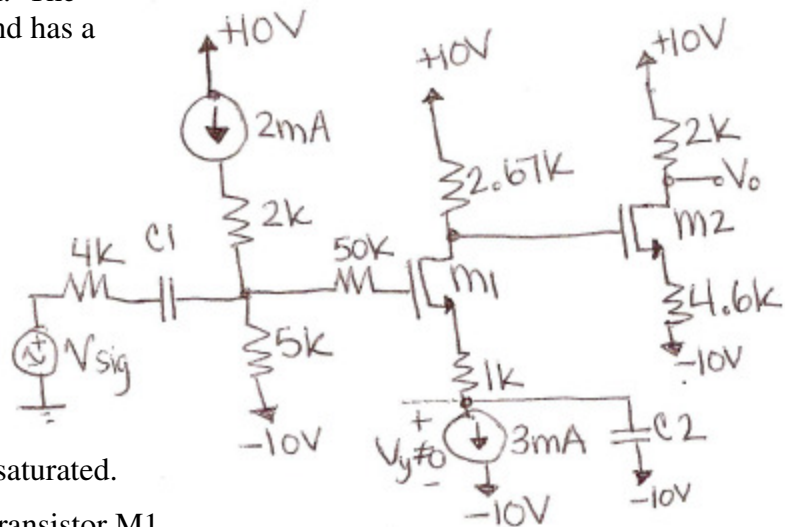


1. Understand the basic operation of a MosFet:
 - 3 regions of operation: cutoff, triode, saturation and know all current equations associated with them.
 - the I_D versus V_{DS} graph
2. Understand the bias point concept for linear amplification.
3. Be able to separate the DC and AC analysis for a circuit containing MosFets.
4. Be able to analyze a circuit (with or without cap in it) containing MosFets for DC operation.
5. Be able to draw a small-signal model of MosFets in a circuit.
6. Be able to analyze a small-signal circuit to find overall gain, midband gain, input resistance, and output resistance.
7. Determine ω_L and ω_H or f_L and f_H .

Example 1

Use: $V_t=2V$
 $k_n'(W/L)=6mA/V^2$
 $\lambda=0$
 $V_{sig} = 3+0.002\sin(20t)$
 For DC analysis, assume that the capacitors act as an open. The current source is not ideal and has a voltage drop across it.

- (a) Solve for the DC currents:
 - a. $I_{D1} = I_{S1} = 3mA$
 - b. $I_{S2} = I_{D2} = 2mA$
- (b) Solve for the DC voltages:
 - a. $V_{G2} = 2V$
 - b. $V_{S2} = -0.82V$
 - c. $V_{S1} = -3V$



- (c) Verify that transistor M2 is saturated.
- (d) State the DC bias point for transistor M1.
- (e) Assuming that the transistor amplification is $V_o/V_{sig} = 3V/V$. Assume the input frequency is operating within the circuits operating range. What is the **total** (AC and DC) instantaneous output for V_o using the V_{sig} value stated above.

$$V_{o_{total}} = 6 + 6m\sin(20t)$$

Example 2

Use: $V_t=2V$

$$k_n'(W/L)=10mA/V^2$$

V_{sig} is an AC source

Transistor 1 has DC values: $V_{GS}=3V$

Transistor 2 has DC values: $V_{GS}=12V$


$\lambda=0$ (for all transistors) and assume all transistors are saturated

For the following hybrid- π equivalent circuit, find the following values:

(a) R_{in} (input resistance –ignore the input source, V_{sig})

(b) R_{out} (output resistance–ignore R_L {no load is connected})

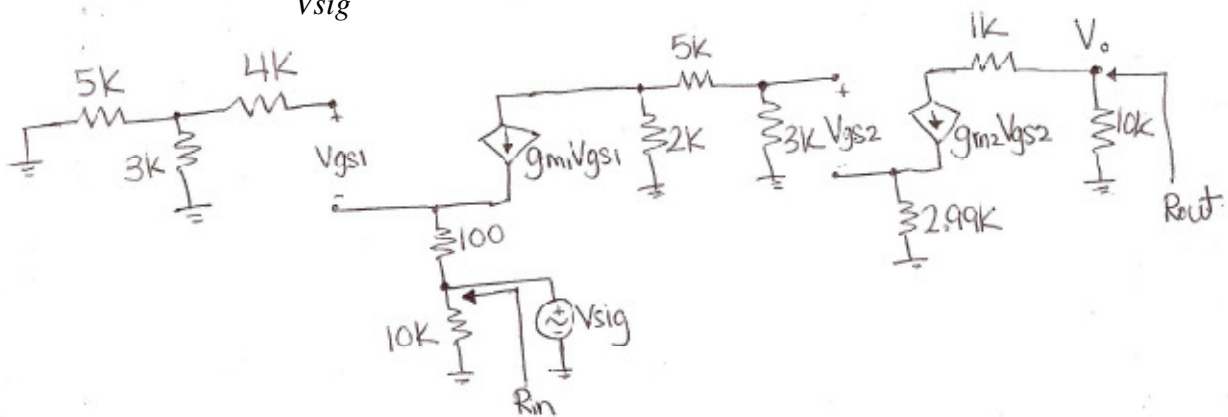
(c) ideal midband gain, $\frac{V_o}{V_{sig}}$



$R_{in}=98\Omega$, $R_{out}=10k$, $V_o/V_{sig}=10V/V$

Example 3


For the circuit shown below, **draw** the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , v_{gs2} , r_{o1} , etc.). $\lambda \neq 0$ for all transistors. (i.e. draw the small-signal with r_o included). $v_{sig} = 0.005 \sin(20t)$ AC. Draw the small-signal equivalent circuit **WITH** capacitors shown.

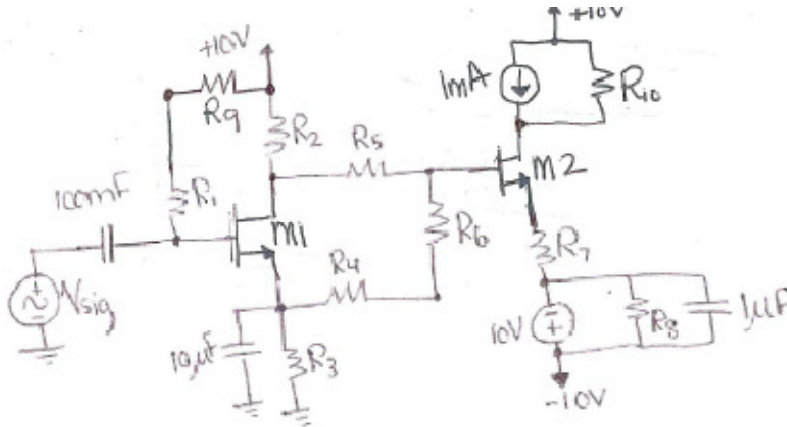

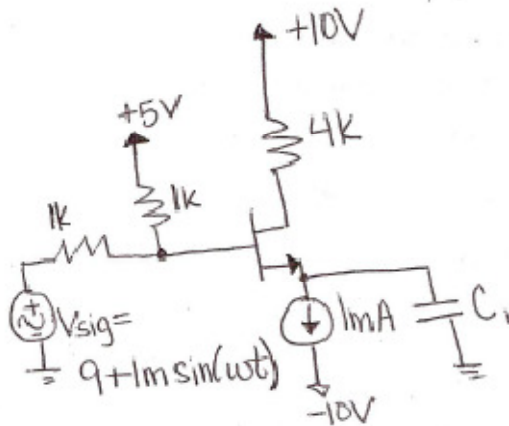Example 4

Use: $g_m = 2.2 \text{ mA/V}$, $\lambda = 0$, and $C_{gs} = C_{gd} = 5 \text{ pF}$.

What is the operating range for the amplifier below (in Hz)?




478Hz to 5.3MHz

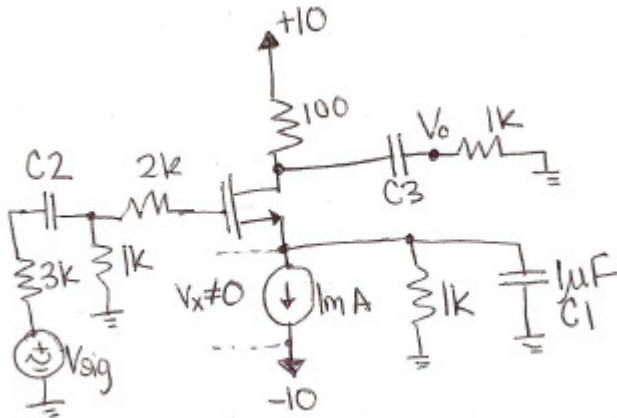Example 5

$V_t=2V$, $\lambda=0$, $k_n'(W/L)=2mA/V^2$. Does this circuit operate as a **linear** AC amplifier? If so, what is the gain, $\frac{V_o}{V_{sig}}$, of the following circuit? If not, explain why.

$V_{sig} = 2.5 + \sin(\omega t)$. (assume that ω is in the operating range of the circuit). If not, explain why.



No, does not amplify.