

The material we have covered so far this semester is summarized (but NOT limited to) below:

1. Understand the basic operation of a BJT:
  - Cutoff, saturation, active. Analyze a circuit for all current equations and voltages (current relationships)
    - Make sure to be able to take a Thevenin Equivalence and use Resistance Reflection Rules.
  2. Understand the bias point concept for linear amplification.
  3. Be able to separate the DC and AC analysis for a circuit containing a BJT.
  4. Be able to analyze a circuit (with or without cap in it) containing a BJT for DC operation.
  5. Be able to draw a small-signal model of a BJT circuit.
  6. Analyze a small-signal circuit to find overall gain, midband gain, input resistance, and output resistance
  7. Determine  $\omega_L$  and  $\omega_H$  or  $f_L$  and  $f_H$ .
- 

### Example 1

Use: ignore  $r_o$ ,  $|V_{BE}|=0.7$ ,  $\beta=50$

$$V_{sig} = 20 + 0.001 \sin(20t)$$

For DC analysis, assume that the capacitors are open

(a) Solve for the DC currents:

- a.  $I_B = 111\mu A$
- b.  $I_E = 5.7mA$
- c.  $I_C = 5.6mA$

(b) Solve for the DC voltages:


- a.  $V_B = 15.4V$
- b.  $V_E = 14.7V$
- c.  $V_o = 17.2V$

(c) What region of operation is this transistor acting?

ACTIVE  $V_C > V_B$   
 $17.2 > 15.4$

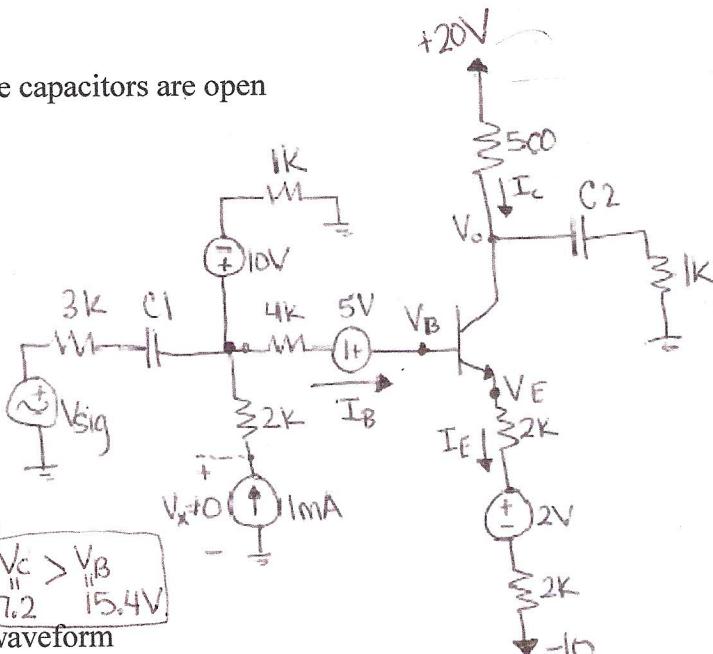(d) Sketch the total instantaneous waveform observed for  $V_o$  if  $V_o/V_{sig} = 5V/V$ .

$$V_o \text{ total} = 17.2 + 5 \sin(20t)$$



## Example 2

Use: ignore  $r_o$  and  $r_x$ ,  $|V_{BE}|=0.7$ ,  $\beta=100$ ,  $V_T=25mV$   
 $V_I = 10+0.002\sin(20t)$


$$r_{\pi 1}=50k\Omega, g_{m2}=50mA/V$$

For the following hybrid- $\pi$  equivalent circuit below, find the following values:

(a)  $R_{in}$  (input resistance –ignore only the input source,  $V_{sig}$  and include all resistors at the emitter)

(b)  $R_{out}$  (output resistance-include all resistors at the collector{no load is connected})

(c) midband gain,  $\frac{V_o}{V_{sig}}$

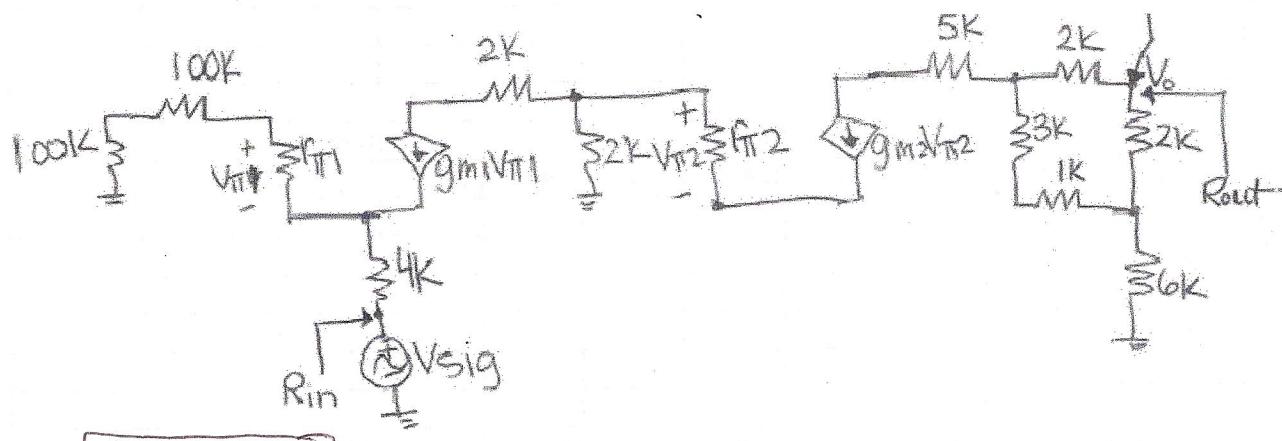


$$R_{in} = 8.9K$$

$$R_{out} = 7.5K$$

$$\frac{V_o}{V_{sig}} = -26V/V$$
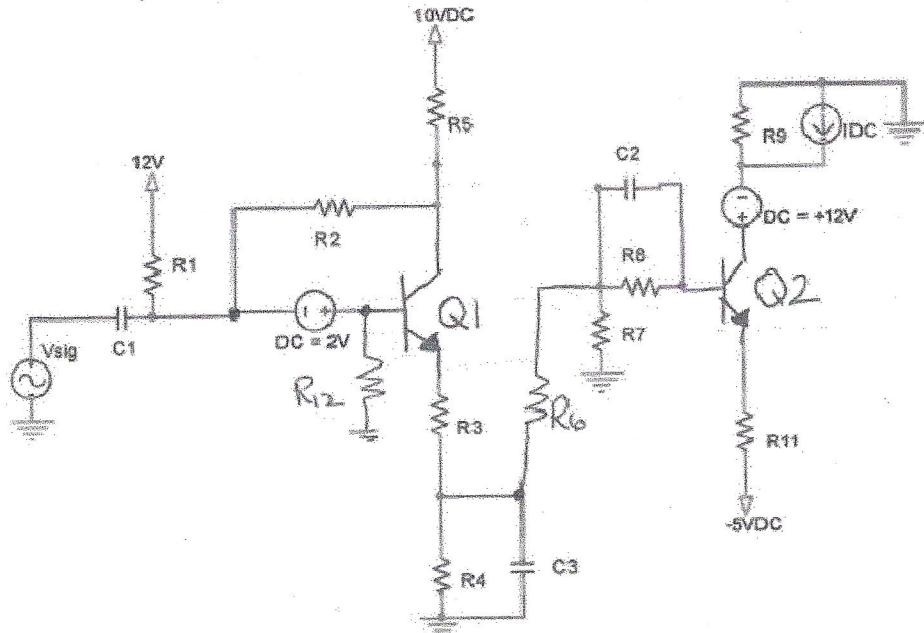
### Example 3

For the circuit shown below, draw the AC small-signal equivalent circuit (use hybrid- $\pi$  or model T). Make sure that everything is labeled in terms of the transistor number. (e.g.  $g_{m1}$ ,  $v_{π2}$ , etc.). Include  $r_o$  for all transistors.  $v_{sig} = 0.001\sin(10t)$  AC. Assume that the capacitors act as a short.




### Example 4

Use:  $g_m = 80 \text{ mA/V}$ ,  $V_T = 25 \text{ mV}$ ,  $\beta = 100$ , ignore  $r_o$  and use  $r_x = 20\Omega$ . Use the attached datasheet for all other values: (Assume C1 yields the highest pole value.)

- (a) What frequency pole value does C1 create? (express the answer in rad/sec.)
- (b) What is the frequency range for this circuit (Hint: Find the high frequency value)?

47.8 rad/sec

7.5Hz to 459kHz

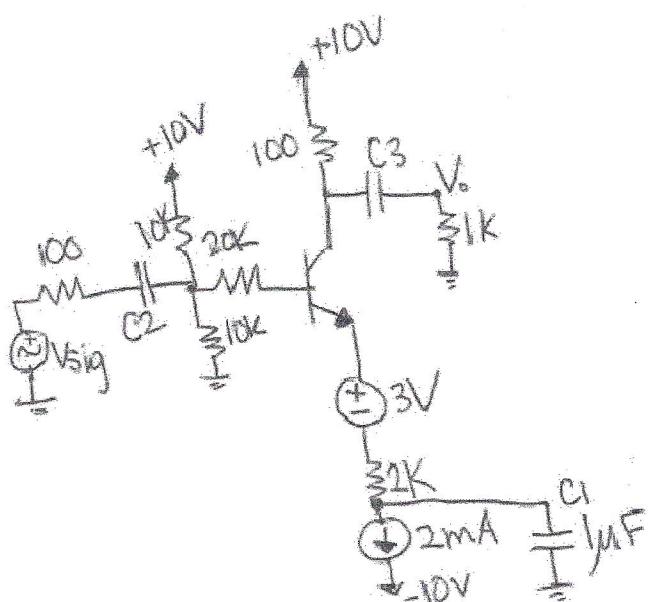


## Example 5

$|V_{BE}|=0.7$ ,  $\beta=100$ ,  $V_T=25\text{mV}$ , ignore  $r_o$  and  $r_x$ ,  $v_{sig} = \{2+0.1\sin(\omega t)\}\text{Volts}$ . Assume that the capacitor acts as an open for DC operation and short for AC operation. Does this circuit operate as a linear AC amplifier? If

so, what is the gain,  $\frac{V_o}{V_{sig}}$ , of the following circuit? If not, explain why. Assume output is taken at

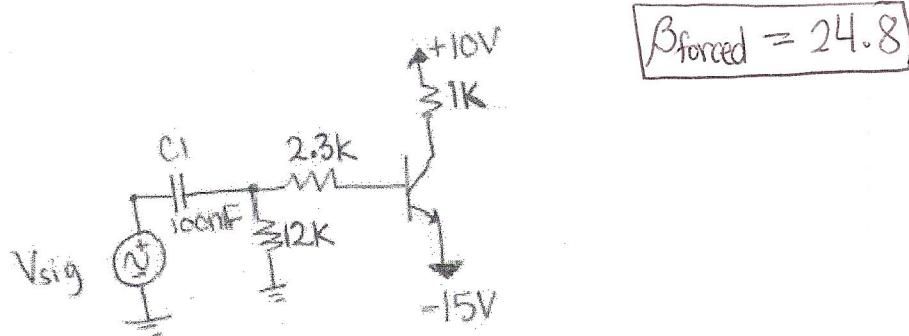collector of transistor. If in saturation, use the datasheet values to determine  $\beta_{\text{forced}}$ .



NPN General Purpose Amplifier (continued)					
Electrical Characteristics		$T_A = 25^\circ\text{C}$ unless otherwise noted			
Symbol	Parameter	Test Conditions	Min	Max	Units
<b>OFF CHARACTERISTICS</b>					
$V_{BRCEO}$	Collector-Emitter Breakdown Voltage	$I_C = 1.0\text{ mA}, I_B = 0$			V
$V_{BRBEO}$	Collector-Base Breakdown Voltage	$I_C = 10\text{ }\mu\text{A}, I_B = 0$			V
$V_{BERBO}$	Emitter-Base Breakdown Voltage	$I_E = 10\text{ }\mu\text{A}, I_C = 0$			V
$I_{BL}$	Base Cutoff Current	$V_{CE} = 30\text{ V}, V_{EB} = 3\text{ V}$			nA
$I_{CEX}$	Collector Cutoff Current	$V_{CE} = 30\text{ V}, V_{EB} = 3\text{ V}$			nA
<b>ON CHARACTERISTICS*</b>					
$I_{CIE}$	DC Current Gain	$I_C = 0.1\text{ mA}, V_{CE} = 1.0\text{ V}$ $I_C = 1.0\text{ mA}, V_{CE} = 1.0\text{ V}$ $I_C = 10\text{ mA}, V_{CE} = 1.0\text{ V}$ $I_C = 50\text{ mA}, V_{CE} = 1.0\text{ V}$ $I_C = 100\text{ mA}, V_{CE} = 1.0\text{ V}$	30		
$V_{CEsat}$	Collector-Emitter Saturation Voltage	$I_C = 10\text{ mA}, I_B = 1.0\text{ mA}$ $I_C = 50\text{ mA}, I_B = 5.0\text{ mA}$		0.2 0.3	V
$V_{BEsat}$	Base-Emitter Saturation Voltage	$I_B = 10\text{ mA}, I_E = 1.0\text{ mA}$ $I_B = 50\text{ mA}, I_E = 5.0\text{ mA}$	0.65	0.85 0.95	V
<b>SMALL SIGNAL CHARACTERISTICS</b>					
$f_T$	Current Gain - Bandwidth Product	$I_C = 10\text{ mA}, V_{CE} = 20\text{ V}, f = 100\text{ MHz}$	300		MHz
$C_{obs}$	Output Capacitance	$V_{CE} = 5.0\text{ V}, I_C = 0, f = 1.0\text{ MHz}$		4.0	pF
$C_{ib}$	Input Capacitance	$V_{CE} = 0.5\text{ V}, I_C = 0, f = 1.0\text{ MHz}$		8.0	pF
NF	Noise Figure	$I_C = 100\text{ }\mu\text{A}, V_{CE} = 5.0\text{ V}, R_E = 1.0\text{k}\Omega, f = 10\text{ Hz to } 15.7\text{ kHz}$		5.0	dB

2N3904 / MMBT3904 / PZT3904