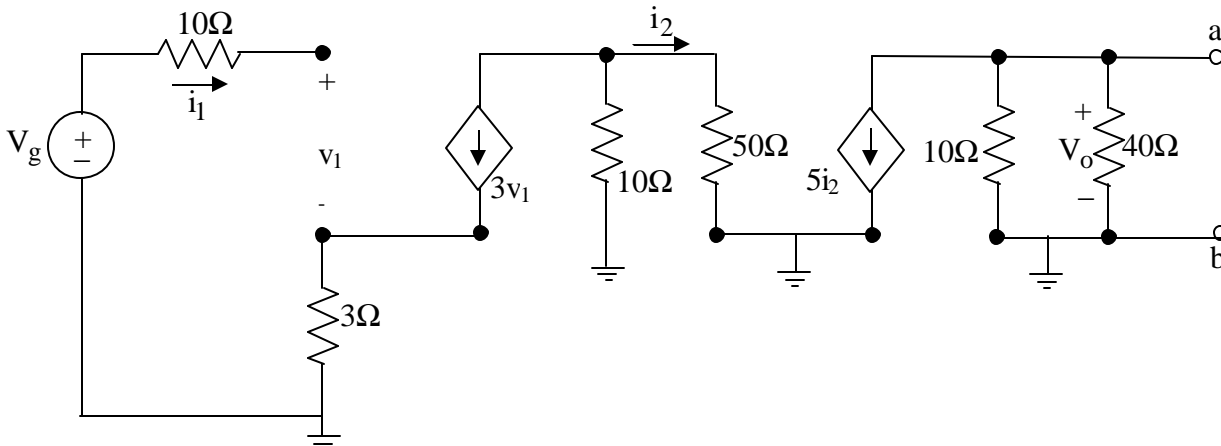


Homework #1:

1. Given $V_g=10mV$, find V_o . Find the Thevenin equivalent between terminals a-b. (Note: $v_1 \neq V_g$)



2. Sketch the following waveforms. Identify the dc component of the waveform and the ac component of the waveform.

- a. $V_s=3\sin(20t)$ V
- b. $V_s=8V + 2\sin(15t-90^\circ)$ V
- c. $V_s=6V \pm 0.5V$

3. Explain in your own words the procedural steps for plotting Bode Plots.

4. Sketch the Bode plots using a straight-line approximation (procedures described in class) and then use Matlab for each function listed below to obtain the Bode Plot. Compare the two:

a.
$$H(s) = \frac{10,000s}{(s+10000)(s+10)}$$


b.
$$H(s) = \frac{100(s+1)^2}{(s+100)(s+1000)}$$

c.
$$H(s) = \frac{10000}{s(s+100,000)}$$

5. (a) Analyze the following circuit to find the transfer function V_o/V_i .

- (i) Solve the circuit symbolically first (with R_1, R_2, R_3, C).
- (ii) Find V_o/V_i with values.

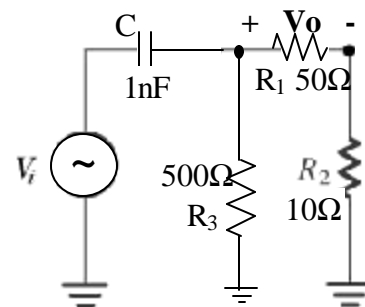(b) Sketch the transfer function using a straight-line approximation procedure.



6. Use PSPICE to simulate the circuit of #5 and determine the Bode Plots. Print out the schematic, along with the plots. Compare to (b)

7. Analyze the following circuit to find the transfer function V_i/V_s . Solve the circuit symbolically first (with R_s, R_i, R_1, C_i) and then plug in their values. Sketch the transfer function using a straight-line approximation procedure.

