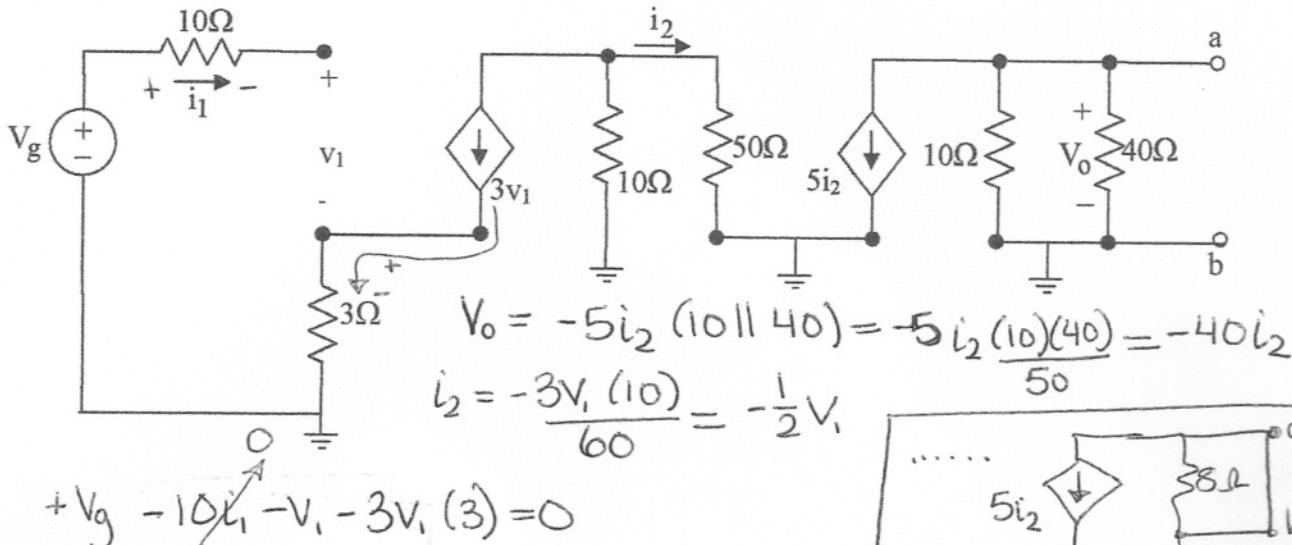


Homework #1:

1. Given $V_g = 10\text{mV}$, find V_o . Find the Thevenin equivalent between terminals a-b. (Note: $v_1 \neq V_g$)




$$10V_1 = V_g$$

$$V_1 = \frac{V_g}{10}$$

$$\therefore V_o = -40(-\frac{1}{2})(\frac{V_g}{10}) = +2Vg = \boxed{\pm 20\text{mV}}$$



$$V_o = V_{Th}$$

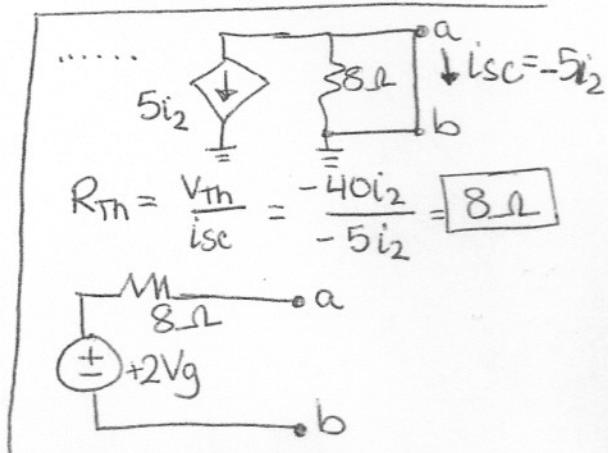


2. Sketch the following waveforms. Identify the dc component of the waveform and the ac component of the waveform.

a. $V_s = 3\sin(20t)$

b. $V_s = 8V + 2\sin(15t - 90^\circ)$

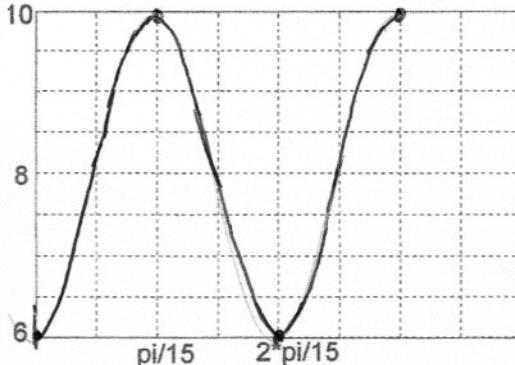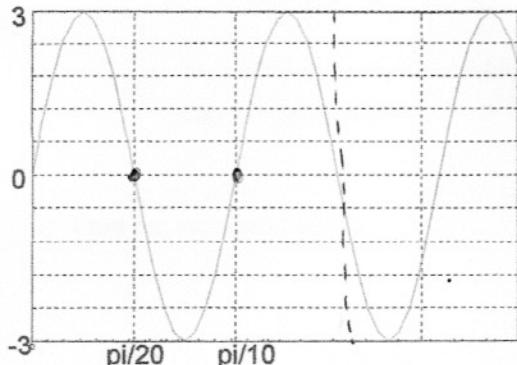


c. $V_s = 6V \pm 0.5V$

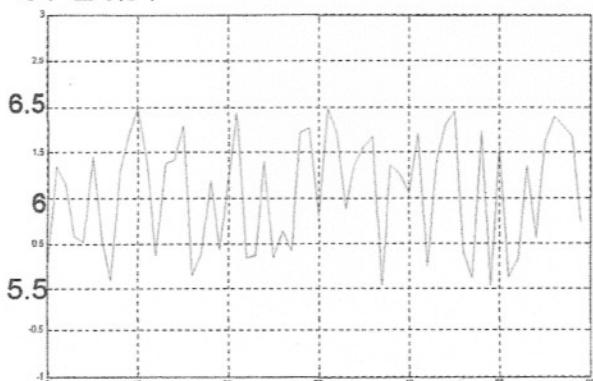

$$H(s) = \frac{10,000s}{(s+10000)(s+10)} = \frac{10,000s}{10,000 \cdot 10 \cdot \left(\frac{s}{10,000} + 1\right) \left(\frac{s}{10} + 1\right)} \Rightarrow @ w=1 \Rightarrow \frac{10K \cdot (1)}{10K \cdot 10 \cdot \left(\frac{1}{10,000}\right)^2 + 1^2 \cdot \left(\frac{1}{10}\right)^2 + 1^2}$$

4. a. -20dB/dec.

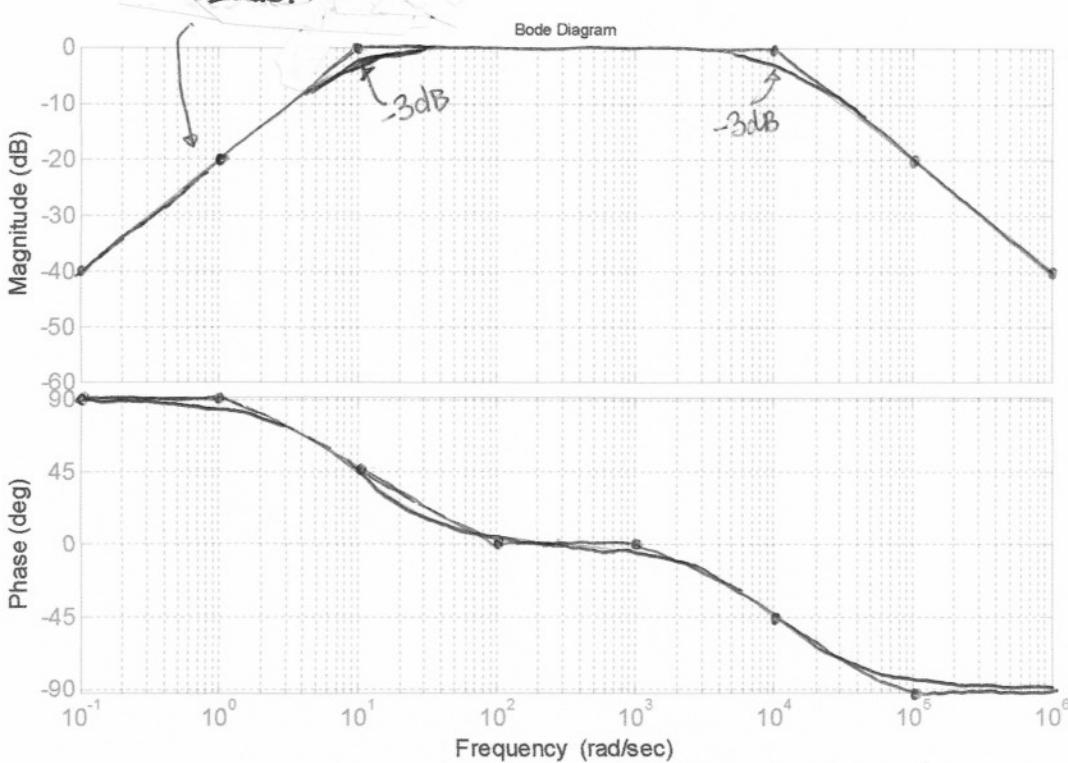


critical freq:
 $10 \rightarrow -20 \text{dB/dec.}$
 $-45^\circ \text{ slope between } 1 \text{ to } 100$
 $10,000 \rightarrow -20 \text{dB/dec.}$
 $-45^\circ \text{ slope between } 1\text{K} \rightarrow 100\text{K}$

starting \Rightarrow
 $-20 \text{dB at } w=1$
 $1(90^\circ) = 90^\circ \text{ to start}$

$$H(s) = \frac{100(s+1)^2}{(s+100)(s+1000)} = \frac{100(s+1)^2}{100 \cdot 1,000 \left(\frac{s}{100} + 1\right) \left(\frac{s}{10K} + 1\right)} \Rightarrow @ w=1 \Rightarrow \frac{100 (1.1^2 + 1^2)^2}{100 \cdot 1,000 \left(\sqrt{\frac{1}{100}^2 + 1^2}\right) \left(\sqrt{\frac{1}{10K}^2 + 1^2}\right)}$$

$$= -60 \text{dB}$$

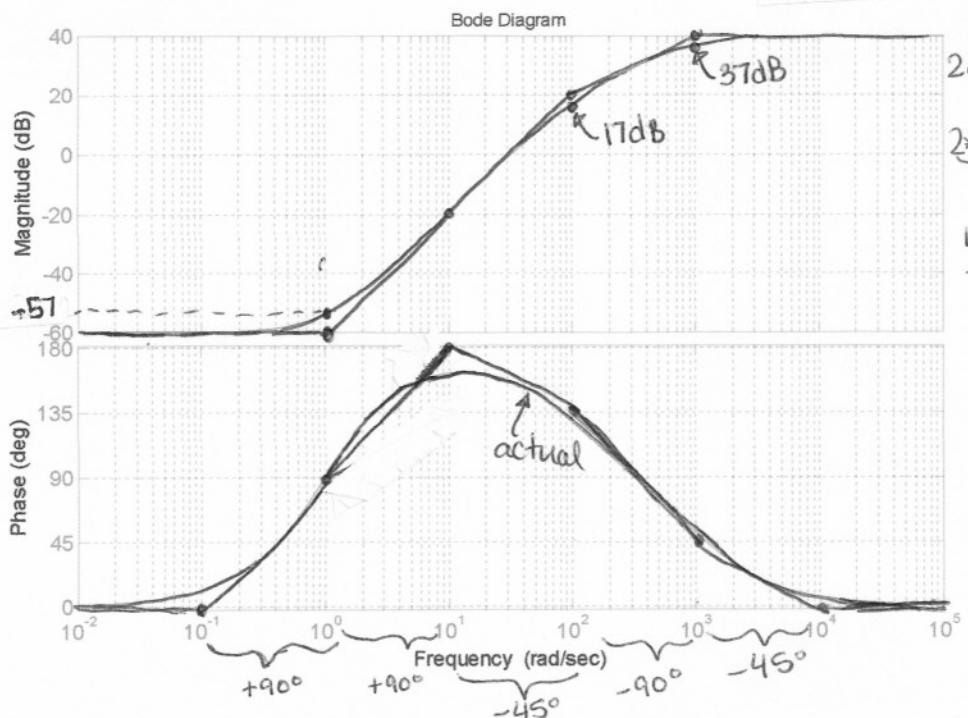


critical freq.:
 $1 \Rightarrow +40 \text{dB/dec.}$
 $2 \times 45^\circ \text{ slope between } 90^\circ \text{ at } w=1 \text{ to } w=10$

$100 \Rightarrow -20 \text{dB/dec.}$
 $-45^\circ \text{ slope between } w=10 \text{ to } w=1\text{K}$

$1\text{K} \Rightarrow -20 \text{dB/dec.}$
 $-45^\circ \text{ slope between } w=100 \text{ to } w=10\text{K}$

$$4. c. \quad H(s) = \frac{10000}{s(s+100,000)}$$

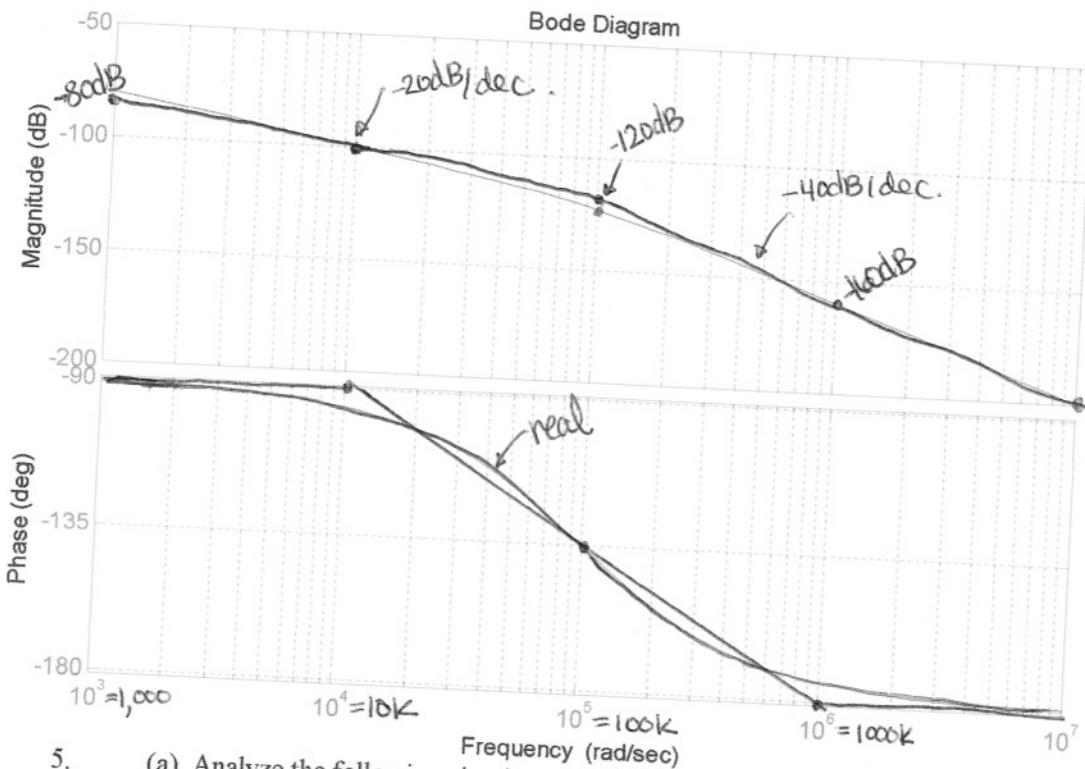② $\omega = 10^3 \Rightarrow \frac{10,000}{100k \cdot 10^3 \left(\sqrt{\left(\frac{10^3}{100k}\right)^2 + 1^2} \right)} = -80\text{dB}$




frequencies \Rightarrow
at origin \Rightarrow
 -20dB/dec.
 -90°

$100\text{k} \Rightarrow -20\text{dB/dec.}$
 -45° slope between
 $\omega = 10\text{k}$ to $\omega = 100\text{k}$

5. (a) Analyze the following circuit to find the transfer function V_o/V_i .

- (i) Solve the circuit symbolically first (with R_1, R_2, R_3, C).
(ii) Find V_o/V_i with values.

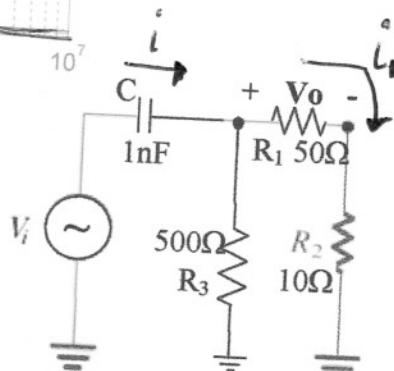- (b) Sketch the transfer function using a straight-line approximation procedure.



$$V_o = i_1 R_1$$

$$i_1 = \frac{i \cdot R_3}{R_1 + R_2 + R_3}$$



$$i = \frac{V_i}{\frac{1}{CS} + R_3 \parallel (R_1 + R_2)} \cdot \frac{(CS)}{(C \cdot S)} = \frac{V_i \cdot C \cdot S}{1 + [R_3 \parallel (R_1 + R_2)]CS}$$

$$\frac{V_o}{V_i} = \frac{\frac{C \cdot S \cdot R_1 R_3}{R_1 + R_2 + R_3}}{1 + [R_3 \parallel (R_1 + R_2)]CS}$$


$$\approx \frac{8.9 \times 10^{-10} S}{(1 + 5.4 \times 10^{-8} S)}$$

$$\begin{aligned} @ \omega = 1 &\Rightarrow \\ &8.9 \times 10^{-10} (1/1^2) \\ &(1 + 5.4 \times 10^{-8} \cdot 1) \approx 1 \\ &= 8.9 \times 10^{-10} V/V \approx -181\text{dB} \end{aligned}$$

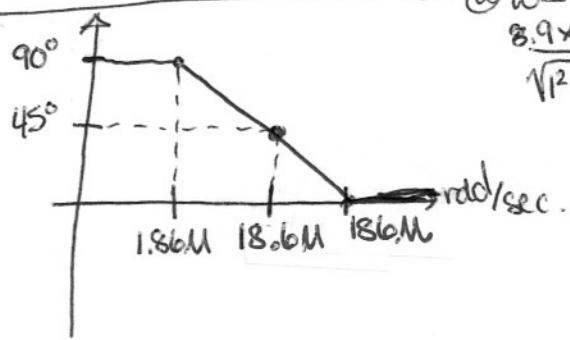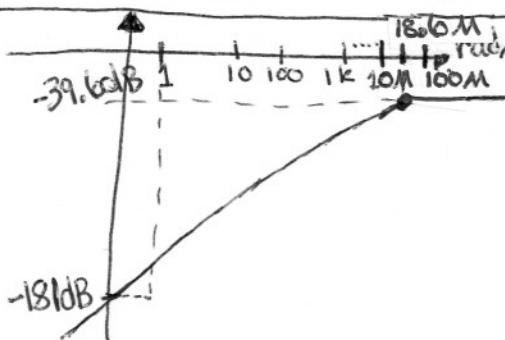
$$\begin{aligned} @ \omega = 18.6\text{M} &\Rightarrow \\ &8.9 \times 10^{-10} (18.6\mu) \\ &\sqrt{1^2 + 5.4 \times 10^{-8} (18.6\mu)} = 0.012 \end{aligned}$$



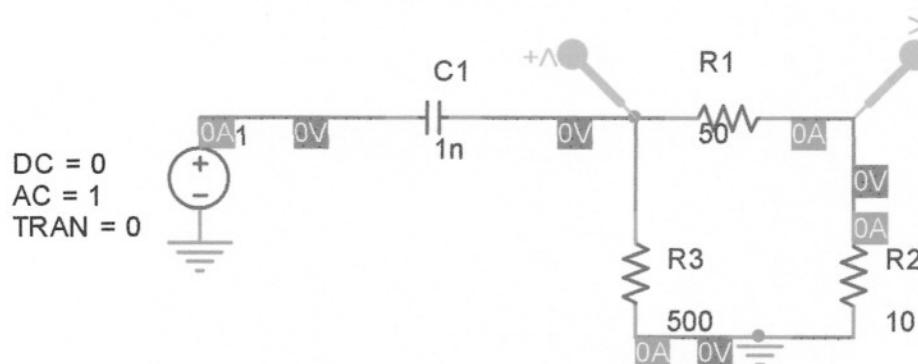
6. Use PSPICE to simulate the circuit of #5 and determine the Bode Plots.
Print out the schematic, along with the plots. Compare to (b)



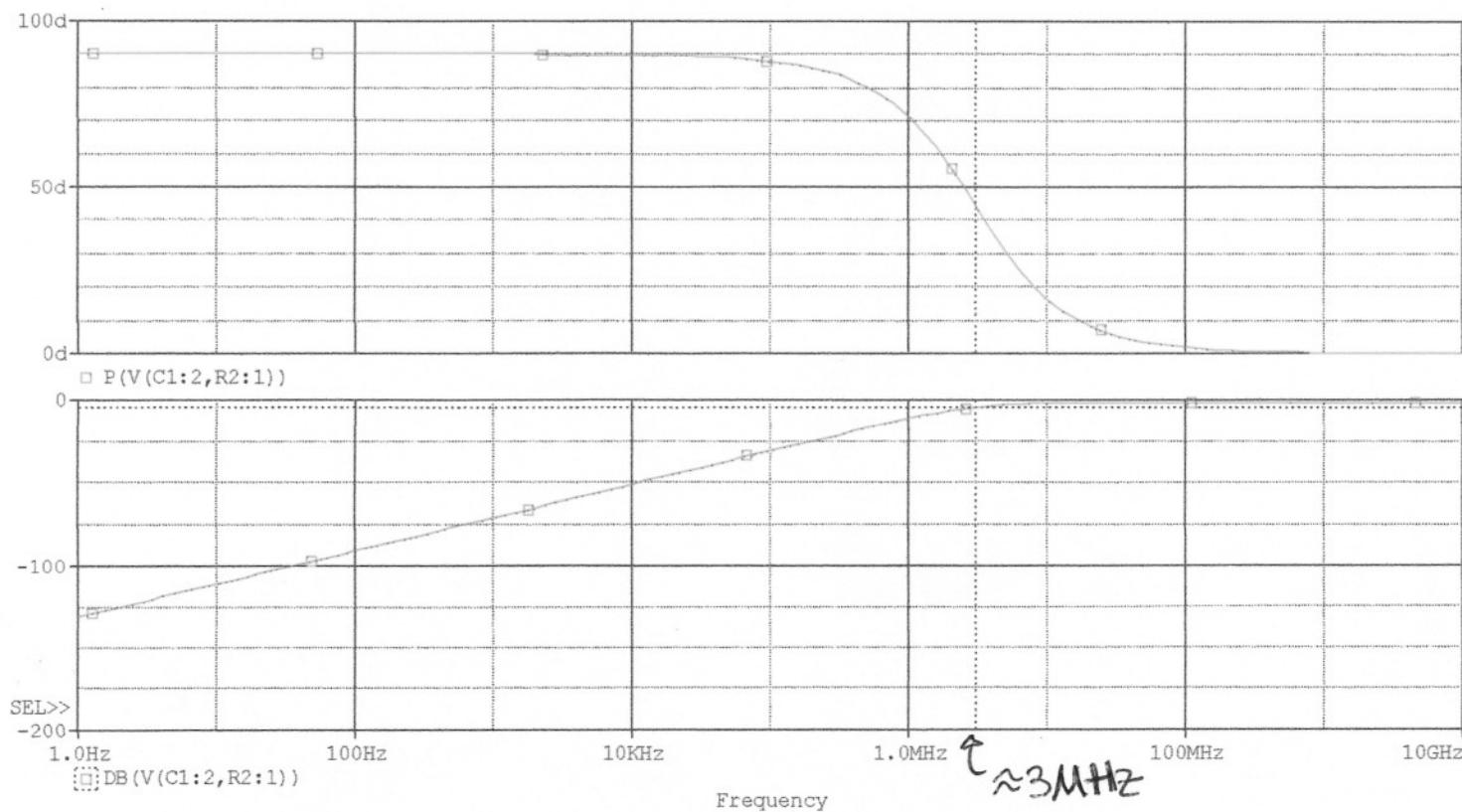3dB point is approximately 3Meg Hz. $\cong 18.7M\text{ rad/sec.}$




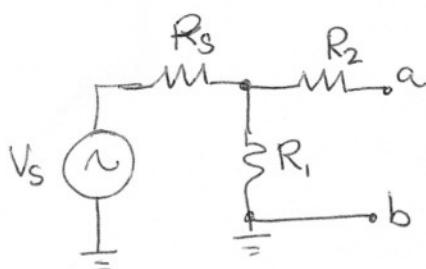
7. Analyze the following circuit to find the transfer function V_i/V_s . Solve the circuit symbolically first (with R_s , R_i , R_2 , C_i) and then plug in their values. Sketch the transfer function using a straight-line approximation procedure.



$$V_{Th} = \frac{V_s (R_1)}{R_1 + R_s}$$

$$R_{Th} = R_2 + \frac{R_1 R_s}{R_1 + R_s} \text{ OR}$$

$$= R_2 + (R_1 \parallel R_s)$$

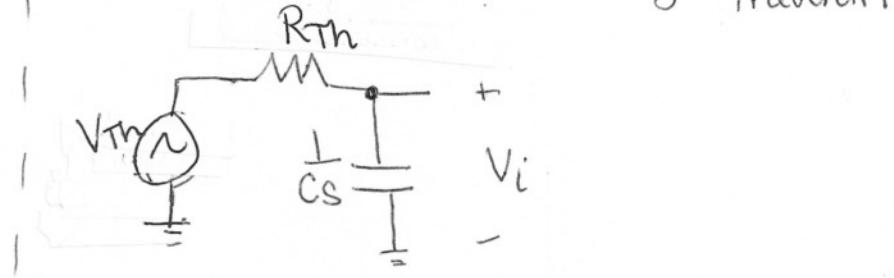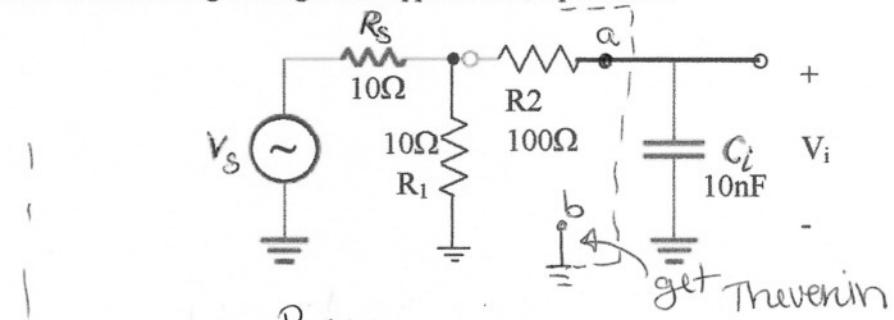

$$V_i = \left[\frac{V_{Th} \cdot \frac{1}{Cs}}{R_{Th} + \frac{1}{Cs}} \right] \left(\frac{1}{Cs} \right) = \frac{V_{Th}}{(R_{Th} C_s + 1)}$$

$$\frac{V_i}{V_s} = \frac{\frac{V_s R_1}{R_1 + R_s}}{(R_2 + R_1 \parallel R_s) C \cdot s + 1}$$

$$\frac{V_i}{V_s} = \frac{R_1}{(R_1 + R_s)[(R_2 + R_1 \parallel R_s) \cdot C \cdot s + 1]}$$

$$\frac{V_i}{V_s} = \frac{10}{20[(100+5) \cdot 10nF \cdot s + 1]}$$

$$= \frac{0.5}{(1.05 \times 10^{-6} s + 1)}$$

