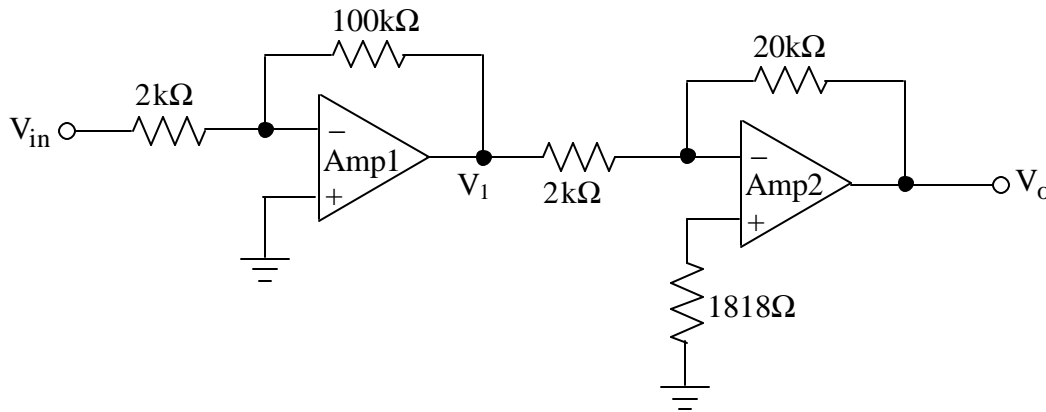


**Homework #2:**


1. (a) Explain how an amplifier works in your own words.  
 (b) Explain in your own words what  $R_i$  is.  
 (c) Explain in your own words what  $R_o$  is.  
 (d) Describe the ideal characteristics for an amplifier (i.e. ideal value for  $R_i$ ,  $R_o$ ,  $A_{vo}$ )  
 (e) Describe the characteristics for a buffer amplifier.
2. Use the circuit below:



Amp1 is a CA3140 and Amp2 is an LM741. (See attached datasheet information)

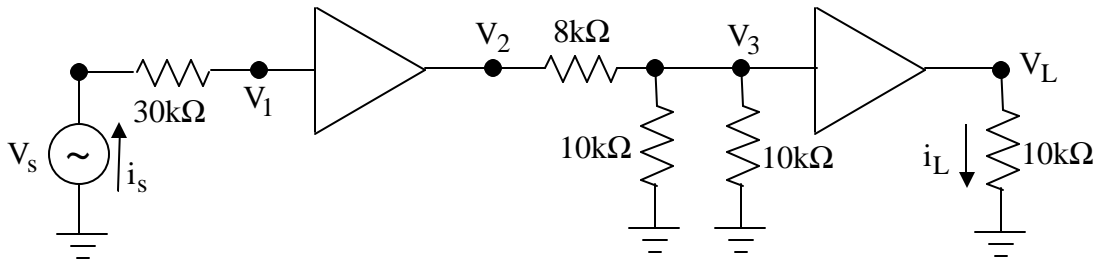
- (a) State each amplifiers frequency response transfer function ( $V_1/V_{in}$  and  $V_o/V_1$ )
  - (b) State the overall transfer function ( $V_o/V_{in}$ )
  - (c) Solve for the overall  $f_{3dB}$  of the above circuit.
3.  $v_s$  is an AC signal. Both amplifiers have the following characteristics:

$$A_{vo}=20, \quad R_i=10k\Omega, \quad R_o=2k\Omega, \quad \text{Clipping levels: } L=-^{+}12V \text{ (unloaded)}$$




- (a) Redraw this 2 stage amplifier using the voltage amplifier model. Make sure to label  $V_s$ ,  $V_1$ ,  $V_3$ , and  $V_o$  on the schematic.
- (b) Find  $A_v = \frac{v_L}{v_s}$ . Express your answer as a ratio(V/V) and in dB. [Round answer to the nearest whole number]
- (c) Find  $A_i = \frac{i_L}{i_s}$ . Express your answer as a ratio(A/A) and in dB. [Round the answer to the nearest whole number]

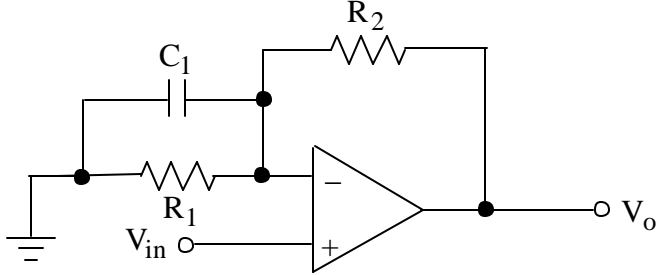4. Analyze the circuit below to obtain the transfer function,  $V_o/V_{in}$ . Assume an ideal op amp. Sketch the straight line approximation for the Bode Plots.



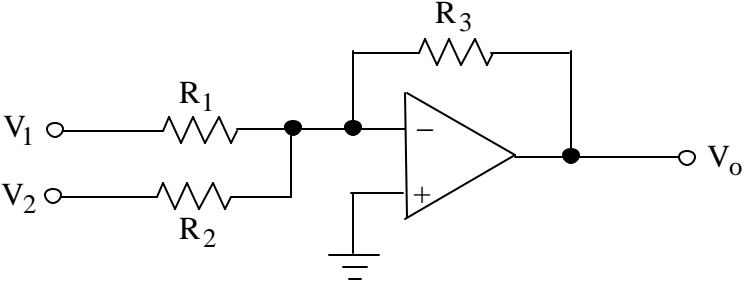5. Redraw or add to the schematic below to show how to reduce the **input bias current**. State the symbolic value(s) of any components added to the schematic.



**Electrical Specifications**  $V_{SUPPLY} = \pm 15V, T_A = 25^{\circ}C$

PARAMETER	SYMBOL	TEST CONDITIONS	TYPICAL VALUES		UNITS	
			CA3140	CA3140A		
Input Offset Voltage Adjustment Resistor		Typical Value of Resistor Between Terminals 4 and 5 or 4 and 1 to Adjust Max $V_{IO}$	4.7	18	$k\Omega$	
Input Resistance	$R_I$		1.5	1.5	$T\Omega$	
Input Capacitance	$C_I$		4	4	$\mu F$	
Output Resistance	$R_O$		60	60	$\Omega$	
Equivalent Wideband Input Noise Voltage, (See Figure 27)	$e_N$	$BW = 140kHz, R_S = 1M\Omega$	48	48	$\mu V$	
Equivalent Input Noise Voltage (See Figure 35)	$e_N$	$R_S = 100\Omega$	f = 1kHz	40	40	$nV/\sqrt{Hz}$
			f = 10kHz	12	12	$nV/\sqrt{Hz}$
Short Circuit Current to Opposite Supply	$I_{OM+}$		Source	40	40	mA
	$I_{OM-}$		Sink	18	18	mA
Gain-Bandwidth Product, (See Figures 6, 30)	$f_T$		4.5	4.5	MHz	
Slew Rate, (See Figure 31)	SR		9	9	$V/\mu s$	
Sink Current From Terminal 8 To Terminal 4 to Swing Output Low			220	220	$\mu A$	
Transient Response (See Figure 28)	$t_r$	$R_L = 2k\Omega$ $C_L = 100pF$	Rise Time	0.08	0.08	$\mu s$
	OS		Overshoot	10	10	%
Settling Time at 10Vp.p, (See Figure 5)	$t_S$	$R_L = 2k\Omega$ $C_L = 100pF$ Voltage Follower	To 1mV	4.5	4.5	$\mu s$
			To 10mV	1.4	1.4	$\mu s$

**Electrical Specifications** For Equipment Design, at  $V_{SUPPLY} = \pm 15V, T_A = 25^{\circ}C$ , Unless Otherwise Specified

PARAMETER	SYMBOL	CA3140			CA3140A			UNITS
		MIN	TYP	MAX	MIN	TYP	MAX	
Input Offset Voltage	$ V_{IO} $	-	5	15	-	2	5	mV
Input Offset Current	$ I_{IO} $	-	0.5	30	-	0.5	20	$\mu A$
Input Current	$I_I$	-	10	50	-	10	40	$\mu A$
Large Signal Voltage Gain (Note 3) (See Figures 6, 29)	$A_{OL}$	20	100	-	20	100	-	$kV/V$
		86	100	-	86	100	-	dB
Common Mode Rejection Ratio (See Figure 34)	CMRR	-	32	320	-	32	320	$\mu V/V$
		70	90	-	70	90	-	dB
Common Mode Input Voltage Range (See Figure 8)	$V_{ICR}$	-15	-15.5 to +12.5	11	-15	-15.5 to +12.5	12	V

LM741:

