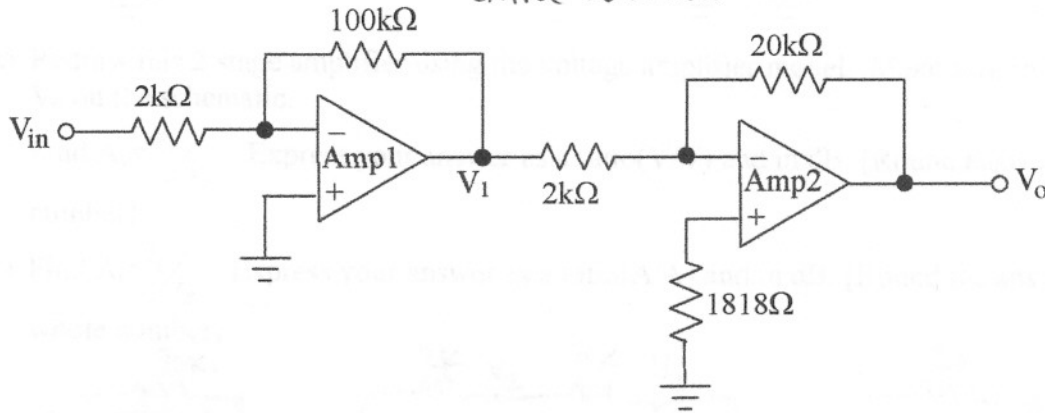


Homework #2:

- Explain how an amplifier works in your own words.: multiplies an input by a "gain" amount
 - Explain in your own words what R_i is.: input resistance
 - Explain in your own words what R_o is.: output resistance
 - Describe the ideal characteristics for an amplifier (i.e. ideal value for R_i , R_o , A_{vo})
 - Describe the characteristics for a buffer amplifier.
 ∞ 0 ∞
provides $V_o = V_{in}$ and supplies extra current.
- Use the circuit below:



Amp1 is a CA3140 and Amp2 is an LM741. (See attached datasheet information)

- State each amplifiers frequency response transfer function (V_1/V_{in} and V_o/V_1)
- State the overall transfer function (V_o/V_{in})
- Solve for the overall f_{3dB} of the above circuit.


a. Amp 1 $\Rightarrow f_c = \frac{4.5 \text{ MHz}}{50} = 90,000 \text{ Hz}$

$$\frac{V_1}{V_{in}} = \frac{-50}{\left(\frac{s}{90 \text{ kHz}} + 1\right)}$$

Amp 2 $\Rightarrow f_c = \frac{1 \text{ MHz}}{\left(\frac{20 \text{ k}}{2 \text{ k}}\right)} = 100 \text{ kHz}$

$$\frac{V_o}{V_1} = \frac{-10}{\left(\frac{s}{100 \text{ kHz}} + 1\right)}$$

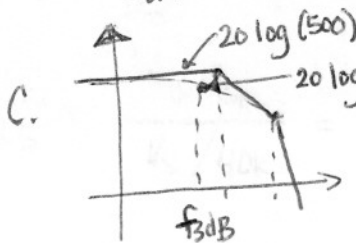b. $\frac{V_o}{V_{in}} = \frac{V_o}{V_1} \cdot \frac{V_1}{V_{in}} = \frac{-50}{\left(\frac{s}{90 \text{ kHz}} + 1\right)} \cdot \frac{-10}{\left(\frac{s}{100 \text{ kHz}} + 1\right)} = \frac{+500}{\left(\frac{s}{90 \text{ kHz}} + 1\right) \left(\frac{s}{100 \text{ kHz}} + 1\right)}$




$$354 \text{ V/V} = \frac{500}{\sqrt{1 + \left(\frac{f_{3dB}}{90 \text{ k}}\right)^2} \cdot \sqrt{1 + \left(\frac{f_{3dB}}{100 \text{ k}}\right)^2}}$$

solve with matlab

$$f_{3dB} \approx 57 \text{ kHz}$$

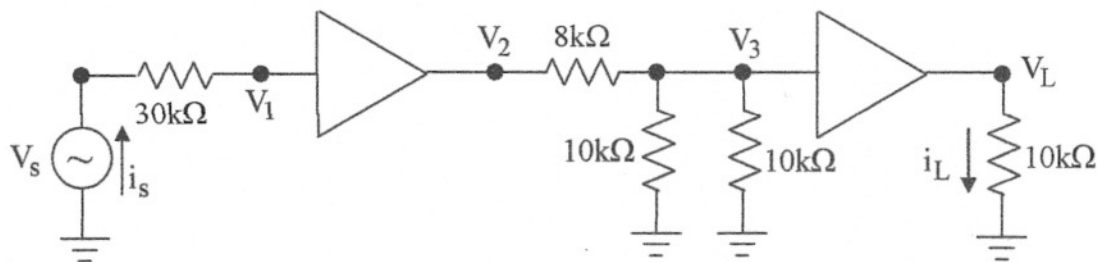3. v_s is an AC signal. Both amplifiers have the following characteristics:


$$A_{vo}=20, \quad R_i=10k\Omega, \quad R_o=2k\Omega, \quad \text{Clipping levels: } L=\pm 12V \text{ (unloaded)}$$



(a) Redraw this 2 stage amplifier using the voltage amplifier model. Make sure to label V_s , V_1 , V_3 , and V_0 on the schematic.

(b) Find $A_v = \frac{v_L}{v_s}$. Express your answer as a ratio(V/V) and in dB. [Round answer to the nearest whole number]

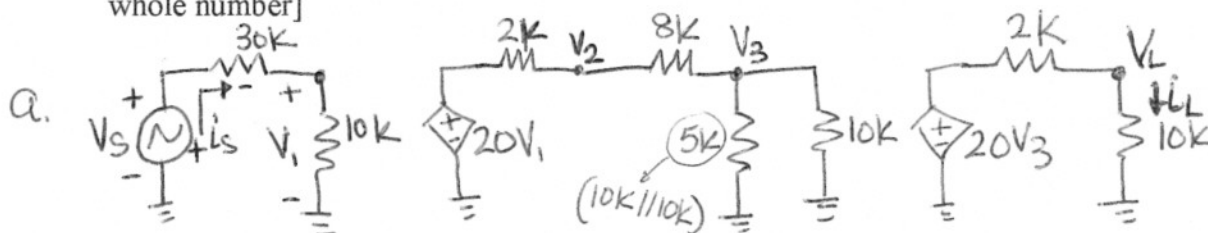(c) Find $A_i = \frac{i_L}{i_s}$. Express your answer as a ratio(A/A) and in dB. [Round the answer to the nearest whole number]



$$b. \quad V_L = \frac{20V_3 \cdot 10K}{12K} = \frac{200}{12} V_3$$

$$V_3 = \frac{20V_1 \cdot (5K \parallel 10K)}{(5K \parallel 10K) + 8K + 2K}$$


$$V_1 = \frac{V_s (10K)}{40K}$$

$$V_L = \frac{200}{12} \cdot \frac{20 (5K \parallel 10K)}{(5K \parallel 10K) + 10K} \cdot \frac{10K}{40K} \cdot V_s \Rightarrow \boxed{\frac{V_L}{V_s} = 21 \text{ V/V} \approx 26\text{dB}}$$

$$c. \quad i_L = \frac{V_L}{10K} \quad ; \quad i_s = \frac{V_s}{40K}$$

$$\frac{i_L}{i_s} = \frac{V_L / 10K}{V_s / 40K} = \frac{V_L}{V_s} \cdot \frac{40K}{10K} = \boxed{84 \text{ V/V} \approx 39\text{dB}}$$

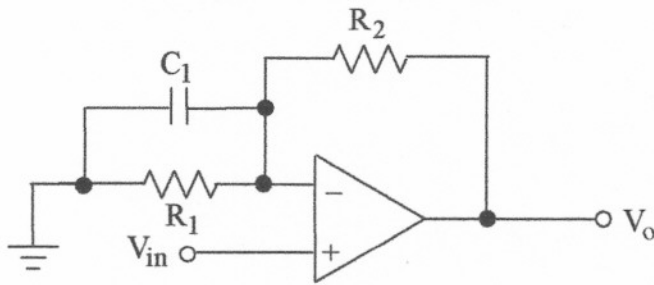4. Analyze the circuit below to obtain the transfer function, V_o/V_{in} . Assume an ideal op amp. Sketch the straight line approximation for the Bode Plots.





$$\frac{V_o}{V_{in}} = \left(\frac{R_2}{(R_1 \parallel \frac{1}{C_1 s})} + 1 \right)$$

$$R_1 \parallel \frac{1}{C_1 s} = \left[\frac{R_1 (\frac{1}{C_1 s})}{R_1 + \frac{1}{C_1 s}} \right] \frac{C_1 s}{C_1 s}$$

$$\frac{V_o}{V_{in}} = \frac{R_2(C_1 R_1 s + 1) + R_1}{R_1} = \frac{(R_1 + R_2) \left(\frac{R_1 C_1 s R_2}{(R_1 + R_2)} + 1 \right)}{R_1} = \frac{R_1}{R_1 C_1 s + 1}$$

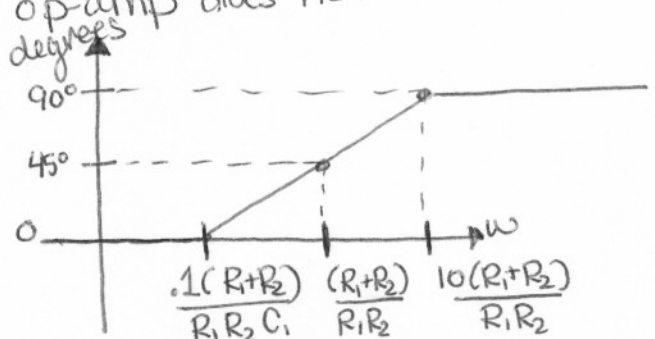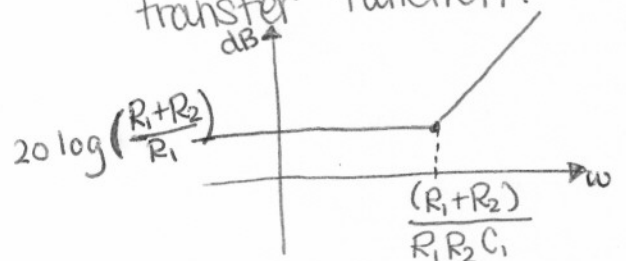Assume ideal $\Rightarrow f_T$ huge so op-amp does not affect transfer function:



5. Redraw or add to the schematic below to show how to reduce the effect of the input bias current. State the symbolic value(s) of any components added to the schematic.

