
 


1. Referring to a forward biased pn junction diode, determine the following:

- a) For p-type and n-type material, state the majority and minority carriers (holes or electrons).
p-type: majority = holes, minority = e⁻ / n-type: majority = e⁻, minority = holes
- b) Explain what happens as the temperature changes (increase and decreases) to the number of MAJORITY carriers in this p-type and n-type material?
T ↑ ↓, p-type holes / n-type e⁻ No change $P_{po} = N_A$, $n_{po} = N_D$
- c) Explain what happens as the temperature changes (increase and decreases) to the number of MINORITY carriers in this p-type and n-type material?
T ↑, p-type e⁻ ($n_{po} = n_i^2 / N_A$) ↑, n-type holes ($p_{no} = n_i^2 / N_D$) ↑, T ↓ both ↓
- d) Explain in your own words, how the diffusion current, I_D , is created.
when p-n junction is forward biased, depletion region becomes smaller and e⁻ from n-type are injected into p-type which creates current flow I_D .
- e) Explain what happens as the temperature changes (increase and decreases) to the diffusion current, I_D ?
T ↑ ⇒ I_S ↑ (eg. 3.64) which causes I_D ↑, T ↓, I_D ↓ (same reason)





 
2. a) Draw the cross section of a mosfet.



$V_{DS} \leq (V_{GS} - V_t)$ triode ⇒ rectangular shaped channel

SAT ⇒ channel becomes triangular shaped and then pinched off

     - b) Explain in your own words and drawings as needed how, when (under what conditions), and in what direction the current flows in the mosfet. $V_{GS} \geq V_t$ for I to flow ⇒ NMOS I flows D to S, PMOS I flows S to D.
- c) Explain in your own words all the different regions for Fig. 4.6 by drawing cross-sections of the mosfet to correspond to each region in that figure and explaining how each region operates (i.e. how the channel looks, how the current flows, etc).




$i_D = \frac{1}{2} k_n \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$
 Fig 4.6
 SAT

Fig. 4.11

- d) Explain in your own words what the difference between Fig. 4.6 and Fig. 4.11.
- e) What equation and region of operation is graphed in Fig. 4.12. *one VGS curve, multiple VGS curves*
- f) Explain in your own words how the PMOS differs from the NMOS transistor.
PMOS: I flows Source to Drain same eq. as NMOS just take absolute values for comparisons. V_t is negative

 3. Analyze the circuit shown below to determine the voltages (V_D , V_G , V_S) at all nodes and the currents through all branches (5 currents). Let $V_t=1.5V$ and $k_n'(W/L)=2A/V^2$. Neglect the channel length modulation effect (i.e. $\lambda=0$).



$$I_1 = \frac{5}{50k} = 100\mu A$$

$$I_G = 0A$$

$$V_G = \frac{5(25k)}{50k} = 2.5V$$

$$I_D = I_S = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2$$

$$V_{GS} = V_G - V_S = 2.5 - 10(I_D)$$

$$I_D = \frac{1}{2} (2) (2.5 - 10(I_D) - 1.5)^2 = (1 - 10I_D)^2 = 1 - 20I_D + 100I_D^2$$

$$0 = 1 - 20I_D + 100I_D^2$$

$$I_D = \frac{20 \pm \sqrt{20^2 - 4(100)}}{200} = 0.137 \text{ or } 0.073$$

$$I_D = 0.137 :$$


$$V_{GS} = V_S = 2.5 - 1.37 = 1.13 < V_t \text{ (would be off)}$$

$$\therefore I_D = 0.073A \Rightarrow \begin{cases} V_S = 0.73V \\ V_D = 5V \end{cases}$$

SATURATION conditions satisfied \Rightarrow

$$V_{DS} \geq V_{GS} - V_t$$

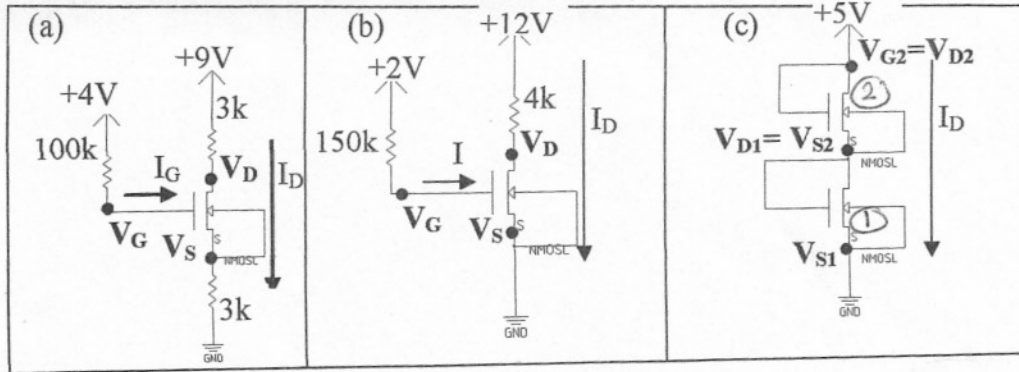4. Solve the circuits below to find V_G , V_D , and V_S . Find the currents in all branches. Assume $\lambda=0$ and $k_n'(W/L)=1\text{mA/V}^2$.



a. Assume sat \Rightarrow

$$I_G = 0$$

$$V_G = +4V \quad V_S = I_D(3k)$$

$$I_D = \frac{1}{2}(1m)(4 - I_D(3k) - 1)^2$$

$$2kI_D = (3^2 - 18kI_D + I_D^2(9k^2))$$

$$\therefore I_D^2(9k^2) - 20kI_D + 9 = 0$$

$$I_D = \frac{+20k \pm \sqrt{400M - 324M}}{2(9k^2)}$$

$$I_D = \frac{20k \pm 8.7k}{18M} \approx 1.6m, 628\mu$$

$$I_D = 1.6m \Rightarrow V_S = 4.8V$$

$$V_{GS} = 4 - 4.8 = 0.8V < V_t \text{ x off}$$

$$I_D = 628\mu \Rightarrow V_S = 1.884V$$

$$V_{GS} = 2.116 > V_t \therefore \text{ON}$$

$$+9 - I_D(3k) = V_D$$

$$V_D = 7.116V$$

$$V_{DS} \geq (V_{GS} - V_t) \checkmark \text{SAT}$$

b. Assume Sat \Rightarrow

$$I = 0, V_G = +2V$$

$$V_{GS} = +2V > V_t \text{ ON}$$

$$I_D = \frac{1}{2}k_n'(W/L)(V_{GS} - V_t)^2$$

$$I_D = \frac{1}{2}(1m)(+2 - 1)^2$$

$$I_D = 500\mu A$$

$$V_D = +12 - 4k \cdot I_D$$

$$V_D = +10V$$

$$V_{DS} \geq (V_{GS} - V_t) \checkmark \text{SAT}$$

$$V_S = 0V$$

$$c. V_{G2} = V_{D2} = +5V$$

$$V_{S1} = 0V$$

$$I_D = \frac{1}{2}k_n'(W/L)(+5 - V_{S2} - 1)^2$$

For ②

$$I_D = \frac{1}{2}k_n'(W/L)(V_{S2} - 1)^2$$

From ①

$$\frac{1}{2}k_n'(W/L)(4 - V_{S2})^2 = \frac{1}{2}k_n'(W/L)(V_{S2} - 1)^2$$

$$(4 - V_{S2}) = (V_{S2} - 1)$$

$$4 + 1 = V_{S2} + V_{S2}$$

$$V_{S2} = \frac{+5}{2}$$


Use ② or ①

$$\textcircled{2} I_D = \frac{1}{2}(1m)\left(5 - \frac{5}{2} - 1\right)^2 = 1.125\text{mA}$$

$$\textcircled{1} I_D = \frac{1}{2}(1m)\left(\frac{5}{2} - 1\right)^2 = 1.125\text{mA}$$

 5. Use: $V_t=2V$, $K_n'(W/L)=50\mu A/V^2$, $\lambda=0$
 $V_I = 5+0.001\sin(10t)$
 Assume all capacitors are open for DC analysis and shorted for AC analysis

- Solve for the DC currents: I_1 , I_D , and I_S
- Solve for the DC voltages: V_G , V_S and V_O
- State the operating point, bias point, or quiescent point for this amplifier
- Draw the small-signal equivalent circuit
- Analyze the small-signal circuit for V_O/V_I .



a. $I_1 = 0$ $I_D = I_S$

$$I_D = \frac{1}{2}(50\mu)(V_{GS} - V_t)^2$$

$$V_{GS} = V_G - V_S$$

$$V_G = 0$$

$$V_S = I_D(1k) - 10$$

$$\therefore I_D = \frac{1}{2}(50\mu)(0 - I_D(1k) + 10 - 2)^2$$

$$I_D(40k) = (I_D^2(1k)^2 + 64 - 16(1k)I_D)$$

$$I_D = \frac{56k \pm \sqrt{(56k)^2 - 4(1k)^2(64)}}{2(1k)^2} = 1.2m, 54.8m \rightarrow \text{Gives } V_{GS} \approx -45$$

$$V_S = -8.8V$$


d) $V_{GS} = 8.8V$ which gives $\Rightarrow I_D = 1.2m$

$$V_D = V_O = 15 - I_D(1k) = 13.8V$$

$$\therefore V_{DS} = 22.6 > (V_{GS} - V_t) = 6.8V$$

\therefore bias point (operating point, or q point) is the voltage, V_{GS} .

d) AC analysis \rightarrow

 

Note: $R_{in} = 2M$
 R_{out} (ignore load $1k \parallel 2k$) = $1k$

$$V_g = \frac{V_I(2M)}{4M} = \frac{1}{2}V_I$$

$$V_s = 0 \quad \therefore V_{gs} = \frac{1}{2}V_I$$

$$V_o = -g_m V_{gs} \left(\frac{1}{2}1k\right) \text{ DC value}$$

$$g_m = K_n'(W/L)(V_{GS} - V_t) = 50\mu(8.8 - 2)$$

$$g_m = 340\mu A/V$$


$$\therefore V_o = -340\mu \left(\frac{1}{2}V_I\right)(500)$$

$$\frac{V_o}{V_I} = -85m$$

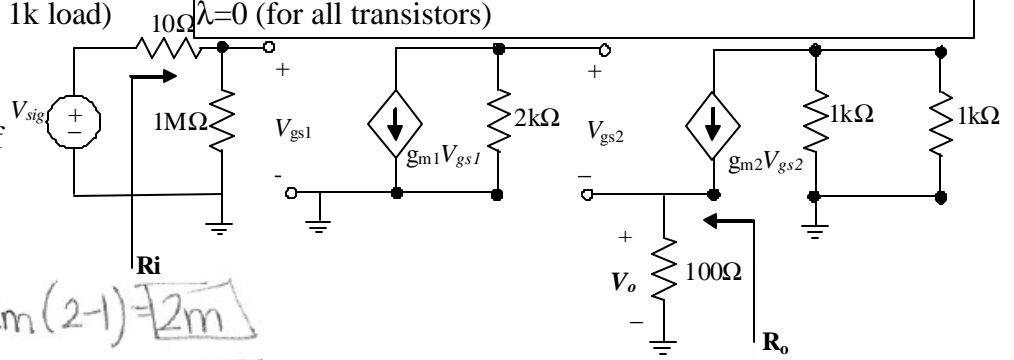6. For the following hybrid- π equivalent circuit, find the following values:

- R_i (input resistance - ignore the 10Ω and V_{sig})
- R_o (output resistance - ignore the $1k$ load)
- gain, $\frac{V_o}{V_{sig}}$
- Draw the transistor schematic of this circuit

Use: $V_t=1V$, $K_n'(W/L)=2mA/V^2$, V_{sig} is an AC source
 Transistor 1 has DC values: $V_{GS1}=2V$, $I_{D1}=1mA$
 Transistor 2 has DC values: $V_{GS2}=3V$, $I_{D2}=4mA$
 $\lambda=0$ (for all transistors)



$$g_{m1} = \sqrt{2(2m)1m} = 2m(2-1) = 2m$$

$$g_{m2} = \sqrt{2(2m)4m} = 2m(3-1) = 4m$$

a) $R_i = 1M$

b) $R_o = 100\Omega \parallel \frac{1}{g_{m2}} = 100 \parallel 250 \approx 71\Omega$


c) $V_o = +g_{m2} V_{gs2} (100)$

$$V_{gs2} = V_{g2} - V_o = -g_{m1} V_{gs1} (2k) - g_{m2} V_{gs2} (100)$$

$$V_{gs1} = \frac{V_{sig}(1M)}{1M+10} \approx V_{sig}$$

$$V_{gs2} = \frac{-g_{m1}(2k)V_{sig}}{1+g_{m2}(100)}$$
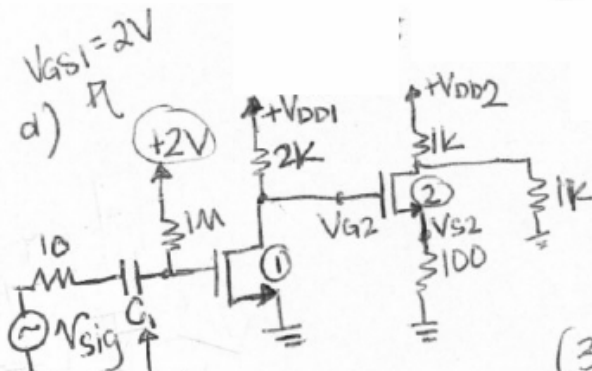
$$\frac{V_o}{V_{sig}} = \frac{g_{m2}(100)(-g_{m1})(2k)}{1+g_{m2}(100)} = -1.14V/V$$



Cap has to be here so that DC analysis does not ground this node due to V_{sig} shorting for DC analysis.

$$V_{s2} = 4m(100) = 0.4V$$

$$V_{G2} = V_{GS2} + V_{S2} = 3 + 0.4 = 3.4V$$



$$(3.4V = V_{G2}) = V_{DD1} - 1m(2k)$$

$$\therefore V_{DD1} = 5.4V$$



$$V_{DD2} - 4m(1k) \geq (V_{G2} - V_t) = 3.4 - 1 = 2.4V$$

$$\therefore V_{DD2} \geq 2.4 + 4 = 6.4V$$

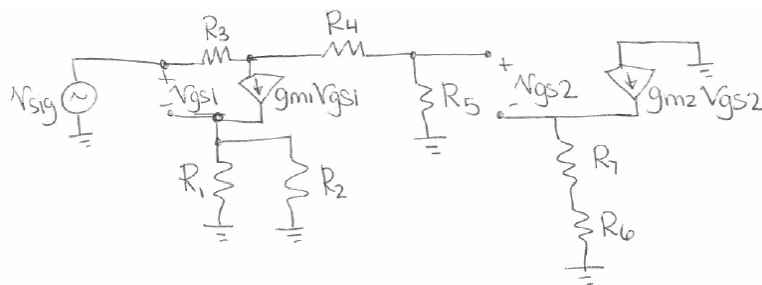 7. For the circuit shown below, **draw** the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , v_{gs2} , etc.). $\lambda=0$ for all transistors. $v_{sig}=0.001\sin(10t)$ AC and $V_2=10V$ DC.



  8. $v_{sig} = \{8 + 0.01\sin(\omega t)\}$ Volts. Does this circuit operate as a **linear** AC amplifier? If so, what is the gain, $\frac{V_o}{V_{sig}}$, of the following circuit in terms of V_{DD} , V_{sig} , R_{sig} , $k'(W/L)$? If not, explain why. The graph below shows measurements for this circuit.



This mosfet is biased at a gate voltage of $V_G=8V$ and $V_S=0$.
 $\therefore V_{GS} = 8V$.

It looks like the transistor will be in triode \Rightarrow

$$V_{DS} \approx 0 < (V_{GS} - V_{t}) = 8 - 1 = 7V$$

\therefore TRIODE Region \rightarrow will not amplify linearly