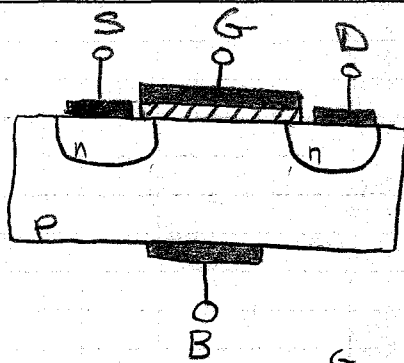


1) a)

NMOS




- - Metal (Al)
- ▨ - Oxide ( $\text{SiO}_2$ )
- - Semiconductor (Si)


S  $\equiv$  SourceG  $\equiv$  GateD  $\equiv$  DrainB  $\equiv$  Body

or

PMOS

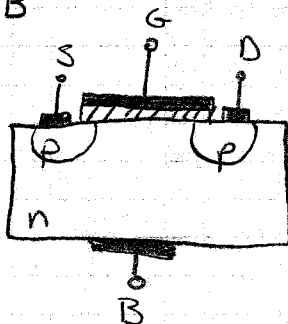

b)

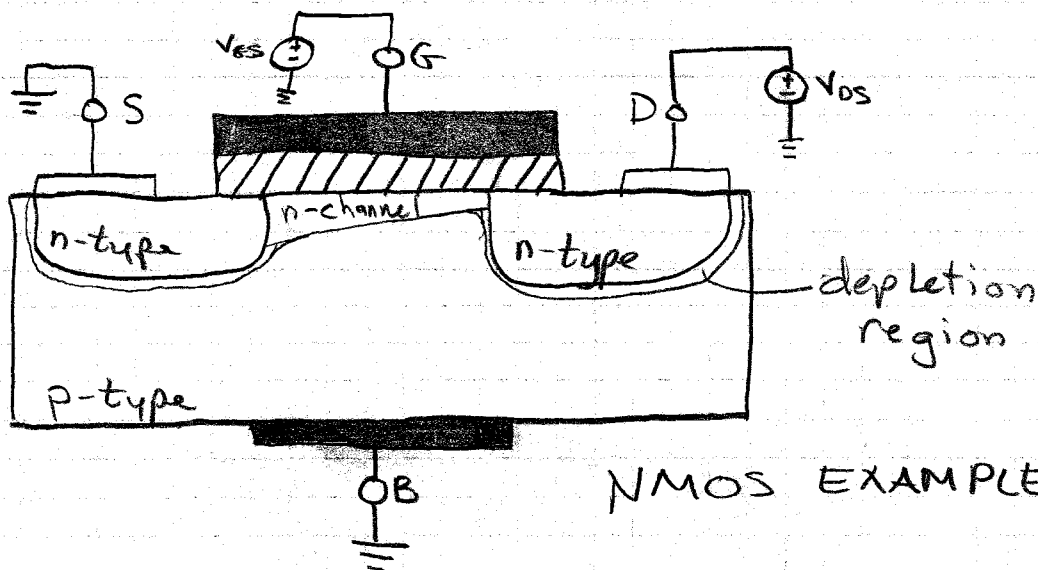



NMOS EXAMPLE

Current flows in the MOSFET when:

①  $V_{GS} > V_t$

②  $V_{DS} \neq 0V$

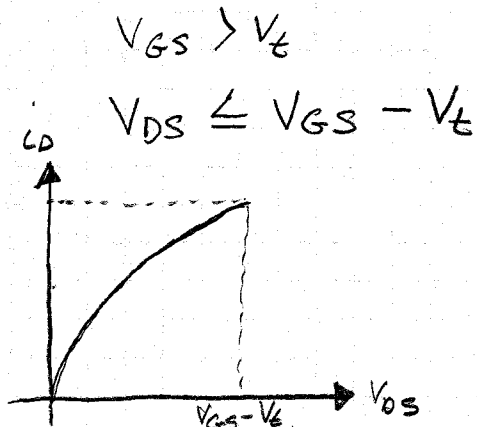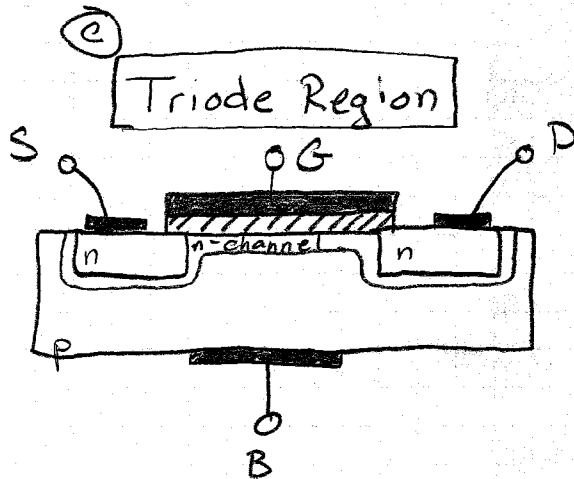Note: If  $V_{DS} < 0$ , then the source becomes the drain and the drain becomes the source since the MOSFET as shown is symmetrical (not true for discrete transistors since the body is usually tied to the source).



Induced channel increases at nearly the same rate in all directions with increased  $V_{DS}$  in this region. The I-V relationship is shown on the graph. It is characterized by the following equation.

$$I_D = k'_n \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

where:

$$k'_n = \mu_n C_{ox}$$

$\mu_n$   $\equiv$  electron mobility of semiconductor material

$$\frac{W}{L} \equiv \text{aspect ratio}$$

$C_{ox} \equiv$  gate capacitance per unit gate area  
 $(C_{ox} = \epsilon_{ox} / t_{ox})$


$W \equiv$  channel width

$t_{ox} \equiv$  oxide thickness  
 $\epsilon_{ox} \equiv$  oxide permittivity

$L \equiv$  channel length


$V_t \equiv$  threshold voltage

### Saturation Region

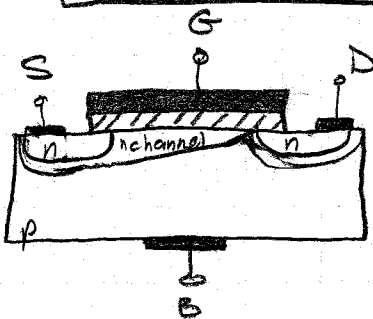

$V_{GS} > V_t$   
 $V_{DS} \geq V_{GS} - V_t$
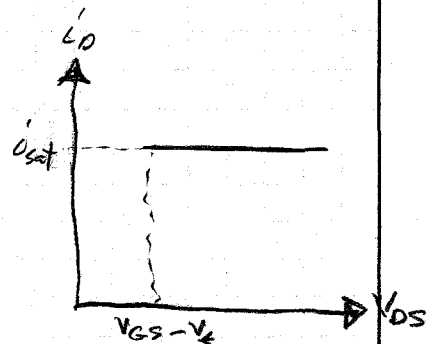
$$I_D = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2$$



$$I_{Dsat} = \frac{1}{2} k'_n \frac{W}{L} (V_{GS} - V_t)^2$$

Induced channel is uneven and "pinched off" stopping the current from increasing with the voltage.

$V_{DS}$ . Note: It still increases by a small amount. See page 254, figure 4.16 of the textbook.

2) a) Figure 4-6 is demonstrating the  $I_D$ - $V_{DS}$  relationship of a MOSFET for a fixed value of  $V_{GS}$ .

Figure 4-11 is demonstrating the same thing for various values of  $V_{GS}$ .

Fig. 4-6

$I_D$  varies

$V_{DS}$  varies

$V_{GS}$  constant

Fig 4-11

$I_D$  varies

$V_{DS}$  varies

$V_{GS}$  varies

b) This is the saturation region when  $V_{DS}$  is held constant and  $V_{GS}$  is varied.

c) As shown in the figure for question #1a, a PMOS is built in an n-type substrate so that it must induce a p-type channel. An NMOS is built in a p-type substrate so that it must induce an n-type channel.

3) Find  $V_D$ ,  $V_G$ ,  $V_S$ ,  $I_D$ ,  $I_S$ ,  $I_G$ ,  $I_1$ ,  $I_2$   
Neglect channel length modulation.

Assume  $I_G = 0$ , then

$$I_1 = I_2 = \frac{10V - 2V}{2k\Omega} = 4mA$$

$$V_G = (4mA)(1k\Omega) = 4V$$

$$V_S = I_S(20\Omega)$$

$$V_D = 10V - I_D(10\Omega)$$


Assume Triode

$$I_D = \frac{2A}{V^2} \left[ (V_{GS} - V_E) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

$$I_S = \frac{V_S}{20\Omega}$$

$$I_D = \frac{10V - V_D}{10\Omega}$$

$$I_S = I_D$$

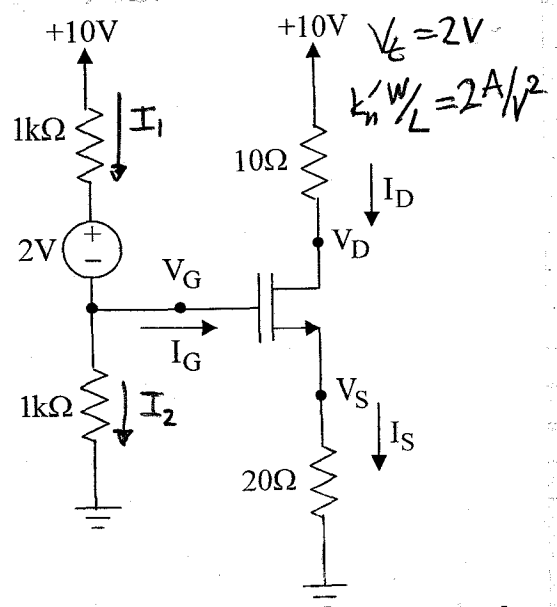

$$I_S = I_D \Rightarrow \frac{V_S^2}{20\Omega} = \frac{10V - V_D}{10\Omega} \Rightarrow V_D = 10V - \frac{1}{2} V_S$$

$$\Rightarrow V_{DS} = 10V - \frac{3}{2} V_S$$

Substitute into triode equation.

$$\frac{V_S}{20\Omega} = 2 \frac{A}{V^2} \left[ (2V - V_S)(10V - \frac{3}{2} V_S) - \frac{1}{2} (10V - \frac{3}{2} V_S)^2 \right]$$

$$V_S = 40 \frac{1}{V} \left[ 200V^2 - 3V_S - 10V_S + \frac{3}{2} V_S^2 - \frac{1}{2} (100V^2 - 30V_S + \frac{9}{4} V_S^2) \right]$$

$$75V_S^2 + 79V_S - 1200 = 0$$

$$V_S^2 + \frac{79}{15} V_S - 80 = 0$$

$$V_S = 6.691V \Rightarrow$$

$$V_{GS} = V_G - V_S = 4V - 6.691V$$

$V_{GS} < 0$ ? Wrong! Assume Saturation.

$$I_D = (V_{GS} - 2)^2 = (2 - V_S)^2 = \frac{V_S}{20}$$

$$\Rightarrow V_S^2 - 4V_S - \frac{V_S}{20} + 4 = 0$$

$$\Rightarrow V_S^2 - \frac{81}{20} V_S + 4 = 0$$


$$V_S = 2.3422V \text{ or } 1.7078V$$

$$V_{GS} = 4V - 2.34 = 1.66V < V_t = 2V \text{ wrong!}$$

$$V_{GS} = 4V - 1.71 = 2.29V > V_t = 2V \text{ right!}$$

$$I_D = I_S = \frac{V_S}{20\Omega} = \frac{1.71V}{20\Omega} = 85.5mA$$
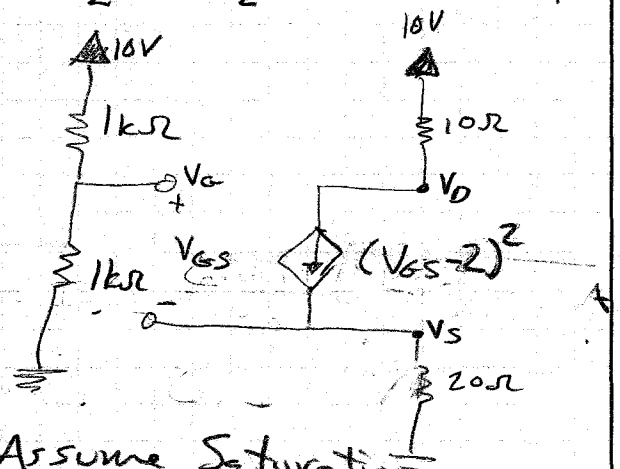
$$V_D = 10V - 10\Omega (85.5mA) = 9.15V$$



Answers:

The MOSFET IS IN SATURATION:  $V_{GS} > V_t$ 

$$V_{GS} = 4V - 1.71V = 2.29V > V_t \quad V_{DS} \geq V_{GS} - V_t$$

$$V_{DS} = 9.15V - 1.71V = 7.44V > V_{GS} - V_t$$

Voltages:

$$V_S = 1.71V$$

$$V_D = 9.15V$$

$$V_G = 4V$$

Currents:

$$I_S = I_D = 85.5mA$$

$$I_G = 0A$$

$$I_1 = I_2 = 4mA$$

④ Find  $V_S$ ,  $\lambda=0$ ,  $|V_t| = 1$ ,  $k_n \frac{W}{L} = 1mA/V^2$

$$V_G = V_D \Rightarrow V_{DS} > V_{GS} - |V_t| \Rightarrow \text{MOSFET Sats}$$

$$I_D = I_S = \frac{k_n}{2} \frac{W}{L} (V_{GS} - |V_t|)^2$$

$$I_S = \frac{1mA}{2} V^2 (9V - V_S)^2$$


$$I_S = \frac{V_S}{1k\Omega}$$

$$2V_S = (9 - V_S)^2$$

$$V_S^2 - 20V_S + 81 = 0$$

$$V_S = \frac{20 \pm \sqrt{20^2 - 4(81)}}{2} = \frac{20 \pm \sqrt{76}}{2} = \frac{20 \pm 8.72}{2} = \frac{28.72}{2} \text{ or } \frac{11.28}{2}$$


$$\therefore V_S = 5.64V$$

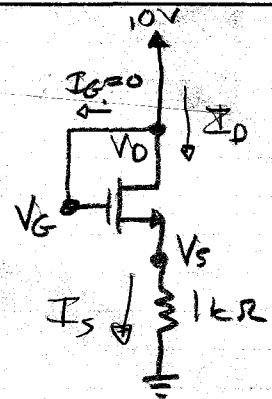

Not Possible

Exceeds Source Voltages.
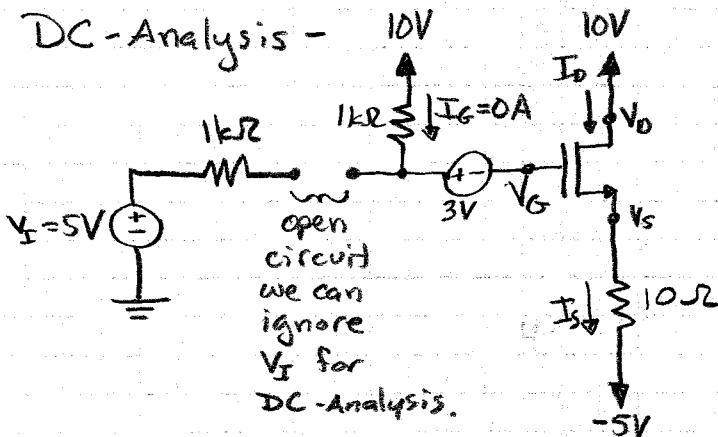
$$5) V_t = 1V \quad K_n' \frac{W}{L} = 10 \mu A/V^2 \quad \lambda = 0$$



Note:  $I_G = 0A$ , so  $V_G = 10V - 3V = 7V$

$$V_D = 10V$$

$$V_D > V_G - V_t \Leftrightarrow 10V > 7V - 1V = 6V \quad (\text{MOSFET SAT.})$$

$$I_S = I_D = \frac{1}{2} K_n' \frac{W}{L} (V_{GS} - V_t)^2 = \frac{1}{2} 10 \mu A/V^2 (6V - V_S)^2$$

$$I_S = \frac{V_S + 5V}{10 \Omega} \Rightarrow V_S = -5V + 10 \Omega I_S$$

$$I_S = 10 \mu \frac{1}{2} (6 + 5 - 10 I_S)^2$$

$$200 \mu I_S = (11 - 10 I_S)^2 \Rightarrow 100 I_S^2 - 100.22k \cdot I_S + 121 = 0$$

$$\Rightarrow I_S^2 - 200.22k I_S + 121 = 0$$

$$I_S = \frac{200.22k \pm \sqrt{(200.22k)^2 - 4(121)}}{2} =$$

$$0.6e-3 \square$$


200e5  
not physically possible (transistor would burn out first)

$$a) I_G = 0A, I_D = I_S = 0.6mA$$

$$b) V_G = 7V, V_D = 10V, V_S = -4.998V$$

$$c) \text{The } Q\text{-point is } V_{GS} = 11.998V$$

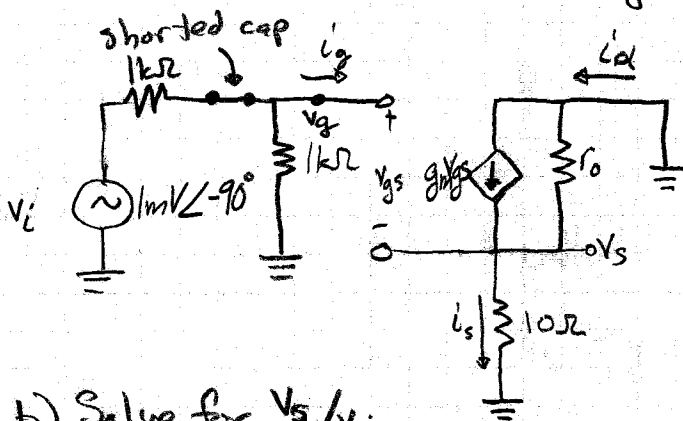6) a) Draw the small signal equivalent circuit.



$$r_o = \frac{1}{\lambda I_D} = \infty \text{ (open)}$$

$$\Rightarrow i_d = i_s = g_m v_{gs}$$

$$g_m = \frac{2I_D}{V_{GS} - V_t} = \frac{2 \times 0.18 \text{ mA}}{11.998 \text{ V}} = 30 \mu\text{A/V}$$

b) Solve for  $v_s/v_i$ .

$$v_g = \frac{1}{2} v_i \quad \leftarrow \text{voltage divider}$$

$$v_g/v_i = 1/2$$

$$v_s = 10 \Omega i_s = 10 \Omega \cdot g_m v_{gs} = 10 \Omega \cdot 30 \mu\text{A/V} (v_g - v_s)$$

$$v_s = \frac{300 \mu\text{A/V} v_g}{1 + 300 \mu\text{A/V}}$$


$$\frac{v_s}{v_g} = 300 \mu\text{A/V}$$

$$\frac{v_g}{v_i} \cdot \frac{v_s}{v_g} = \frac{v_s}{v_i} = 300 \mu\text{A/V} \cdot \frac{1}{2} = 150 \mu\text{A/V}$$

$$\therefore v_s/v_i = 150 \mu\text{A/V}$$

$$7) V_t = 2V, k_n' W/L = 100 \mu A/V^2, \lambda = 0 \quad V_I = 3 + 1 \text{msin}(10t) \text{ V}$$

DC Analysis:

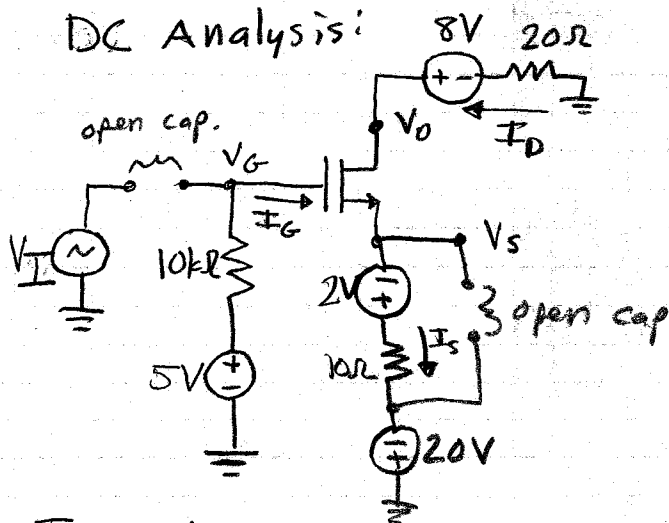

$$I_G = 0A$$

$$V_G = 5V - (0A) \cdot 10k\Omega = 5V$$

$$V_D = 8V - I_D (20\Omega) \text{ and } I_D = \frac{8V - V_D}{20\Omega}$$

$$V_S = -20V + I_S (10\Omega) - 2V$$

$$I_S = I_D \Rightarrow V_S = -22V + I_D (10\Omega) \text{ and } I_D = \frac{V_S + 22V}{10\Omega}$$

For now - assume saturation:

$$I_S = I_D = \frac{1}{2} k_n' \frac{W}{L} (V_{GS} - V_t)^2 =$$

$$\frac{1}{2} 100 \mu (3 - V_S)^2 = \frac{V_S + 22V}{10}$$

$$\frac{1}{2} (3 - V_S)^2 = 1k V_S + 22k$$

$$\frac{1}{2} V_S^2 - \frac{6}{2} V_S + \frac{9}{2} - 1k V_S - 22k = 0$$

$$V_S^2 - 6V_S + 9 - 2kV_S - 44k = 0$$

$$V_S = -21.7V \text{ or } 2.027kV \text{ not physically possible}$$

$$V_{GS} = 5 - (-21.7) = 26.7V \quad I_D = \frac{V_S + 22V}{10\Omega} = 30mA$$


$$V_{DS} = V_D - V_S = 8V - 20\Omega(I_D) - (-21.7) = 29.1V$$

$$V_{DS} - V_{GS} = 2.4 > V_t \text{ (FET in Saturation)} \checkmark$$



- (a)  $I_G = 0$ ,  $I_D = I_S = 30 \text{ mA}$   
 (b)  $V_G = 5 \text{ V}$ ,  $V_S = -21.7 \text{ V}$ ,  $V_D = 7.4 \text{ V}$   
 (c)  $V_{GS} = 26.7 \text{ V}$

8)

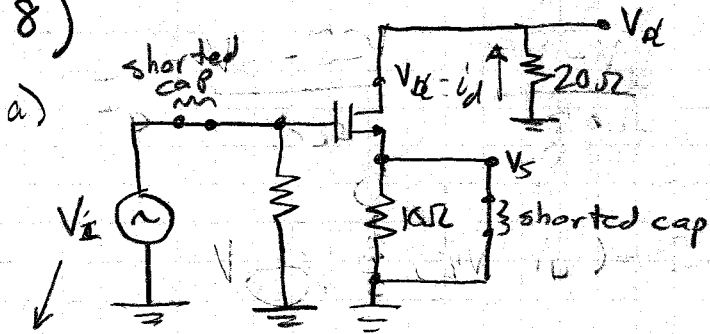

$$v_i = 1 \text{ m} \sin(10t)$$

b) From circuit  $v_s = 0 \text{ V}$

$$i_d = g_m v_{gs} = \frac{2 I_D v_{gs}}{V_{ov}} = \frac{2 (30 \text{ mA})}{24.7} v_{gs} = 2.43 \text{ mA/V} \cdot v_{gs}$$

$$v_{gs} = v_i \Rightarrow \frac{v_{gs}}{v_i} = 1 \quad \frac{v_{gs}}{v_i} = \frac{v_g}{v_i} = 1$$

$$v_d = -i_d (20 \Omega)$$

$$\frac{v_d}{i_d} = -20 \Omega \quad \frac{i_d}{v_{gs}} = 2.43 \text{ mA/V} \quad \frac{v_{gs}}{v_i} = 1$$

$$\frac{v_d}{i_d} \cdot \frac{i_d}{v_{gs}} \cdot \frac{v_{gs}}{v_i} = \frac{v_d}{v_i} = -20 \frac{\text{V}}{\text{A}} (2.43 \text{ mA/V}) \cdot 1 \frac{\text{V}}{\text{V}} = -48.6 \frac{\text{mV}}{\text{V}}$$

$$\therefore \frac{v_d}{v_i} = -48.6 \frac{\text{mV}}{\text{V}}$$