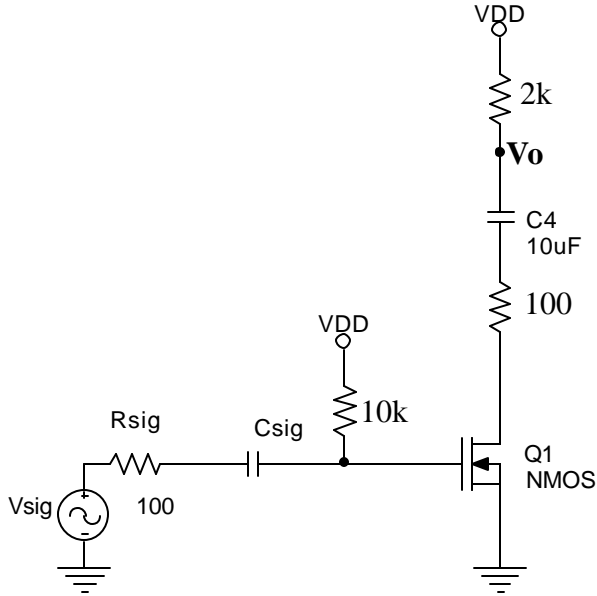


1. Use: $g_m=100\text{mA/V}$ for the circuit below. V_{sig} is an AC signal source.

- (a) Derive the frequency response transfer function for V_o/V_{sig} in terms of C_{sig} .
- (b) Find the value of C_{sig} where the low 3db frequency value, $f_L = 10\text{ Hz}$ (note this is in Hz – not rad/sec).



- 2. (a) Solve the DC circuit(schematic below) to find I_D and V_{GS} (assume caps open)
- (b) Use Matlab to find the value that V_{dd} can be reduced and still keep the transistor in saturation.
- 3. Solve the AC circuit(schematic below):

 - (a) Draw the small-signal equivalent circuit (assume caps shorted)
 - (b) Find the midband gain $\frac{V_o}{V_i}$ (V_i is an AC source)
 - (d) Find R_{in} (node to right of capacitor, remove V_i and 1k)
 - (e) Find R_{out} (node to left of capacitor, remove 4k)

Given:


$$V_t=2.831\text{V}$$

$$k_n'(W/L)=3.1\text{A/V}^2$$

4. Solve the circuit(schematic below) by including the capacitors in the AC small-signal equivalent circuit. Solve the frequency transfer function V_o/V_i .


- 5. Simulate the circuit using PSPICE and IRF150 for the MosFet.

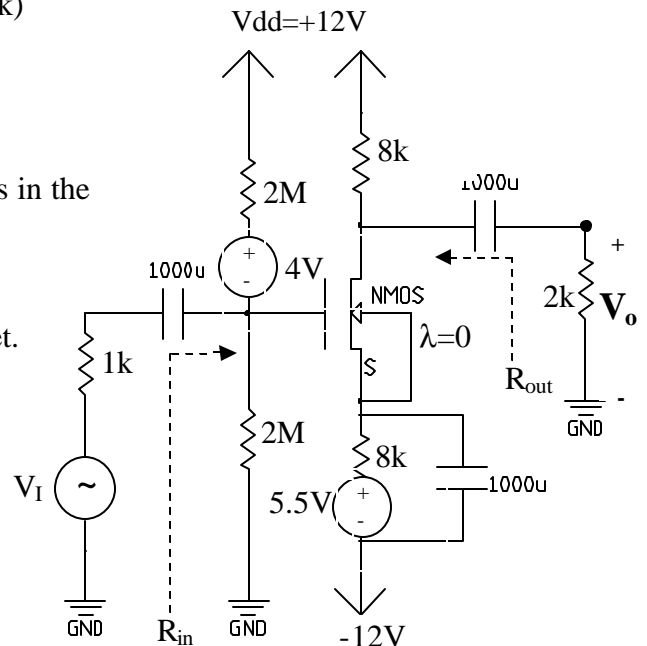 - (a) Find and compare the simulated AC bode plot with the theoretical function found in (4).
 - (b) Find and compare the DC values found in (2). If there are differences describe why.



6. V_I is an AC voltage source. Use $\lambda=0$, $g_m=1\text{mA/V}^2$
 $R_G=10\Omega$, $R_{G1}=2\text{M}\Omega$, $R_{G2}=10\text{M}\Omega$, $R_d=10\text{k}\Omega$, $R_S=1\text{k}\Omega$, $R_L=10\text{k}\Omega$.

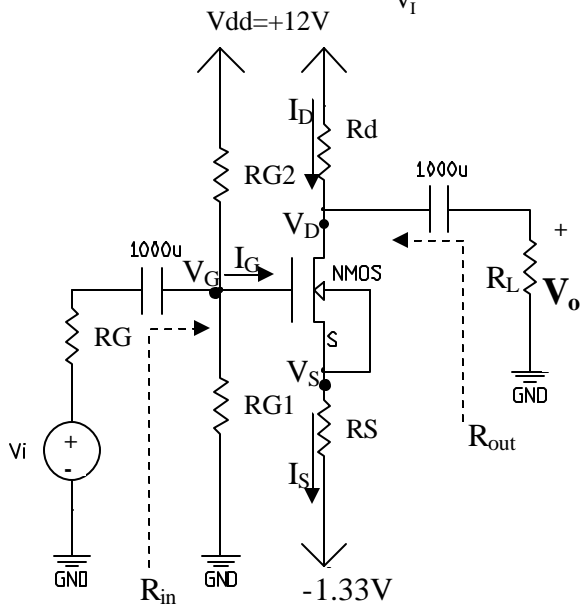(a) Find the midband gain $A_v = \frac{V_o}{V_I}$ (use small-signal model), R_{in} (remove R_G) and R_{out} (remove R_L)



7. Use $V_t=2\text{V}$, $k_n'(W/L)=3\text{mA/V}^2$, $\lambda=0$, V_s is an AC voltage source. $g_m=10\text{mA/V}^2$

(a) Find the midband gain $A_v = \frac{V_o}{V_s}$ (use small-signal model), R_{in} (remove 10) and R_{out} (remove 10k)

