
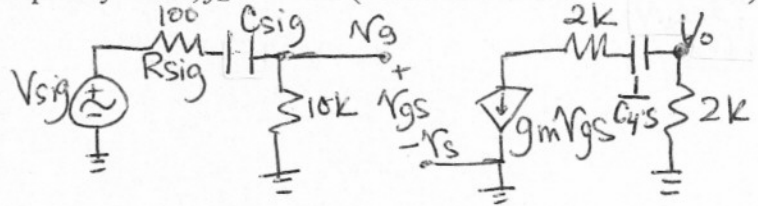


1. Use: $g_m = 100 \text{ mA/V}$ for the circuit below. V_{sig} is an AC signal source.

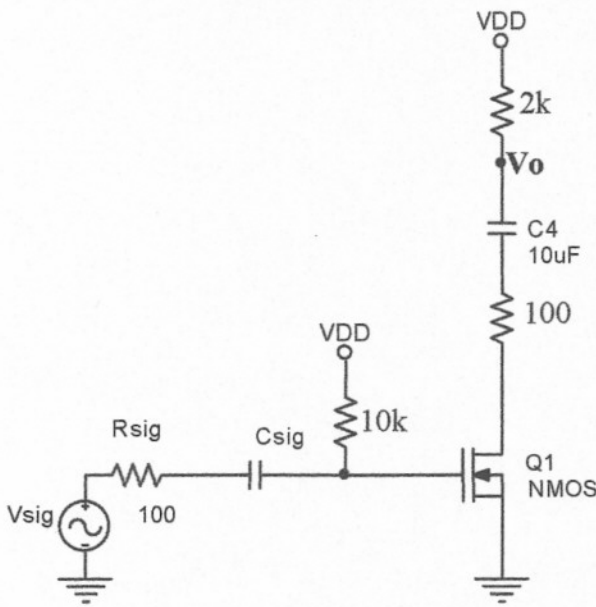- (a) Derive the frequency response transfer function for V_o/V_{sig} in terms of C_{sig} .
- (b) Find the value of C_{sig} where the low 3db frequency value, $f_L = 10 \text{ Hz}$ (note this is in Hz – not rad/sec).



$$V_o = -g_m V_{gs} (2k)$$

$$V_{gs} = \left[\frac{V_{sig}(10k)}{10k + 100 + \frac{1}{C_{sig} \cdot s}} \right] \frac{C_{sig} \cdot s}{C_{sig} \cdot s}$$

$$V_{gs} = \frac{V_{sig}(10k)(C_{sig} \cdot s)}{C_{sig} \cdot s (10k + 100) + 1}$$

$$\frac{V_o}{V_{sig}} = \frac{-g_m (10k)(2k)(C_{sig} \cdot s)}{[C_{sig} \cdot s (10k + 100) + 1]} = \boxed{\frac{-2 \text{ Meg} \cdot s \cdot C_{sig}}{(10,100 \cdot C_{sig} \cdot s + 1)}}$$

$$f_L = 10 \text{ Hz} \quad \therefore \omega = 2\pi f \approx 63 \text{ rad/sec.}$$

$$s = \frac{1}{10,100 \cdot C_{sig}} = 63 \text{ rad/sec.} \Rightarrow \boxed{C_{sig} \approx 1.6 \mu\text{F}}$$

2. (a) Solve the DC circuit (schematic below) to find I_D and V_{GS} (assume caps open)
- (b) Use Matlab to find the value that V_{DD} can be reduced and still keep the transistor in saturation.
3. Solve the AC circuit (schematic below):
 - (a) Draw the small-signal equivalent circuit (assume caps shorted)
 - (b) Find the midband gain $\frac{V_o}{V_i}$ (V_i is an AC source)
 - (d) Find R_{in} (node to right of capacitor, remove V_i and 1k)
 - (e) Find R_{out} (node to left of capacitor, remove 4k)

Given:


$$V_t = 2.831V$$

$$k_n'(W/L) = 3.1A/V^2$$

4. Solve the circuit (schematic below) by including the capacitors in the AC small-signal equivalent circuit. Solve the frequency transfer function V_o/V_i .

5. Simulate the circuit using PSPICE and IRF150 for the MosFet.

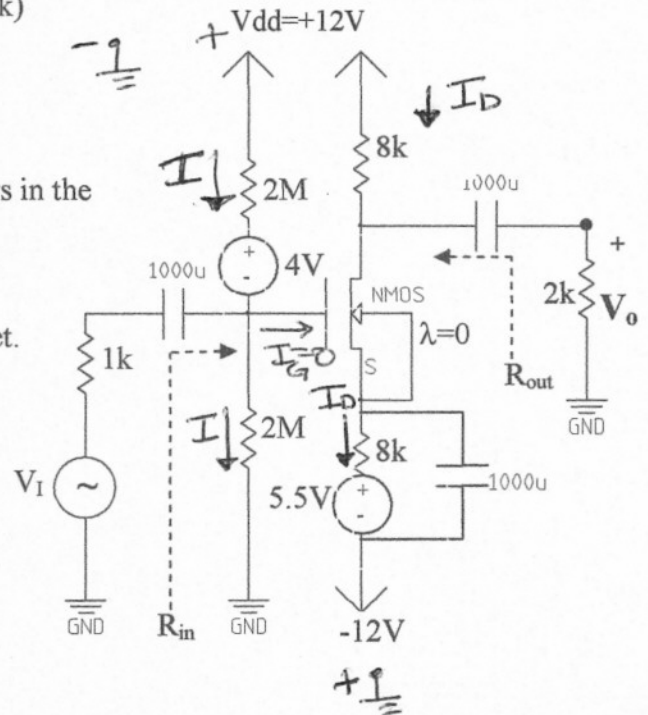- (a) Find and compare the simulated AC bode plot with the theoretical function found in (4).
- (b) Find and compare the DC values found in (2). If there are differences describe why.



2.(a)

$$+12 - I(2M) - 4 - I(2M) = 0$$

$$I = \frac{8}{4M} = 2\mu A$$

$$V_G = I(2M) = 4V$$

$$+V_S - I_D(8k) - 5.5 + 12 = 0 \Rightarrow V_S = I_D(8k) - 6.5$$

SAT:


$$I_D = \frac{1}{2}(3.1)(4 - I_D(8k) + 6.5 - 2.831)^2$$

↓ solving

$$I_D = \boxed{.956m}, .962m \rightarrow V_S = .962m(8k) - 6.5 = 1.96$$


$$V_S = .956m(8k) - 6.5 = 1.148$$
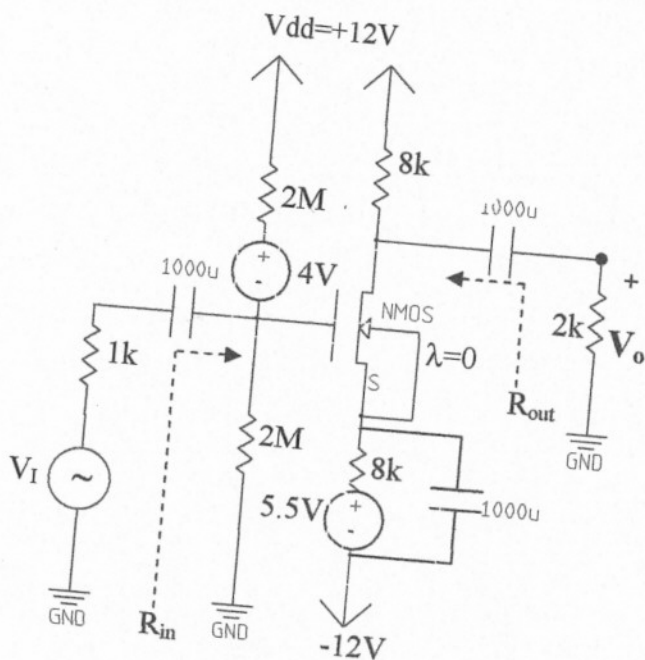
$$V_{GS} = 4 - 1.148 = \boxed{2.852V} > V_t$$



$$g_m = \sqrt{2(3.1)(.956\text{mA})} \approx .077 \frac{\text{A}}{\text{V}^2}$$
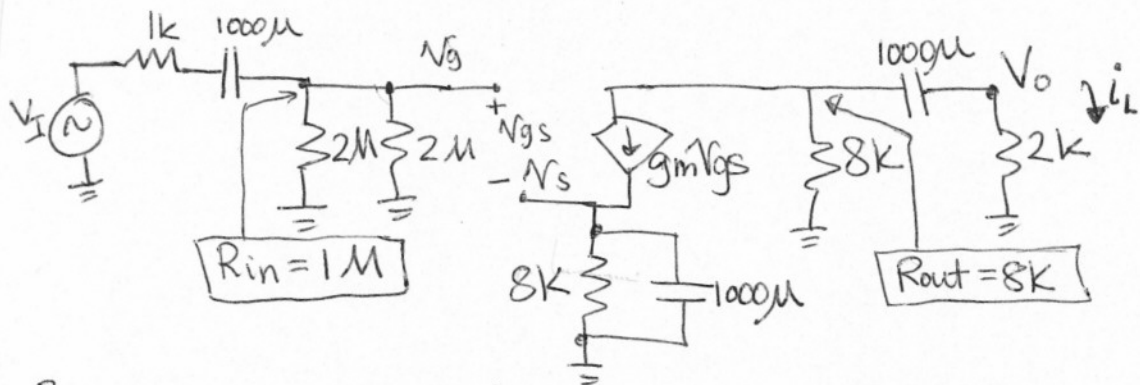
$$4. \frac{V_o}{V_i} = \frac{-1997 \cdot s^2 (8s+1)}{(10s+1)(1,001s+1)(\frac{8s}{617}+1)}$$



3. when caps shorted: $V_o = -g_m V_{gs} (8k \parallel 2k) = -g_m V_{gs} (1600)$

$$V_g = \frac{V_i (1M)}{1M + 1k} \approx V_i \quad \therefore V_{gs} \approx V_i$$

$$\Rightarrow \frac{V_o}{V_i} \approx -123.2 \frac{V_o}{V_i} \approx 41.8 \text{dB}$$

4. with caps: $i_L = \frac{-g_m V_{gs} (8k)}{8k + 2k + \frac{1}{1000\mu \cdot s}} = \frac{-g_m (8k) V_{gs} (1000\mu \cdot s)}{10k(1000\mu \cdot s) + 1} = \frac{-616 V_{gs} \cdot s}{(10s+1)}$

$$V_o = i_L \cdot 2k = \frac{-1232 \cdot V_{gs} \cdot s}{(10s+1)}$$


$$V_g = \frac{V_i (1M)}{1M + 1k + \frac{1}{1000\mu \cdot s}} = \frac{V_i (1M) 1000\mu \cdot s}{(1M+1k)(1000\mu \cdot s) + 1} = \frac{1000 \cdot V_i \cdot s}{(1001 \cdot s + 1)}$$

$$V_s = g_m V_{gs} (8k \parallel \frac{1}{1000\mu \cdot s}) = \frac{g_m V_{gs} (8k)}{(8s+1)} \Rightarrow V_{gs} = \frac{1,000 V_i \cdot s}{(1001 \cdot s + 1)} \cdot \frac{616 V_{gs}}{(8s+1)}$$

$$\therefore \frac{V_o}{V_i} = \frac{-1232 \cdot s \cdot 1,000 \cdot s (8s+1)}{47(10s+1)(1,001 \cdot s + 1)(\frac{8s}{617} + 1)} \rightarrow \text{see top 2 of page}$$

PSpice Simulation:

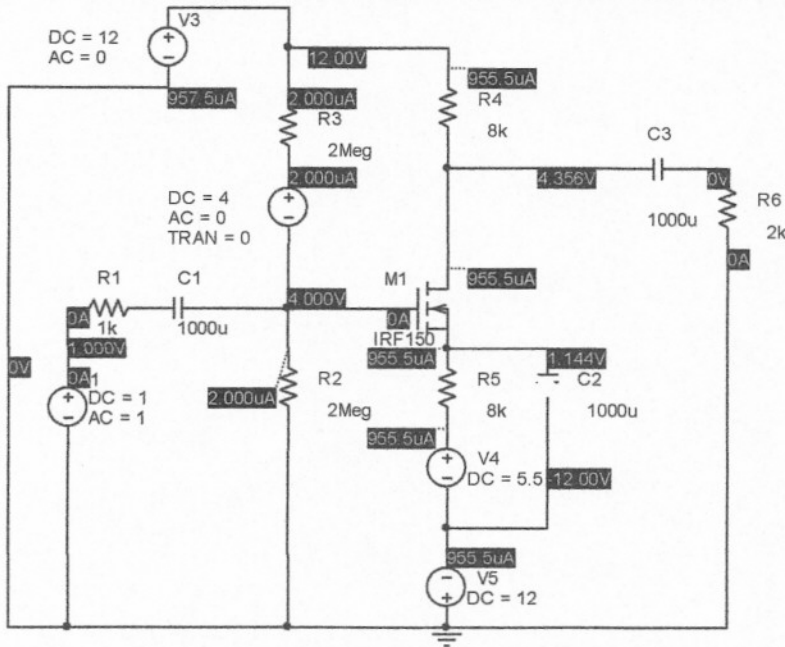DC values are similar to analysis in (2). Difference is due to rounding I_D .




Graph below is has dB for the y-axis. Comparing to (3) =>

- Midband gain = 123.2V/V which is 41.8dB. Graph below shows midband gain at 41.7dB.
- 3dB value from calculation is the highest pole value which is $617/8=77\text{rad/sec} = 12\text{Hz}$. The graph below had a measurement of the 3dB at 12.6Hz.

○ Differences are very slight between the hand calculations and the simulation

PSPICE Simulation:

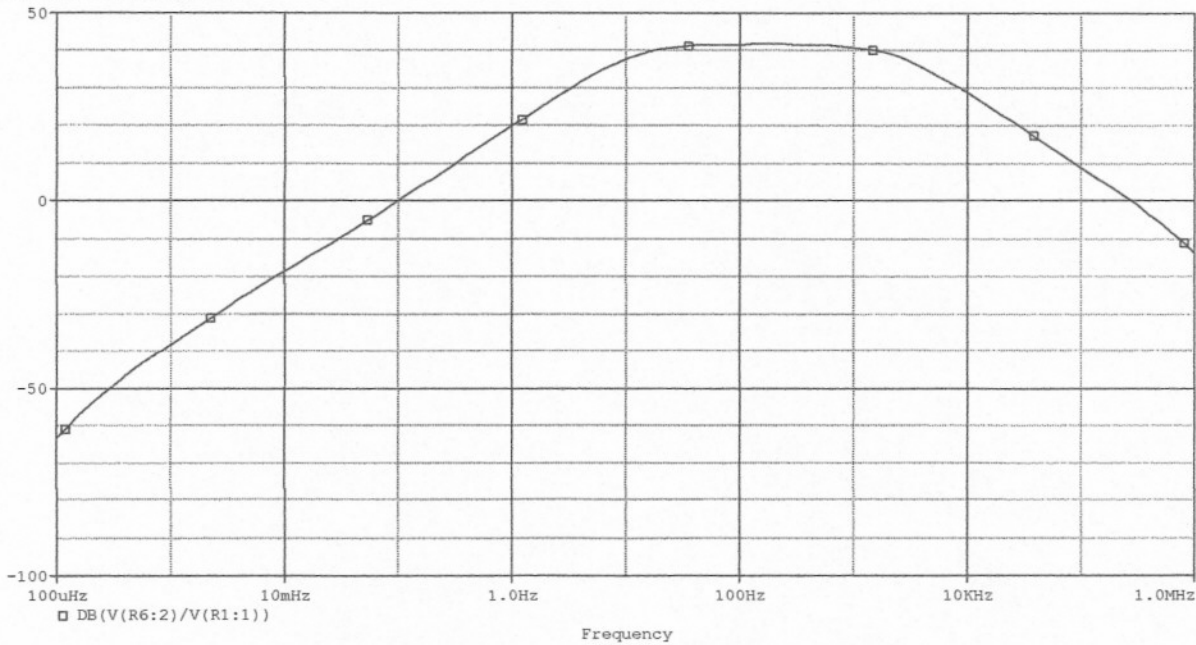

6. V_I is an AC voltage source. Use $\lambda=0$, $g_m=1\text{mA/V}^2$
 $R_G=10\Omega$, $R_{G1}=2\text{M}\Omega$, $R_{G2}=10\text{M}\Omega$, $R_d=10\text{k}\Omega$, $R_S=1\text{k}\Omega$, $R_L=10\text{k}\Omega$.

(a) Find the midband gain $A_v = \frac{V_o}{V_i}$ (use small-signal model), R_{in} (remove R_G) and R_{out} (remove R_L)

• Common-Source Configuration with emitter resistance.

$$R_{in} = 2\text{M} \parallel 10\text{M}$$

$$R_{in} \approx 1.7\text{M}$$

$$R_{out} = 10\text{k}$$

Note: Amplifier part without input (V_I & R_G) and output load $R_L = 10\text{k}$

$$\rightarrow A_{vo} = \frac{V_o}{V_g}$$


$$V_o = -g_m V_{gs} (10\text{k})$$

$$V_{gs} = V_g - g_m V_{gs} (1\text{k})$$

$$V_{gs} = \frac{V_g}{1+1} = \frac{V_g}{2}$$

$$\frac{V_o}{V_g} = \frac{-10}{2} = -5 \text{ V/V}$$

with model:

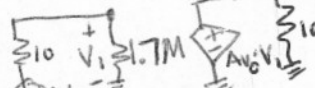



$$\Rightarrow V_o = A_{vo} V_i \cdot \frac{10\text{k}}{10\text{k} + 10\text{k}}$$

$$V_i \approx V_I$$

$$\therefore \frac{V_o}{V_I} = \frac{-5}{2} = -2.5 \text{ V/V (same)}$$

$$\frac{V_o}{V_I} = -2.5 \text{ V/V}$$
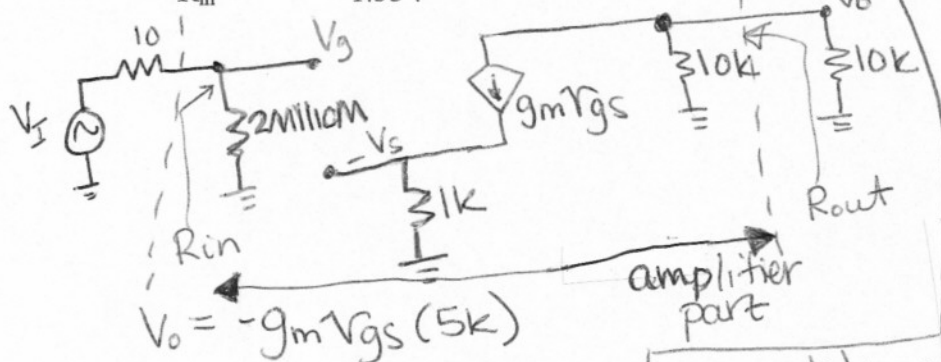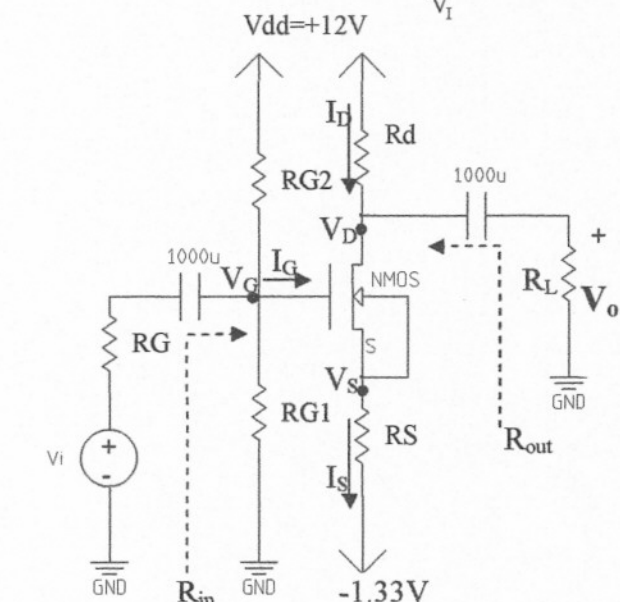
$$V_o = -5 \frac{V_I}{2} = -2.5 V_I \Rightarrow$$



$$V_o = -g_m V_{gs} (5\text{k})$$

$$V_g \approx V_I$$

$$V_s = g_m V_{gs} (1\text{k})$$


$$\therefore V_{gs} = V_I - g_m V_{gs} (1\text{k})$$

$$V_{gs} + g_m V_{gs} (1\text{k}) = V_I$$

$$V_{gs} = \frac{V_I}{1+1} = \frac{V_I}{2}$$

7. Use $V_t=2V$, $k_n'(W/L)=3mA/V^2$, $\lambda=0$, V_s is an AC voltage source. $g_m=10mA/V^2$

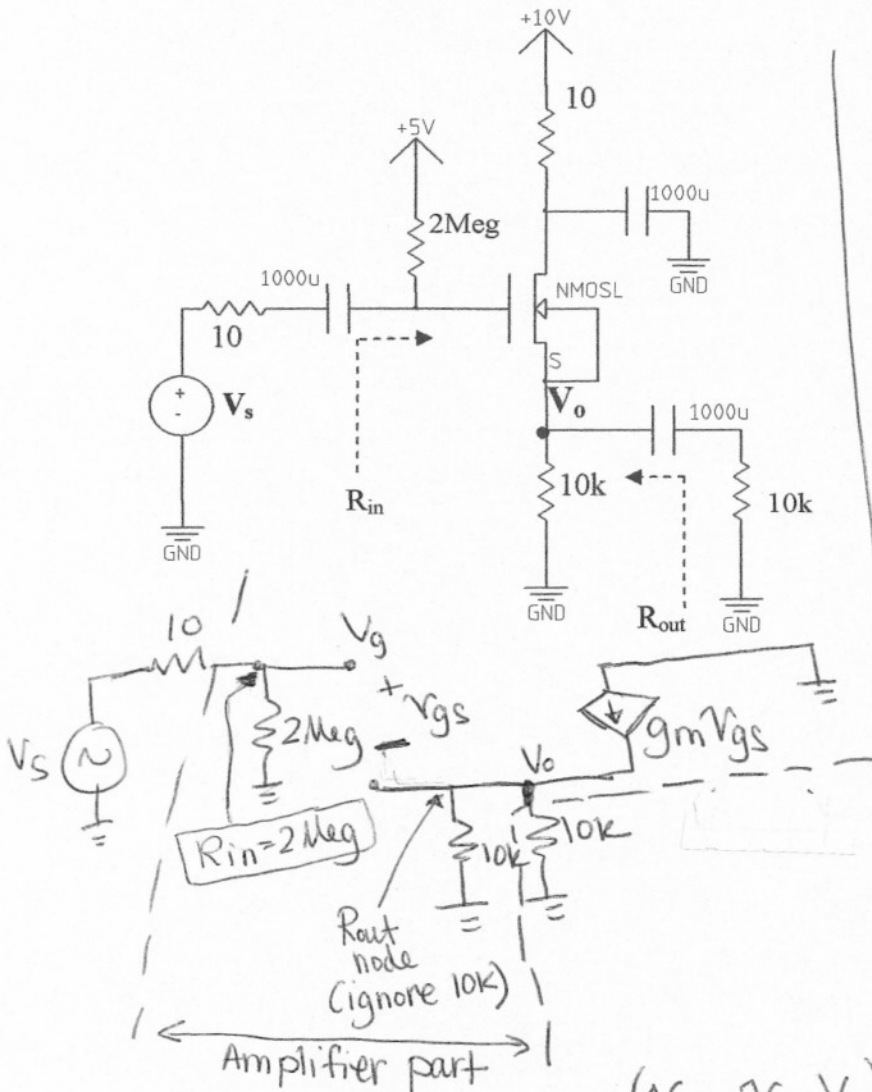(a) Find the midband gain $A_v = \frac{V_o}{V_s}$ (use small-signal model), R_{in} (remove 10) and R_{out} (remove 10k)



$$V_o = g_m V_{gs} (10k \parallel 10k)$$

$$V_g = V_s \frac{2Meg}{2Meg + 10} \approx V_s$$

$$V_o = g_m V_{gs} (5k)$$


$$V_{gs} = V_g - g_m V_{gs} (5k)$$

$$V_{gs} = \frac{V_s}{1 + 50} = \frac{V_s}{51}$$

$$\frac{V_o}{V_s} = \frac{50}{51} \approx \boxed{.98 V/V}$$

$$(V_{gs} = V_g - V_o)$$

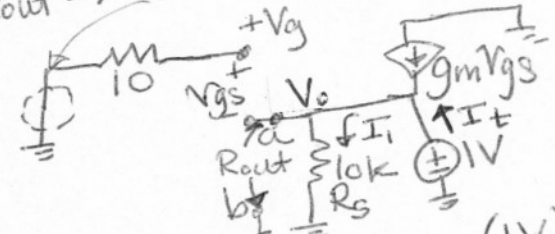
Common-Drain
 $R_{out} \Rightarrow$ ① short input \Rightarrow



② Apply test voltage (1V)

③ Measure $I_t \Rightarrow$

④ $R_{th} = \frac{1V}{I_t}$

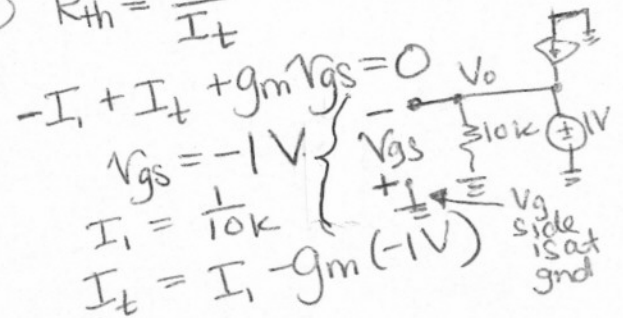

$$-I_t + I_t + g_m V_{gs} = 0$$

$$V_{gs} = -1V$$

$$I_t = \frac{1}{10k}$$

$$I_t = I_t - g_m (-1V)$$

$$I_t = \frac{1}{10k} + g_m$$

$$R_{th} = \frac{1}{\frac{1}{10k} + g_m} \quad (\text{note} \rightarrow \text{This is } R_{th} = R_s \parallel \frac{1}{g_m})$$


$$R_{th} = \boxed{R_{out} \approx 99 \Omega}$$

Note: with model of opamp \Rightarrow

$$A_{vo} = \frac{V_o}{V_g}$$

$$V_o = g_m V_{gs} (10k) = g_m (10k) \left(\frac{V_g}{1 + g_m (10k)} \right)$$
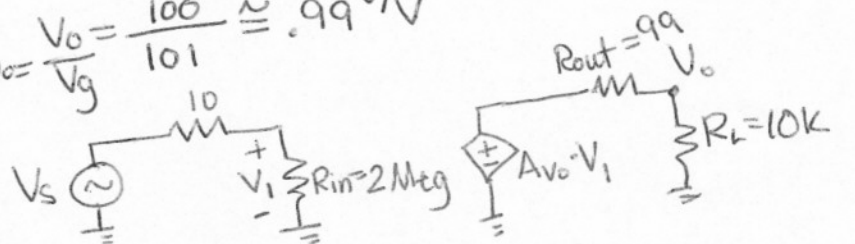
$$A_{vo} = \frac{V_o}{V_g} = \frac{100}{101} \approx .99 V/V$$



$$V_o = A_{vo} \cdot V_i \cdot \frac{10k}{10k + 99} = \frac{.99 V_s (10k)}{10k + 99}$$

$$V_i \approx V_s \Rightarrow \frac{V_o}{V_s} \approx .98 V/V \quad (\text{same})$$