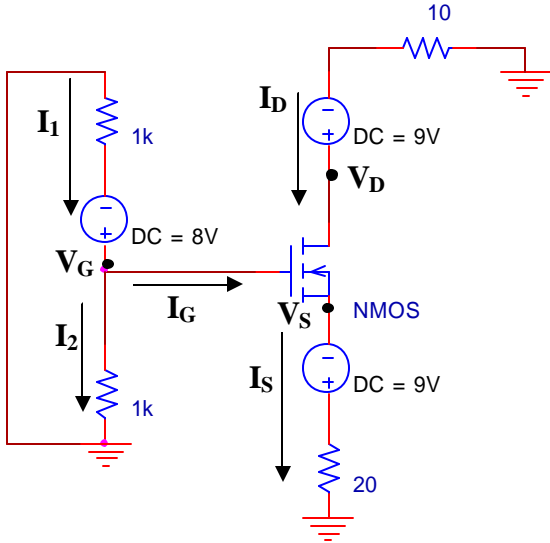


- Analyze the circuit shown below to determine the voltages (V_D , V_G , V_S) at all nodes and the currents through all branches (I_1 , I_2 , I_G , I_D , I_S). Let $V_t=2V$ and $k_n'(W/L)=180\mu A/V^2$. Neglect the channel length modulation effect (i.e. $\lambda=0$).
- If an AC source is applied at node V_G state the condition that needs to be satisfied for the ac input amplitude. (what is the small-signal condition?)



$$\begin{aligned}
 & I_D = I_S \quad I_1 = I_2 \\
 & I_G = 0 \\
 & -I_1(1k) + 8 - I_1(1k) = 0 \\
 & I_1 = \frac{8}{2k} = 4mA \\
 & V_G = I_2(1k) = 4m(1k) = 4V \\
 & +V_S + 9 - I_S(20) = 0 \\
 & V_S = I_S(20) - 9
 \end{aligned}$$

$$V_S = I_S(20)$$

$$I_S = I_D = \frac{1}{2} (180\mu) (4 - I_S(20) + 9 - 2)^2$$

$$I_S(11,111) = (121 - 440I_S + 400I_S^2)$$

$$0 = 400I_S^2 - 11,551I_S + 121$$

$$I_S = \frac{11,551 \pm \sqrt{(11,551)^2 - 4(121)(400)}}{2(400)} = 28.9, 0.0105 A$$

$$V_S = 569 \quad V_{GS} = -565$$

$$V_S = -8.79 \quad V_{GS} = 12.79V$$

$$+I_D(10) - 9 + V_D = 0$$

$$V_D = -I_D(10) + 9 = (-0.0105)(10) + 9 \approx 8.9V$$

$$V_{DS} \geq V_{GS} - V_t$$


$$8.9 = V_D \geq (V_G - V_t) = 2V \quad \checkmark$$

SAT

- $V_{ac} \ll 2(V_{GS} - V_t)$
 $V_{ac} \ll 2*(12.8-2)$
 $V_{ac} \ll 2*(10.8)$

Let $V_t=2V$, $k_n'(W/L)=180\mu A/V^2$, $I_D=I_S=10mA$, and $\lambda=0$.

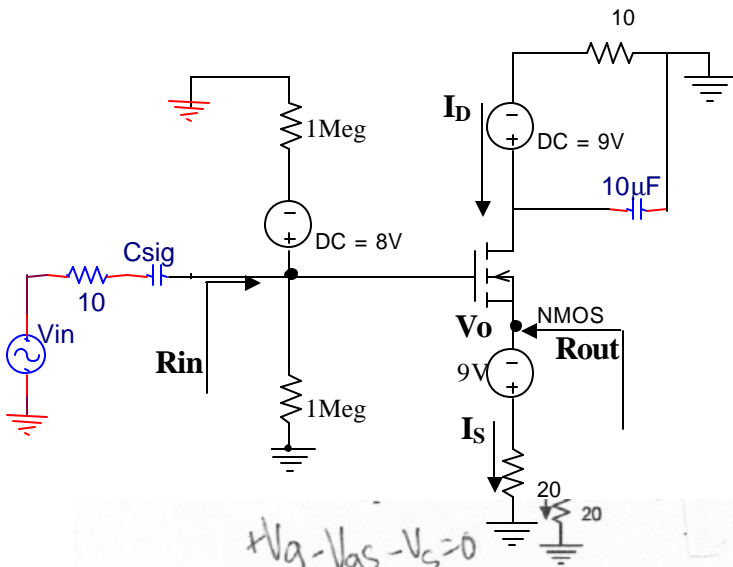2. Draw the small-signal equivalent circuit by assuming all capacitors become shorts.
3. Analyze the circuit to find $A_v=V_o/V_{in}$, R_{in} (remove 10Ω) and R_{out}
4. Explain how to make the input resistance, R_{in} more ideal. State exact resistors that could be changed and how they could be changed. If this resistors were changed, how does this effect the gain?
5. How could the overall gain be increased. By making that change, what is the tradeoff or what do you have to be careful about?
6. Derive the frequency response transfer function for V_o/V_{in} in terms of C_{sig} .
7. Find the value of C_{sig} where the low 3db frequency value, $f_L = 10$ Hz (note this is in Hz – not rad/sec).



$$g_m = \sqrt{2k_n'(W/L)I_D} = \sqrt{2(180\mu A/V^2)(10mA)}$$

$$g_m = \sqrt{3.6\mu A/V^2} \approx 1.9m$$

$+V_g - V_{gs} - V_s = 0$

$R_{in} = 500k$

$R_{out} = 20 \parallel \frac{1}{g_m}$

$R_{out} = \frac{20(527)}{527+20}$

$R_{out} \approx 19 \Omega$

$V_o = g_m V_{gs} (20)$

$(V_{gs} = V_g - V_s)$

$V_{gs} = \frac{V_{in}(500k)}{500k+10} - g_m V_{gs} (20)$

$V_{gs} + g_m V_{gs} (20) \approx V_{in}$

$V_{gs} = \frac{V_{in}}{1+g_m(20)}$

$\therefore V_o = \frac{g_m(20)}{1+g_m(20)} V_{in}$

$\frac{V_o}{V_{in}} = \frac{g_m(20)}{1+g_m(20)} \approx 3.7mV/V$

4. R_{in} can be increased to become more ideal \Rightarrow Change into Mega Ohms. No effect on gain.
5. Increase g_m which means to increase I_D . This will put the circuit at risk of moving out of the saturation region. Increasing the 20ohm will increase gain.