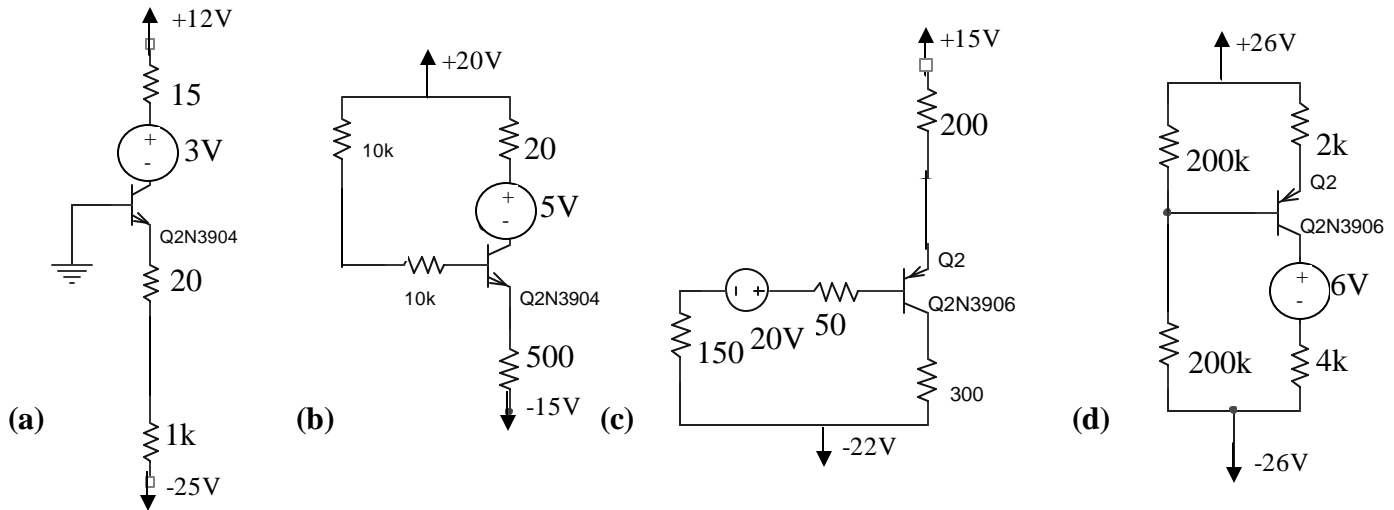


1.
  - a) Draw the cross section of a BJT.
  - b) Explain in your own words and drawings as needed how, when (under what conditions), and in what direction the current flows in the BJT for the 3 regions of operation.
2. Voltages are measured at the emitter, E, base, B, and collector, C, as shown below for an **npn** transistor. Determine what mode or operation the transistor is in.

Case	E	B	C	Mode
1	0	0.7	0.3	
2	-0.2	4	5	
3	1.2	1.2	15	
4	-1.4	-0.7	3	
5	0.7	0.7	0	
6	-0.7	0	-0.2	
7	5	5.7	5.7	
8	4	3	0	

3. Use  $|V_{BE}|=0.7$ ,  $\beta=100$ . Find voltages at all nodes and currents through all branches. (worth 4 problems)




- Use the circuit at the right for Problems 2 and 3
4. Assume active operation for all transistors.  
( $V_{sig}$  is an ac source)  
Assume that the capacitors act as an open for DC operation.

Find the symbolic equations for the DC values for  $I_{E1}$ ,  $V_{B2}$ ,  $I_{B2}$ ,  $V_{E2}$ ,  $V_{B3}$ ,  $V_o$

**You may use only  $R_{B1}$ ,  $R_{B2}$ ,  $R_{B3}$ ,  $R_{B4}$ ,  $R_{C1}$ ,  $R_{E1}$ ,  $R_{E2}$ ,  $R_{E3}$ ,  $R_L$ ,  $+10$ ,  $-10$ ,  $V_{BE}$ ,  $V_{EB}$ , and  $b$  or  $\alpha$ .**

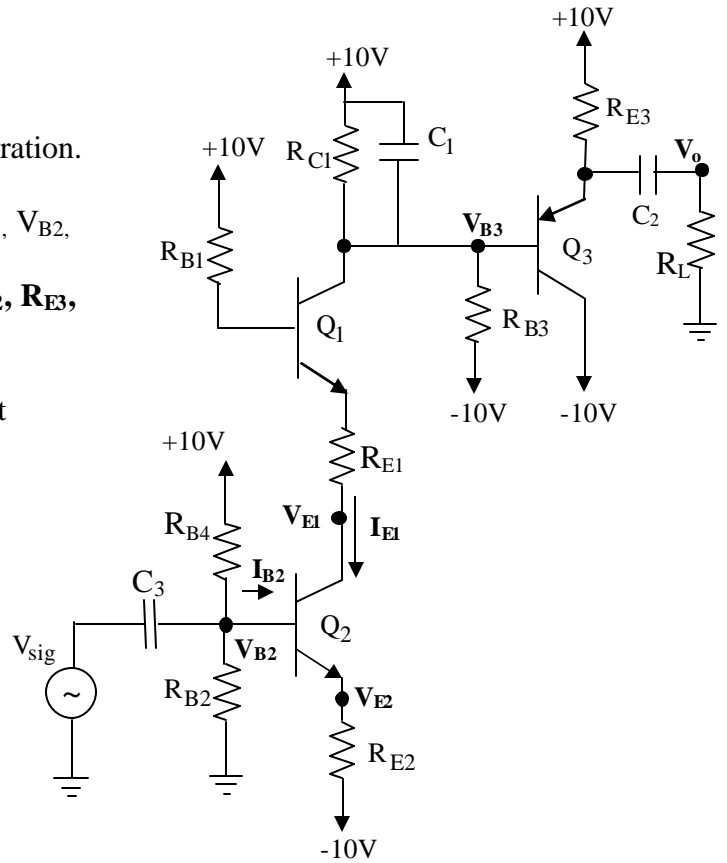5. Draw the hybrid- $\pi$  or model-T small signal circuit



6. Use  $|V_{BE}|=0.7$ ,  $\beta=20$ ,  $V_T=25mV$  ( $V_{sig}$  is an ac source), ignore  $r_o$ .

This small-signal model circuit is shown below. It was found through a DC analysis that  $I_{C1}=1mA$  and  $I_{C2}=2mA$ . The subscripts represent the 1<sup>st</sup> transistor by a subscript 1 and the 2<sup>nd</sup> transistor by a 1 subscript.

- Find the ac parameters,  $r_{\pi 1}$  and  $g_{m2}$
- Find a symbolic equation for the input resistance,  $R_{in}$ . (Ignore the AC input source and  $R_{sig}$ , include  $R_1$ )
- Find a symbolic expression for the overall gain,  $\frac{V_o}{V_{sig}}$ .

