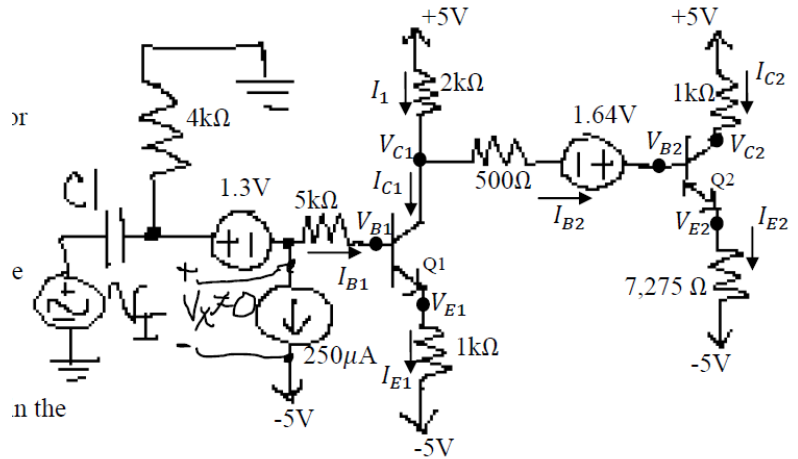



1. Use: ignore r_o , $|V_{BE}|=0.7$, $\beta=100$

- (a) Assume active mode and solve for the DC values:
 - a. $I_{B1}, I_{B2}, I_{E1}, I_{E2}, I_{C1}, I_{C2}$
 - b. $V_{B1}, V_{B2}, V_{E1}, V_{E2}, V_{C1}, V_{C2}$
- (b) Prove or disprove operation in the active region for both transistors.
- (c) What will be the maximum input for V_i if $V_{C2}/V_i = -5V/V$? (Assume the circuit is operating in the correct frequency range.)



2. Use: ignore r_o , $|V_{BE}|=0.7$, $\beta=100$

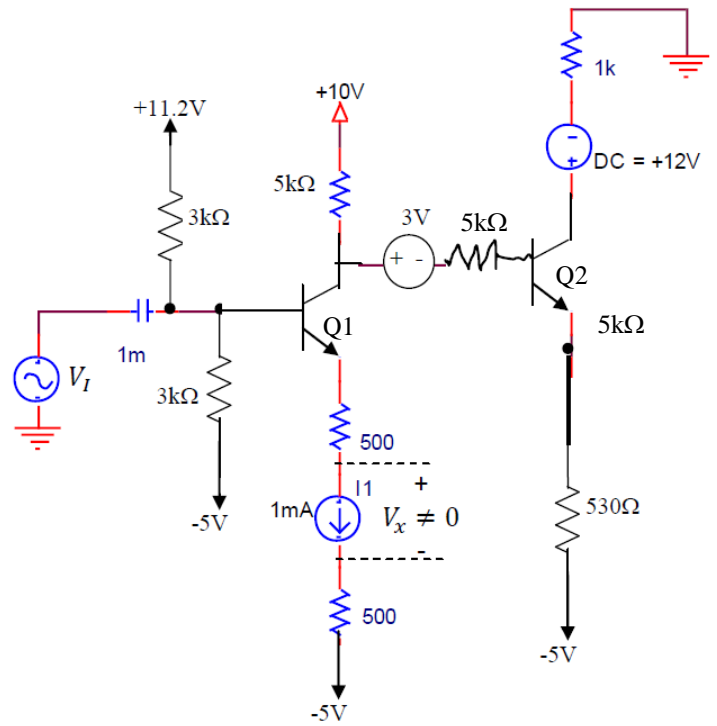- (a) Assume active mode and solve for the DC values:
 - a. $I_{B1}, I_{B2}, I_{E1}, I_{E2}, I_{C1}, I_{C2}$
 - b. $V_{B1}, V_{B2}, V_{E1}, V_{E2}, V_{C1}, V_{C2}$
- (b) Prove or disprove operation in the active region for both transistors.
- (c) What will be the maximum input for V_i if $V_{C2}/V_i = -5V/V$? (Assume the circuit is operating in the correct frequency range and that the amplification does not pull the transistors out of active region).




3. Use: ignore r_o , $|V_{BE}|=0.7$, $\beta=100$, $V_T=25mV$

$V_{sig} = 10 + 0.002\sin(20t)$

$r_{\pi 1} = 4,000$ and $g_{m2} = 10mA/V$

For the following hybrid- π equivalent circuit below, find the following values:

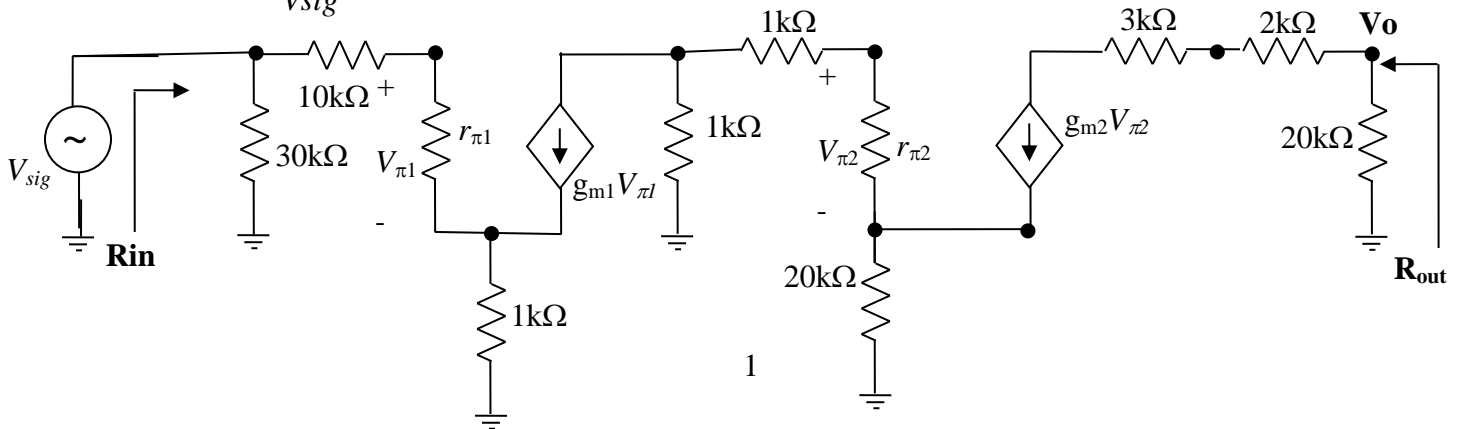- (a) R_{in} (input resistance –ignore only the input source, V_{sig} and include all resistors at the base)
- (b) R_{out} (output resistance-include **all** resistors {no load is connected})
- (c) midband gain, $\frac{V_o}{V_{sig}}$



4. Use: ignore r_o , $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$

$$V_{sig} = 10 + 0.002\sin(20t)$$


$$r_{\pi 1}=4,000 \text{ and } g_{m2}=10\text{mA/V}$$

For the following hybrid- π equivalent circuit below, find the following values:

(a) R_{in} (input resistance –ignore only the input source, V_{sig} and include all resistors)


(b) R_{out} (output resistance–ignore R_L)

(c) midband gain, $\frac{V_o}{V_{sig}}$

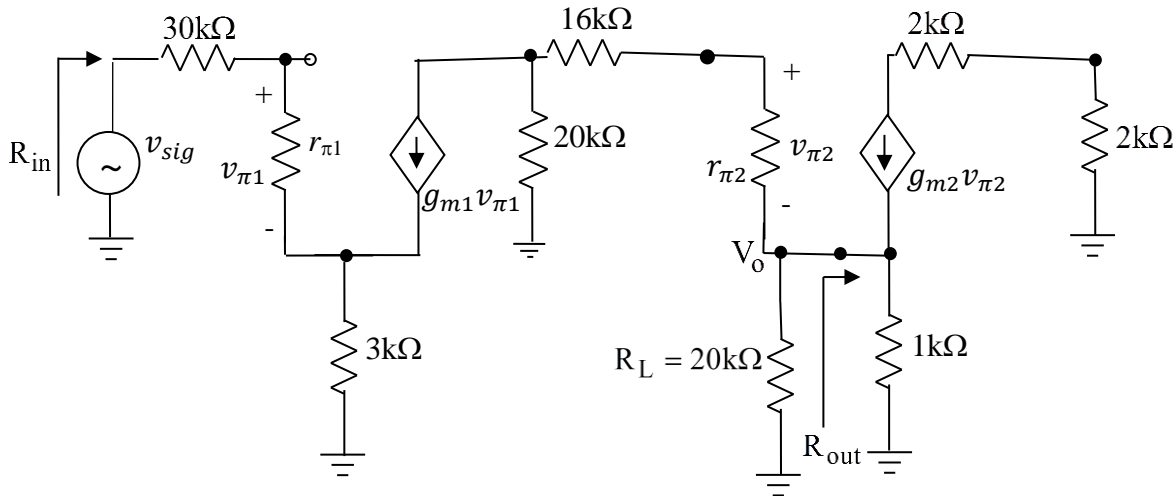


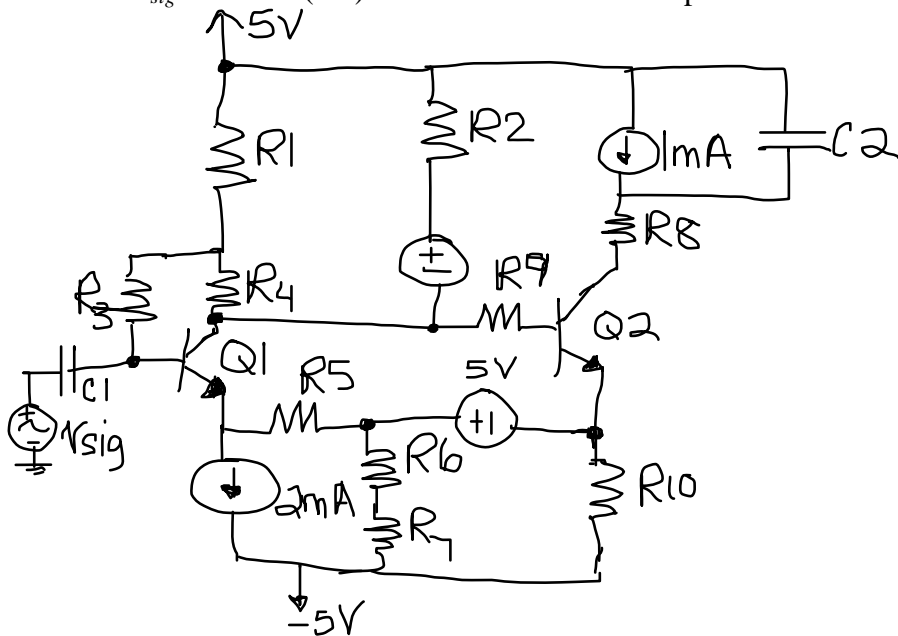5. For the circuit shown below, **draw** the AC small-signal equivalent circuit (use hybrid- π or model T).

Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , $v_{\pi 2}$, etc.). **Include r_o** for all transistors. $v_{sig}=0.001\sin(10t)$ AC. Assume that the capacitors act as a short.




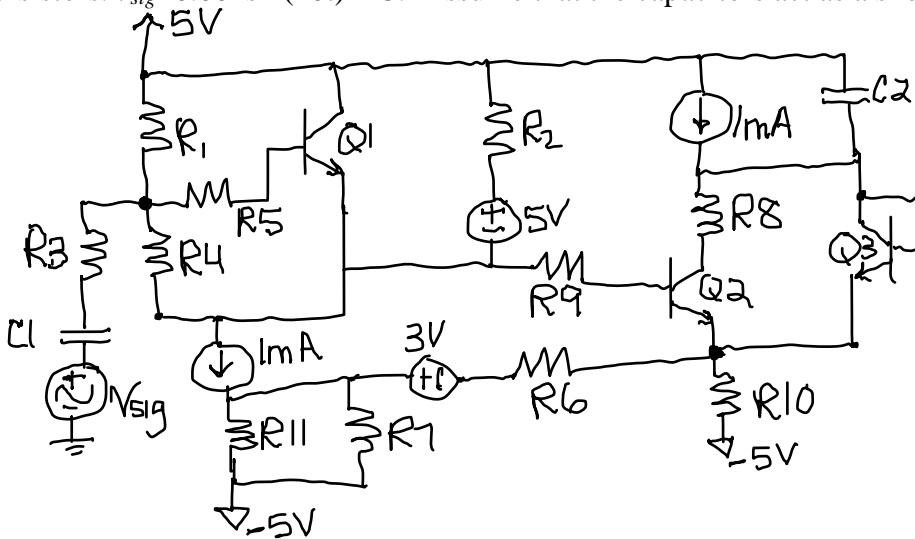6. For the circuit shown below, **draw** the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , $v_{\pi 2}$, etc.). **Include r_o** for all transistors. $v_{sig} = 0.001 \sin(10t)$ AC. Assume that the capacitors act as a short.




7. $|V_{BE}| = 0.7$, $\beta = 100$, $V_T = 25\text{mV}$, $|V_{CE\text{SAT}}| = 0.2\text{V}$, ignore r_o , $v_{sig} = \{2 + 0.1 \sin(\omega t)\}$ Volts. Assume that the capacitor acts as an open for DC operation and short for AC operation.

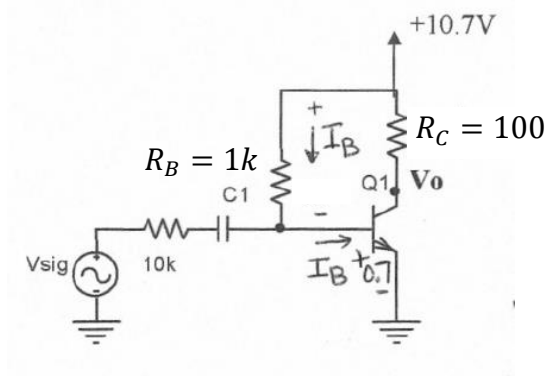- Assume transistor is acting in saturation, **solve** for I_B , I_C , and β_{forced} .
- Express the condition for R_B , without changing any other supply voltage or resistors, that will move the transistor to the **active region**.



8. $|V_{BE}| = 0.7$, $\beta = 100$, $V_T = 25\text{mV}$, $|V_{CE\text{SAT}}| = 0.2\text{V}$.

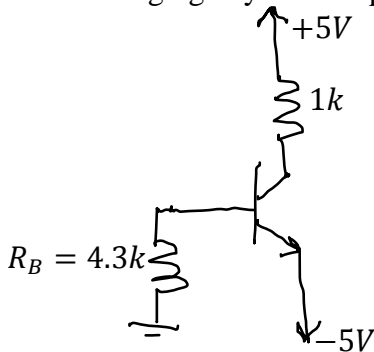- Assume transistor is acting in saturation, **solve** for I_B , I_C , and β_{forced} .
- How can R_B be changed so that the transistor moves into the active region? Express the condition for R_B , without changing any other supply voltage or resistors, that will keep the transistor in the **active region**.



9. Use: ignore r_o , $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$

$$V_{sig} = 10 + 0.002\sin(20t)$$


$$r_{\pi 1}=4,000 \text{ } g_{m2}=100\text{mA/V, and } I_{B2}=25\mu\text{A}$$

For the following hybrid- π equivalent circuit below, find the following values:

(a) R_{in} (input resistance –ignore only the input source, V_{sig} and include all resistors at the base)

(b) R_{out} (output resistance-include **all** resistors {no load is connected})

(c) midband gain, $\frac{V_o}{V_{sig}}$

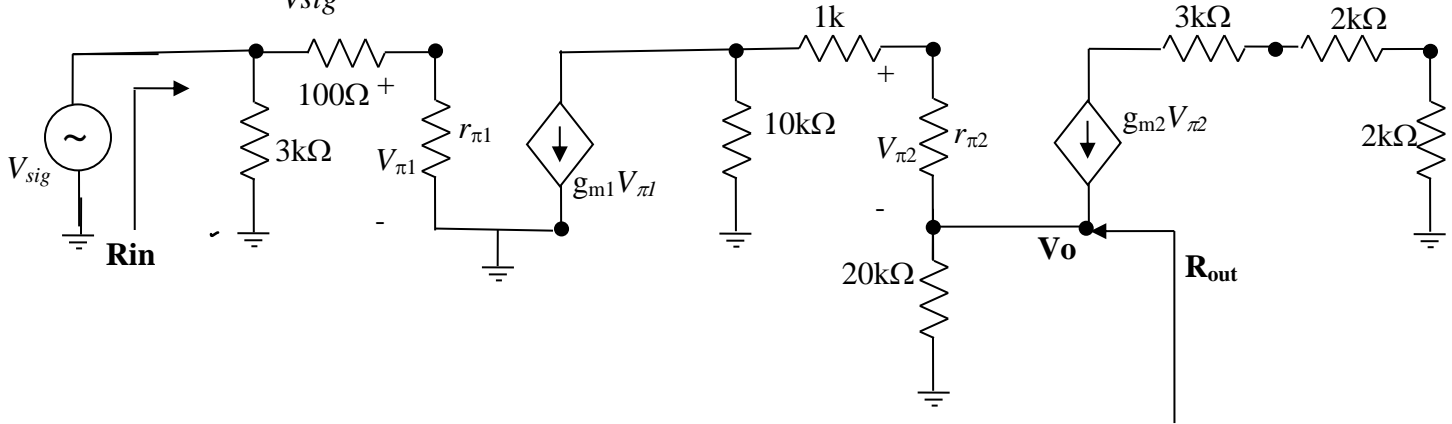

10. ignore r_o , $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$

$$V_{sig} = 10 + 0.002\sin(20t)$$

$$r_{\pi 1}=4,000 \text{ } g_{m2}=100\text{mA/V, and } I_{B2}=25\mu\text{A}$$

For the following hybrid- π equivalent circuit below, find the following values:

(a) R_{in} (input resistance –ignore only the input source, V_{sig} and include all resistors at the base)

(b) R_{out} (output resistance-include **all** resistors {no load is connected})

(c) midband gain, $\frac{V_o}{V_{sig}}$

(d) Is this a good amplifier? why or why not?

