

1. If $V_t=2$, $k_n'(W/L)=2\text{mA/V}^2$, $\lambda=0$, what is the value of the current, I_D , flowing through an NMOS transistor for the following applied voltages:

(a) $V_G=5$, $V_D=10$, $V_S=4$

(b) $V_G=5$, $V_D=10$, $V_S=-5$

(c) $V_G=5$, $V_D=2$, $V_S=-5$

(d) $V_G=3$, $V_D=1$, $V_S=1$

(e) $V_G=-5$, $V_D=0$, $V_S=-10$

(a) $V_{GS} = 5 - 4 = 1\text{V} < V_t \therefore \text{off}$
 $I_D = 0$

(b) $V_{GS} = 5 - (-5) = +10 > V_t \therefore \text{ON}$
 $V_{DS} = 10 - (-5) = 10 + 5 = 15$

$15 = V_{DS} > (V_{GS} - V_t) = 10 - 2 = 8\text{V}$ SAT

$I_D = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS} - V_t)^2 = \frac{1}{2} (2\text{m}) (+10 - 2)^2 = 64\text{mA}$

(c) $V_{GS} = 5 - (-5) = +10 > V_t \therefore \text{ON}$

$V_{DS} = 2 - (-5) = +7$

$(V_{DS} = 7) < (V_{GS} - V_t) = 8 \therefore \text{Triode}$

$I_D = k_n' \left(\frac{W}{L}\right) \left[(V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right] = 2\text{m} \left[8(7) - \frac{1}{2} 7^2 \right] = 63\text{mA}$

(d) $V_{GS} = V_G - V_S = 3 - 1 = 2$

$V_D = 1 = (V_G - V_t) = 3 - 2 = 1$ (either eq.)

SAT: $I_D = \frac{1}{2} (2\text{m}) (2 - 2)^2 = 0\text{A}$. $V_{GS} = V_t$ (just on the threshold of turning on $\therefore I = 0$)

(e) $V_{GS} = -5 + (+10) = 5\text{V}$


$V_{DS} = +10$

$10 = V_{DS} \geq (V_{GS} - V_t) = 5 - 2 = +3\text{V}$ SAT

$I_D = \frac{1}{2} (2\text{m}) (3)^2 = 9\text{mA}$

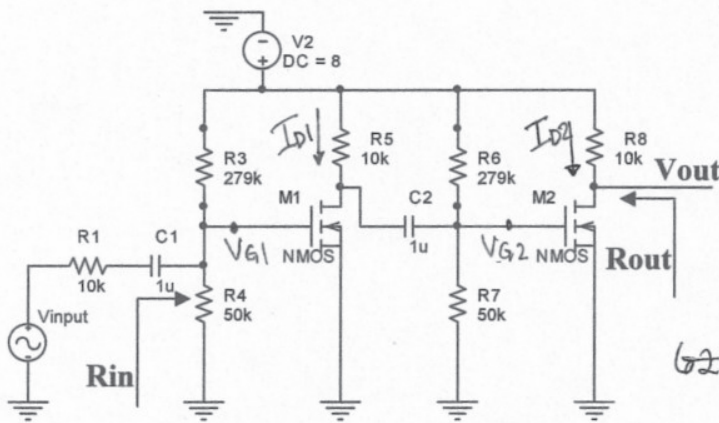2. (for each circuit: (a) worth 1 problem (b)-(e) worth 1 problem, (f)-(g) worth 1 problem; total=9 problems)
 For each circuit below, answer the following using: (i) $V_t=0.8V$, $k_n'(W/L)=3.2mA/V^2$, $\lambda=0$; (ii) $V_t=1V$, $k_n'(W/L)=1.6mA/V^2$, $\lambda=0$; (iii) $V_t=1.5V$, $k_n'(W/L)=1mA/V^2$, $\lambda=0$. Assume V_{input} is an AC signal.

- Solve the DC circuit to find I_D and V_{GS} (assume caps open) for transistor(s)
- Draw the small-signal equivalent circuit (assume caps shorted)
- Find the midband gain V_{out}/V_{input} (V_{input} is an AC source)
- Find R_{in}
- Find R_{out}
- Solve the circuit below by including the capacitors in the AC small-signal equivalent circuit. Solve the frequency transfer function V_{out}/V_{input} and state the low frequency value, f_L in Hz.
- State the upper corner frequency for the entire amplifier, f_H in Hz if $C_{gs}=1pF$ and $C_{gd}=0.1pF$.



a. DC: $V_{G1} = V_{G2}$


$I_{D1} = I_{D2}$
 Assume SAT:

$$V_{G1} = \frac{8(50k)}{50k + 279k} = 1.22V = V_{GS}$$

$$I_D = \frac{1}{2} (3.2m) (V_G - V_s - 0.8)^2$$

$$625 I_D = 1.6m (.42)^2 = 282 \mu A$$

(i)

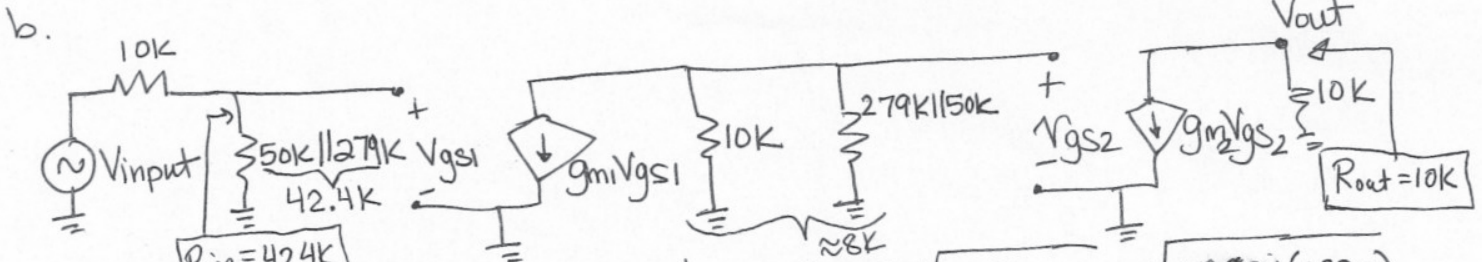

c. $V_{out} = -g_{m2} V_{gs2} \cdot 10k$

$$V_{gs2} = -g_{m1} V_{gs1} (10k \parallel 279k \parallel 50k)$$

$$V_{gs1} = \frac{V_{in} (42.4k)}{(42.4k + 10k)} = 0.81 V_{in}$$


$$V_{gs2} = -1.34m V_{gs1} (8k) = -10.72 V_{gs1}$$

$$V_{out} = -1.34m V_{in} (0.81) (-10.72) \cdot 10k$$


$$\frac{V_{out}}{V_{in}} = 117$$

$$g_{m1} = g_{m2} = \sqrt{2k_n' \left(\frac{W}{L}\right) I_D} = \sqrt{2(3.2) (282\mu)}$$

$$= \sqrt{1.805 \mu} A/V = 1.34 mA/V$$

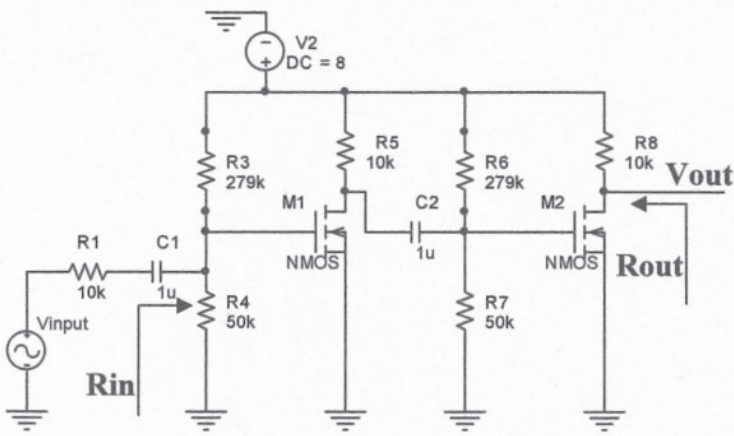

$$g_m = 1.34 \text{ mS}$$

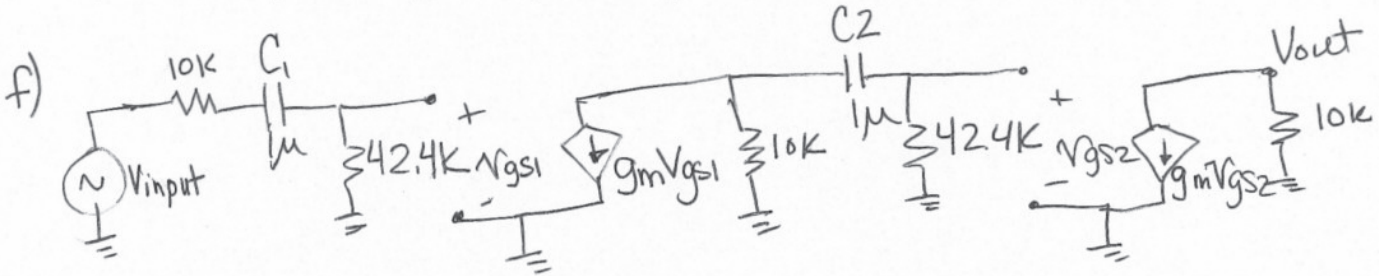

$$V_o = -g_m V_{gs2} \cdot 10k$$

$$V_{gs2} = \left[\frac{-g_m V_{gs1} (10k)}{10k + 42.4k + \frac{1}{\mu s}} \right] \cdot 42.4k = \frac{-1.34m (10k) (1\mu s) (42.4k) V_{gs1}}{((52.4k)(\mu s) + 1)} = \frac{-13.4\mu \cdot s V_{gs1} \cdot 42.4k}{(52.4m \cdot s + 1)}$$

$$V_{gs1} = \frac{V_{input} (42.4k)}{52.4k + \frac{1}{\mu s}} = \frac{V_{input} (42.4k)(\mu s)}{(52.4k)(\mu s) + 1} = \frac{42.4m V_{input} \cdot s}{(52.4m \cdot s + 1)}$$

$$\frac{V_o}{V_{input}} = \frac{+(1.34m)(13.4\mu s)(42.4m)(42.4k)(10k)}{(52.4m \cdot s + 1)^2} = \frac{0.323 \cdot s^2}{(52.4m \cdot s + 1)^2}$$

pole value = $\frac{1}{\text{cap} * R_{seen \text{ by cap}}}$

$$f_z = \frac{1}{2\pi \cdot 52.4m} = \boxed{3 \text{ Hz}}$$

(Note this value is $\frac{1}{C_1 (R_1 + R_3 || R_4)}$ OR $\frac{1}{C_2 (10k + 279k || 50k)}$)
 $52.4m = 19 \frac{\text{rad}}{\text{sec}} \neq \frac{1}{C_2 (10k + 279k || 50k)}$

$$C_{eq1} = C_{gd} (1 + g_m R_L') = 0.1p (1 + 1.34m (8k))$$

$$C_{eq1} = 1.172 \times 10^{-12}$$

$$9. \omega_{H1} = \frac{1}{R_{sig}' (C_{eq1} + C_{gs1})}$$

$$\omega_{H1} = \frac{1}{8k (1.172 \times 10^{-12} + 1p)} = 57.6 \text{ Mrad/sec}$$


lower value $\rightarrow \omega_{H2}$

$$\omega_{H2} = \frac{1}{8k [0.1p (1 + 1.34m (10k)) + 1p]} = 51.2 \text{ Mrad/sec} = \boxed{8.2 \text{ MHz}}$$

$V_t = 1V, K_n' (\frac{W}{L}) = 1.6mA/V^2$

DC: $V_G = \frac{10(100k)}{187k} = 5.35V$

(ii)

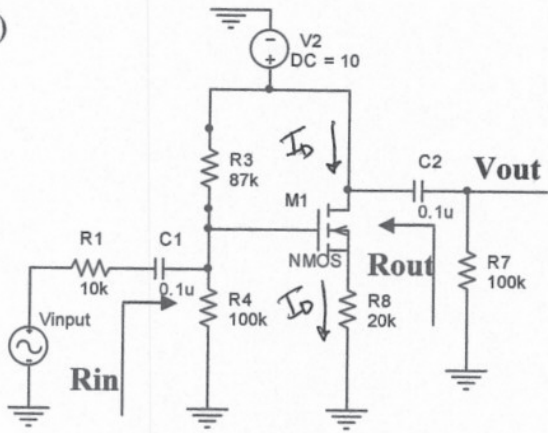

a.

Assume $V_s = I_D (20k)$
Assume SAET:

$I_D = \frac{1}{2} (1.6m) (5.35 - I_D (20k) - 1)^2$

↓ solve


$I_D = 0.193mA, 0.245mA$
 $V_s = .245m(20k) = 4.9V$

$V_s = .193m(20k) = 3.86$

$V_{GS} = .45 < V_t \therefore \text{off}$

$V_{GS} = 5.35 - 3.86$
 $V_{GS} = 1.49 > V_t \therefore \text{ON}$

b.

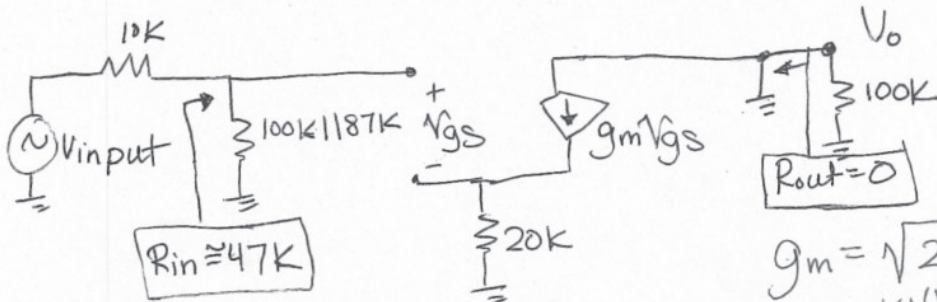


$V_o = 0V$ so

$\frac{V_o}{V_{input}} = 0V/V$

$g_m = \sqrt{2(1.6m)(0.193m)} = 0.79m$
 $g_m = K_n' (\frac{W}{L}) (V_{GS} - V_t) \approx 0.78m$

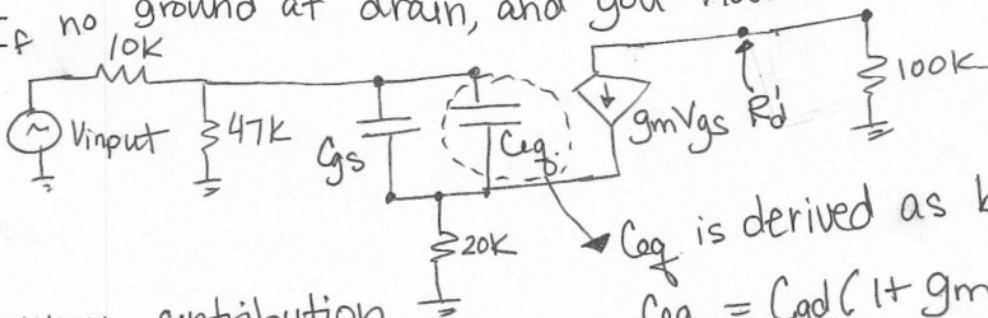(f) $\frac{V_o}{V_{input}} = 0V/V$ no change, no low or high freq. since 0V gain. (no gain) (does not ever work)

Note: If no ground at drain, and you have:



frequency contribution is still: $\frac{1}{C * R_{seen \text{ by cap.}}}$


C_{eq} is derived as before so
 $C_{eq} = C_{gd} (1 + g_m R'_d)$
↑ resistance seen at drain node

$C_{eq} = 0.1p (1 + 8m(100k))$

$C = (C_{gs} + C_{eq})$

$\frac{1}{[(47k || 100k) + 20k] (C_{gs} + C_{eq})} = \frac{1}{28.2k (8.1p + 1p)} = 3.9M \frac{rad}{sec.}$

(ii)

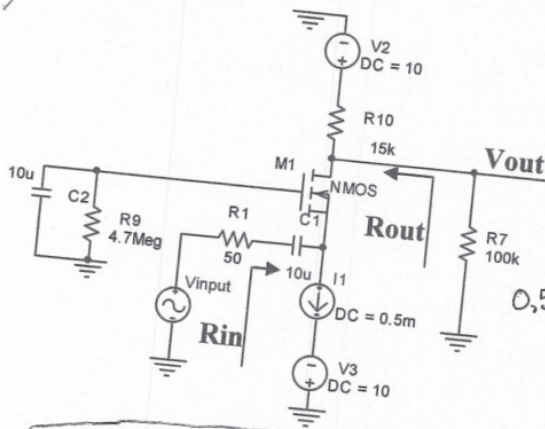

$\therefore V_{GS} = +2.5, I_D = 0.5m$

DC: $V_G = 0$

$K_n(\frac{W}{L}) = 1mA/V^2$
 $V_t = 1.5V$

$I_D = 0.5m$


Assume SAT:

$0.5m = I_D = \frac{1}{2}(1m)(0 - V_s - 1.5)^2$

$\sqrt{1} = -V_s - 1.5$

$V_s = -1.5 \pm 1 = -2.5, -0.5$

NOT ON SINCE $V_{GS} < 1.5$

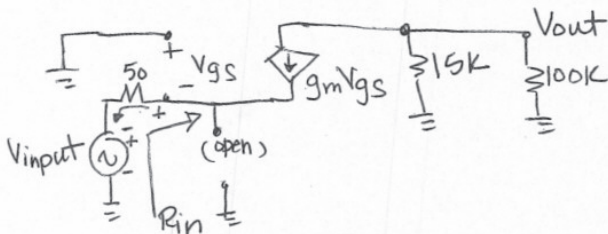

OR $g_m = \sqrt{2K_n(\frac{W}{L})I_D} = \sqrt{2(1m)(.5m)} = 1mA/V$
 $g_m = K_n(\frac{W}{L})(V_{GS} - V_t) = 1m(2.5 - 1.5) = 1mA/V$


$V_{out} = -g_m V_{gs} (15k \parallel 100k)$

$V_{gs} = 0 - (g_m V_{gs} (50) + V_{input})$

$V_{gs} (1 + g_m(50)) = V_{input}$

$V_{gs} = \frac{V_{input}}{1 + g_m(50)} = 0.95 V_{input}$

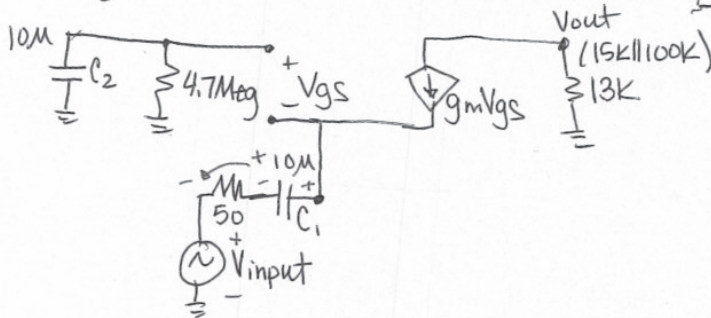$V_{out} = -13(0.95) V_{input} \Rightarrow \frac{V_{out}}{V_{input}} \approx -12.7 V/V$



$V_{out} = -g_m V_{gs} (13k)$

$V_{gs} = 0 - (g_m V_{gs} (\frac{1}{C_1 s} + 50) + V_{input})$

$V_{gs} = \frac{V_{input}}{1 + g_m (\frac{1}{C_1 s} + 50)} = \frac{V_{input} C_1 s}{C_1 s (1 + g_m 50) + 1}$

$V_{gs} = \frac{V_{input} (10\mu)s}{10.5\mu \cdot s + 1m} = \frac{V_{input} (10\mu)s}{1m (10.5\mu s + 1)}$

$V_{gs} = \frac{10m V_{input} \cdot s}{(0.5m \cdot s + 1)}$

$V_{out} = -13(10m)s \cdot V_{input} / (0.5m \cdot s + 1) \Rightarrow$


$\frac{V_{out}}{V_{input}} = \frac{0.13s}{(0.5m \cdot s + 1)}$

Note $\Rightarrow C_1 (\frac{1}{g_m} + 50) = 10.5\mu = 95$

cap * Rseen by cap

$f_L = 15Hz$
 $f_H = 1.3 \times 10^9 Hz$

ω_H :

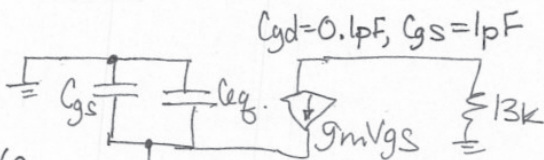

R seen by $(C_{gs} + C_{eq})$ is 50Ω (V_{input} is shorted) so

$\omega_H = \frac{1}{50(C_{gs} + C_{eq})}$ where $C_{eq} = C_{gd}(1 + g_m(13k))$
 $C_{eq} = 1.4pF$
 $= \frac{1}{50(p + 1.4p)} = 8.3 \times 10^9 rad/sec$