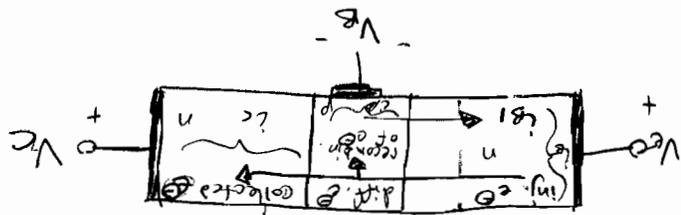


②

- 1) Sat.
- 2) Active
- 3) Active/cutoff edge
- 4) Active
- 5) Cutoff
- 6) Active
- 7) Sat/Active edge
- 8) Cutoff


Forward bias V_{BE} causes an exponential current to flow in the i_c terminal. Collector current is independent of V_{CE} . Collector voltage as long as V_{CE} is reverse biased.




Forward bias on the emitter-base junction causes current to flow across that junction. Some electrons diffuse to the junction (CB) and are swept across.

b) In a BJT, there is always some thermal drift current across the pn junctions, but it is very small and will be neglected in the description below.

① a) BJT Cross section

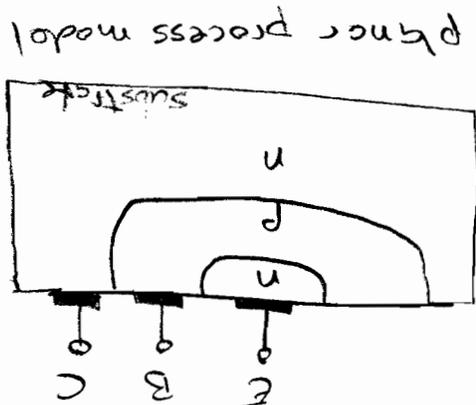


Planar process model

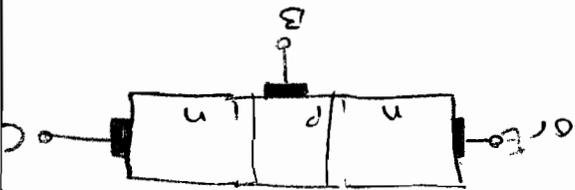

Cylinder model

3) $|V_{BE}| = 0.7$

$\beta = 100$

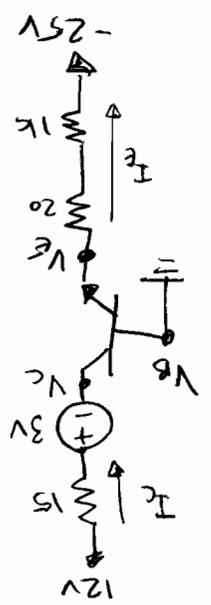

$V_B = 0V$
 $V_C = 12V - I_C(15\Omega) - 3V = 9V - I_C(15\Omega)$
 $V_E = -25V + I_E(1020\Omega)$

Assume Active

$I_C = \alpha I_E = \beta I_B$ and $\alpha = \frac{\beta}{\beta + 1}$
 $\therefore V_C = 9V - I_E \cdot \frac{101}{100} \cdot 15\Omega$

Also from active mode $V_{BE} \approx 0.7V$

$\therefore V_E \approx -0.7V$

$\Rightarrow \frac{24.3V}{1020\Omega} = I_E = 23.8mA$


$I_C = \frac{\alpha}{I_E} = \frac{I_E(\beta + 1)}{\beta} = 24.1mA$

$I_B = \frac{I_C}{\beta} = 241\mu A$

$V_B = 0V$
 $V_C = 8.64V$
 $V_E = -0.724V$
 $I_B = 241\mu A$
 $I_C = 24.1mA$
 $I_E = 23.8mA$

$V_{BE} = 0.724 \approx 0.7$
 $V_{CE} = 9.36 > 0.7$

active on

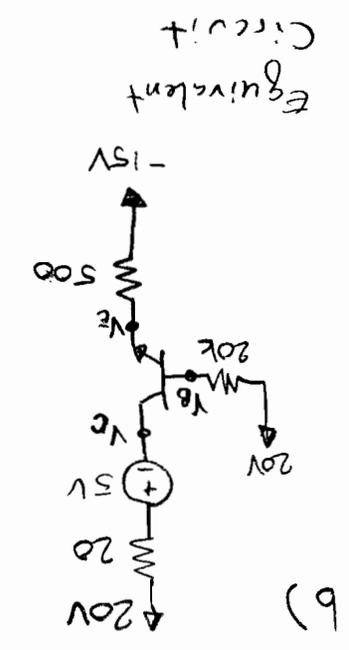

Assume Active On

$$V_c = 15V - 20I_c$$

$$V_E = -15V + 500I_E = -15V + 500I_c$$

$$V_B = 20V - 20kI_B = 20V - 20kI_c$$


$$V_{BE} = 0.7 = 35V - I_c \left(\frac{20k}{\beta} + \frac{500}{\alpha} \right)$$

$$I_c = 48.7 \text{ mA}$$

$$I_B = 487 \mu\text{A} \quad I_E = 49.2 \text{ mA}$$

$V_c = 14.0V \quad V_E = 9.59V \quad V_B = 10.3V$

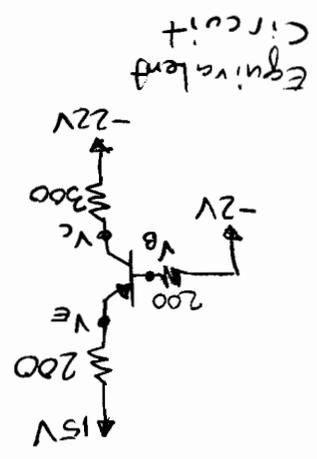$V_{BE} = 10.3 - 9.59 = 0.71 \approx 0.7V$ ✓
 $V_{CE} = 14.0 - 9.59 = 4.41 > 0.7V$ ✓
 Active on



Assume Active on (PNP)

$$15V - I_E(200) = V_E$$

$$-22V + I_B(200) = V_B$$

$$-22V + I_C(300) = V_C$$

$$V_{EB} = 0.7 = 17V - I_C(200) + \frac{\alpha}{\beta} I_C(200)$$

$$I_C = \frac{0.7 - 17V}{\frac{200}{\beta} - \frac{200}{\alpha}} = 79.9 \text{ mA} = I_E$$

$$I_B = 799 \mu\text{A}$$

$V_E = -1.14V \quad V_B = -1.84V \quad V_C = -1.97V$

$|V_{EB}| = 0.7 \quad |V_{CB}| = 3V > 0.7$ Active on

$V_E = 0.7V$ and $|V_{CE}| > 0.7V$ Active on

$V_E = 9.08V$	$I_E = 8.5mA$
$V_B = 8.38V$	$I_B = 84\mu A$
$V_C = 13.51V$	$I_C = 8.4mA$

Assume Active on.

$$V_B = I_B (100k)$$


$$V_E = 2.6V - I_E (2k)$$

$$V_C = -20V + I_C (4k)$$

$$V_E - V_B = 0.7V$$


$$\beta I_B - I_C = 0A$$

$$\frac{\beta}{\beta+1} I_E - I_C = 0A$$

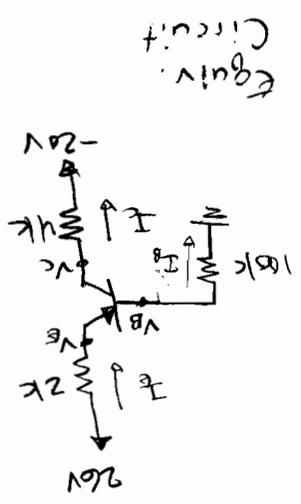


d)
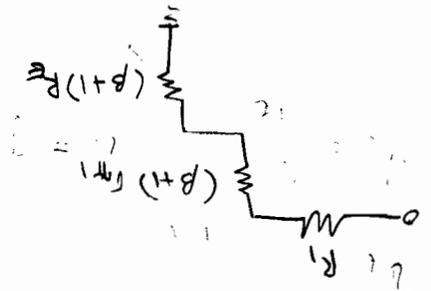
$$R_{in} = R_1 + (\beta + 1)(r_{\pi 1} + R_E)$$




Use Resistance Reflection

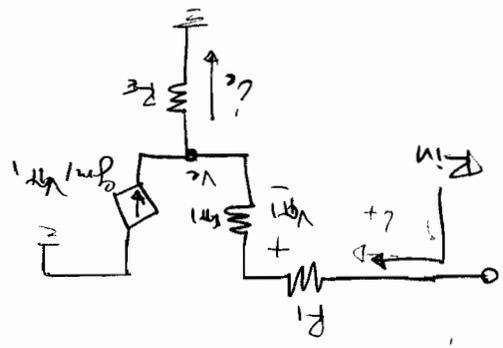

b)

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{2 \text{ mA}}{25 \text{ mV}} = 80 \text{ mS}^{-1}$$
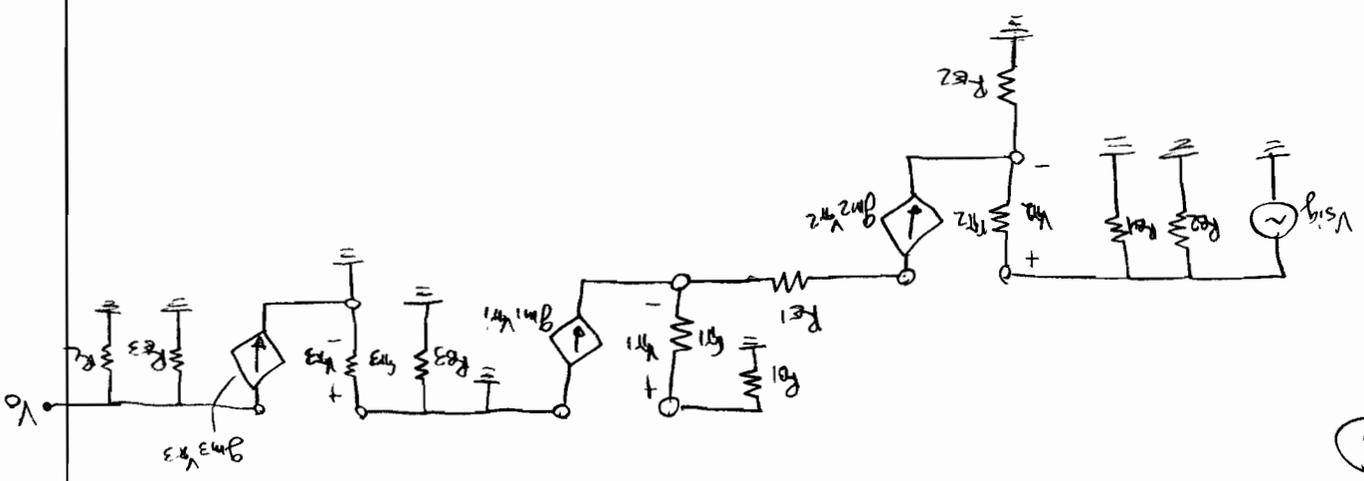
$$a) r_{\pi 1} = \frac{V_T}{I_{B1}} = \frac{25 \text{ mV} \cdot 20}{0.1 \text{ mA}} = 500 \Omega$$



5)

$$V_o = \frac{V_{sig}}{R_{in}} \left(-g_m R_3 \right) \left(-g_m R_L \right) = \frac{g_m^2 R_3 R_L}{r_{\pi 1} (R_3 + r_{\pi 2})}$$

$$\frac{V_{sig}}{R_{in}} = \frac{V_{\pi 1}}{r_{\pi 1}}$$

$$V_{\pi 1} = r_{\pi 1} I_{in} = \frac{r_{\pi 1} V_{sig}}{R_{in}}$$

$$I_{in} = \frac{V_{sig}}{R_{in}}$$

$$\frac{V_{\pi 2}}{R_3 + r_{\pi 2}} = \frac{V_{\pi 1}}{g_m R_3}$$

$$V_o = -g_m R_L V_{\pi 2}$$