
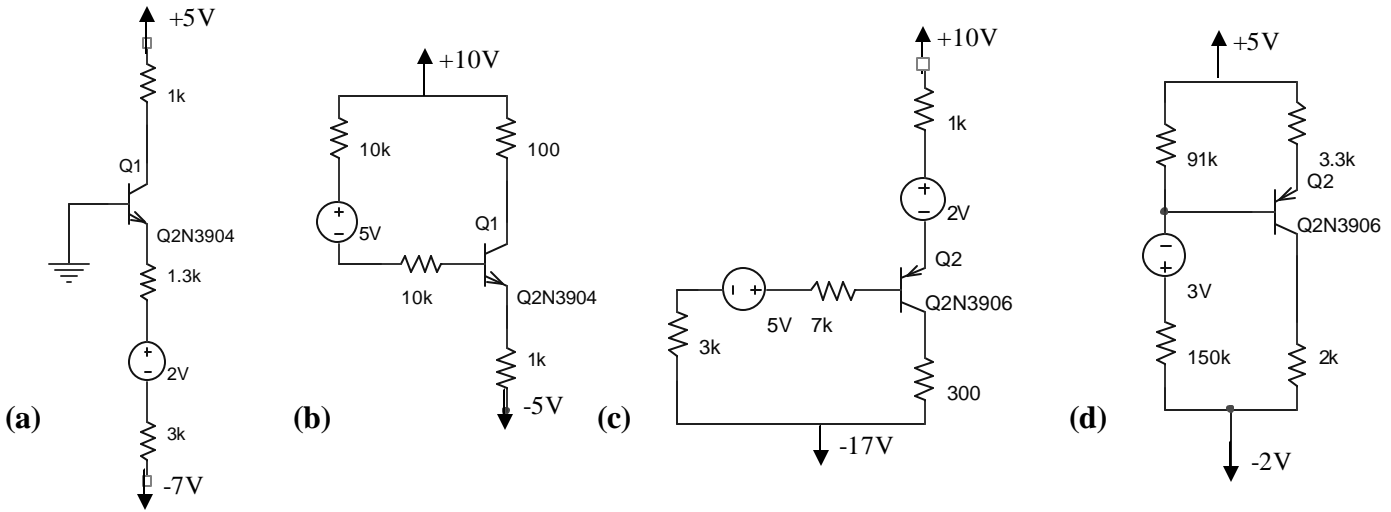


1. Use  $|V_{BE}|=0.7$ ,  $\beta=100$ . Find voltages at all nodes and currents through all branches. (worth 4 problems)

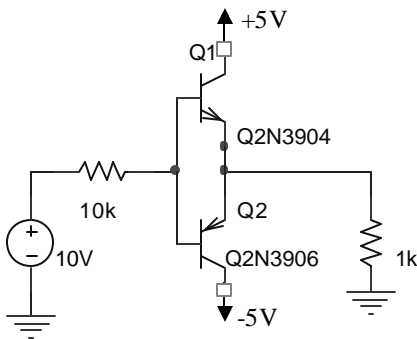


2. Use  $|V_{BE}|=0.7$ ,  $\beta=100$ . Find voltages at all nodes and the currents through all branches.



3. Assume active operation for all transistors. ( $V_{sig}$  is an ac source)  
Assume that the capacitors act as an open for DC operation.

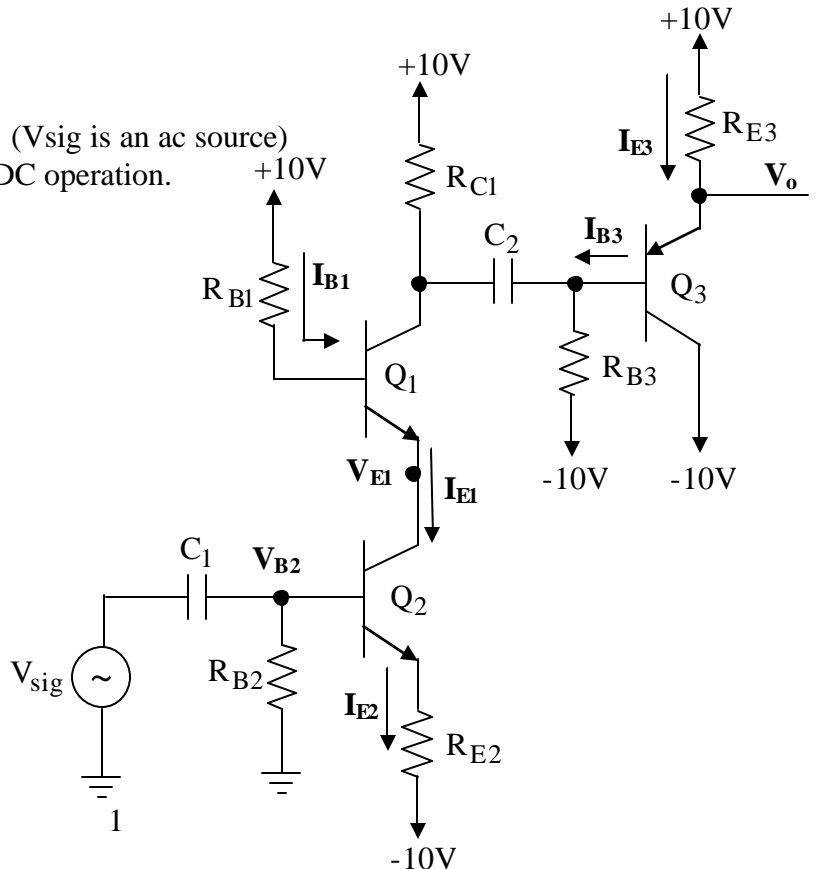
- (a) Find the symbolic equations for the DC values for  $I_{E1}$ ,  $I_{E2}$ ,  $I_{B1}$ ,  $I_{E3}$ ,  $I_{B3}$ ,  $V_o$ ,  $V_{E1}$
- (b) Draw the hybrid- $\pi$  or model-T AC circuit



4. Use  $|V_{BE}|=0.7$ ,  $\beta=20$ ,  $V_T=25\text{mV}$  ( $V_{sig}$  is an ac source), ignore  $r_o$ .

This small-signal model circuit is shown below. It was found through a DC analysis that  $I_{C1}=1\text{mA}$  and  $I_{C2}=2\text{mA}$ .

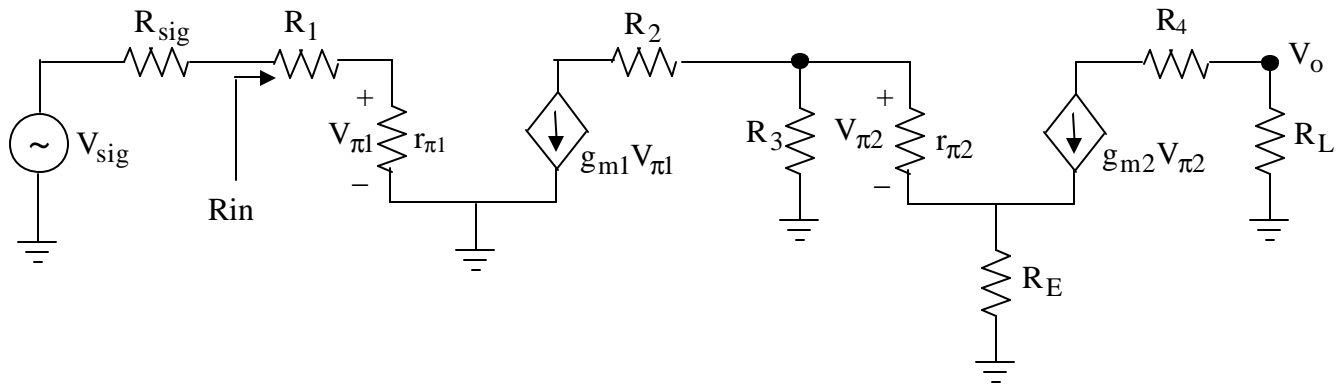- Find the ac parameters,  $r_{\pi 1}$  and  $g_{m2}$
- Find a symbolic equation for the input resistance,  $R_{in}$ . (Ignore the AC input source and  $R_{sig}$ , include  $R_1$ )
- Find a symbolic expression for the overall gain,  $\frac{V_o}{V_{sig}}$ .



5. Use  $|V_{BE}|=0.7$ ,  $\beta=100$ ,  $V_T=25\text{mV}$  ( $V_s$  is an ac source), ignore  $r_o$ . This small-signal model comes from a circuit that has 2 transistors Q1 and Q2 denoted below as subscripts 1 and 2. It was found that  $I_{E1}=2.525\text{mA}$  and  $I_{E2}=1.2625\text{mA}$ . Find  $R_{in}$  (ignore  $V_s$  and  $10\Omega$ ),  $R_{out}$  (ignore  $R_L$ ), and midband gain,  $V_o/V_s$ .

