
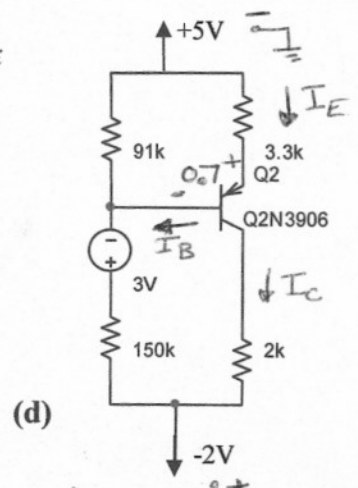
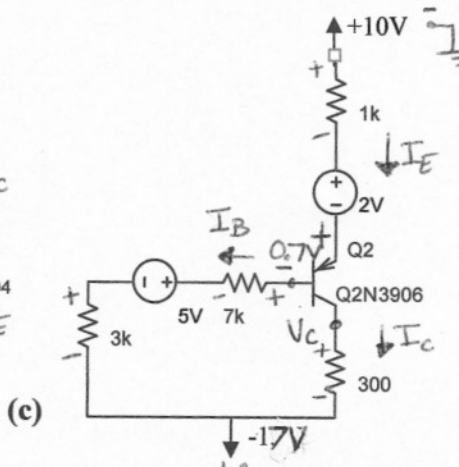
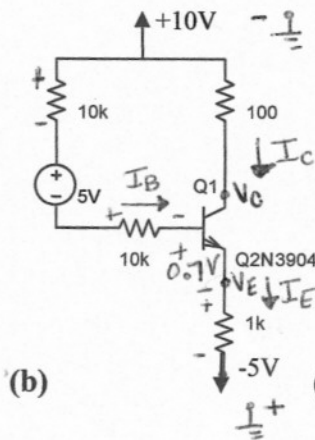


1. Use $|V_{BE}|=0.7, \beta=100$. Find voltages at all nodes and currents through all branches. (worth 4 problems)

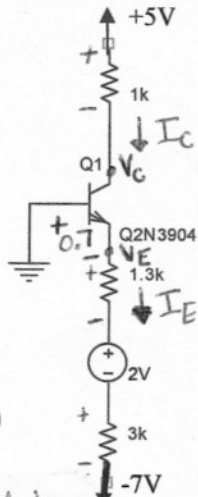

Assume Active

a. $10.7 + 1.3k(I_E) + 2 + 3k(I_E) - 7 = 0$

$$I_E = \frac{5 - 0.7}{4.3k} = 1mA$$

$$-7 + I_E(3k) + 2 + I_E(1.3k) - V_E = 0$$

$$V_E = -5 + I_E(4.3k) = -0.7V$$

$$I_C = \alpha I_E = \frac{100}{101}(1m) = 0.99m$$

$$V_B = 0$$

$$5 - I_C(1k) - V_C = 0$$

$$V_C = 5 - I_C(1k) \approx 4V$$

$V_C > V_B > V_E \rightarrow$ Active mode ✓

b. $+10 - I_B(10k) - 5 - I_B(10k) - 0.7 - I_E(1k) + 5 = 0$

$$I_B = \frac{I_E}{\beta + 1} \Rightarrow I_E = \frac{9.3}{\frac{20k}{100} + 1k} = 7.76mA$$

$$I_C = \beta \cdot I_B \Rightarrow I_C = \alpha I_E = 7.69mA$$

$$I_B = 76.9\mu A$$

$$V_B \approx 5 - I_B(20k) = 3.5V$$

$$V_E \approx -5 + 1k(I_E) = 2.8V$$

$$V_C = 10 - 100(I_C) = 9.2V$$

$V_C > V_B > V_E$ Active ✓

c. $+10 - I_E(1k) - 2 - 0.7 - I_B(7k) - 5 - 3k(I_B) + 17 = 0$

$$I_B = I_E / \beta \Rightarrow I_E = \frac{19.3}{\frac{10k}{100} + 1k} = 17.6mA$$

$$I_C = \alpha I_E = 17.4mA$$

$$I_B = I_C / \beta \approx 174\mu$$


$$-17 + 3k(I_B) + 5 + 7k(I_B) = V_B \Rightarrow V_B = -12 + 10k(I_B)$$

$$V_B = -10.26V$$

$$+10 - I_E(1k) - 2 - V_E = 0 \Rightarrow V_E = -9.6V$$

$$-17V + I_C(300) - V_C = 0 \Rightarrow V_C = -11.78V$$

$V_C < V_B < V_E$ ✓

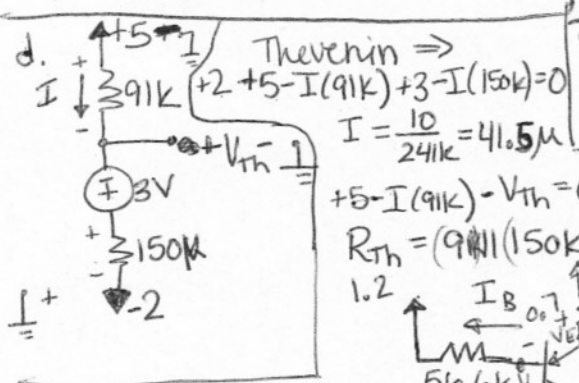

Thevenin \Rightarrow

$$I = \frac{10}{241k} = 41.5\mu$$

$$+5 - I(91k) - V_{Th} = 0 \Rightarrow V_{Th} \approx 1.2V$$

$$R_{Th} = (91k || 150k) = 56.6k$$

$$+5 - I_E(3.3k) - 0.7 - I_B(56.6k) - 1.2 = 0$$

$$I_B = \frac{I_E}{\beta + 1} \Rightarrow I_E = \frac{3.1}{3.3k + \frac{56.6k}{100}} = 3.1mA$$

$$I_C = \alpha I_E = \frac{100}{101}(1.8m) \approx 1.8m$$

$$I_B = \frac{I_E}{101} = 8\mu A$$


$$V_E = 5 - I_E(3.3k) = 2.36V$$

$$V_B = V_E - V_{EB} = 1.66V$$

$$V_C = -2 + I_C(2k) = -0.4V$$

$V_C < V_B < V_E$ ✓ Active

2. Use $|V_{BE}|=0.7, \beta=100$. Find voltages at all nodes and the currents through all branches. $V_{CE-SAT}=0.2V$

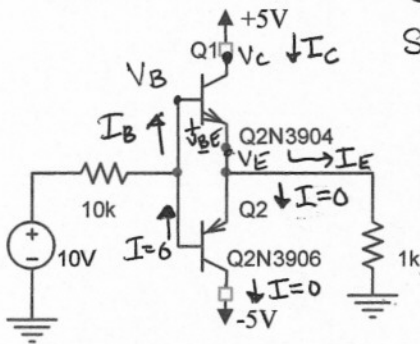

Q1 on, Q2 off: they can not both be on at the same time. (See Example 5.12 in the book).
 { Can not have current flow "into" the +10V supply }


Assume active: $+10 - I_B(10k) - 0.7 - I_E(1k) = 0$ $I_B = \frac{I_E}{\beta+1}$
 $\Rightarrow I_E = 8.5m$ $\therefore V_E = 8.5V, V_B = 9.2V$
 $\therefore V_C < V_B > V_E$!! NOT ACTIVE

Assume SAT: $V_{CE} = 0.2V$
 $+5 - V_{CESAT} - I_E(1k) = 0$
 $\therefore V_E = 4.8V$

$V_B = 4.8 + 0.7 = 5.5V$ $I_E = \frac{V_E}{1k} = 4.8m$
 $V_C = 5V$ $I_B = \frac{10 - 5.5}{10k} = 0.45m$
 $5 < V_B > V_E$ ✓ SAT $I_C = I_E - I_B = 4.35m$
 For Q2: $V_{EB} = 4.8 - 5.5 = -0.7 < 0.7$ off

3. Assume active operation for all transistors. (V_{sig} is an ac source)
 Assume that the capacitors act as an open for DC operation.

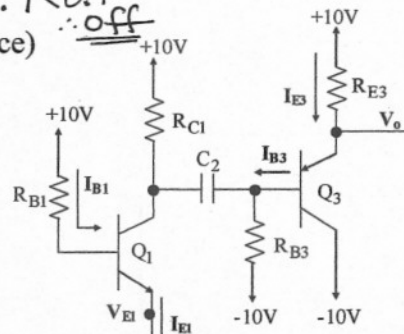- (a) Find the symbolic equations for the DC values for $I_{E1}, I_{E2}, I_{B1}, I_{E3}, I_{B3}, V_o, V_{E1}$
 (b) Draw the hybrid- π or model-T AC circuit



(a)
 $-I_{B2}(R_{B2}) - V_{BE} - R_{E2}(I_{E2}) + 10 = 0$
 $I_{B2} = \frac{I_{E2}}{\beta+1} \Rightarrow I_{E2} = \frac{10 - V_{BE}}{R_{E2} + \frac{R_{B2}}{\beta+1}}$


$I_{E1} = I_{C2} = \alpha I_{E2} = \frac{\alpha(10 - V_{BE})}{R_{E2} + \frac{R_{B2}}{\beta+1}}$ or $\frac{(10 - V_{BE})\beta}{R_{E2}(\beta+1) + R_{B2}}$

$I_{B1} = \frac{I_{E1}}{\beta+1} = \frac{(10 - V_{BE})\beta}{R_{E2}(\beta+1)^2 + R_{B2}(\beta+1)}$

$-10 + I_{B3}(R_{B3}) + V_{BE} + I_{E3}(R_{E3}) - 10 = 0$
 $I_{E3} = \frac{20 - V_{BE}}{R_{E3} + \frac{R_{B3}}{\beta+1}}$ $I_{B3} = \frac{(20 - V_{BE})}{R_{B3}(\beta+1) + R_{B3}}$

$V_o = 10 - I_{E3} \cdot R_{E3}$

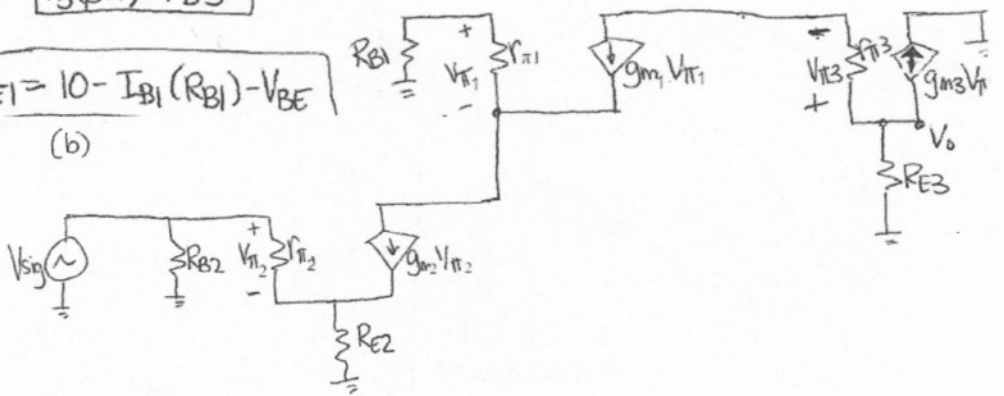
$V_{E1} = 10 - I_{B1}(R_{B1}) - V_{BE}$
 (b)



4. Use $|V_{BE}|=0.7$, $\beta=20$, $V_T=25\text{mV}$ (V_{sig} is an ac source), ignore r_o .

This small-signal model circuit is shown below. It was found through a DC analysis that $I_{C1}=1\text{mA}$ and $I_{C2}=2\text{mA}$.

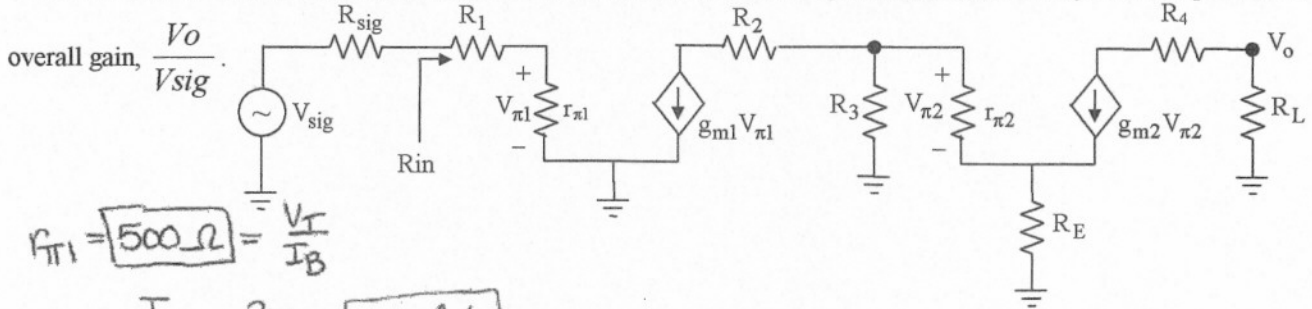Find the ac parameters, $r_{\pi 1}$ and g_{m2} , R_{in} . (Ignore the AC input source and R_{sig} , include R_1), Find a symbolic expression for the



$$r_{\pi 1} = \boxed{500 \Omega} = \frac{V_T}{I_B}$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \frac{2\text{m}}{25\text{m}} = \boxed{80\text{mA/V}}$$

$$R_{in} = R_1 + r_{\pi 1}$$

$$V_o = -g_{m2} V_{\pi 2} \cdot R_L$$


$$V_{\pi 2} = -g_{m1} V_{\pi 1} (R_3) \cdot r_{\pi 2}$$

$$[R_3 + r_{\pi 2} + R_E(\beta + 1)]$$

$$\frac{V_o}{V_{sig}} = \frac{-g_{m2} R_L (r_{\pi 1}) (-g_{m1}) (R_3) (r_{\pi 2})}{(r_{\pi 1} + R_1 + R_{sig}) (R_3 + r_{\pi 2} + R_E(\beta + 1))}$$

$$V_{\pi 1} = \frac{V_{sig} (r_{\pi 1})}{(r_{\pi 1} + R_1 + R_{sig})}$$

5. Use $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$ (V_s is an ac source), ignore r_o . This small-signal model comes from a circuit that has 2 transistors Q1 and Q2 denoted below as subscripts 1 and 2. It was found that $I_{E1}=2.525\text{mA}$ and $I_{E2}=1.2625\text{mA}$. Find R_{in} (ignore V_s and 10Ω), R_{out} (ignore R_L), and midband gain, V_o/V_s .

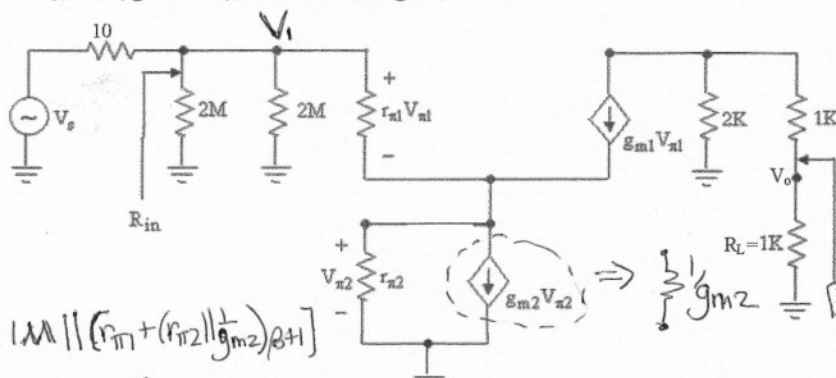

AC parameters \Rightarrow

$$r_{\pi 1} = \frac{V_T}{I_B} = \frac{25\text{m}}{\left(\frac{2.525\text{m}}{101}\right)} = 1,000 \Omega$$

$$g_{m1} = \frac{I_{C1}}{V_T} \approx 100\text{mA/V}$$

$$r_{\pi 2} = \frac{25\text{m}}{\left(\frac{1.2625\text{m}}{101}\right)} \approx 2\text{K} \Omega$$

$$g_{m2} = \frac{I_{C2}}{V_T} \approx 50\text{mA/V}$$

$$R_{in} = 1\text{M} \parallel [r_{\pi 1} + (r_{\pi 2} \parallel \frac{1}{g_{m2}}) (\beta + 1)]$$


$$R_{in} \approx \boxed{2,991 \Omega}$$

$$V_o = \left[-g_{m1} \frac{V_{\pi 1} (2\text{K})}{4\text{K}} \right] 1\text{K}$$

$$V_{\pi 1} = \frac{V_i (r_{\pi 1})}{r_{\pi 1} + 2\text{K}} = 0.33 V_i$$

$$\therefore V_o = -g_{m1} (500) (0.33 V_s)$$
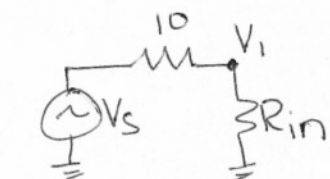
$$\frac{V_o}{V_s} \approx \boxed{-16.7 \text{V/V}}$$



$$V_i = \frac{V_s (R_{in})}{R_{in} + 10} \approx V_s$$

