
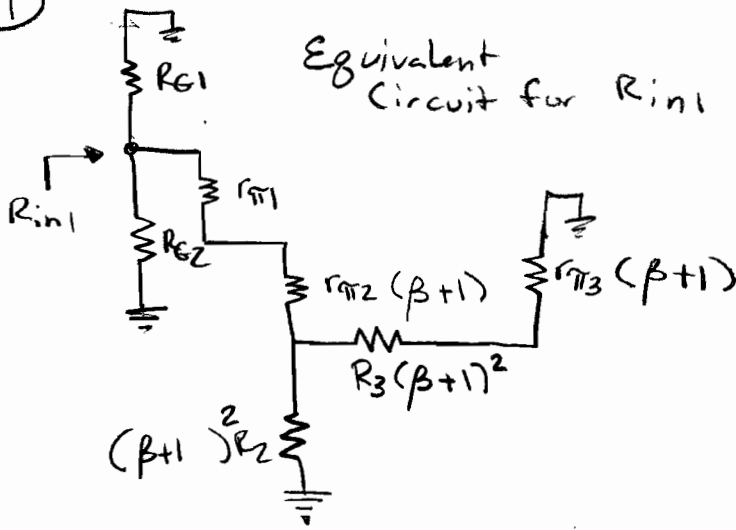


①

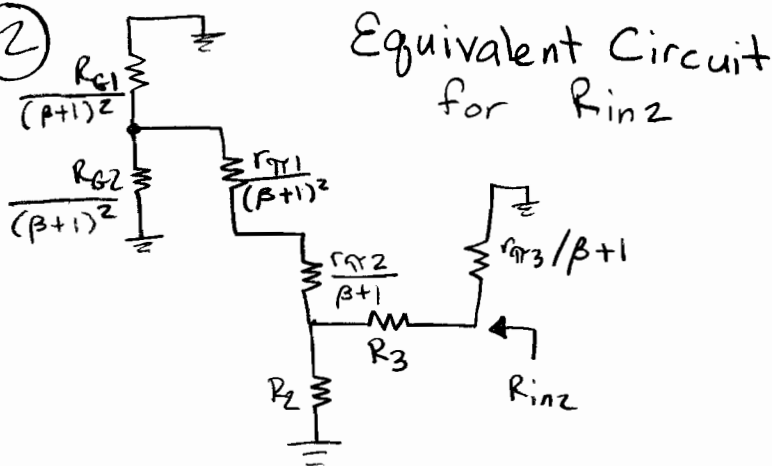


$$R_{in1} = R_{G1} \parallel R_{G2} \parallel \left(r_{\pi 1} + r_{\pi 2} (\beta + 1) + R_2 (\beta + 1)^2 \right) \parallel \left(R_3 (\beta + 1)^2 + r_{\pi 3} (\beta + 1) \right)$$

②



$$R_{in2} = \frac{r_{\pi 3}}{\beta + 1} \parallel \left(R_3 + R_2 \parallel \left(\frac{r_{\pi 2}}{\beta + 1} + \frac{r_{\pi 1}}{(\beta + 1)^2} + \frac{R_{G1} \parallel R_{G2}}{(\beta + 1)^2} \right) \right)$$

3

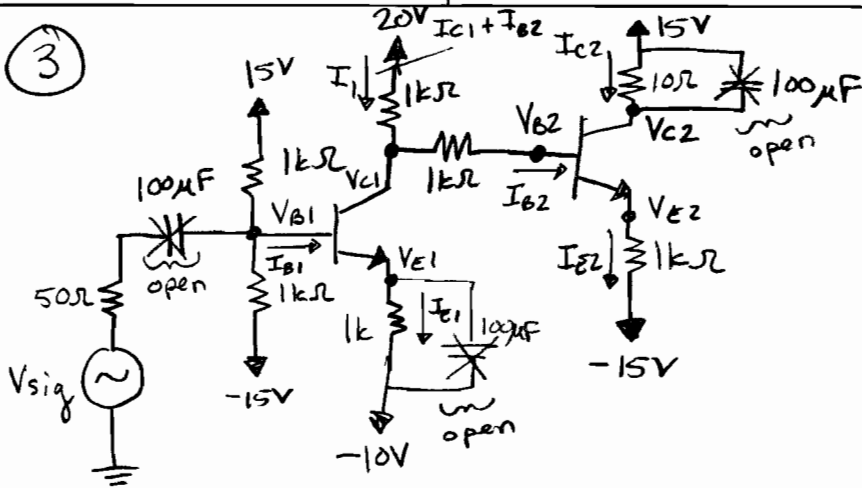

$V_{out} = V_{E2}$

Assume Active On (both)

$$V_{B1} = 15 - 1k(I_{B1})$$

$$V_{B1} - V_{E1} = 0.7V$$

$$V_{E1} = -10V + 1k(I_{E1})$$

$$V_{C1} = 20 - 1k(I_{C1} + I_{B2})$$

$$I_{C1} = \alpha I_{E1} = \frac{\beta}{\beta + 1} I_{E1} = \frac{160}{161} I_{E1}$$

$$I_{C1} = \beta I_{B2} = 160 I_{B2}$$

$$V_{B2} = V_{C1} - 1k(I_{B2})$$

$$V_{B2} - V_{E2} = 0.7V$$

$$V_{E2} = -15V + 1k(I_{E2})$$

$$V_{C2} = 15V - 10(I_{C2})$$

$$I_{C2} = \beta I_{B2} = 160 I_{B2}$$

$$I_{C2} = \frac{\beta}{\beta + 1} I_{E2} = \frac{160}{161} I_{E2}$$

$$V_{B1} = -1k \left(\frac{I_{C1}}{\beta} \right) \frac{1}{2} = V_{E1} + 0.7V = -9.3 + 1k \frac{I_{C1}}{\alpha}$$

$$9.3V = 1k I_{C1} \left(\frac{1}{2\beta} + \frac{\beta+1}{\beta} \right)$$

$$I_{C1} = \frac{-9.3V}{1k \left(\frac{1}{2(160)} + \frac{161}{160} \right)} = 9.21 \text{ mA}$$

$$I_{B1} = \frac{I_{C1}}{\beta} = 57.6 \mu\text{A}$$

$$I_{E1} = \frac{I_{C1}}{\alpha} = \frac{9.21 \text{ mA}}{160/161} = 9.27 \text{ mA}$$

$$V_{B1} = -\frac{500}{160} (9.21 \text{ mA}) = -28.8 \text{ mV}$$

$$V_{E1} = V_{B1} - 0.7 = -0.729 \text{ V}$$

$$V_{C1} = 20V - (I_{C1} + I_{B2})(1k)$$

$$V_{B2} = V_{C1} - I_{B2}(1k) = 20V - 2kI_{B2} - 1kI_{C1}$$

$$V_{B2} - V_{E2} = 0.7 \quad V_{E2} = -15V + 1kI_{E2}$$

$$10.79 - \frac{2k I_{C2}}{160} + 15 - \frac{1k I_{C2}}{160/161} = 0.7$$

$$25.09 = I_{C2} \left(\frac{2k}{160} + \frac{161k}{160} \right) = I_{C2} \left(\frac{163k}{160} \right)$$

$$\Rightarrow I_{C2} = 24.6 \text{ mA}$$

$$I_{B2} = 154 \mu\text{A} \quad I_{E2} = 24.8 \text{ mA}$$

$$V_{E2} = -15V + 24.8V = 9.8V$$

$$V_{B2} = 10.5V$$

$$V_{C2} = 15 - (10)(24.6 \text{ mA}) = 14.75V$$

$$V_{B1} = -28.8 \text{ mV}$$

$$V_{E1} = -0.729 \text{ V}$$

$$V_{C1} = 20 - (9.21 \text{ mA} + 154 \mu\text{A})(1 \text{ k}) = 10.6 \text{ V}$$

$$V_{C1} = 10.6 \text{ V}$$

$$V_{B2} = 10.5 \text{ V}$$

$$V_{E2} = 9.8 \text{ V}$$

$$V_{C2} = 14.75 \text{ V} = V_{\text{out}}$$

$$I_{C1} = 9.21 \text{ mA}$$

$$I_{B1} = 57.6 \mu\text{A}$$

$$I_{E1} = 9.27 \text{ mA}$$

$$I_{C2} = 24.6 \text{ mA}$$

$$I_{B2} = 154 \mu\text{A}$$

$$I_{E2} = 24.8 \text{ mA}$$

$$I_1 = I_{B2} + I_{C1} = 9.36 \text{ mA}$$

$$I_1 = 9.36 \text{ mA}$$

$$\textcircled{4} \quad r_{\pi 1} = \frac{V_T}{I_{B1}} = \frac{0.0259 \text{ V}}{57.6 \mu\text{A}} = 450 \Omega$$

$$r_{\pi 2} = \frac{V_T}{I_{B2}} = \frac{0.0259 \text{ V}}{154 \mu\text{A}} = 168 \Omega$$

$$R_{th1} = 10 \Omega \quad \text{Pole} = \frac{1}{10 \Omega \cdot 100 \mu\text{F}} = 1 \text{ k} \frac{\text{rad}}{\text{sec}}$$

$$R_{th2} = 1 \text{ k} \Omega \parallel \frac{450 \Omega + 500 \Omega}{161} = 5.9 \Omega$$


$$\text{Pole} = \frac{1}{5.9 \Omega \cdot 100 \mu\text{F}} = 1.7 \text{ k} \frac{\text{rad}}{\text{sec}}$$

$$R_{th3} = 550 + (450 + 1 \text{ k} \Omega) = 2 \text{ k} \Omega$$

$$\text{Pole} = \frac{1}{2 \text{ k} \Omega \cdot 100 \mu\text{F}} = 5 \frac{\text{rad}}{\text{sec}}$$

$$f_L = \frac{1.7 \text{ k} \frac{\text{rad}}{\text{sec}}}{2\pi} = 271 \text{ Hz}$$

$$f_L = 271 \text{ Hz}$$


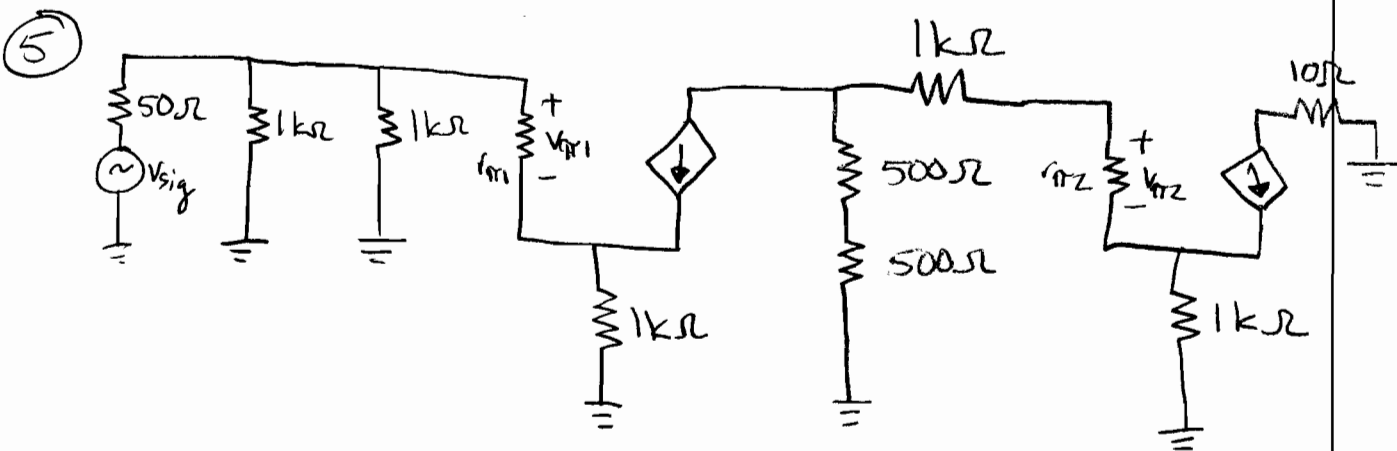


$$6) R_{in} = 500\Omega + (161)(r_{\pi 1} + 1k\Omega) = 234k\Omega$$

$$R_{out} = 1k\Omega \parallel \frac{2k\Omega}{(161)} = 12.3\Omega$$


$$7) \frac{V_{out}}{V_{sig}} = ?$$

use Thv. Equivalents to simplify

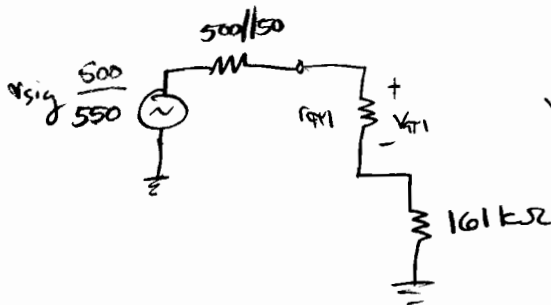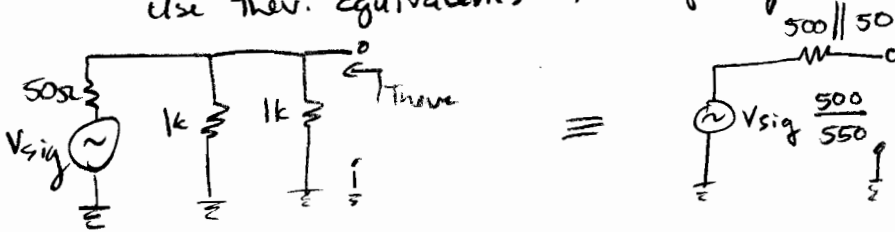

$$V_{\pi 1} = V_{sig} \frac{500}{550} \cdot \frac{r_{\pi 1}}{500 \parallel 50 + r_{\pi 1} + 161k\Omega}$$
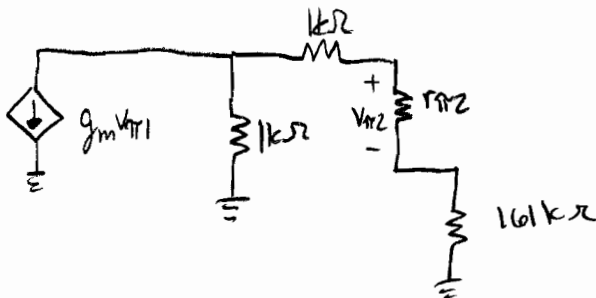
$$\frac{V_{\pi 1}}{V_{sig}} = \frac{500}{550} \cdot \frac{r_{\pi 1}}{500 \parallel 50 + r_{\pi 1} + 161k\Omega}$$



$$V_{\pi 2} = -g_{m1} V_{\pi 1} \frac{1k}{163k + r_{\pi 2}} r_{\pi 2}$$

$$\frac{V_{\pi 2}}{V_{\pi 1}} = \frac{-g_{m1} r_{\pi 2} (1k)}{163k + r_{\pi 2}}$$

$$\frac{V_{out}}{V_{\pi 1}} = \frac{-g_{m1} (1k) (161k)}{163k + r_{\pi 2}}$$

$$\frac{V_{out}}{V_{sig}} = \frac{V_{out}}{V_{\pi 1}} \frac{V_{\pi 1}}{V_{sig}} = \frac{500}{550} \frac{r_{\pi 1}}{(500 \parallel 50 + 161k\Omega + r_{\pi 1})} \frac{(-g_{m1} (1k) (161k))}{(163k + r_{\pi 2})}$$

$$\frac{V_{out}}{V_{sig}} = \frac{-500 r_{\pi 1} g_{m1} (161k)}{550 (500 \parallel 50 + 161k + r_{\pi 1}) (163k + r_{\pi 2})}$$

$$\frac{V_{out}}{V_{sig}} = -0.889 V/V$$

8) Changing the Bias on V_{B2} by changing the $1k\Omega$ resistor could increase the gain. (or on V_{B1})

Increasing the $1k\Omega$ resistor at V_{out} would also increase the output.