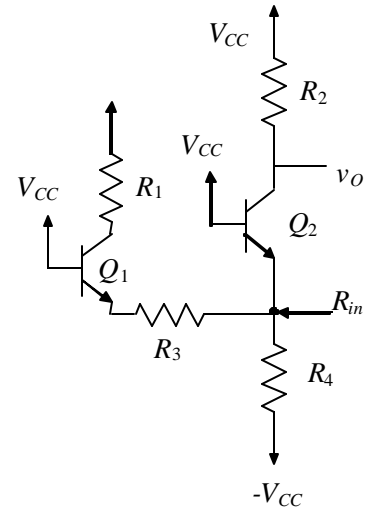



1. Assume the transistors at the right have a finite β and an infinite Early voltage. Write an expression for the input resistance R_{in} in the circuit shown below. Your expression should include *only* real resistances (R_1, R_2, R_3, R_4 , or a subset of these) and possibly β, r_{e1} or $r_{\pi1}$, and r_{e2} or $r_{\pi2}$. (Assume all transistors have the same β .) Circle your answer



2. The transistors below are identical, use $V_{BE}=0.7$, $\beta=100$, $g_m=80\text{m A/V}$, $r_{\pi}=1250\Omega$, $C_1=C_2=100\mu\text{F}$.

(a) Find the complete frequency response for V_o/V_{sig} , ignore r_o and the parasitic capacitors.

(b) Find the low frequency pole values.

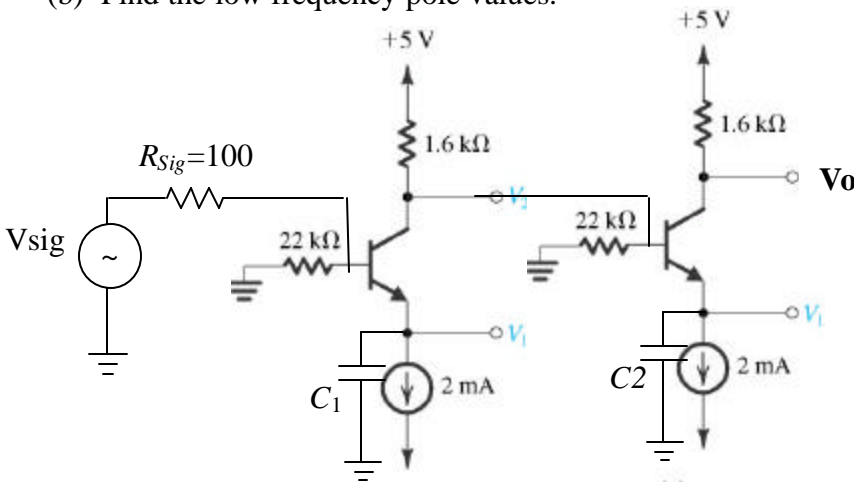

3. Use the following circuit for both problems #3 and #4: $\beta=100$, $|V_{BE}|=0.7$ Find $V_{E1}, V_{C1}, V_{C2}, V_{E2}, V_{E3}, V_{C3}, I_{E1}, I_{E2}$, and I_{E3} .

4. Analyze the circuit to find the midband gain V_o/V_{sig} , R_{in} (ignore input source, V_{sig}), and R_{out} (ignore $R_L=1\text{k}$).

