

1. Use: ignore r_o , $|V_{BE}|=0.7$, $b=100$

$V_t=1V$


$k_n'(W/L)=10mA/V^2$

$l=0$

$V_{DO}=0.8V$

$V_{IN} = 5+0.001\sin(20t)$

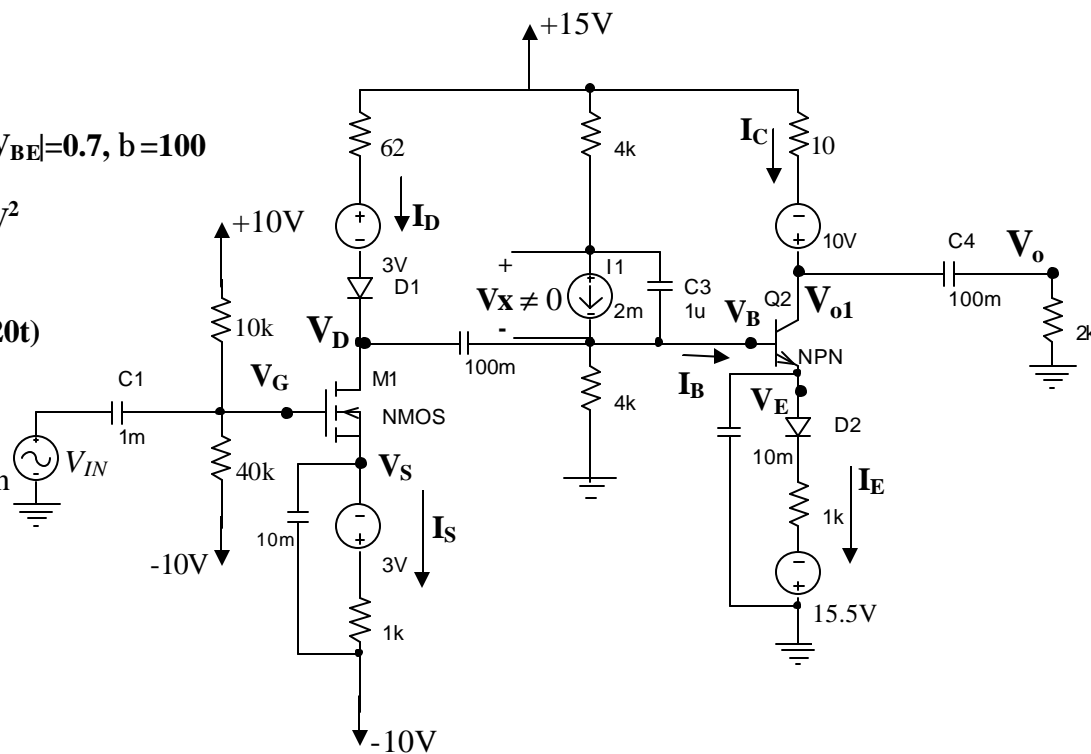For DC analysis, assume that the capacitors are open



(a) Solve for the DC currents:

- a. I_D
- b. I_S
- c. I_B
- d. I_E
- e. I_C

(b) Solve for the DC voltages:

- a. V_G
- b. V_S
- c. V_D
- d. V_B
- e. V_E

(c) Verify that the MosFet transistor, M1 is saturated. Verify that the BJT transistor, Q2 is active.



2. Create a rough sketch of the total waveforms seen at V_o and V_{o1} given V_{IN} stated above, $V_B/V_{IN}=-3V/V$, and $V_o/V_B=-27V/V$. Make sure to label all relevant y-axis values (maximum, minimum, etc.). First draw V_{o1} and then draw V_o . There should be 2 sketches.

3. Use the circuit on the next page: ignore r_o and l , $|V_{BE}|=0.7$, $b=100$, $n=1$, $V_T=25mV$, $V_t(\text{threshold voltage})=1V$, $k_n'(W/L)=10mA/V^2$, $V_{sig} = 0.02\sin(20t)$, $I_{E3}=4mA$, $I_{D1ODE}=2mA$, $I_D=20mA$

For the following hybrid- π equivalent circuit below, find the following values:


- (a) Find r_d , $r_{\pi3}$, g_{m2} , and g_{m3} values.
- (b) R_{in} (input resistance –ignore only the input source, V_{sig} ; include **all** resistors seen above V_{sig})
- (c) R_{out} (output resistance-include **all** resistors at node {**no load is connected**})
- (d) midband gain, $\frac{V_o}{V_{sig}}$

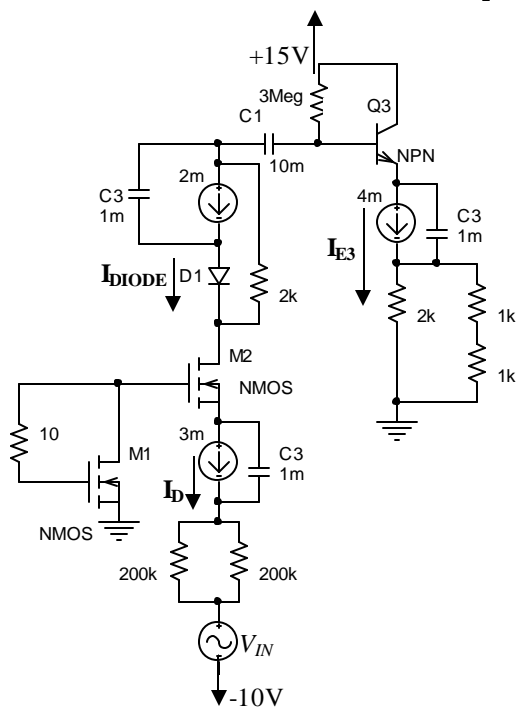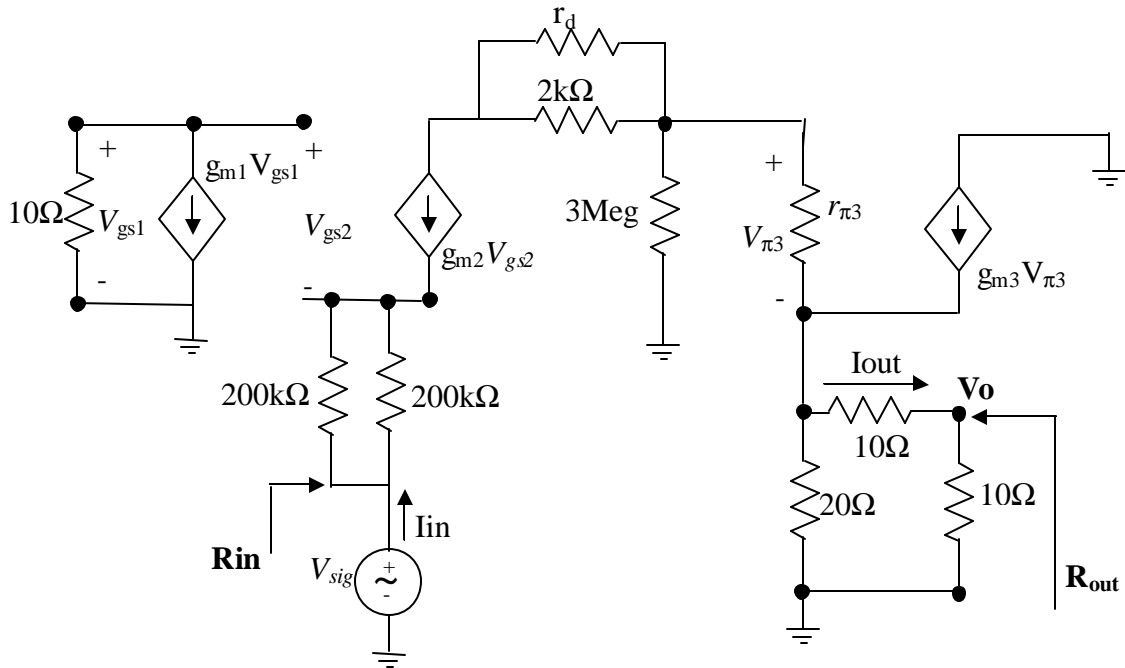4. (a) Explain why or why not this is a good amplifier for voltage amplification, V_o/V_{sig} .
 (b) Explain why or why not this is a good amplifier for current amplification, I_{out}/I_{in} .



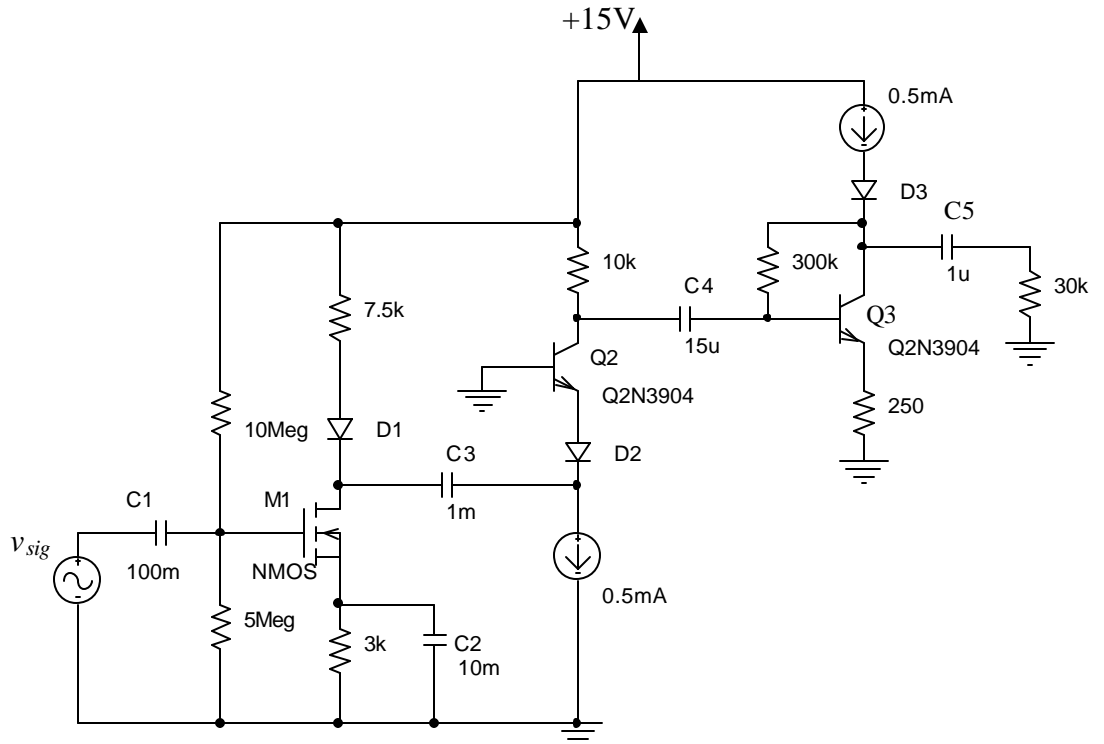5. For the circuit shown below:

Draw the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , $v_{\pi2}$, etc.). **Include** r_o for all transistors. $v_{sig} = 0.001\sin(10t)$ AC.



6. $|V_{BE}|=0.7$, $\beta=100$, ignore r_o , $V_4 = \{0.1\sin(\omega t)\}$ Volts. Assume that the applied signal frequency is adequate to keep the circuit operating in the flat midband region. Assume that the capacitors act as an open for DC operation and a short for AC operation. The following DC values were measured:
 $I_D=1.3\text{mA}$, $V_D=9\text{V}$, $V_G=6\text{V}$, $V_S=3.1\text{V}$, $I_E=12\text{mA}$, $V_E=2.3\text{V}$, $V_B=3\text{V}$, $V_C=10\text{V}$.

The AC gain was measured to be $V_{o1}/V_4=83\text{V/V}$, $V_{o2}/V_{o1}=1\text{V/V}$, $r_{\pi}=200\Omega$, $g_{m_MOSFET}=5\text{mA/V}$.

- Does this circuit operate as a **linear** AC amplifier with the applied shown voltage? If so, what is the gain, $\frac{V_o}{V_{sig}}$, of the following circuit? If not, explain why.

7. Assume that C2 and C6 contribute pole values less than 1rad/sec . Calculate the pole contributions of C2 and C4. What is f_L (in rad/sec)?

