
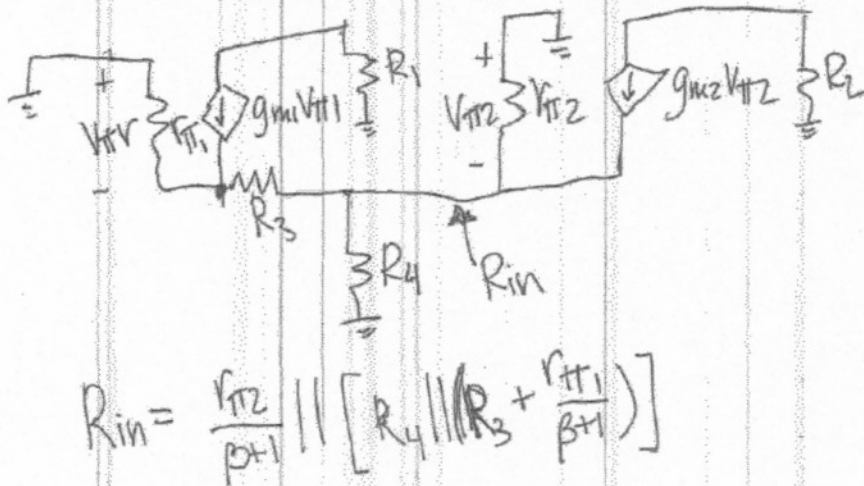


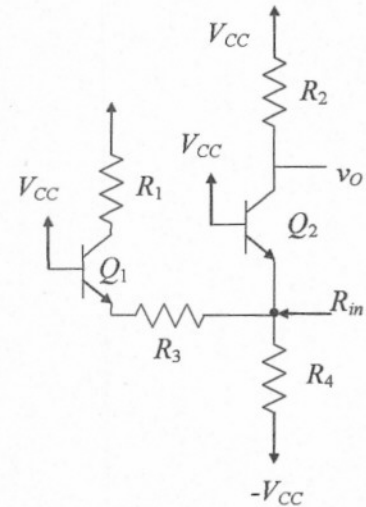1. Assume the transistors at the right have a finite β and an infinite Early voltage. Write an expression for the input resistance R_{in} in the circuit shown below. Your expression should include *only* real resistances (R_1, R_2, R_3, R_4 , or a subset of these) and possibly β, r_{e1} or $r_{\pi 1}$, and r_{e2} or $r_{\pi 2}$. (Assume all transistors have the same β .) Circle your answer





$$R_{in} = \frac{r_{\pi 2}}{\beta + 1} \parallel \left[R_4 \parallel \left(R_3 + \frac{r_{\pi 1}}{\beta + 1} \right) \right]$$



2. The transistors below are identical, use $V_{BE}=0.7, \beta=100, g_m=80\text{m A/V}, r_{\pi}=1250\Omega, C_1=C_2=100\mu\text{F}$.

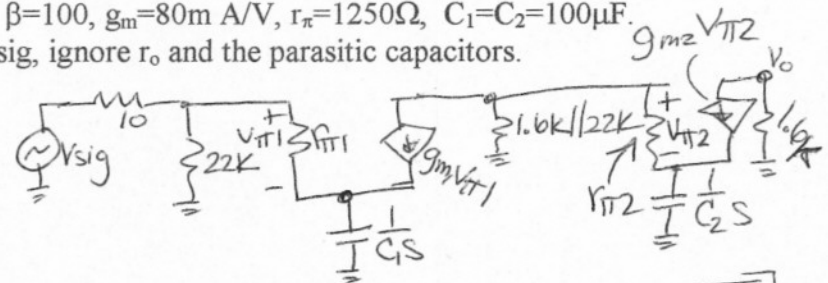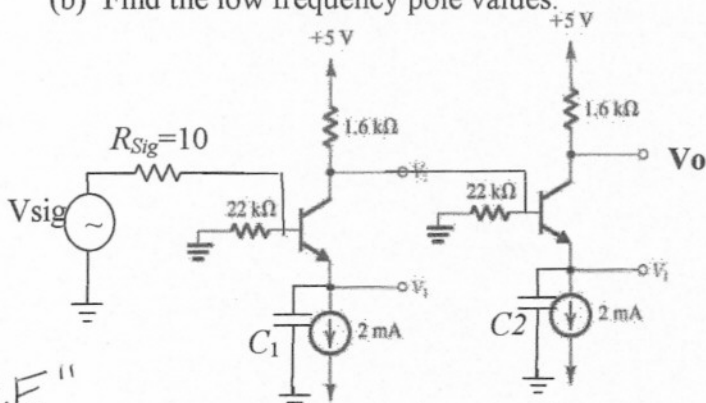- (a) Find the complete frequency response for V_o/V_{sig} , ignore r_o and the parasitic capacitors.
- (b) Find the low frequency pole values.



poles:

$$C_1 \Rightarrow \frac{1}{C_1 (r_{\pi 1} + 22k \parallel 10)} \approx \frac{1}{128 \text{ Hz}} \approx 808 \text{ rad/sec}$$

$$C_2 = \frac{1}{C_2 (r_{\pi 2} + 1.6k \parallel 22k)} \approx \frac{1}{59 \text{ Hz}} \approx 368 \text{ rad/sec}$$

"CE"

See Eq: 5.183 \Rightarrow Assume no interaction between capacitors:

midband gain \Rightarrow


$$V_o = -g_{m2} V_{tr2} (1.6k) = -g_{m2} (1.6k) (-g_{m1}) (1.6k \parallel 22k \parallel r_{\pi}) \cdot V_{\pi 1}$$

$$V_{\pi 1} = \frac{V_{sig} (22k \parallel r_{\pi})}{(22k \parallel r_{\pi}) + 100} \Rightarrow \frac{V_o}{V_{sig}} = 6420 \text{ V/V}$$

freq:
$$\frac{V_o}{V_{sig}} = \frac{6420 \text{ S}^2}{(s + 808)(s + 368)}$$

3. Use the following circuit for both problems #3 and #4: $\beta=100$, $|V_{BE}|=0.7$ Find V_{E1} , V_{C1} , V_{C2} , V_{E2} , V_{E3} , V_{C3} , I_{E1} , I_{E2} , and I_{E3} .

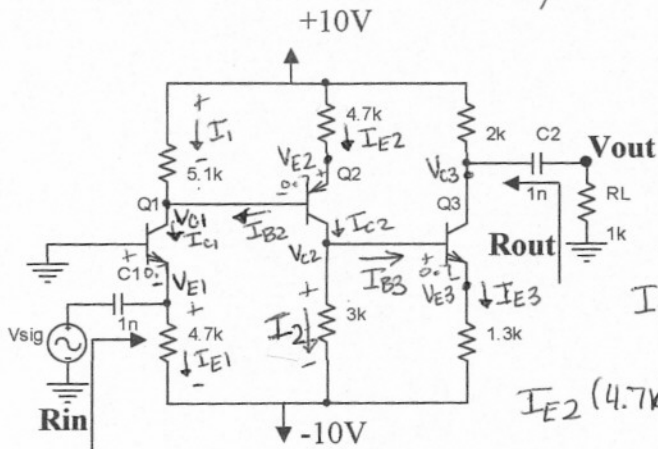4. Analyze the circuit to find the midband gain V_o/V_{sig} , R_{in} (ignore input source, V_{sig}), and R_{out} (ignore $R_L=1k$).



$$-10 + I_{E1}(4.7k) + V_{BE} = 0$$

$$I_{E1} = \frac{10 - 0.7}{4.7k} \approx 2mA \text{ OR } 1.98m$$

$$-10 + I_{E1}(4.7k) - V_{E1} = 0 \Rightarrow V_{E1} = -0.6V \text{ OR } -0.7V$$

$$I_{C1} = \alpha I_{E1} = 1.98m \text{ (1.96m)}$$

$$+10 - I_{E2}(4.7k) - V_{EB} + I_1(5.1k) - V_0 = 0$$

$$I_1 = I_{B2} + I_{C1} \text{ and } I_{B2} = \frac{I_{E2}}{(\beta+1)}$$

$$I_{E2}(4.7k) + 0.7 + \frac{I_{E2}}{(\beta+1)} 5.1k - I_{C1}(5.1k) = 0$$

$$I_{B2} = \frac{I_{E2}}{(\beta+1)} = 19.6\mu$$

$$I_{E2} = \frac{-0.7 + (1.98m)(5.1k)}{(4.7k) + \frac{5.1k}{(\beta+1)}} = 1.98m \Rightarrow I_{C2} = \alpha I_{E2} = 1.93m$$

$$I_{E2} = 1.96m$$

$$+10 - I_1(5.1k) = V_{C1}$$

$$10 - (-19.6\mu + 1.98m)(5.1k) = V_{C1}$$

$$V_{C1} = 0.196V = V_{B2}$$

$$V_{E2} = V_{EB2} + V_{B2} = 0.896V$$

$$V_{C2} = I_{E2}(3k) - 10 = -4.2V$$

$$I_2 = I_{C2} - I_{B3} = 1.96m - 39\mu = 1.92m$$

$$+I_2(3k) - 0.7 - I_{E3}(1.3k) = 0$$

$$I_{B3} = \frac{I_{E3}}{(\beta+1)} \Rightarrow I_{B3} = 39\mu$$

$$I_{C2}(3k) - \frac{I_{E3}(3k)}{(\beta+1)} - 0.7 - I_{E3}(1.3k) = 0$$


$$I_{E3} = \frac{I_{C2}(3k) - 0.7}{\frac{3k}{(\beta+1)} + 1.3k} = 3.9m$$

$$V_{E3} = +I_{E3}(1.3k) - 10 = -4.93V$$

$$I_{C3} = \alpha I_{E3} = 3.86mA$$

$$10 - I_{C3}(2k) = V_{C3} = 2.28V$$

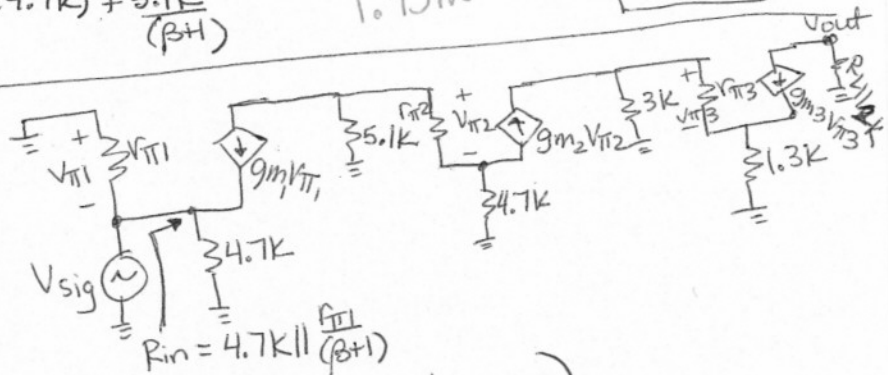check: Q1: $0.196 > 0 > -0.6V$
 Q2: $-4.2 < 0.196 < 0.9V$
 Q3: $2.28 > -4.2 > -4.93$



(continued on next page)

$$R_{out} = 2k$$

$$r_{\pi 1} = \frac{V_T}{I_{B1}} = \frac{25m(101)}{2m} = 1263$$

$$g_{m1} = \beta / r_{\pi 1} = 79.2m$$


$$r_{\pi 2} = \frac{25m(101)}{1.98m} = 1275\Omega$$

$$g_{m2} = \beta / r_{\pi 2} = 78.4\mu$$


$$r_{\pi 3} = \frac{25m(101)}{3.9m} = 647$$

$$g_{m3} = \beta / r_{\pi 3} = 0.154$$

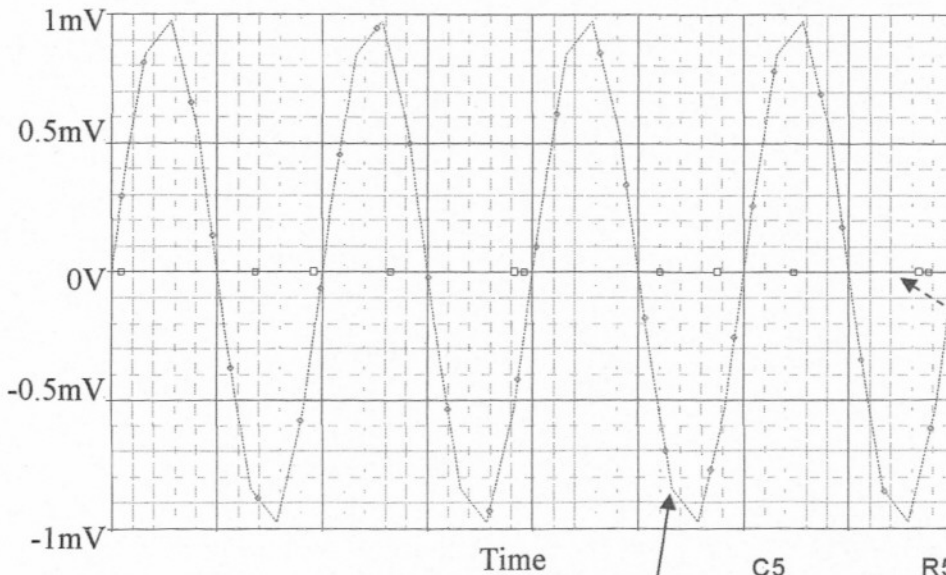5. The input and output curves vs time are shown below. Explain in detail why this circuit is not amplifying the signal and is instead 0V. $V_{CE_SAT}=0.2V$, $V_{BE}=0.7V$, and $\beta=100$.



VOFF = 0
VAMPL = 1m
FREQ = 1k

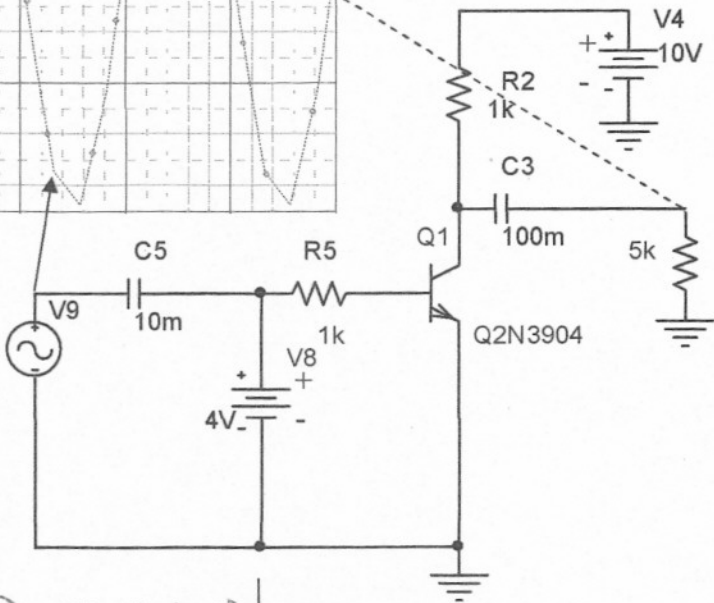

$$4V - I_B(1k) - 0.7 = 0$$

$$I_B = \frac{4 - 0.7}{1k} = 3.3mA$$

$$\therefore V_B = 4V - 3.3V = 0.7V$$

$$V_C = 10 - 1k(I_C) = 10 - 1k(\beta I_B) = 10 - 1k(33)$$

$$\Rightarrow V_C = 10 - 330V \text{ ! Not possible}$$

Is it cutoff? No $\rightarrow V_{BE} > 0.7$ since input = 4V
- must be saturated \Rightarrow


$$I_C = \frac{10 - 0.2}{1k} = 9.8mA$$

$$V_C = 0.2V, < V_B = 0.7, > V_E = 0$$

\therefore SAT \Rightarrow

$$\beta_{forced} = \frac{I_C}{I_B} = \frac{9.8m}{3.3m} \approx 3 < \beta_{forward} = 100$$

Look at hybrid- $\pi \Rightarrow$

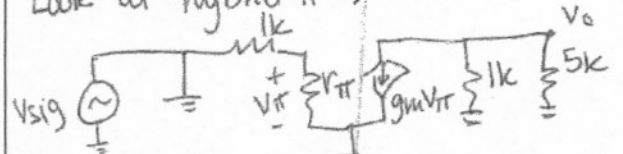


$$\frac{V_o}{V_{sig}} = 0!$$

$$V_{\pi} = 0$$

No amplification

• Can not amplify when in saturation operation!

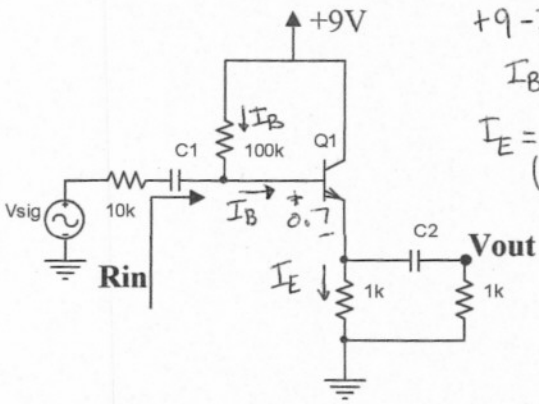6. β can range from 40 to 200. For the two extreme values of β ($\beta=40$ and $\beta=200$) find I_E , V_E , V_B , R_{in} (ignore the source resistance 10k), and the midband voltage gain V_{out}/V_{sig} .



$$+9 - I_B(100k) - 0.7 - I_E(1k) = 0$$

$$I_B = \frac{I_E}{\beta + 1}$$

$$I_E = \frac{8.3}{\left(\frac{100k}{\beta + 1}\right) + 1k}$$

$\beta=40$:

$$I_E = 2.41m$$

$$V_E = 1k(I_E) = 2.41V$$



$$V_B = V_E + 0.7 = 3.11V$$

$\beta=200$:

$$I_E = 5.54m$$

$$V_E = 5.54V$$

$$V_B = 6.24V$$

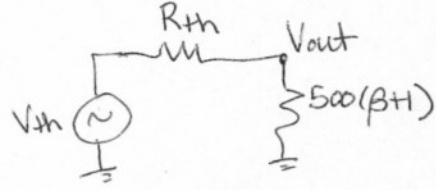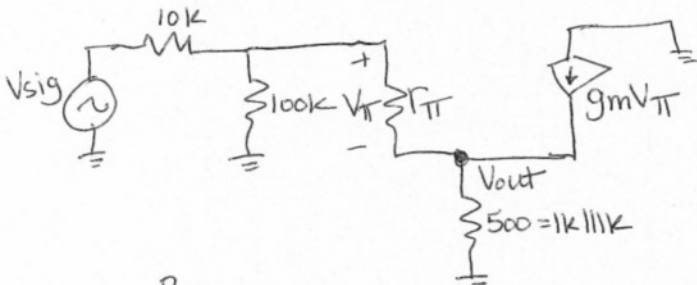

$$V_{out} = \frac{V_{th}(500)(\beta + 1)}{500(\beta + 1) + R_{th}}$$

$\beta=40$: $r_{\pi} = \frac{V_T}{I_B} = \frac{25m(41)}{2.41m} = 425\Omega$

$g_m = \beta / r_{\pi} = 0.094$


$$R_{in} = 100k \parallel (r_{\pi} + 500(\beta + 1)) = 17.3k$$

$$\frac{V_{out}}{V_{sig}} = \frac{0.91(500)(41)}{500(41) + 425 + 100k \parallel 10k} = 0.622 V/V$$


$\beta=200$: $r_{\pi} = \frac{25m(201)}{5.54m} = 907\Omega$, $g_m = 0.22$

$$R_{in} = 100k \parallel (907 + 500(201)) = 50.3k$$
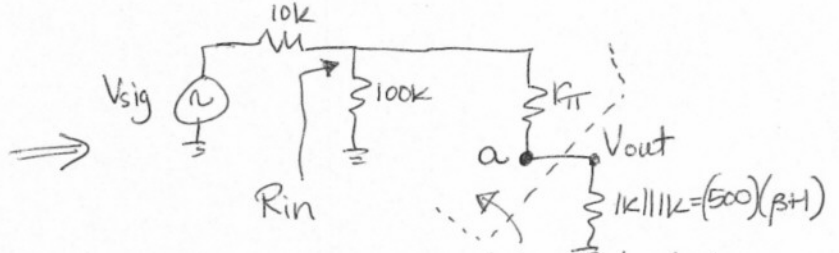
$$\frac{V_{out}}{V_{sig}} = \frac{0.91(500)(201)}{500(201) + 907 + 9091} = 0.83 V/V$$



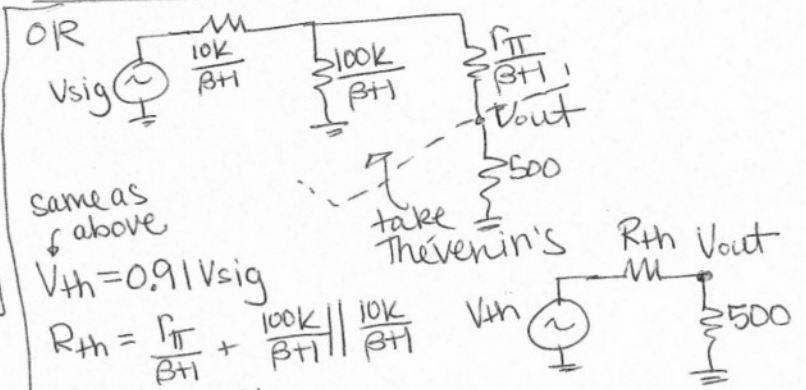Voltage at @ when circuit is disconnected or open \Rightarrow
 $V_{th} =$ Voltage at @ in reference to grd.
 $V_{th} = \frac{V_{sig}(100k)}{110k}$ { r_{π} has no current through it }
 $R_{th} = r_{\pi} + 100k \parallel 10k$



OR
 same as above

$$V_{th} = 0.91 V_{sig}$$

$$R_{th} = \frac{r_{\pi}}{\beta} + \frac{100k}{\beta + 1} \parallel \frac{10k}{\beta + 1}$$

$$V_{out} = \frac{500 \cdot V_{th}}{500 + R_{th}}$$

$\beta=40$:
 $R_{th} = 232$

$$\frac{V_{out}}{V_{sig}} = 0.622 V/V$$

same

$\beta=200$:
 $R_{th} = 49.7$

$$\frac{V_{out}}{V_{sig}} = \frac{500(0.91)}{500 + (907 + 9091)/201}$$

$$\frac{V_{out}}{V_{sig}} = 0.83 V/V$$

same