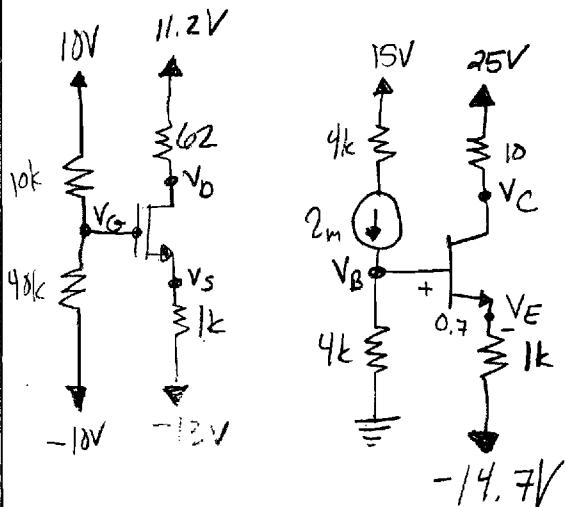


$$\textcircled{1} \quad r_o = \infty \quad N_{BSI} = 0.7 \quad \beta = 100$$

$$V_t = 1V \quad k_n' W_L = 10mA/V^2$$


$$V_{DS} = 0.8V \quad V_{in} = 5 + 1m\sin 2\omega t$$

$$\beta I_B = \frac{\beta}{\beta+1} I_E = I_C$$



$$I_G = 0 \quad I_D = I_S$$
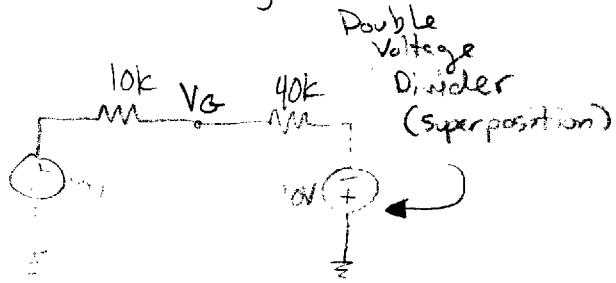
$$V_G = \frac{4}{5} 10 + \frac{1}{5} (-10) = 6V$$



$$V_S = -13V + I_D 1k \Rightarrow I_D = \frac{V_S + 13}{1k}$$

$$V_D = 11.2V - 62I_D$$

$$I_D = \frac{1}{2} k_n' W_L (V_{GS} - V_t)^2 = 5mA/c \left( 6 - V_S - 1 \right)^2 = 5m \left( 5 - V_S \right)^2$$

$$\frac{V_S + 13}{5} = (5 - V_S)^2 = 25 - 10V_S + V_S^2$$

$$V_S + 13 = 125 - 50V_S + 5V_S^2$$

$$V_S^2 - \frac{51}{5}V_S + \frac{112}{5} = 0 \Rightarrow V_S = \frac{16}{5} \text{ or } \cancel{V_S = 16.2V} \Rightarrow I_D = 16.2mA \text{ or } \cancel{20mA}$$

Not in Sat.

Not in Sat.

$$V_S = 3.2V \quad V_D = 10.2V \quad V_G = 6V$$

$$I_D = 16.2mA \quad I_S = 16.2mA \quad I_G = 0A$$

(a)  $I_D = 16.2mA$

$$I_S = 16.2mA$$

$$I_B = 209.5\mu A$$

$$I_E = 21.16mA$$

$$I_C = 20.95mA$$

(b)  $V_G = 6V$

$$V_S = 3.2V$$

$$V_D = 10.2V$$

$$V_B = 7.16V$$

$$V_E = 6.46V$$

(c) M<sub>1</sub> in Saturation?

$$V_{GS} \geq V_t ?$$



$$2.8V \geq 1V \text{ yes } \checkmark$$

$$V_{DS} - V_{GS} \geq -V_t ?$$


$$7V - 2.8V \geq -1V ?$$

$$4.2V \geq -1V \text{ yes } \checkmark$$

②  $\frac{V_o}{V_{in}} = 81V/V$

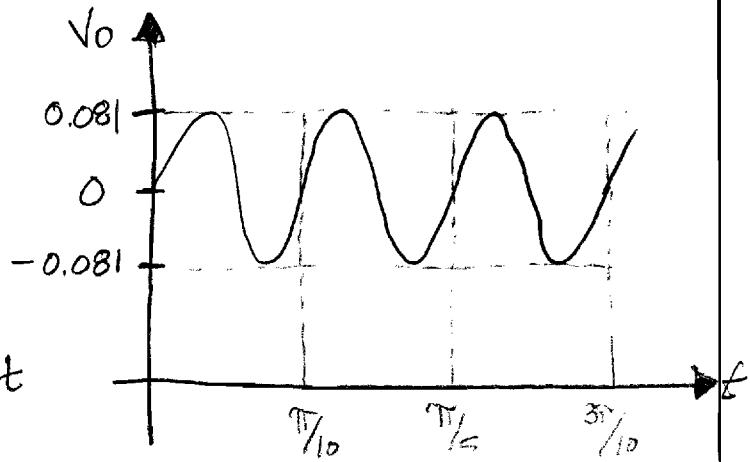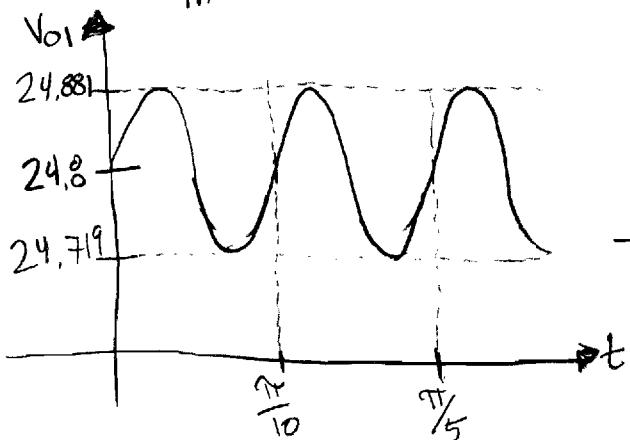

(3)

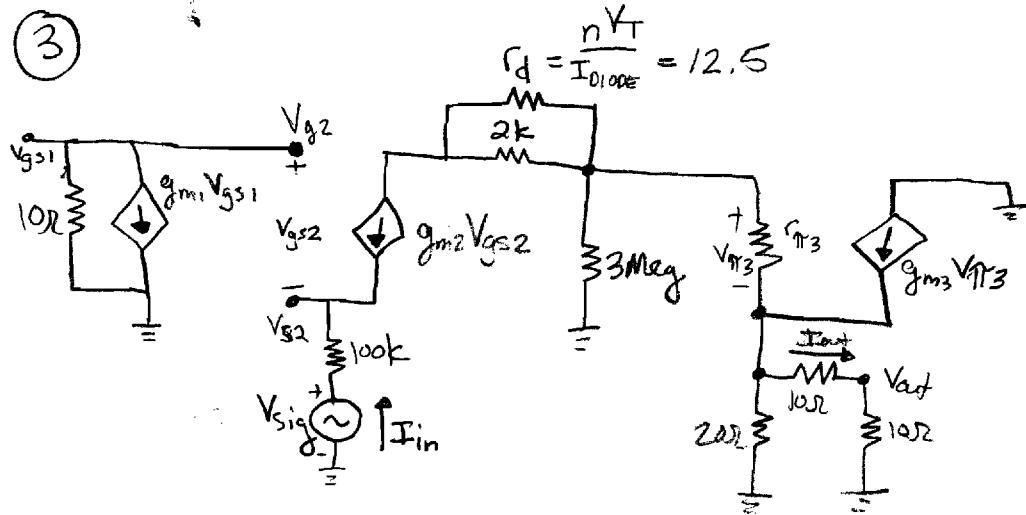

$$V_{gs1} = -g_m1 V_{gs1} \cdot 10\Omega$$

$$(1 + 10g_m1)V_{gs1} = 0$$

$$V_{gs1} = 0 \text{ since } 1 + 10g_m1 \neq 0$$

$$\text{which means } V_{gs2} = -V_{s2}$$

a)  $r_d = \frac{nV_T}{I_{D100E}} = 12.5\Omega$

$$r_{m2} = \frac{V_T}{I_B} = (\beta + 1) \frac{V_T}{I_E}$$

$$r_{m3} = 631.25$$

$$g_{m2} = 6.32 \text{ mA/V}^2$$

$$g_{m3} = \frac{I_C}{V_T} = \frac{\beta}{\beta + 1} \frac{I_E}{V_T}$$

$$g_{m3} = 158.4 \text{ mA/V}^2$$

b)  $R_{in} = 200k \parallel 200k + \frac{1}{g_{m2}}$   $\therefore 100.2k\Omega = R_{in}$

c)  $R_{out} = 10\Omega \parallel (10 + 20 \parallel \left( \frac{631 + 3\text{Meg}}{101} \right))$

$$R_{out} = 7.5\Omega$$

d) MidBand Gain?  $V_o/V_{sig}$

(3d cont)

$$V_{S2} = V_{sig} \cdot \frac{1}{g_m z} \cdot \frac{1}{R_{in}} \quad V_{GS2} = -V_{S2}$$

$$\frac{V_{GS2}}{V_{sig}} = -\frac{1}{g_m z} \cdot \frac{1}{R_{in}}$$

$$\begin{aligned} I &= -g_m z V_{GS2} (12.5 \parallel 2k + 3 \text{Meg}) (631.25 + (10)(10)) \\ &= -g_m z V_{GS2} (165Z) \Rightarrow \frac{I}{V_{GS2}} = -g_m z (165Z) \end{aligned}$$

$$I_2 = I \cdot \frac{3 \text{Meg}}{3 \text{Meg} + 631.25 + 10 \cdot 10} \approx 0.999 I$$

$$\frac{I_2}{I} = 0.999$$

$$\frac{I_{out}}{I_2} = \frac{20 \cdot (10)}{(20+10+10)(10)} = \frac{1}{2}$$

$$\frac{V_{out}}{I_{out}} = 10 \Omega$$

$$\frac{V_{out}}{V_{sig}} = \frac{V_{GS2}}{V_{sig}} \cdot \frac{Z}{V_{GS2}} \cdot \frac{I_2}{Z} \cdot \frac{I_{out}}{I_2} \cdot \frac{V_{out}}{I_{out}} = \left( -\frac{1}{g_m z} \cdot \frac{1}{R_{in}} \right) \left( g_m z (165Z) \right) \frac{0.999}{2}$$

$$\boxed{\frac{V_{out}}{V_{sig}} = 8.24 \text{ mV/V}}$$

$$\frac{I_{out}}{I_{in}} = \frac{V_{out}}{V_{sig}} \cdot \frac{I_{out}}{V_{out}} \cdot \frac{V_{sig}}{I_{in}} = \frac{R_{in}}{10 \Omega} \cdot 8.24 \text{ mV/V}$$

$$I_{out}/I_{in} = 82.6 \text{ A/A}$$


(4) a)

This is a horrible voltage amplifier because  $V_{o/v_i} = 8.24 \text{ mV/V}$ .

b)

This is a good current amplifier because  $I_o/I_i = 82.6 \text{ A/A}$

(5)

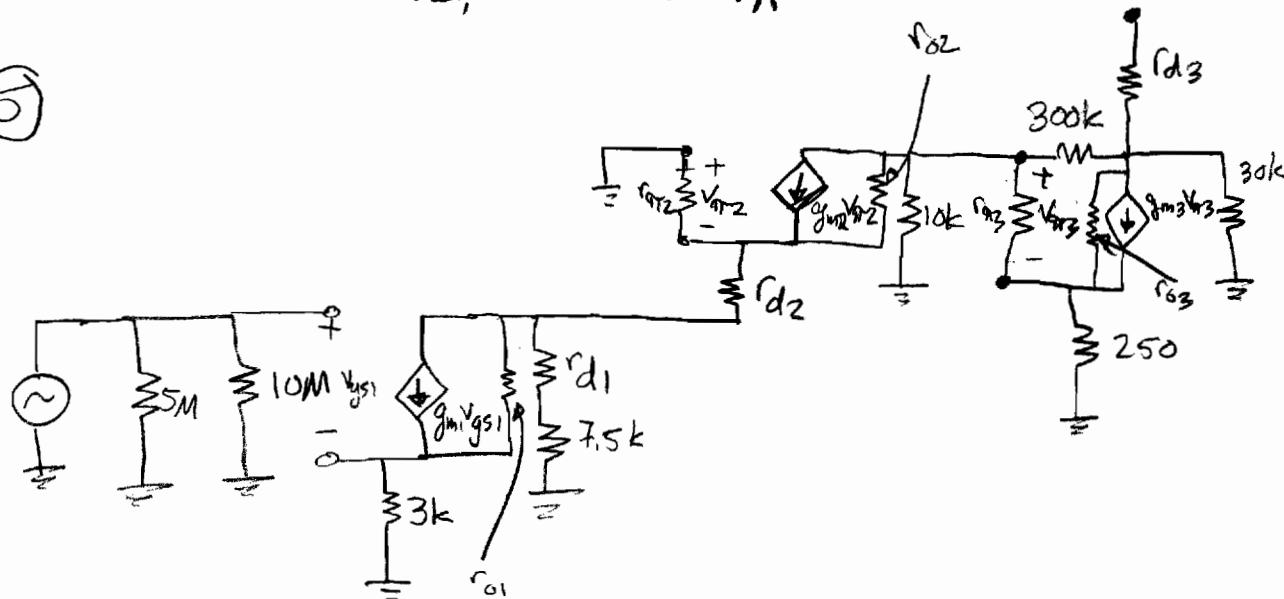

$$\textcircled{6} \quad \frac{V_{o1}}{V_4} = 83 \frac{V}{V} \quad \frac{V_{o2}}{V_{o1}} = 1 \frac{V}{V}$$

$$\frac{V_o}{V_{sig}} = \frac{V_4}{V_{sig}} \cdot \frac{V_{o1}}{V_4} \cdot \frac{V_{o2}}{V_{o1}} \cdot \frac{V_o}{V_{o2}} = 83 \frac{V}{V}$$

$$V_{sig} = 100 \text{mVAC}$$

$$V_o = \underbrace{8.3 \text{ VAC}}$$

This is 42% of the voltage supplies available. (20V)  
 This no longer qualifies as a "small-signal" and there  
 will be significant distortion in the amplifier.

NOT A LINEAR AMPLIFIER

(7)

$$C_3 = 1 \mu F$$

$$R_{th3} = 10k\Omega \parallel \frac{1}{g_m} = 10k \parallel \frac{1}{5m} = 196.07 \Omega$$

$$f_L' = \frac{2\pi}{R_{th3} C_3} = \underline{3.2 \times 10^{-5} \text{ Hz}}$$

$$C_4 = 1 \mu F$$

$$R_{th4} = R_L + R_1 \parallel \left( \frac{r_{in}}{\beta+1} + \frac{R_2}{\beta+1} \right) = 1k + 1k \parallel \left( \frac{200 + 100k}{101} \right) \approx 1.5k\Omega$$

$$f_L'' = \frac{2\pi}{R_{th4} C_4} \approx \underline{4200 \text{ Hz or } 4.2 \text{ kHz}}$$

$$f_L = f_L'' = 4.2 \text{ kHz}$$