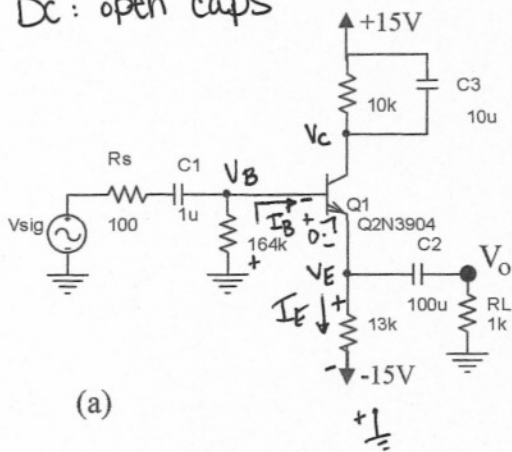


1. Use  $|V_{BE}|=0.7$ ,  $\beta=100$ . Analyze the following circuit(s) to find all DC currents and voltages. Analyze the circuit to find the midband gain,  $V_o/V_{sig}$ ,  $R_{in}$  (ignore  $R_s$ ),  $R_{out}$  (ignore  $R_L$ ), and find the low frequency pole values. {Each circuit below is worth 1 problem for a total of 3 problems}

DC: open caps



$$-15 + I_E(13k) + 0.7 + I_B(164k) = 0$$

$$I_B = I_E/101$$

$$I_E = \frac{14.3}{\frac{164k}{101} + 13k} = 0.98mA \approx 1mA$$

$$I_C = \frac{100}{101} (0.98mA) = 0.978mA \approx 0.99mA$$

$$I_B = 9.78\mu A$$

$$-V_E + I_E(13k) - 15 = 0 \Rightarrow V_E = I_E(13k) - 15$$

$$V_E = -2.3V \approx -2V$$

$$V_B = -I_B(164k) = -1.6V \text{ OR } V_E + 0.7 = V_B$$

$$V_C = 15 - I_C(10k) = +5.2V$$

AC: (short caps)

$$r_{\pi} = \frac{V_T}{I_B} = \frac{25m}{9.78\mu} = 2556$$

$$g_m = \beta / r_{\pi} = 39mA/V$$

$$R_{in} = 164k \parallel (r_{\pi} + (13k \parallel 1k)(\beta+1))$$

$$R_{in} = 164k \parallel 96,342 = 60,690$$


$$R_{out} = 13k \parallel (r_{\pi} + (164k \parallel 100))$$

$$R_{out} = 13k \parallel (26) = 26$$

$$V_o = \frac{V_{sig} \cdot R_{in}}{R_{in} + 100} = 0.998 V_{sig} \approx V_{sig}$$

$$V_o = \frac{V_i (13k \parallel 1k)(\beta+1)}{(13k \parallel 1k)(\beta+1) + r_{\pi}} = 0.97 V_{sig}$$

$$\frac{V_o}{V_{sig}} = 0.97 V/V$$

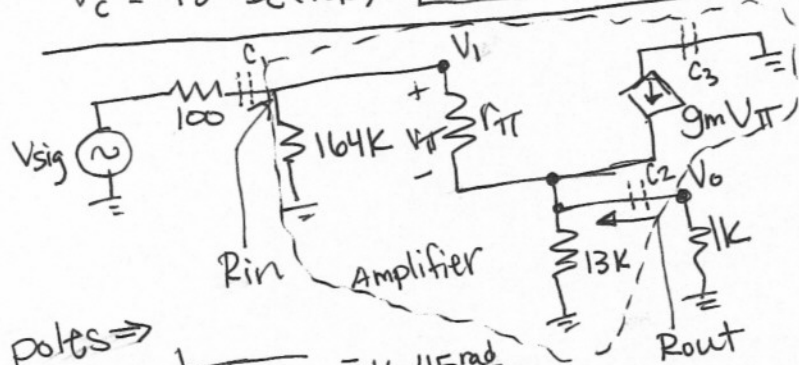

poles  $\Rightarrow$

$$C_1 \Rightarrow \frac{1}{C_1(100 + R_{in})} = 16.45 \text{ rad/sec.}$$


$$C_2 \Rightarrow \frac{1}{C_2(1k + R_{out})} = 9.7 \text{ rad/sec.}$$


$C_3 \Rightarrow$  No contribution at output, isolated from output

$\therefore C_1$  lowest freq. (highest value)

$$16.45 \text{ rad/sec. OR } 2.6 \text{ HZ}$$

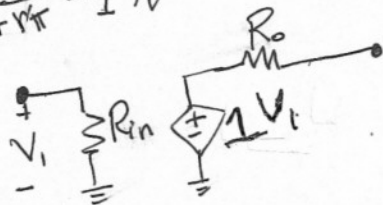$A_{v0} = \frac{V_o}{V_i} = \frac{13k(101)}{(100)13k + r_{\pi}} = 1V/V$   
 high  $R_{in}$   
 low  $R_{out}$   
 $\therefore$  output  $\approx$  input



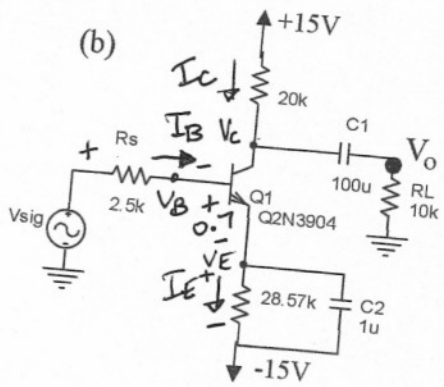

$V_{sig,DC} = 0$  DC: open caps  
 $-15 + I_E(28.57k) + 0.7 + I_B(2.5k) = 0$

$I_B = \frac{I_E}{101}$   
 $I_E = \frac{14.3}{28.57k + \frac{2.5k}{101}} = 0.5mA$

$I_C = \frac{100}{101}(0.5m) = 0.495mA \Rightarrow I_B = 4.95\mu A$

$-15 + I_E(28.57k) - V_E = 0 \Rightarrow V_E = -0.71V$


$V_B = -I_B(2.5k) = V_E + 0.7 = -0.01V$

$V_C = 15 - I_C(20k) = 5.1V$

$V_C > V_B > V_E$  ✓  
ACTIVE

AC: short caps

Amplifier

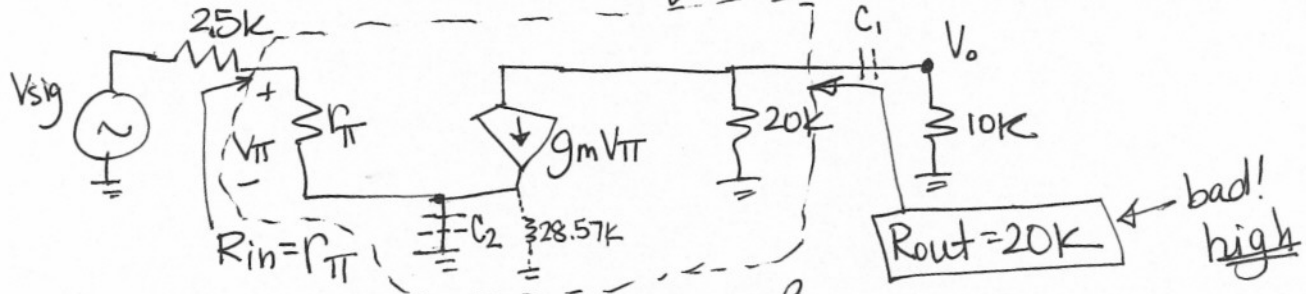

$r_{\pi} = \frac{V_T}{I_B} = \frac{25m}{4.95\mu} = 5,051 = R_{in}$

$g_m = \frac{\beta}{r_{\pi}} = 19.8mA/V$   
 Low! want high

bad! high  
 $R_{out} = 20k$

$V_o = -g_m V_{\pi} (20k \parallel 10k) = -g_m (20k \parallel 10k) \frac{V_{sig} \cdot r_{\pi}}{r_{\pi} + 2.5k}$


$\frac{V_o}{V_{sig}} = -\frac{666,732}{7551} = -88.3V/V$


$A_{vo} = \frac{V_o}{V_{\pi}} = -g_m (20k) = -396$

pole values:

$C_1 \Rightarrow \frac{1}{C_1(30k)} = 3 \text{ rad/sec}$

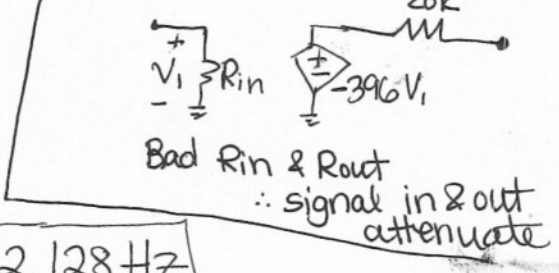$C_2 \Rightarrow \frac{1}{C_2 [28.57k \parallel (\frac{r_{\pi} + 2.5k}{\beta + 1})]} = 13,368 \text{ rad/sec} = 2,128 \text{ Hz}$



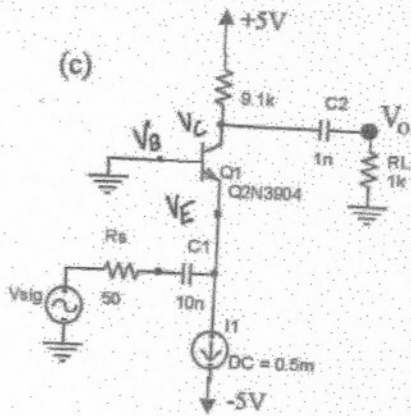

$$I_E = 0.5\text{m}$$

$$I_C = 0.495\text{m}$$


$$I_B = 4.95\mu$$

$$V_B = 0$$

$$V_E = -0.7$$

$$V_C = 5 - I_C(9.1\text{k}) = 0.5\text{V}$$

$$V_C > V_B > V_E \checkmark$$

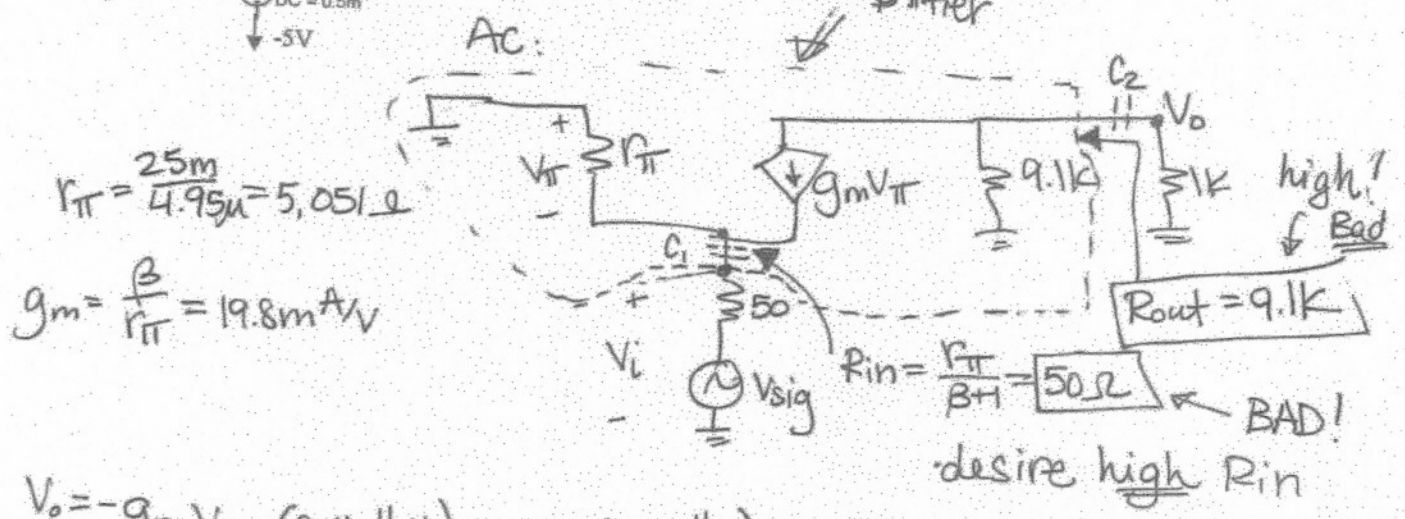

$$r_{\pi} = \frac{25\text{m}}{4.95\mu} = 5,051 \Omega$$


$$g_m = \frac{\beta}{r_{\pi}} = 19.8\text{mA/V}$$

$$R_{in} = \frac{r_{\pi}}{\beta + 1} = 50 \Omega$$

desire high Rin

$$V_o = -g_m v_{\pi} (9.1\text{k} \parallel 1\text{k}) = -g_m (9.1\text{k} \parallel 1\text{k}) V_{sig} \left( \frac{r_{\pi}}{\beta + 1} \right)$$
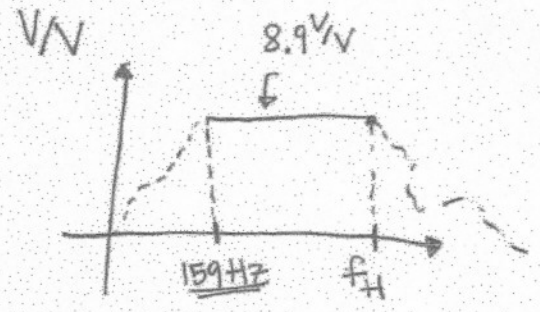
$$\frac{V_o}{V_{sig}} = + \frac{892}{100} = +8.9\text{V/V}$$




$$C_1 \Rightarrow \frac{1}{C_1 (50 + \frac{r_{\pi}}{\beta + 1})} = 1 \times 10^6 \frac{\text{rad}}{\text{sec}} \approx 159\text{Hz}$$

$$C_2 \Rightarrow \frac{1}{C_2 (9.1\text{k} + 1\text{k})} = 99,010 \frac{\text{rad}}{\text{sec}}$$

$$A_{vo} = \frac{V_o}{V_i} \Rightarrow -g_m v_{\pi} (9.1\text{k}) = V_o$$

$$v_{\pi} = -V_i$$

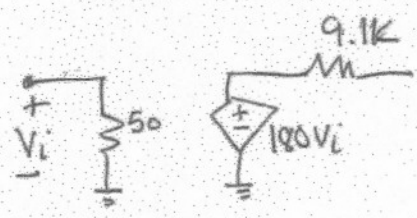
$$\therefore \frac{V_o}{V_i} = +180\text{V/V}$$





ignore  $r_o$

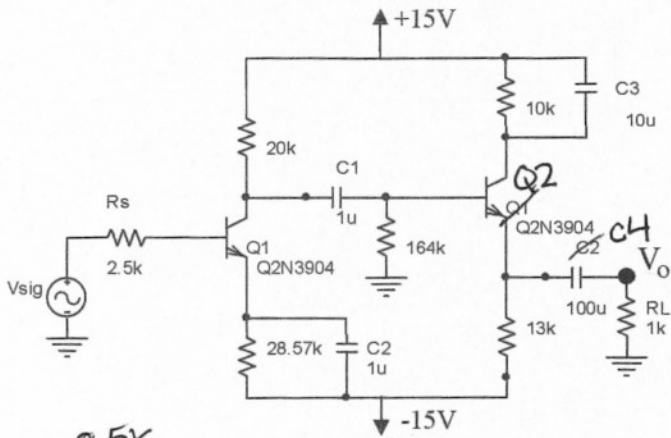
2. Note that the circuit below is the combination of (b) and (a) combined. Analyze the circuit to find the new  $R_{in}$  (ignore  $R_s$ ),  $R_{out}$  (ignore  $R_L$ ), and midband gain,  $V_o/V_{sig}$ . What is the value of  $f_L$  for this circuit?



same DC analysis  $\Rightarrow$

$$r_{\pi 1} = 5,051, g_{m1} = 19.8 \text{ mA/V}$$
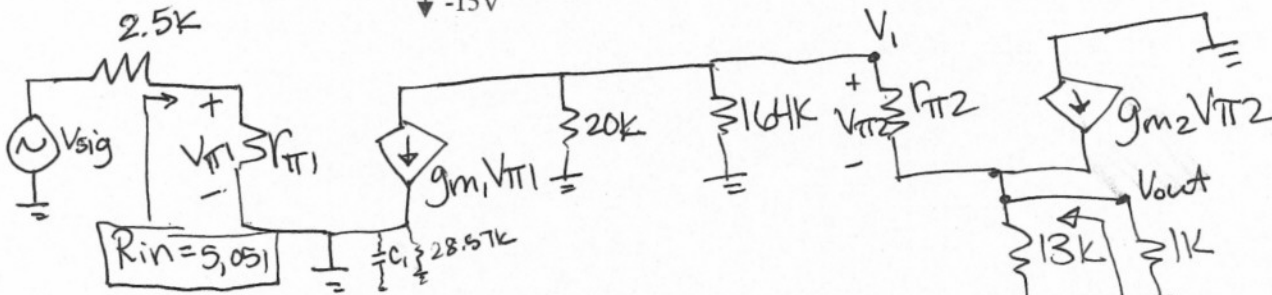
$$r_{\pi 2} = 2,556, g_{m2} = 39 \text{ mA/V}$$



$$V_1 = -g_{m1} V_{\pi 1} \left( \frac{20k \parallel 164k \parallel (r_{\pi 2} + (13k \parallel 1k)(\beta + 1))}{17,826 \parallel 96,342} \right)$$

$$R_{out} = 13k \parallel \frac{(r_{\pi 2} + 164k \parallel 20k)(\beta + 1)}{\beta + 1}$$


$$R_{out} = 13k \parallel 201 = \boxed{198}$$

$$V_1 = -19.8 \text{ m} (15,043) V_{\pi 1} = -298 V_{\pi 1}$$

$$V_{\pi 1} = \frac{V_{sig} (r_{\pi 1})}{r_{\pi 1} + 2.5k} = 0.67 V_{sig}$$

$$V_{out} = \frac{V_1 (13k \parallel 1k)(\beta + 1)}{(13k \parallel 1k)(\beta + 1) + r_{\pi 2}} = 0.67 V_{sig} (-298) (0.97) \Rightarrow \boxed{-194 \text{ V/V} = \frac{V_{out}}{V_{sig}}}$$

OR

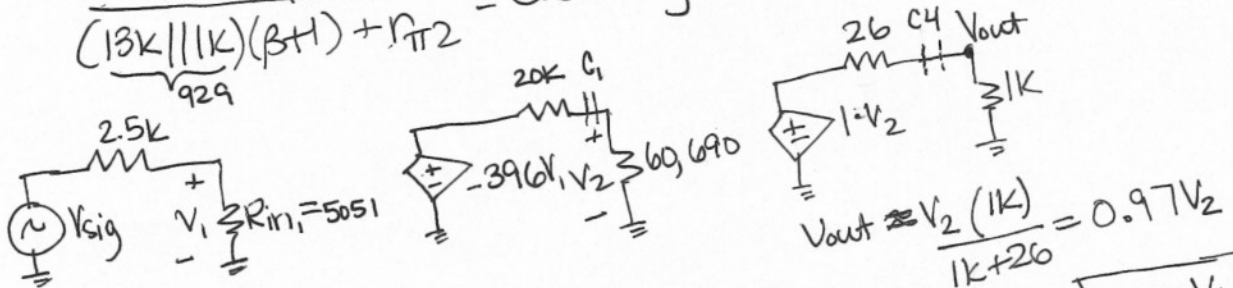

$$V_2 = \frac{-396 V_1 (60,690)}{60,690 + 20k} = -298 V_1$$

$$\Rightarrow \frac{V_{out}}{V_{sig}} = 0.97 (-298) (0.67) = \boxed{-194 \text{ V/V}}$$


$$V_1 = \frac{5,051 \cdot V_{sig}}{5,051 + 2.5k} = 0.67 V_{sig}$$

$$C_4 \Rightarrow \frac{1}{C_4 (26 + 1k)} = 9.75$$

poles:  $C_2 \Rightarrow$  (see (b))  $\boxed{2,128 \text{ Hz}} = f_L$

$$C_1 \Rightarrow \frac{1}{C_1 (20k + 60,690)} = 12.4$$

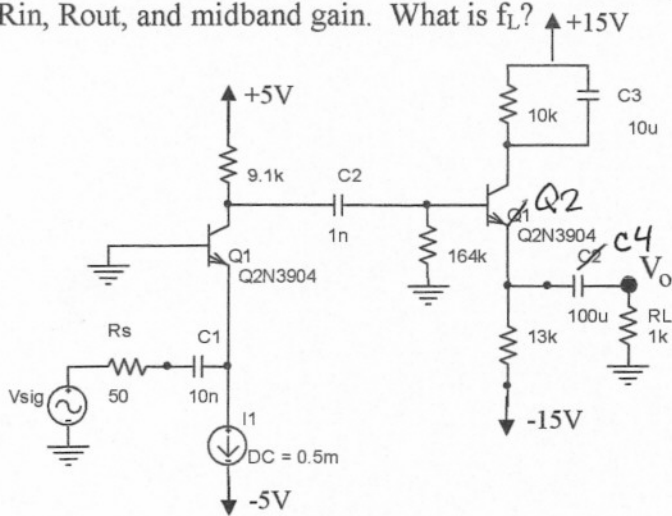3. Note that the circuit below is the combination of (a) and (c) combined. Analyze the circuit to find the new  $R_{in}$ ,  $R_{out}$ , and midband gain. What is  $f_L$ ?




$$r_{\pi 1} = 5,051$$

$$g_{m1} = 19.8m$$

$$r_{\pi 2} = 2,556$$


$$g_{m2} = 39m$$

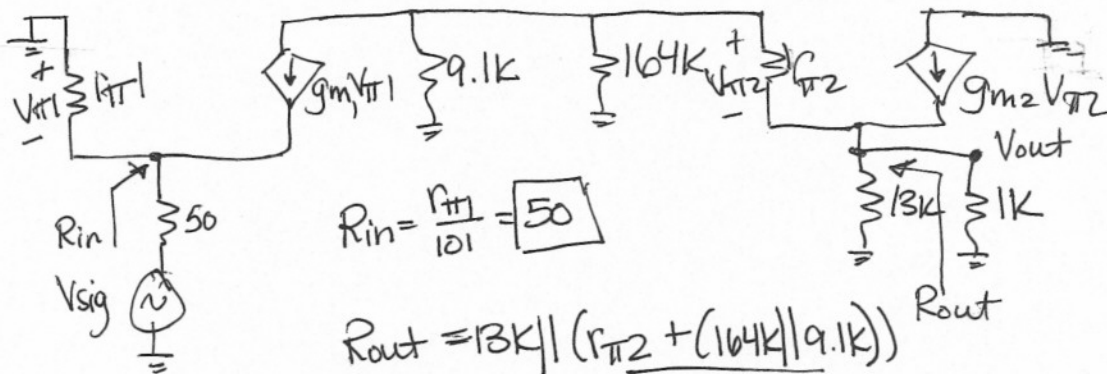

$$R_{in} = \frac{r_{\pi 1}}{\beta + 1} = 50$$

$$R_{out} = 13k \parallel (r_{\pi 2} + (164k \parallel 9.1k))$$

$$R_{out} = 13k \parallel 111 = 110$$

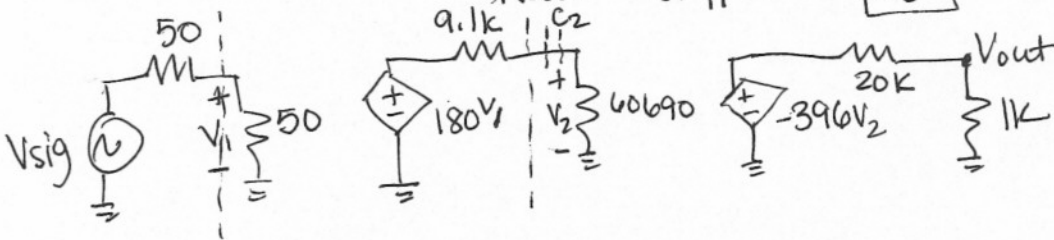

$$\frac{V_{out}}{V_{sig}} = \frac{-396(1k)}{21k} \cdot \frac{180(60,690)}{(60,690 + 9.1k)} \cdot \frac{50}{100} = -1,476 \text{ V/V}$$


$$C_1 \text{ (see (c))} \Rightarrow 159 \text{ Hz} \left( 1 \mu \frac{\text{rad}}{\text{sec}} \right)$$

$$C_2 \Rightarrow \frac{1}{C_2(9.1k + 60,690)} = 14,329$$

$C_3 \Rightarrow$  no contribution (not seen at output)

$$C_4 \Rightarrow \frac{1}{C_4(R_{out} + 1k)} = 9$$

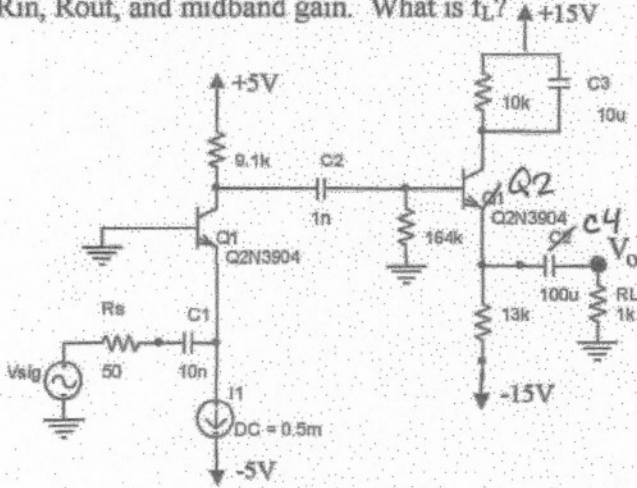3. Note that the circuit below is the combination of (a) and (c) combined. Analyze the circuit to find the new  $R_{in}$ ,  $R_{out}$ , and midband gain. What is  $f_L$ ?




$$r_{\pi 1} = 5,051$$

$$g_{m1} = 19.8m$$

$$r_{\pi 2} = 2,556$$


$$g_{m2} = 39m$$

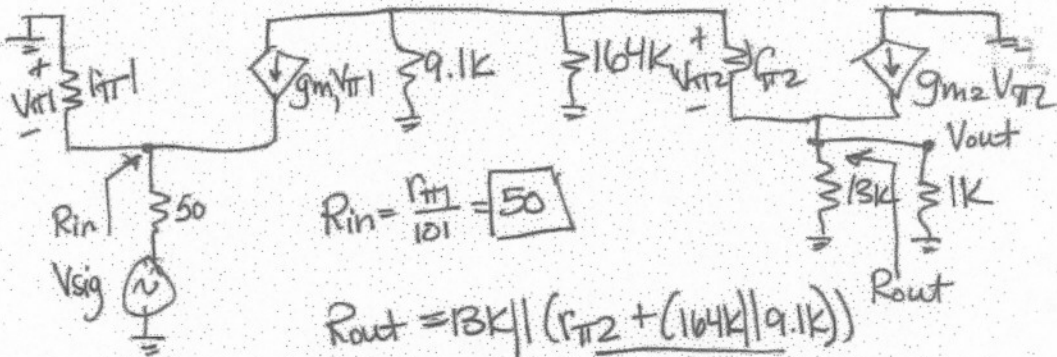

$$R_{in} = \frac{r_{\pi 1}}{101} = 50$$

$$R_{out} = 13k \parallel (r_{\pi 2} + (16.4k \parallel 9.1k))$$

$$R_{out} = 13k \parallel 111 = 110$$

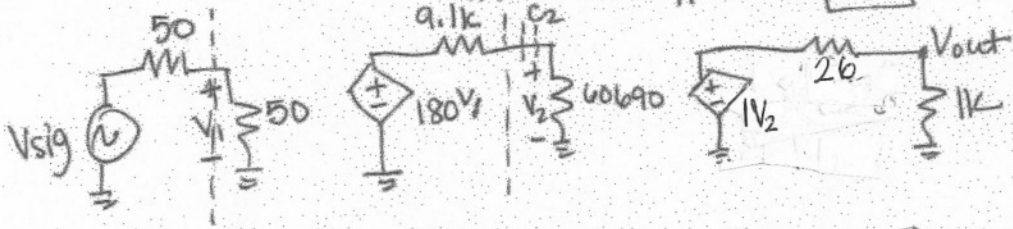

$$\frac{V_{out}}{V_{sig}} = \frac{1(1k)}{1k+26} \left( \frac{180(60,690)}{60,690+9.1k} \right) \left( \frac{50}{100} \right)$$

$$\frac{V_{out}}{V_{sig}} = (0.97)(78.3) = 76.3 \text{ V/V}$$

$$C_1 \text{ (see (c))} \Rightarrow 159 \text{ Hz} \quad (1 \text{ M rad/sec})$$

$$C_2 \Rightarrow \frac{1}{C_2(9.1k + 60,690)} = 14,329$$

$C_3 \Rightarrow$  no contribution (not seen at output)

$$C_4 \Rightarrow \frac{1}{C_4(R_{out} + 1k)} = 9$$