

BJT Analysis:

1. DC (Active mode)
2. AC (hybrid π)
3. Thevenin-Resistance Reflection Rule
4. Saturation

(NPN) $\cdot V_c < V_B$

(PNP) $\cdot V_c > V_B$

Homework 9 due on April 20th

No Quiz Wed. (Quiz on April 18th)

Exam 3 on April 23rd


Final on April 27th

{	Exam 1	<u>distributed</u>	8am	collected 9am
	" 2	"	9am	" 10am
	" 3	"	10am	" 11am

You have to come during correct hour.

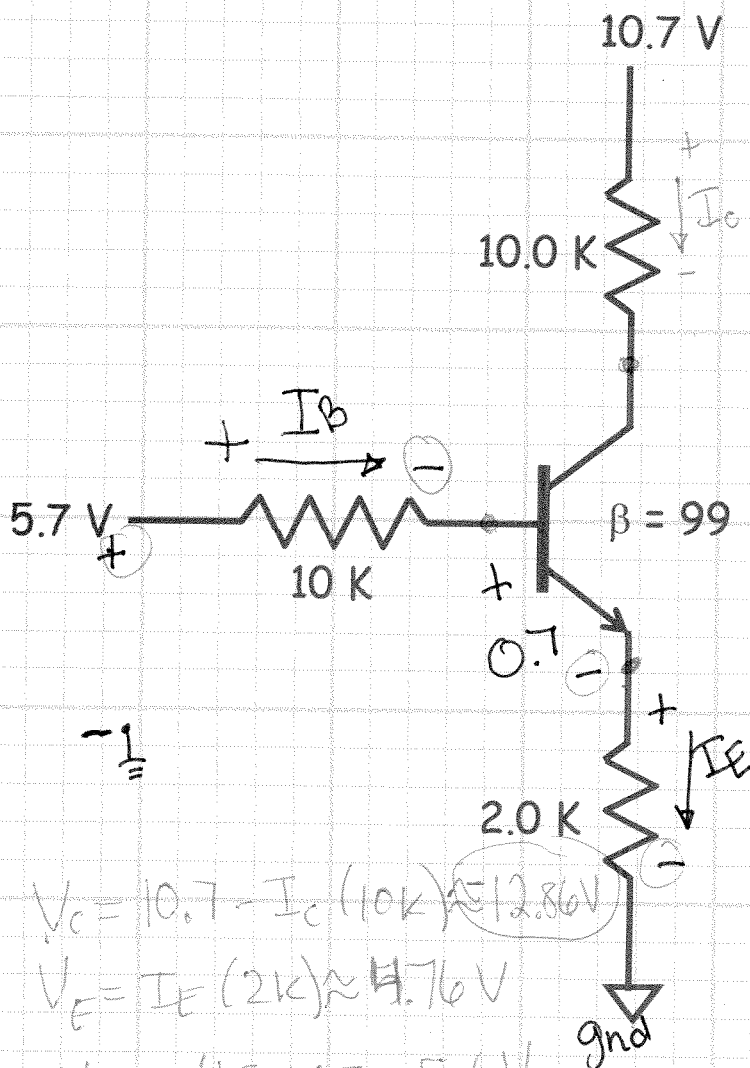Example: A BJT Circuit in Saturation

Determine all currents for the BJT in the circuit below.



Hey! I remember this circuit, its just like a previous example. The BJT is in active mode!

Let's see if you are correct! ASSUME it is in active mode and ENFORCE $V_{CE} = 0.7V$ and $i_C = \beta i_B$.

$\beta = 99$

The B-E KVL is therefore:

$$I_E = (\beta + 1) I_B$$

$$5.7 - 10 i_B - 0.7 - 2 (99 + 1) i_B = 0$$

Therefore $i_B = 23.8 \mu A$

$$I_E = (100)(23.8 \mu) = 2.38 m$$

$$I_C = \beta I_B = 99 (23.8 \mu) = 2.356 m$$

$$V_C = 10.7 - I_C (10k) \approx 12.86V$$

$$V_E = I_E (2k) \approx 4.76V$$

$$V_B = 4.8 + 0.7 = 5.6V$$

$$V_C < V_B$$

(power supply not big enough)

NOT ACTIVE

Q: So what do we do now ?


A: Go to Step 5; change the assumption and try it again!

Lets ASSUME instead that the BJT is in **saturation**. Thus, we ENFORCE the conditions:

OR $V_{CE} = 0.3V$

$$V_{CE} = 0.2 V \quad V_{BE} = 0.7 V \quad V_{CB} = -0.5 V$$

Now lets ANALYZE the circuit !

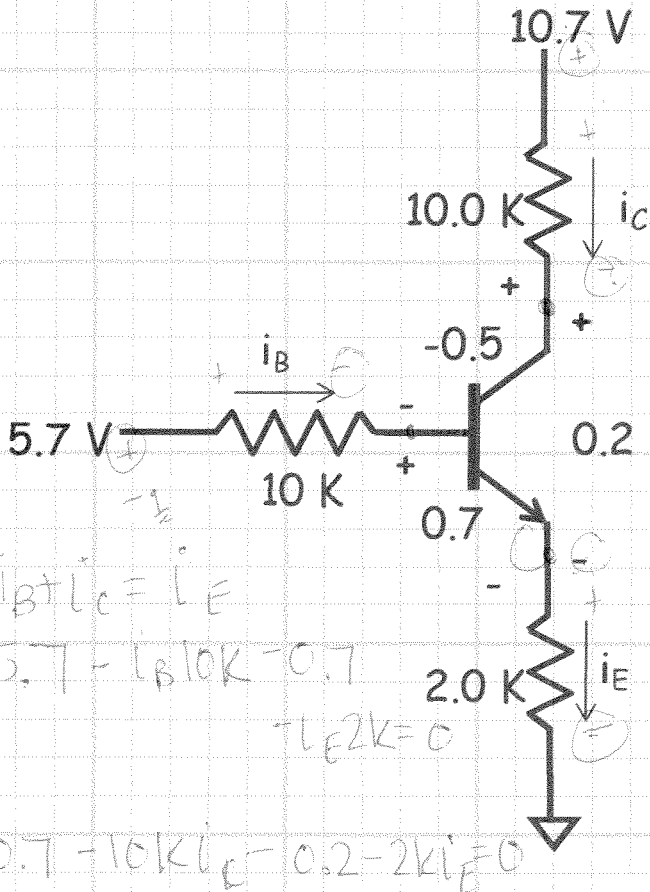

Note that we cannot directly determine the currents, as we do not know the base voltage, emitter voltage, or collector voltage.

But, we do know the differences in these voltages!

For example, we know that the collector voltage is 0.2 V higher than the emitter voltage, but we do not know what the collector or emitter voltages are!

Q: So, how the heck do we ANALYZE this circuit !?

A: Often, circuits with BJTs in saturation are somewhat more difficult to ANALYZE than circuits with active BJTs. There are often many approaches, but all result from a logical, systematic application of Kirchoff's Laws!

ANALYSIS EXAMPLE 1 - Start with KCL

We know that $i_B + i_C = i_E$ (KCL)

But, what are i_B , i_C , and i_E ??

Well, from Ohm's Law:

$$i_B = \frac{5.7 - V_B}{10} \quad i_C = \frac{10.7 - V_C}{10} \quad i_E = \frac{V_E - 0}{10}$$

Therefore, combining with KCL:

$$\frac{5.7 - V_B}{10} + \frac{10.7 - V_C}{10} = \frac{V_E}{10}$$

Look what we have, 1 equation and 3 unknowns.

 We need 2 more independent equations involving V_B , V_C , and V_E !

Q: Two more independent equations!? It looks to me as if we have written all that we can about the circuit using Kirchoff's Laws.

A: True! There are no more independent circuit equations that we can write using KVL or KCL! But, recall the hint sheet:

"Make sure you are using all available information".

There is more information available to us - the ENFORCED conditions!

$$V_{CE} = V_C - V_E = 0.2 \quad \Rightarrow \quad V_C = V_E + 0.2$$

$$V_{BE} = V_B - V_E = 0.7 \quad \Rightarrow \quad V_B = V_E + 0.7$$

Two more independent equations! Combining with the earlier equation:

$$\frac{5.7 - (0.7 + V_E)}{10} + \frac{10.7 - (0.2 + V_E)}{10} = \frac{V_E}{10}$$


One equation and one unknown! Solving, we get $V_E = 2.2 \text{ V}$.

Inserting this answer into the above equations, we get:

$$V_B = 2.9 \text{ V} \quad V_C = 2.4 \text{ V} \quad V_C < V_B \quad \text{is SAT}$$

$$i_C = 0.83 \text{ mA} \quad i_B = 0.28 \text{ mA} \quad i_E = 1.11 \text{ mA}$$

ANALYSIS EXAMPLE 2 - Start with KVL

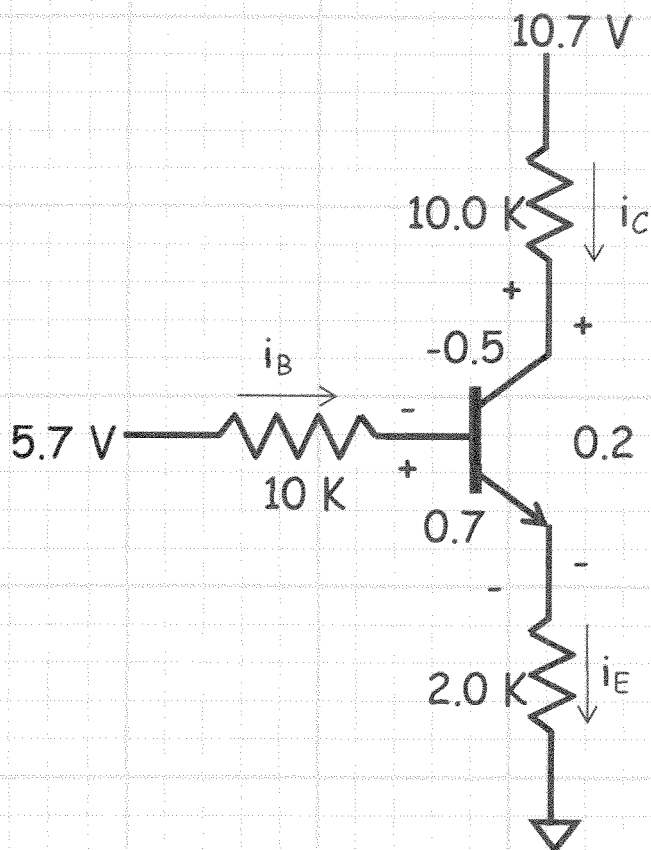

We can write the KVL equation for any two circuit legs:

B-E KVL:

$$5.7 - 10 i_B - 0.7 - 2 i_E = 0.0$$

C-E KVL:

$$10.7 - 10 i_C - 0.2 - 2 i_E = 0.0$$

Note the ENFORCED conditions are included in these KVL equations.

Simplifying, we get these 2 equations with 3 unknowns:

$$5.0 = 10 i_B + 2 i_E$$

$$10.5 = 10 i_C + 2 i_E$$

We need one more independent equation involving i_B , i_C , and i_E .

Try KCL!

$$i_B + i_C = i_E$$

Inserting the KCL equation into the 2 KVL equations, we get:

$$5.0 = 12 i_B + 2 i_C$$

$$10.5 = 2 i_B + 12 i_C$$

Solving, we get the same answers as in analysis example 1.

Lesson: There are multiple strategies for analyzing these circuits; use the ones that you feel most comfortable with!

However you ANALYZE the circuit, you must in the end also CHECK your results.

First CHECK to see that all currents are positive:

$$i_C = 0.83 \text{ mA} > 0 \quad \checkmark \quad i_B = 0.28 \text{ mA} > 0 \quad \checkmark \quad i_E = 1.11 \text{ mA} > 0 \quad \checkmark$$

Also CHECK collector current:

$$i_C = 0.83 \text{ mA} < \beta i_B = 27.7 \text{ mA} \quad \checkmark$$


Our solution is correct !!!

Problem 5 – (10 points)

(10)

$|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$, ignore r_o , and r_x , $v_{sig} = \{2+0.1\sin(\omega t)\}$ Volts. Assume that the capacitor acts as an open for DC operation and short for AC operation. Assume saturation for the transistor. Use the attached datasheet.

What is β_{forced} ?

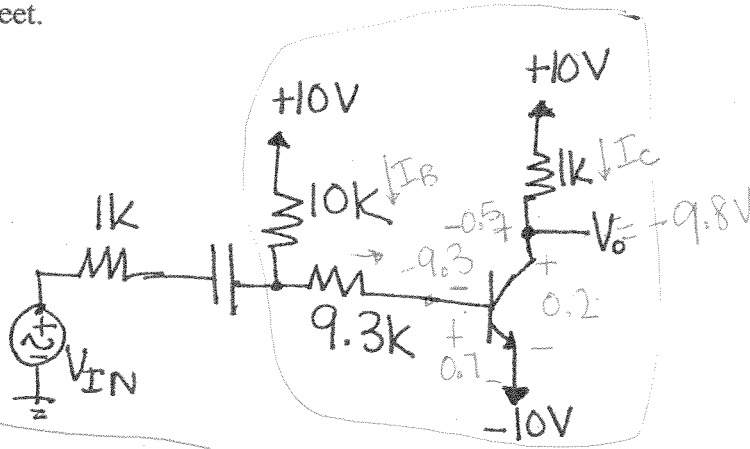


$$I_C = \beta_{\text{forced}} \cdot I_B$$

$$V_{CE\text{SAT}} = -0.2\text{V}$$

when $I_B = 1\text{mA}$

DC:

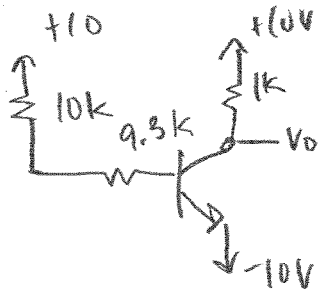

$$V_E = -10\text{V}$$

$$V_B = -(10 + 0.7)$$

$$= -9.3\text{V}$$

$$I_B = \frac{10 + 9.3}{19.3\text{k}} = \frac{19.3}{19.3\text{k}} = 1\text{mA}$$

$$V_{CE} = 0.2$$

$$V_C - V_E = 0.2\text{V}$$

$$V_C = 0.2 + V_E$$

$$= 0.2 - 10$$

$$= -9.8\text{V}$$

$$V_C < V_B$$

In SAT:

$$\beta_{\text{forced}} \ll (\beta = 100)$$

$$I_C = \frac{10 + 9.8}{1\text{k}} = 19.8\text{mA}$$

$$\frac{I_C}{I_B} = \beta_{\text{forced}} = \frac{19.8\text{mA}}{1\text{mA}} = 19.8 \ll \beta$$

$\beta_{\text{forced}} = 19.8$

Problem 1 – (35 points)

Use: ignore r_o , $|V_{BE}|=0.7$, $\beta=99$

$$V_{sig} = 3 + 0.005\sin(20t)$$

For DC analysis, assume that the capacitors act as an open

(a) Solve for the DC currents:


- a. I_B
- b. I_E
- c. I_C

(b) Solve for the DC voltages:


- a. V_B
- b. V_E
- c. V_o

(c) Prove that the transistor is operating in active mode.

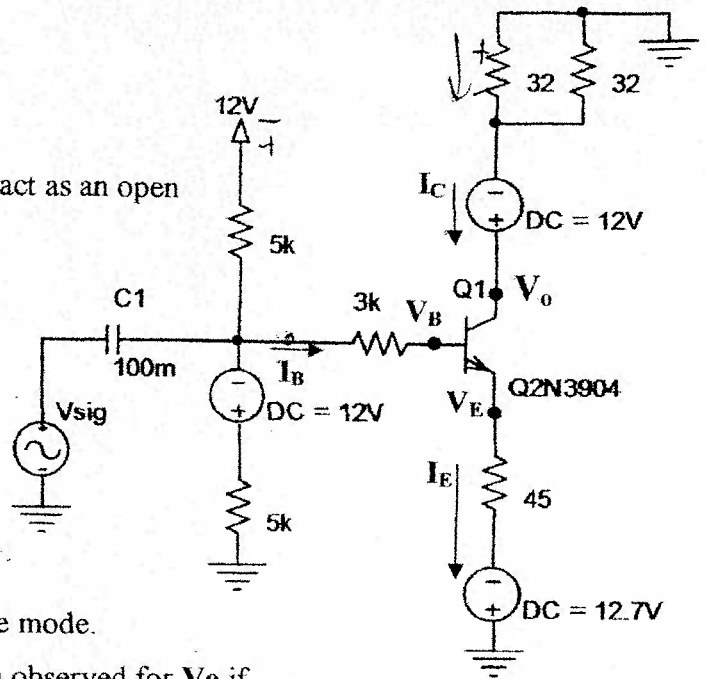(d) Sketch the **TOTAL** instantaneous waveform observed for V_o if the AC amplification is $V_o/V_{sig}=3V/V$.



Exam 3 Solution

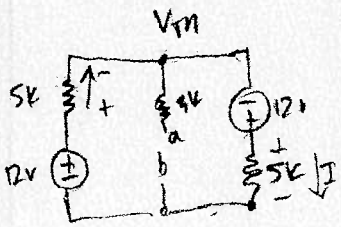


$$5kI - 12 + 5kI - 12 = 0$$

$$I = \frac{24}{10k} = 2.4mA$$

$$V_{th} = 5k(2.4mA) - 12 = 0V$$

$$R_{th} = 5k || 5k + 3k = 5.5k\Omega$$

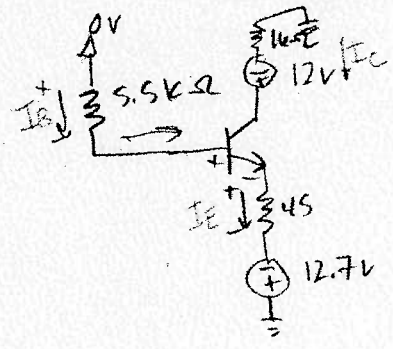

$$I_C = \beta I_B = \alpha I_E$$

$$I_E = I_B(\beta + 1)$$

$$0 - 5.5kI_B - 0.7 - 45I_E + 12.7 = 0$$

$$12V = I_B(5.5k + 45(\beta + 1))$$

(a)

$$I_B = 1.2mA$$

$$I_E = 120mA$$

$$I_C = 118.8mA$$

$$V_B = 0 - 5.5kI_B = -6.6; V_E = 0 - 12.7 + 45(120mA) \approx -7.3$$

$$V_C = 0 - 10kI_C + 12 \approx 10.1V$$

(b)

$$V_B = -6.6V$$

$$V_E = -7.3V$$

$$V_C = 10.1V$$

$$V_{o\ total} = V_{o\ DC} + V_{o\ AC}$$

$$= 10.1V + 3.5m \sin(20t)$$


(c) Active if $V_C \geq V_B > V_E$

$$10.1 \geq -6.6 > -7.3 \quad \therefore \text{Active}$$

(d) $V_{o\ total} = [10.1 + 15m \sin(20t)] V$

$$\omega = 20$$

$$f = \frac{20}{2\pi} = \frac{10}{\pi} \quad T = \frac{1}{f} = \frac{\pi}{10}$$

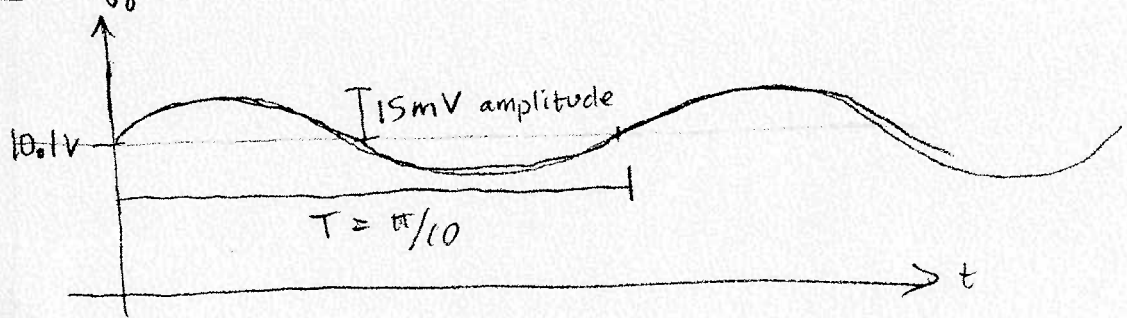

Problem 2 - (40 points)


Use: ignore r_o , $|V_{BE}|=0.7$, $\beta=100$
 $V_I = 7 + 0.004\sin(500t)$

$r_{\pi 1} = 4,000$ $g_{m2} = 100 \text{ mA/V}$, and $I_{B2} = 25 \mu\text{A}$ (DC value)

$r_{\pi 2} = \frac{\beta}{g_{m2}} = 1 \text{ k}\Omega$
 $g_{m1} = \frac{\beta}{r_{\pi 1}} = 25 \text{ mS}$

For the following hybrid- π equivalent circuit below, find the following values:

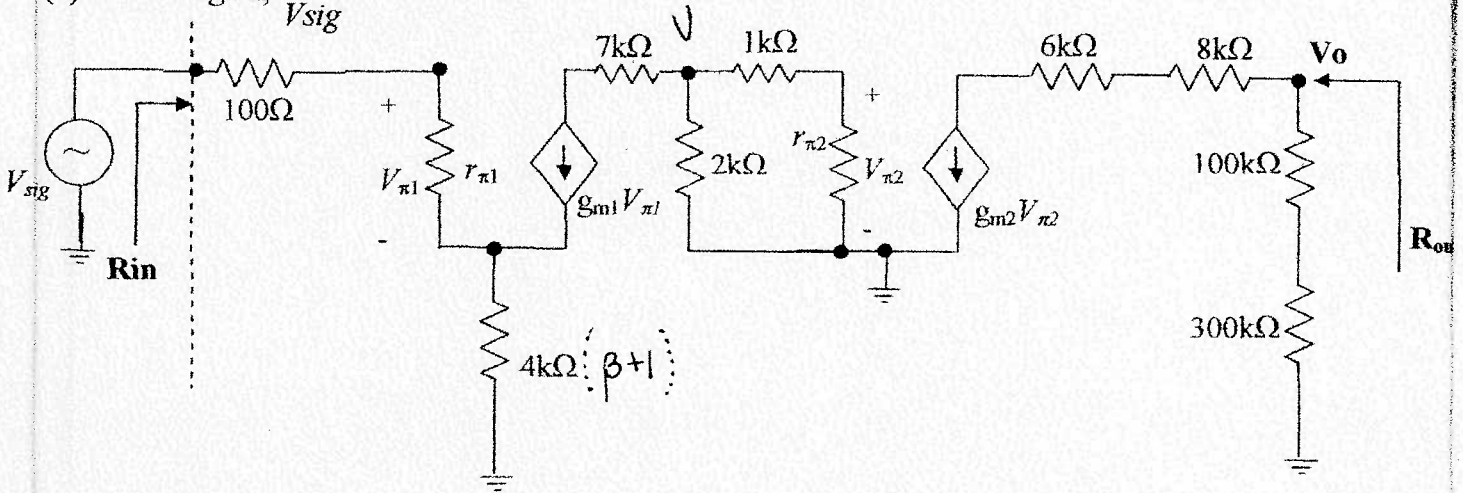- (a) R_{in} (input resistance - ignore only the input source, V_{sig} and include all resistors at the base)
- (b) R_{out} (output resistance - include **all** resistors at the collector {no load is connected}) *Hint: A floating resistor does not have a pathway to ground.*
- (c) midband gain, $\frac{V_o}{V_{sig}}$



$$R_{in} = 100 + r_{\pi 1} + (4k)(\beta + 1)$$

$$R_{in} = 100 + (4k) + (4k)(101)$$

$$R_{in} = 408.1 \text{ k}\Omega$$

$$R_{out} = 100k + 300k$$


$$R_{out} = 400k$$

$$r_{\pi 1} = 4 \text{ k}\Omega$$


$$g_{m1} = \frac{100}{4k} = 25 \text{ mS}$$

$$r_{\pi 2} = 1 \text{ k}\Omega$$

$$g_{m2} = 100 \text{ mS}$$

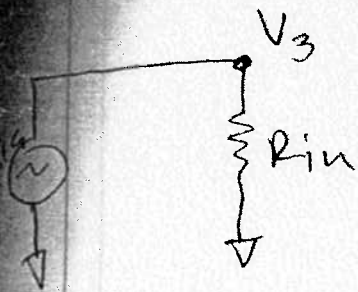


$$V_3 = V_{sig}$$

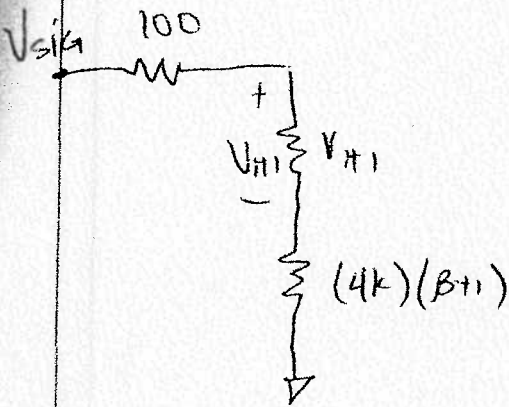


$$V_{\pi 1} = V_{sig} \frac{r_{\pi 1}}{R_{in}}$$
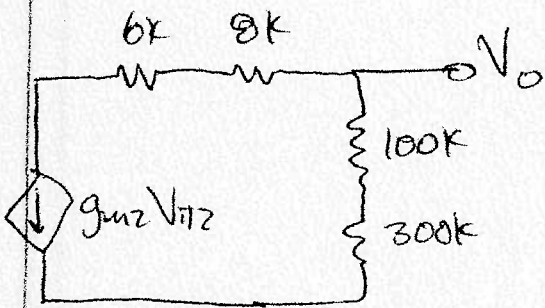
$$\frac{V_{\pi 1}}{V_{sig}} = \frac{r_{\pi 1}}{R_{in}}$$



$$V_o = -g_{m2} V_{t2} (400k)$$

$$\frac{V_o}{V_{t2}} = -g_{m2} (400k)$$

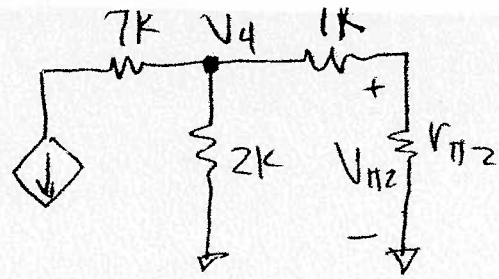

$$V_{\pi 2} = -g_{m1} V_{\pi 1} \frac{2k}{2k + 1k + r_{\pi 2}} \cdot r_{\pi 2}$$




$$\frac{V_{\pi 2}}{V_{\pi 1}} = \frac{-g_{m1} (2k) r_{\pi 2}}{3k + r_{\pi 2}}$$

$$\frac{V_o}{V_{sig}} = \frac{r_{\pi 1}}{R_{in}} \cdot \frac{-g_{m1} (2k) r_{\pi 2}}{3k + r_{\pi 2}} \cdot \frac{-g_{m2} (400k)}{1}$$

$$\frac{V_o}{V_{sig}} = 4901 \frac{V}{V}$$

Problem 5 – (5 points)

$|V_{BE}|=0.7$, $\beta=100$, ignore r_o , v_{sig} is shown in the graph below. Assume that the capacitor acts as an open for DC operation and short for AC operation. Does this circuit operate as a **linear** AC amplifier? If so, what is the gain, $\frac{V_o}{V_{sig}}$, of the following circuit? If not, explain why.

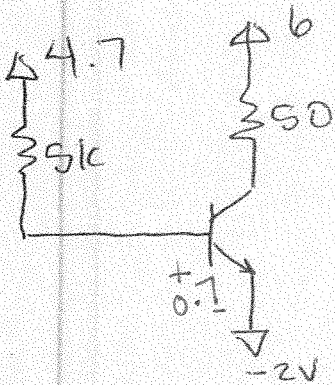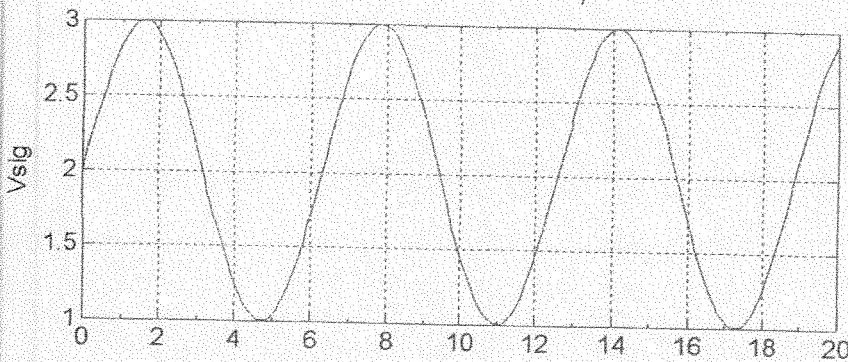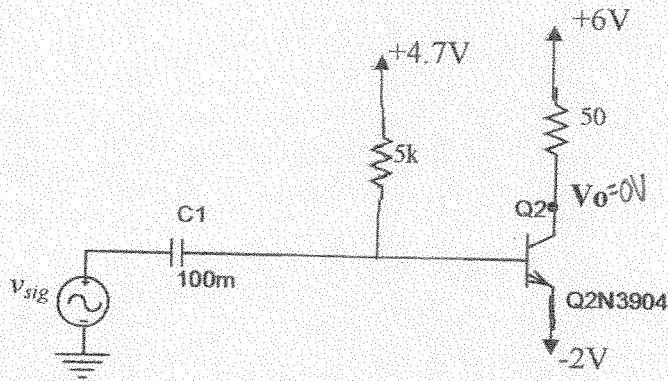

$V_E = -2V$

$V_B = -1.3V$


$V_C = 0$

$V_C \geq V_B > V_E \rightarrow \text{ACTIVE}$

$I_E = 121.2 \text{ mA}$

$I_B = (4.7 - (-1.3)) / 5k = 1.2 \text{ mA}$

$I_C = 120 \text{ mA}$

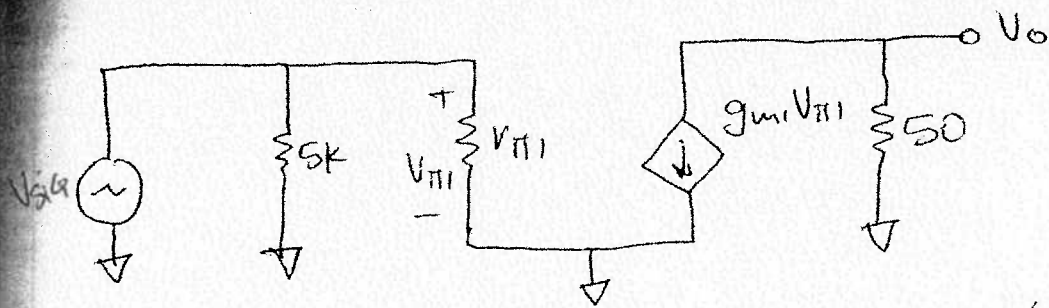

$$V_{\pi 1} = V_{sig}$$

$$\frac{V_{\pi 1}}{V_{sig}} \approx 1$$

$$V_o = -g_{m1} V_{\pi 1} (50)$$

$$\frac{V_o}{V_{\pi 1}} = -g_{m1} (50)$$

$$\frac{V_o}{V_{sig}} = -g_{m1} (50)$$

$$r_{\pi 1} = \frac{V_t}{I_B} = \frac{25m}{1.2m}$$

$$r_{\pi 1} = 20.83 \Omega$$

$$g_m = \frac{100}{r_{\pi 1}} \mu$$

$$g_m = 4.8$$

$$\frac{V_o}{V_{sig}} = -(4.8)(50)$$

$$\boxed{\frac{V_o}{V_{sig}} = -240 \frac{V}{V}}$$

with $V_{sig} = 2 + \sin(\omega t)$ then

$$V_o = -240 (\sin(\omega t))$$

$$V_{total} = 0 - 240 \sin(\omega t)$$

The maximum voltage supplied is $6V$ so there is no way to have an output greater than that. Therefore, the output will clip.

Not linear

ECE 2280 Midterm #3

Name _____

Scores:
Prob 1 _____ of a possible 35p

Prob 2 _____ of a possible 40p

Prob 3 _____ of a possible 15p

Prob 4 _____ of a possible 5p

Prob 5 _____ of a possible 5p

Total _____ of a possible 100