


DC Review

1. Assume Active
2. Label $V_{BE} = 0.7$
3. Take a loop through base & emitter.
4. 1 eq. with 1 unknown (I_E OR I_B)
5. Use $I_C = \alpha I_E = \beta I_B$ $\left[\alpha = \frac{\beta}{\beta + 1} \right]$
6. Then you can get all voltages
7. Check active cond. \Rightarrow npn $V_C \geq V_B$
pnp $V_C \leq V_B$

Small-signal equivalent circuit models

Same concept as that of the MOSFET.

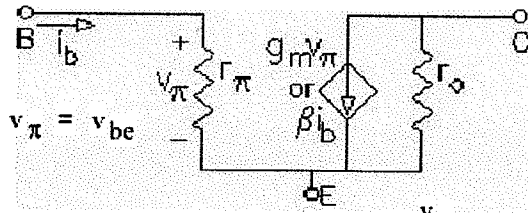- **Hybrid- π** model is used for the BJT:




$$r_{\pi} = (\beta + 1) \cdot r_e \quad i_b = \frac{v_{\pi}}{r_{\pi}}$$

$$\beta \cdot i_b = \beta \cdot \frac{v_{\pi}}{r_{\pi}} = \beta \cdot \frac{v_{\pi}}{(\beta + 1) \cdot r_e}$$

$$g_m = \frac{\beta}{(\beta + 1) \cdot r_e} = \frac{\alpha}{r_e} \approx \frac{1}{r_e} = \text{transconductance}$$


- T-model – uses r_e instead of r_{π}

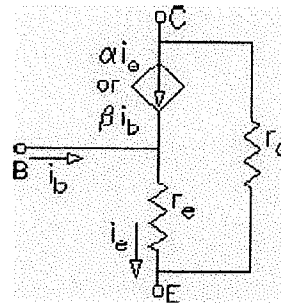

This is equivalent to Hybrid- π :
 $r_e (1 + \beta) = r_{\pi}$

Early Voltage

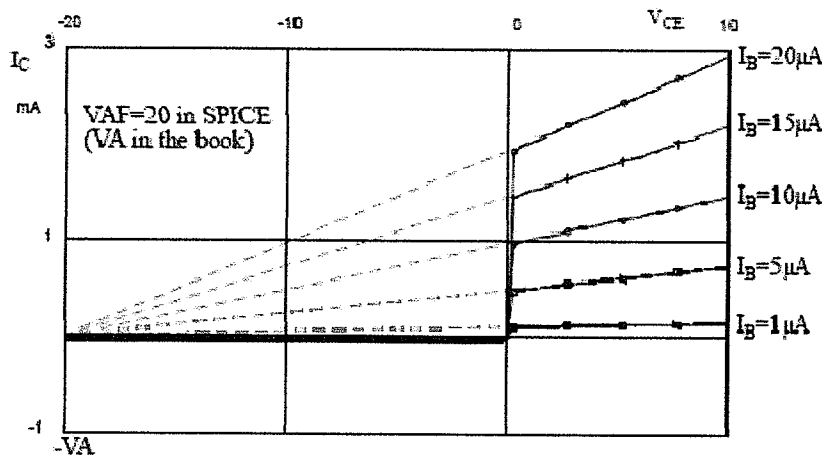- The I_C vs. V_{CE} curves in the active region have a finite slope to them due to this i_c dependence on V_{CB}
- *Early* showed that these slopes all converge to one negative voltage point



The actual equation:

$$i_c = I_s e^{\frac{v_{be}}{V_T}} \left(1 + \frac{v_{ce}}{V_A} \right)$$

This means that the output resistance between the collector and emitter is not infinite!

Method for analyzing transistor amplifier circuits:


- 1). Determine dc operating point, specifically I_C
(Set ac sources to 0!!)
Note: Use method for analyzing BJT circuits at DC
- 2). Calculate small-signal parameters: g_m , r_π , and/or r_e
- 3). Set dc sources to 0
- 4). Replace the transistor with one of the equivalent small-signal models
- 5). Analyze the circuit as usual \rightarrow linear circuit analysis

Example

Circuit:

$\beta = 100$, $V_{BB} = 3V$, $R_C = 3k$
 $R_B = 100k$, $V_{CC} = 10V$

Find the voltage gain, v_o/v_i

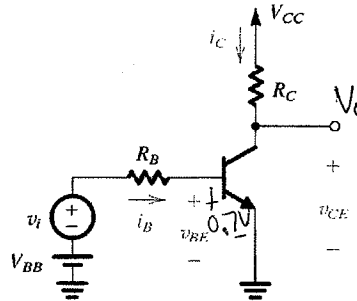

1). **DC analysis:** set v_i to 0 Assume $V_{BE} = 0.7V$ Assume active

Redraw circuit with just dc part:

$$+3 - I_B(100k) - 0.7 = 0$$

$$I_B = \frac{2.3}{100k} = 0.023mA$$


$$I_C = \beta I_B = 2.3mA$$

$$V_C = V_{CC} - I_C R_C = 10V - 2.3mA(3k)$$

$$V_C = 3.1V \Rightarrow V_C \geq V_B$$

$$V_B = 0.7V$$

\therefore **ACTIVE**

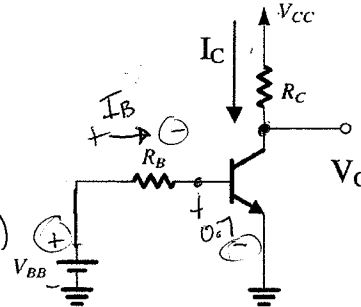

bias pt. $\Rightarrow I_C = 2.3mA$

2). Calculate small-signal parameters:


$$g_m = \frac{I_C}{V_T} = \frac{2.3}{25} = 92mA/V$$

$$r_e = \frac{V_T}{I_E} = \frac{25}{(2.3/0.99)} = 10.8\Omega$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{92} = 1.09k\Omega = \frac{V_T}{I_B}$$

3). And 4). Set dc sources to 0 and replace transistor with equivalent model \swarrow AC \rightarrow NOT DC!

Model:

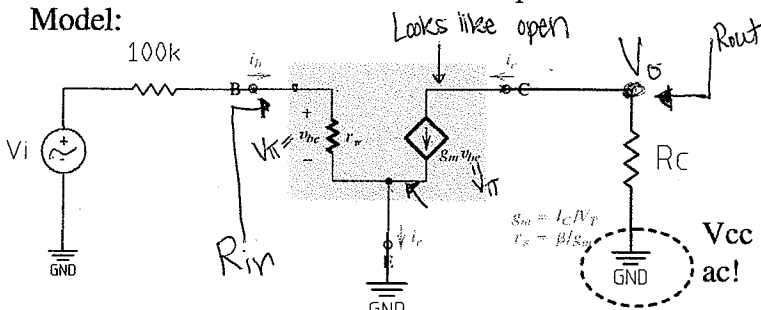

$$V_o = -g_m v_{be} R_C$$

$$v_{be} = \frac{v_i (r_\pi)}{r_\pi + 100k}$$

5). Find requested gain: $v_o/v_i = [\frac{v_c}{v_i}]$

$$R_{in} = r_\pi$$

$$R_{out} = R_C$$

$$\frac{V_o}{V_i} = -g_m \frac{r_\pi}{r_\pi + 100k} \cdot R_C = -92mA/V \cdot \frac{1.09k}{101.9k} \cdot 3k$$

$$\frac{V_o}{V_i} = -3.04 \frac{V}{V}$$

BJT basic amplifier:


DC:

$$I_C = I_s e^{V_{BE}/V_T}$$

$$I_E = \frac{I_C}{\alpha}$$

$$I_B = \frac{I_C}{\beta}$$

$$V_C = V_{CE} = V_{CC} - I_C R_C$$

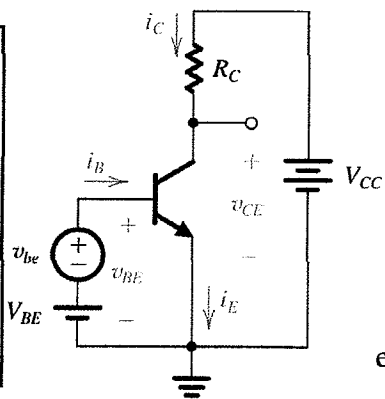

Total (instantaneous -> DC and AC)

$$i_c = I_s e^{(V_{BE} + v_{be})/V_T}$$

DC + AC

$$I_c + i_c = I_s e^{V_{BE}/V_T} e^{v_{be}/V_T}$$

$$= I_c e^{v_{be}/V_T} = I_c \left(1 + \frac{v_{be}}{V_T} \right) = I_c + \frac{I_c}{V_T} v_{be}$$

expand by $e^x \approx 1 + x$ for $x \ll 1$ ($V_{be} \ll V_T$)


Look at signal component only:

$$i_c = \frac{I_c}{V_T} v_{be}$$

$$g_m = \frac{I_c}{V_T}$$

Transconductance

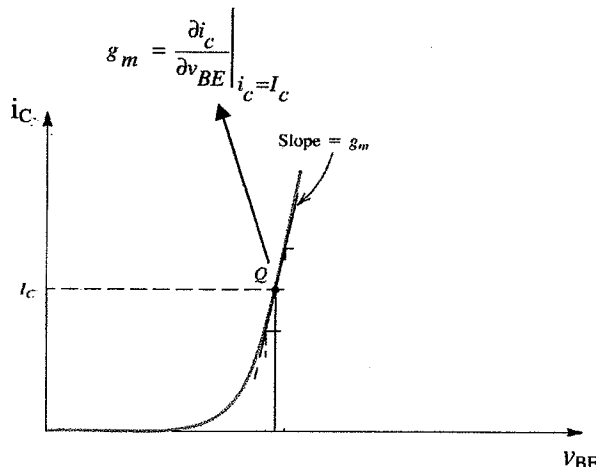Dynamic forward resistance of BE junction



Input Resistance:

- a. Input resistance looking in to base (in terms of
- ib) - from base to emitter

From above: $i_c = I_c + i_c = I_c + \frac{I_c}{V_T} v_{be}$

$$i_B = \frac{i_c}{\beta} = \frac{I_c}{\beta} + \frac{I_c}{\beta V_T} v_{be}$$

$$i_B = I_B + i_b$$

$$(AC) i_b = \frac{I_c}{\beta V_T} v_{be} = \frac{I_B}{V_T} v_{be} \rightarrow \frac{V}{R}$$

$$r_\pi = \frac{V_T}{I_B}$$

if β large ($\alpha \approx 1$): good approximation is $r_e \approx \frac{1}{g_m}$


$$r_\pi = (\beta + 1) r_e$$

Summary of ac parameters:

thermal at room T $\approx 25mV$

$g_m = \frac{I_c}{V_T}$ <p><i>DC</i></p> $r_\pi = \frac{V_T}{I_B} = \frac{\beta}{g_m}$ <p><i>thermal</i></p> $r_o \approx \frac{V_A}{I_c}$ <p><i>DC</i></p> $r_e = \frac{V_T}{I_E}$ <p><i>DC</i></p>	$i_c = g_m v_{be}$ $\frac{v_c}{v_{be}} = -g_m R_C$
--	--

Resistance Reflection rule

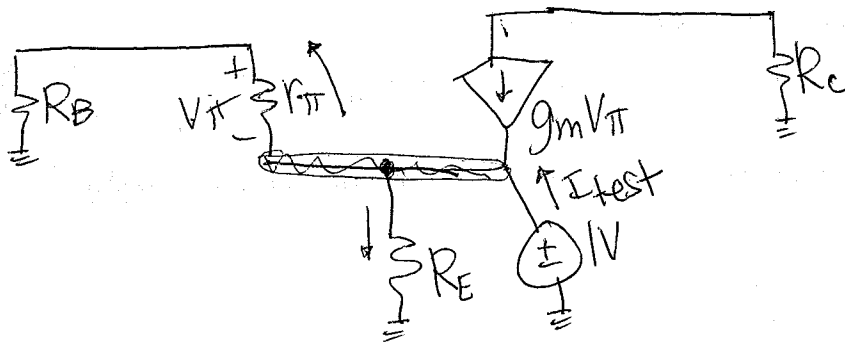

$$R_{th} = \frac{1}{I_{test}}$$

$$-I_{test} + \frac{1}{R_E} - g_m V_{\pi} + \frac{1}{r_{\pi} + R_B} = 0$$


$$V_{\pi} = -\frac{1}{(r_{\pi} + R_B)} \cdot r_{\pi}$$

$$I_{test} = \frac{1}{R_E} + \frac{\beta}{r_{\pi}} \left(\frac{+r_{\pi}}{r_{\pi} + R_B} \right) + \frac{1}{r_{\pi} + R_B} = 0$$

$$I_{test} = \frac{1}{R_E} + (\beta + 1) \left[\frac{1}{r_{\pi} + R_B} \right]$$

$$R_{th} = \frac{1}{I_{test}} = \frac{1}{\frac{1}{R_E} + \frac{(\beta + 1)}{r_{\pi} + R_B}} = R_E \parallel \frac{(r_{\pi} + R_B)}{(\beta + 1)}$$

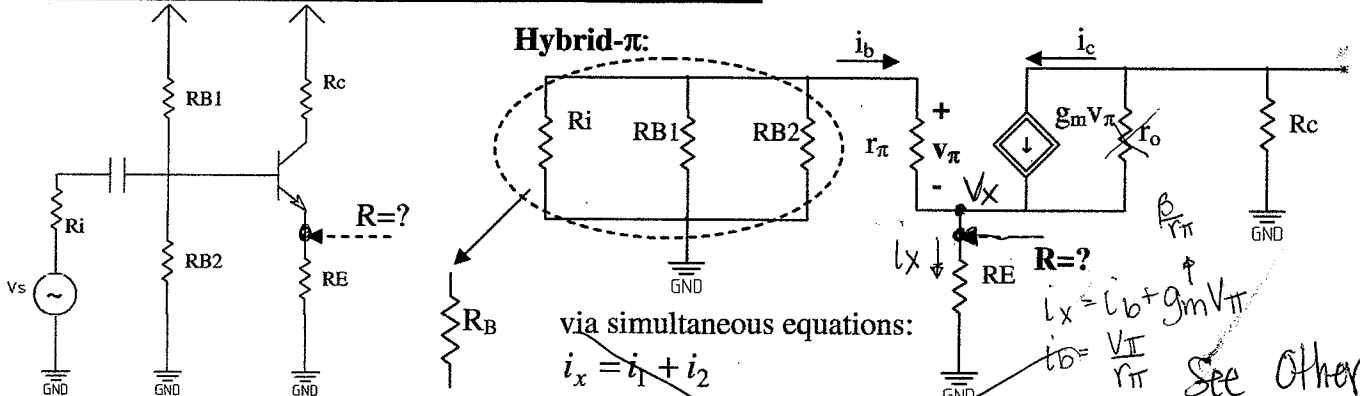Resistance-Reflection Rule Between Base and Emitter:



1. Eliminate VCCS
2. Scale all resistors with i_b through Thevenin by $\frac{1}{(\beta+1)}$ and

via simultaneous equations:

$$i_x = i_1 + i_2$$


$$i_1 = \frac{v_x}{R_E}, \quad i_2 = -i_e = -(i_b + i_c) = -i_b(\beta + 1)$$

$$v_\pi = i_b r_\pi, \quad i_c = g_m v_\pi$$

etc.


$$R_x = R_E \parallel \frac{r_\pi + R_B}{(\beta + 1)} \parallel (r_o + R_c) \approx R_E \parallel (r_e + \frac{R_B}{(\beta + 1)})$$

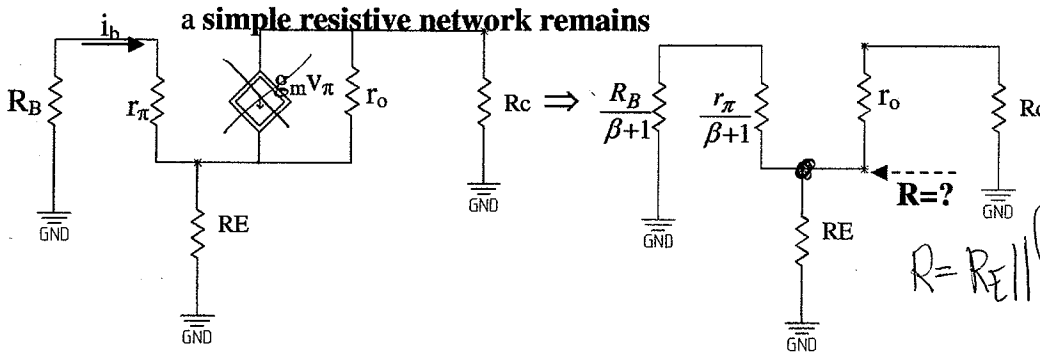$i_x = i_b + g_m v_\pi$
 $i_b = \frac{v_x}{r_\pi}$
 See other page
 $i_x = \frac{1}{r_\pi} (v_\pi + \beta v_\pi)$
 $i_x = \frac{v_\pi}{r_\pi} (1 + \beta)$




$$R = R_E \parallel \left(\frac{r_\pi + R_B}{\beta + 1} \right) \parallel (r_o + R_c)$$

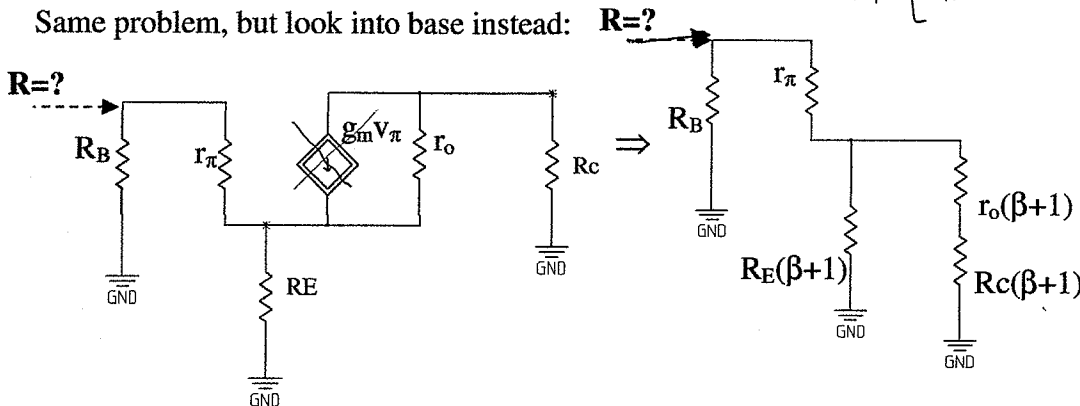Same problem, but look into base instead:



$$R = R_B \parallel \left[r_\pi + R_E(\beta + 1) \parallel (r_o + R_c)(\beta + 1) \right]$$

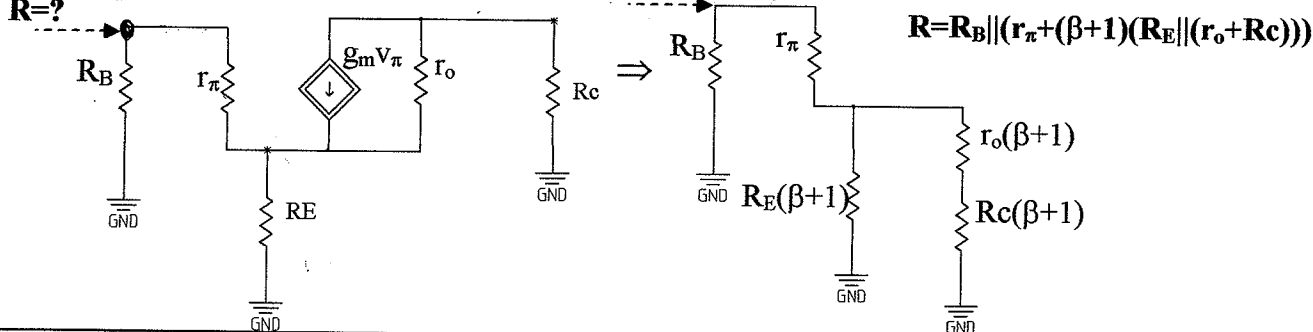Same problem, but look into base instead: $R=?$



Summary of Resistance-Reflection Rule between base and emitter:

Applies only when you want to reflect a resistor from emitter to base or base to emitter circuit

Review of rule:

1). Temporarily remove dependent source βi_b or $g_m v_{be}$

2). When looking into base: Replace resistors on emitter side with " R " $\times (\beta + 1)$ or " R " $/ (\beta + 1)$ or

When looking into emitter: Replace resistors on base side with " R " $/ (\beta + 1)$ or " R " $\times (\beta + 1)$

3). Treat circuit as a resistive network and find equivalent resistance

This works because $i_b = \frac{i_e}{\beta + 1}$

In a nutshell: To reflect a resistor from:

E \rightarrow B multiply by $(\beta + 1)$



B \rightarrow E divide by $(\beta + 1)$

Things to keep in mind:

- Rule does NOT work for impedance looking into collector – it is a reflection rule between base and emitter
- It works because $i_b = \frac{i_e}{\beta + 1}$ which is a relationship between the base and emitter current!
- Finding R_{in} or $R_{out} \rightarrow$ this is just finding Thevenin equivalent resistance, R_{Th}
Possible methods now that you can use:
1). Using the resistance Reflection Rule
2). Using Thevenin equivalent methods – use these to double check homework, but on exam will not likely have time
- R_{in} or R_{out} is always between a node and ground – follow all paths to ground from that node
- Applying the Reflection Rule is like turning off dependent sources and multiplying resistances by $(\beta + 1)$ or dividing resistance by $(\beta + 1)$ and treating circuit as just a resistive network \rightarrow Note that this only works because the dependent source is being accounted for through the $(\beta + 1)$ factor!

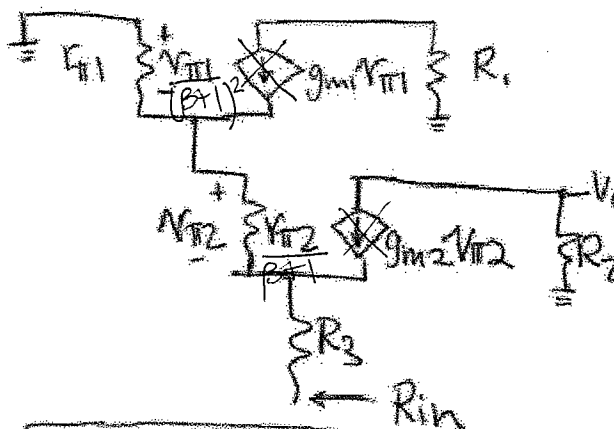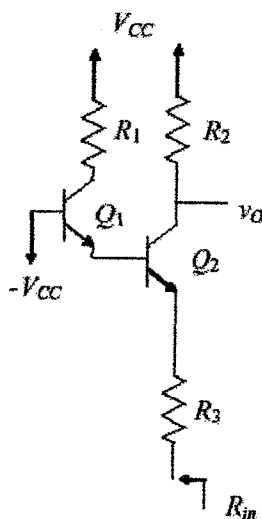
Example: Assume the transistors below have a finite β and an infinite Early voltage.

- Write an expression for the input resistance R_{in} in the circuit shown below. Your expression should include *only* real resistances (R_1, R_2, R_3 , or a subset of these) and possibly $\beta, r_{\pi 1}$ or $r_{\pi 2}$, and r_{e2} or r_{e1} . (Assume both transistors have the same β .) Circle your answer. *Hint: Use Resistance-Reflection rule*



$$R_{in} = R_3 + \frac{r_{\pi 2}}{\beta + 1} + \frac{r_{\pi 1}}{(\beta + 1)^2}$$

Common-Base

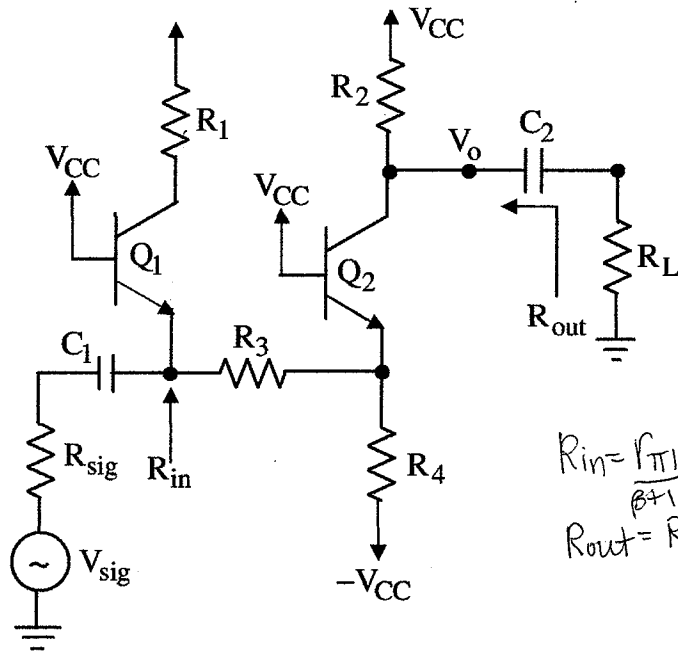


$C_1 = 10 \text{ pF}, C_2 = 10 \text{ nF}, \beta = 100$

Ignore r_o

$$R_{in} = \frac{r_{\pi 1}}{\beta + 1} \parallel \left[R_3 + R_4 \parallel \frac{r_{\pi 2}}{\beta + 1} \right]$$



$$R_{out} = R_2$$

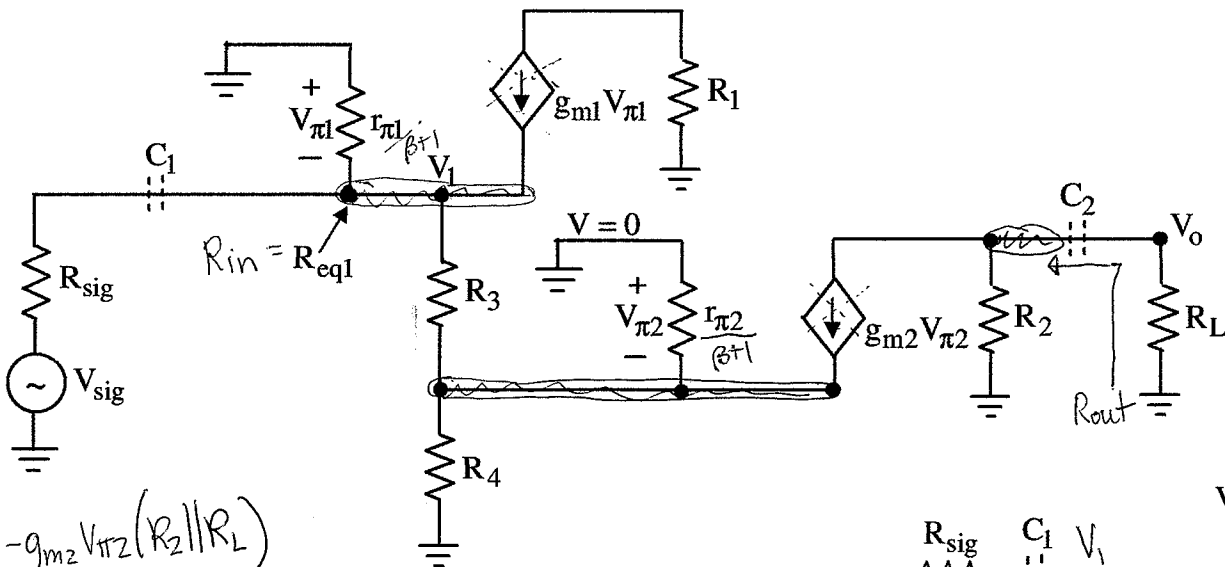


$$V_o = -g_{m2} V_{\pi 2} (R_2 \parallel R_L)$$

$$V_{\pi 2} = \frac{-V_1 (R_4 \parallel \frac{r_{\pi 2}}{\beta + 1})}{(R_4 \parallel \frac{r_{\pi 2}}{\beta + 1}) + R_3}$$
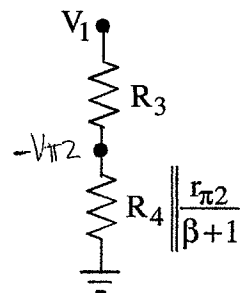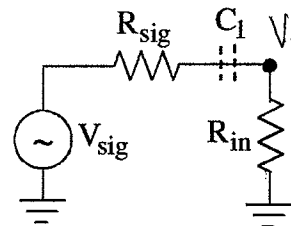
$$V_1 = \frac{V_{sig} (R_{in})}{R_{in} + R_{sig}}$$



Common-Base

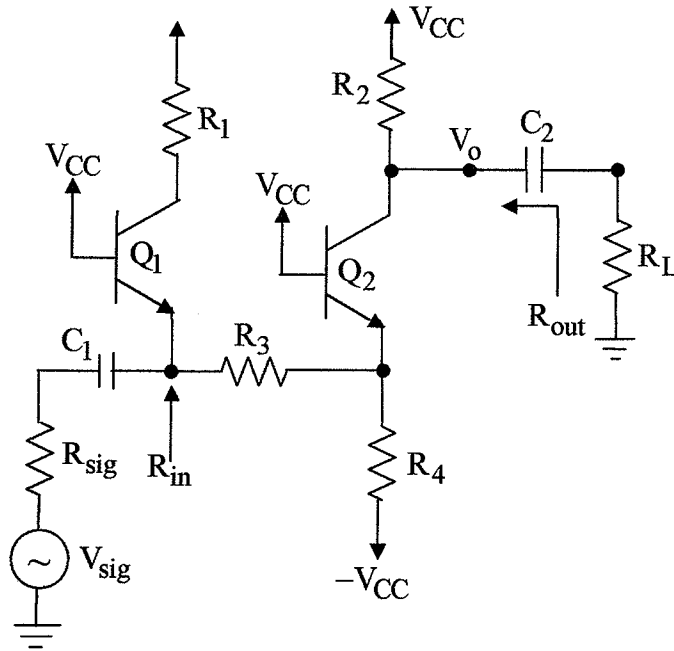


$C_1 = 10 \text{ pF}, C_2 = 10 \text{ nF}, \beta = 100$

Ignore r_o

$$R_{out} = R_2$$

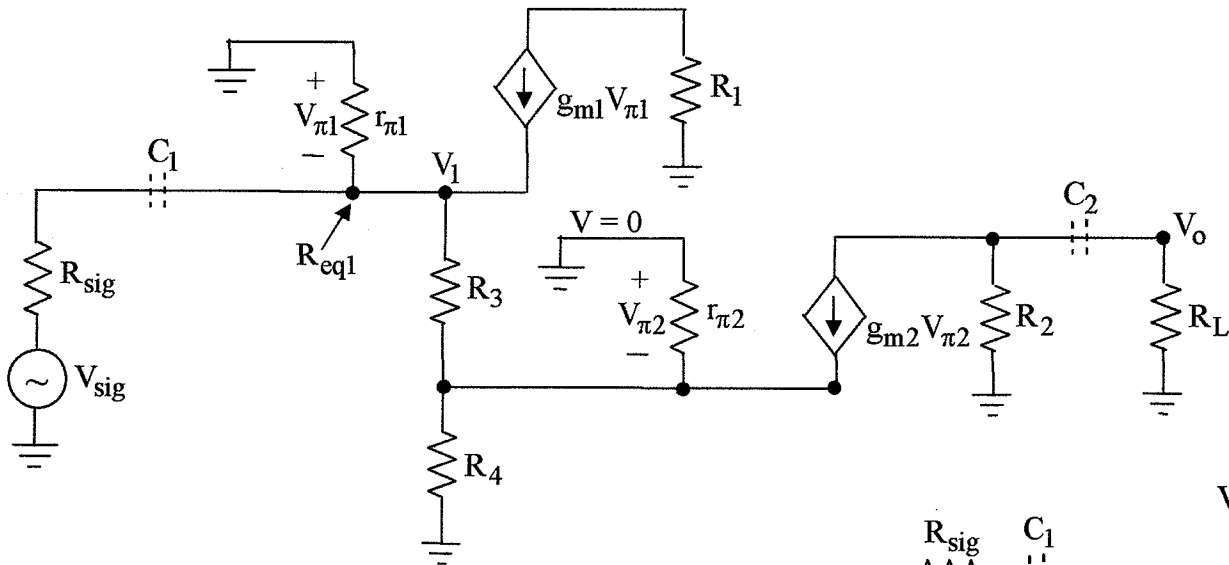
$$R_{in} = \frac{r_{\pi 1}}{\beta + 1} \parallel \left(R_3 + R_4 \parallel \frac{r_{\pi 2}}{\beta + 1} \right)$$



$$V_o = -g_{m2} V_{\pi 2} (R_2 \parallel R_L)$$



$$V_{\pi 2} = \frac{-V_1 \left(R_4 \parallel \frac{r_{\pi 2}}{\beta + 1} \right)}{\left(R_4 \parallel \frac{r_{\pi 2}}{\beta + 1} \right) + R_3}$$
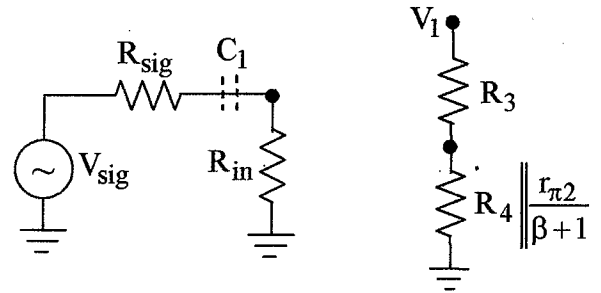
$$V_1 = \frac{V_{sig} (R_{in})}{R_{in} + R_{sig}}$$




$$\frac{V_o}{V_{sig}} = \frac{g_{m2} (R_2 \parallel R_L) \left(R_4 \parallel \frac{r_{\pi 2}}{\beta + 1} \right) R_{in}}{\left[\left(R_4 \parallel \frac{r_{\pi 2}}{\beta + 1} \right) + R_3 \right] [R_{in} + R_{sig}]}$$

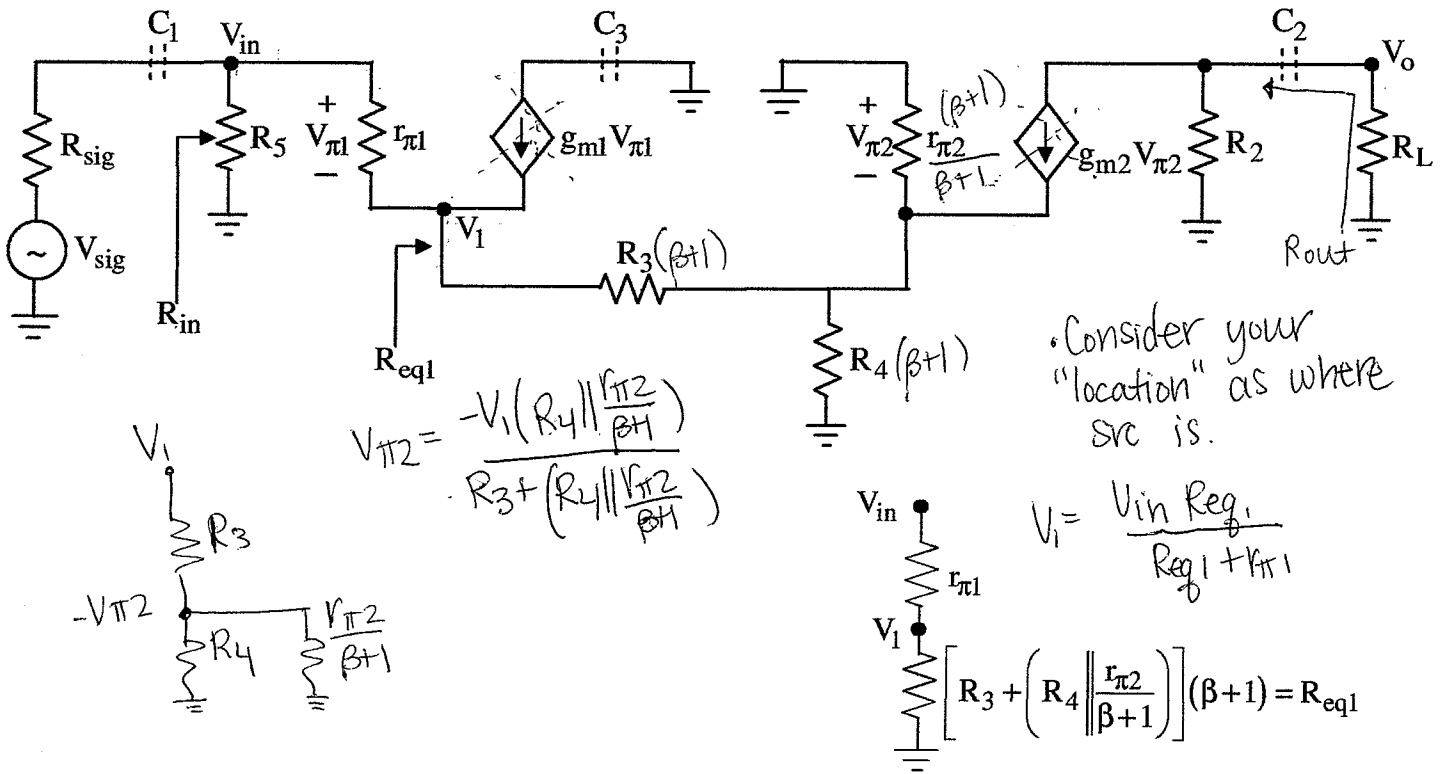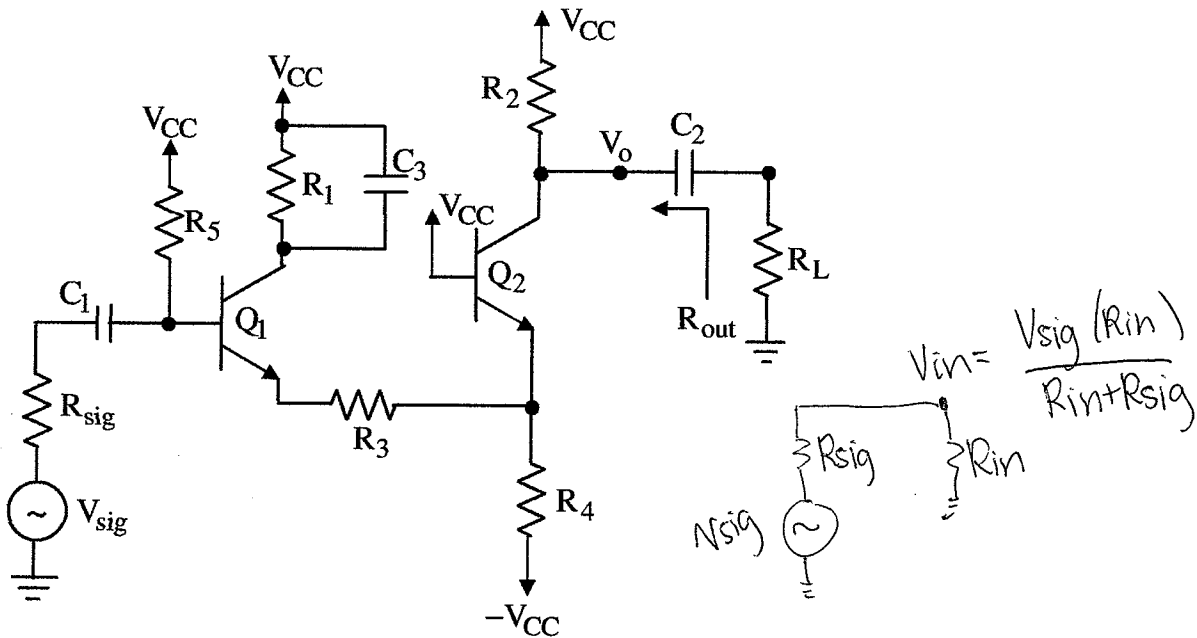2 Stage \Rightarrow Common Collector/Common Base




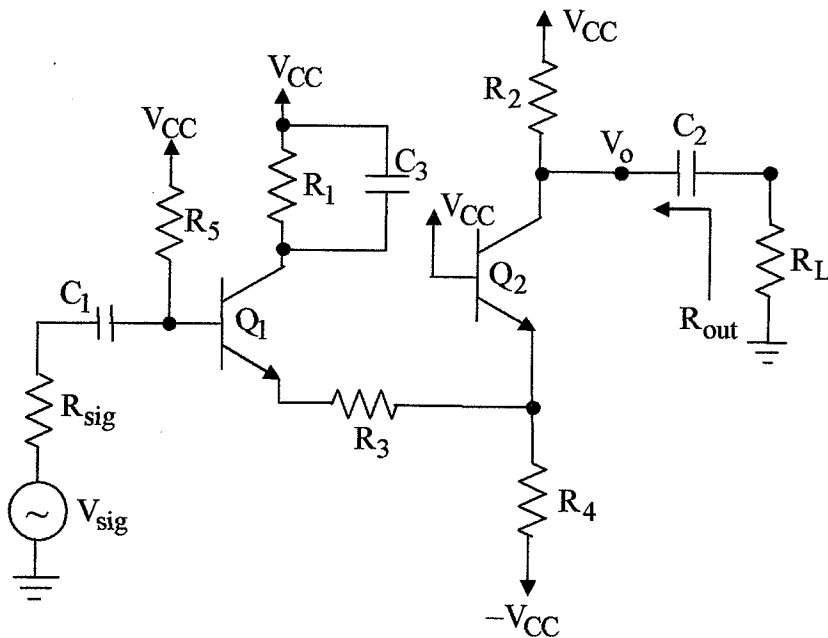2 Stage \Rightarrow Common Collector/Common Base




$$R_{out} = R_2$$

$$R_{in} = R_5 \left\| \left[r_{\pi 1} + \left(R_3 + R_4 \left\| \frac{r_{\pi 2}}{\beta + 1} \right) \right] (\beta + 1) \right] \right.$$

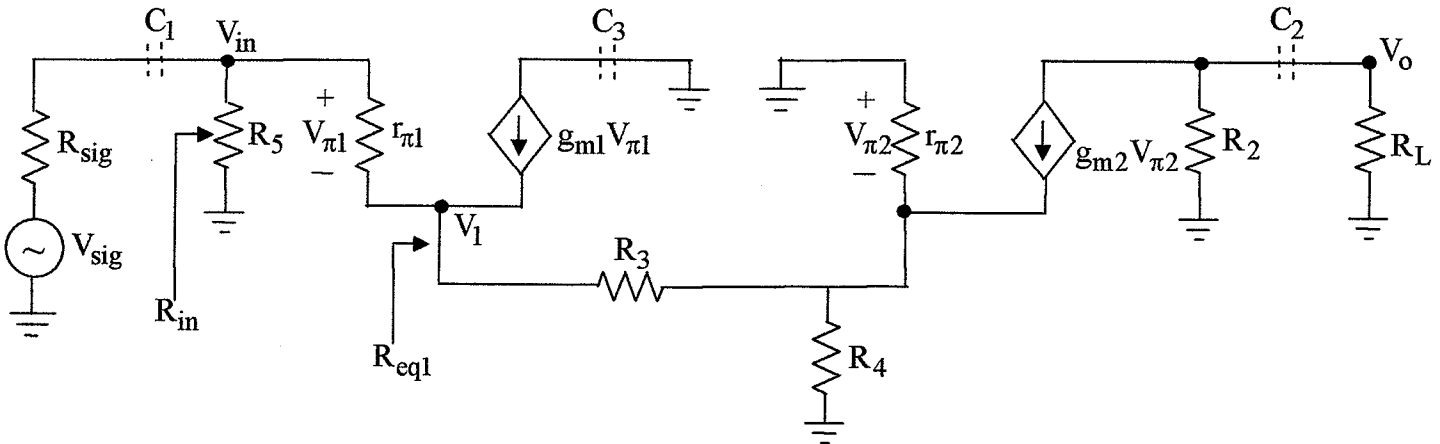

$$V_o = -g_{m2} V_{\pi 2} (R_2 \parallel R_L)$$

$$V_{\pi 2} = \frac{-V_1 \left(R_4 \left\| \frac{r_{\pi 2}}{\beta + 1} \right) \right)}{\left(R_4 \left\| \frac{r_{\pi 2}}{\beta + 1} \right) + R_3} \quad V_1 = \frac{V_{in} \cdot R_{eq1}}{R_{eq1} + r_{\pi 1}}$$

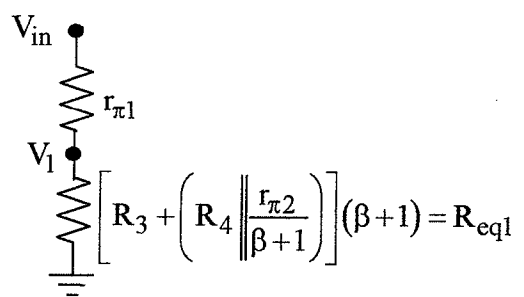

$$V_{in} = \frac{V_{sig} \cdot R_{in}}{R_{in} + R_{sig}}$$

$$\frac{V_o}{V_{sig}} = \frac{g_{m2} (R_2 \parallel R_L) \left(R_4 \left\| \frac{r_{\pi 2}}{\beta + 1} \right) R_{in} \cdot R_{eq1}}{\left[\left(R_4 \left\| \frac{r_{\pi 2}}{\beta + 1} \right) + R_3 \right] [R_{in} + R_{sig}] [R_{eq1} + r_{\pi 1}]}$$