



HW

#5. R in emitter should be 4k
instead of 40.

#10. Base R is 4Meg

Problem 3 – (15 points)

For the circuit shown below, draw the AC small-signal equivalent circuit (use hybrid- π or model T). Make sure that everything is labeled in terms of the transistor number. (e.g. g_{m1} , $v_{\pi 2}$, etc.). Include r_o for all transistors. $v_{sig} = 0.001 \sin(10t)$ AC. Assume that the capacitors act as a short.

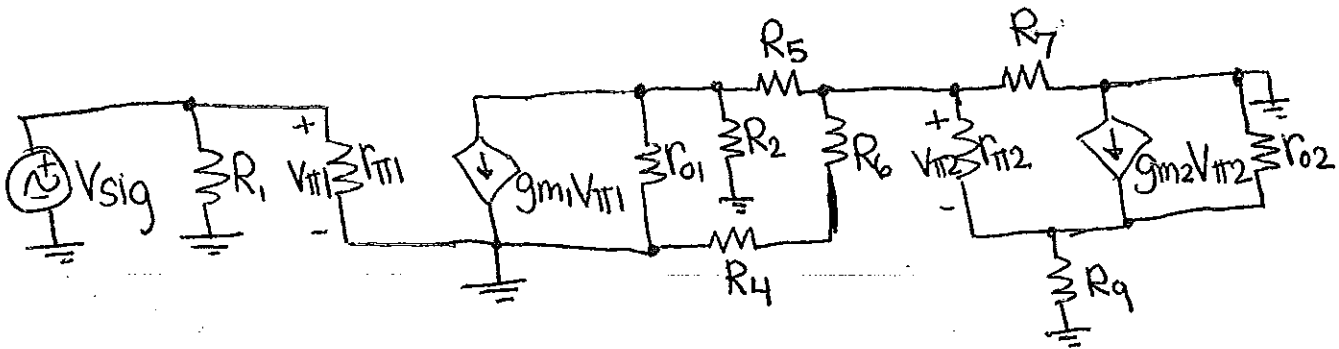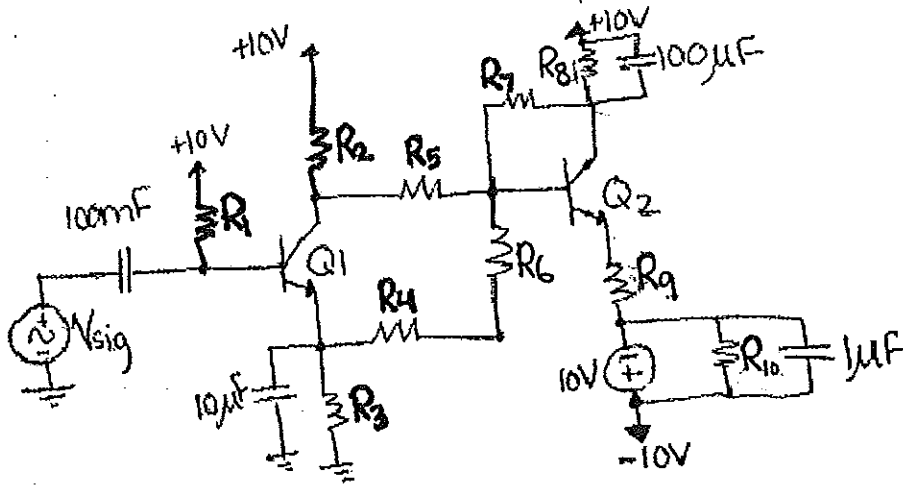

Problem 2


Use: ignore r_o and r_x , $|V_{BE}|=0.7$, $\beta=100$, $V_T=25\text{mV}$
 $V_I = 10 + 0.002\sin(20t)$

$r_{\pi 1}=1,200$ $g_{m2}=25\text{mA/V}$, and $I_{B2}=6.25\mu\text{A}$. Find $r_{\pi 2} = \frac{\beta}{g_{m2}} = \frac{100}{25\text{m}} = 4\text{k}$ OR $r_{\pi 2} = \frac{V_T}{I_B}$
 $r_{\pi 2} = \frac{25\text{m}}{6.25\mu}$

For the following hybrid- π equivalent circuit below, find the following values:

- (a) R_{in} (input resistance – ignore only the input source, V_{sig} and include all resistors at the base)
 (b) R_{out} (output resistance – include all resistors at the collector {no load is connected})

(c) midband gain, $\frac{V_o}{V_{sig}}$

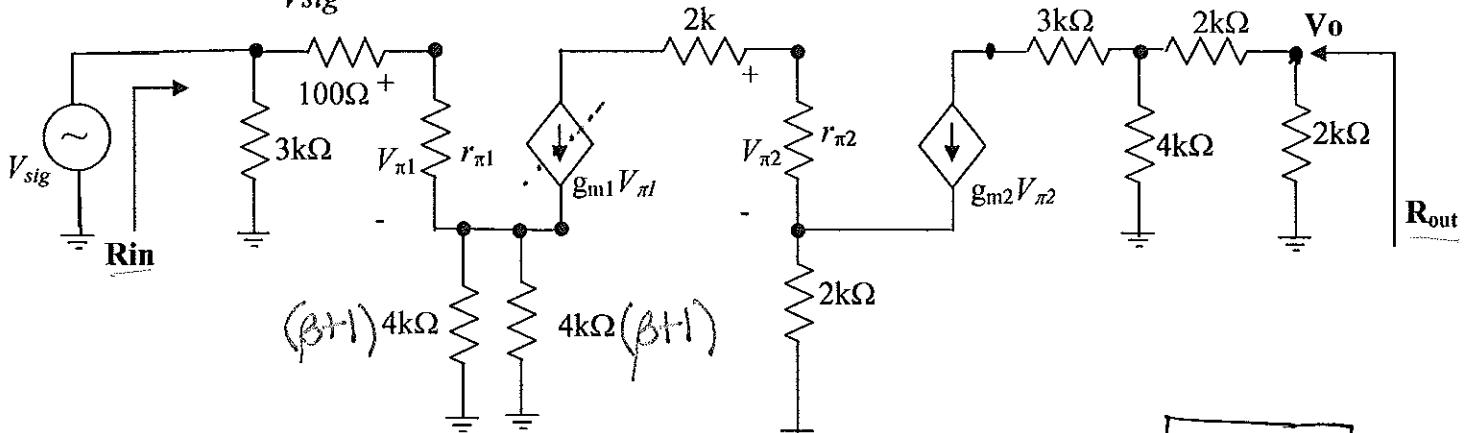

$$R_{in} = 3\text{k} \parallel [100 + r_{\pi 1} + 2\text{k}(\beta + 1)] = 3\text{k} \parallel 206\text{k} = \boxed{2.96\text{k}}$$

$$R_{out} = 2\text{k} \parallel 6\text{k} = \boxed{1.5\text{k}}$$


Problem 2 – (30 points)

Use: ignore r_o and r_x , $|V_{BE}|=0.7$, $\beta=100$, $V_T=25mV$
 $V_I = 10+0.002\sin(20t)$

$$r_{\pi 1}=1,200 \text{ } g_{m2}=25mA/V, \text{ and } I_{B2}=6.25\mu; r_{\pi 2} = \frac{\beta}{g_m} = \frac{100}{25m} = 4K \text{ or } r_{\pi 2} = \frac{V_T}{I_B} = \frac{25m}{6.25\mu}$$

For the following hybrid- π equivalent circuit below, find the following values:

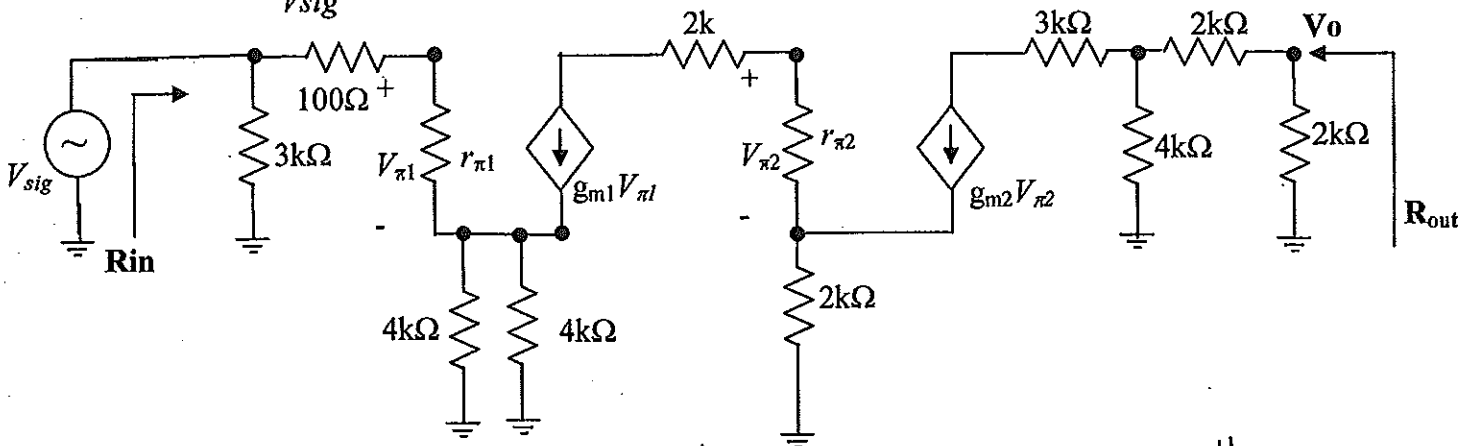- (a) R_{in} (input resistance –ignore only the input source, V_{sig} and include all resistors at the base)
- (b) R_{out} (output resistance-include all resistors at the collector{no load is connected})
- (c) midband gain, $\frac{V_o}{V_{sig}}$



$$R_{in} = 3k \parallel [100 + r_{\pi 1} + 2k(\beta+1)]$$

$$R_{in} = 3k \parallel 206k = \boxed{2.96k\Omega}$$

$$R_{out} = 2k \parallel (2k + 4k) = 2k \parallel 6k$$

$$R_{out} = \boxed{1.5k\Omega}$$

$$V_o = \left[\frac{-g_{m2} V_{\pi 2} (4k)}{4k + 4k} \right] \cdot 2k = -25m \cdot 1k V_{\pi 2} = -25V_{\pi 2}$$

$$V_{\pi 2} = -g_{m1} V_{\pi 1} \cdot r_{\pi 2} = -\frac{\beta}{83.3m} \cdot V_{\pi 1} \cdot 4k = -333V_{\pi 1}$$

$$V_{\pi 1} = \frac{V_{sig} (r_{\pi 1})}{100 + r_{\pi 1} + 2k(\beta+1)} = \frac{V_{sig} (1,200)}{203.3k} = 5.9m V_{sig}$$

$$\frac{V_o}{V_{sig}} = -25(-333)(5.9m) V_{sig} \approx \boxed{+49\%}$$