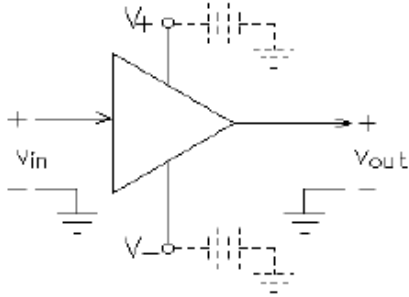


ECE2280 FUNDAMENTALS OF ELECTRICAL ENGINEERING

Amplifiers

Purpose: a weak signal is produced by a transducer (ex. Microphone) → too small for reliable processing, so amplify magnitude, i.e. make it larger


Amplifier → basic element of analog circuits



Transfer Characteristic:

Batteries or power supplies are rarely shown on the schematic.

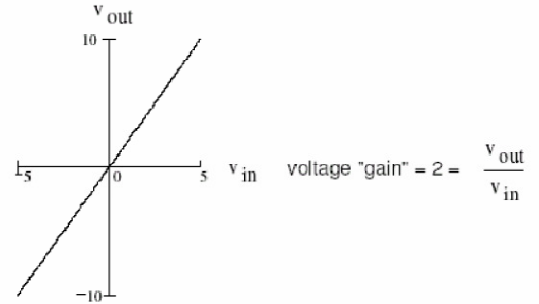Signal voltages are assumed to be referenced to ground even if the grounds aren't shown.





The output of all amplifiers are limited by the power supplies. Usually the limits are less than the power voltages.



Output limits, $L+ \leq V+$, $L- \geq V-$ (usually)

The output can't go beyond these limits no matter what the input does. If you want to avoid the "clipping" distortion in the output, you have to limit the input (make sure it's within an acceptable range).

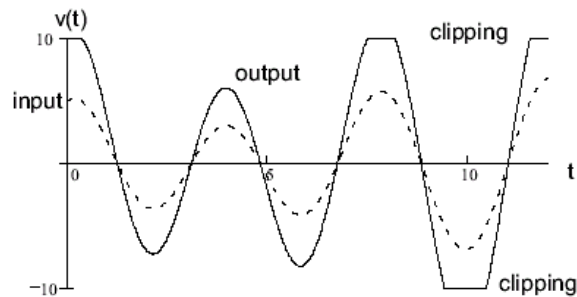
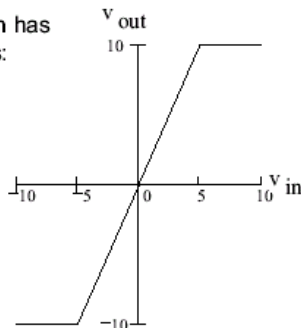
The transfer function has some non-linearities:



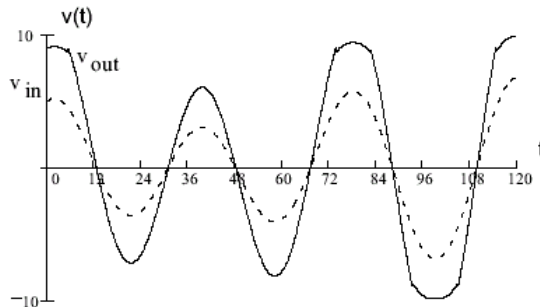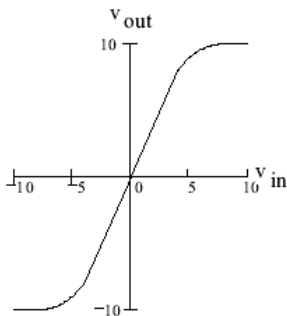Often the clipping levels are not so well defined



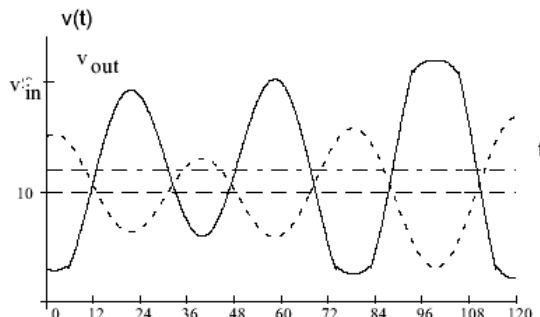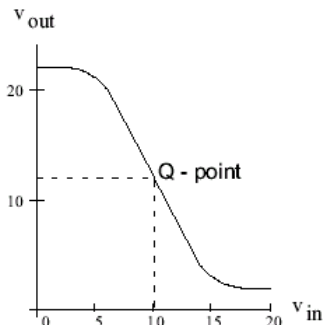Many of the transistor amplifier circuits that we'll see this semester will have DC offsets and will invert the signal.



The signal is considered the AC (changing) part of the waveform and the DC is called "bias" or the "quiescent - point" (Q - point) of the circuit.

ECE2280 FUNDAMENTALS OF ELECTRICAL ENGINEERING

Gain

$$\text{voltage gain} = A_v = \frac{v_{out}}{v_{in}}$$


lower-case letters refer to signal values

$$\text{DC: } \frac{V_{OUT}}{V_{IN}} \text{ is rarely gain}$$

The two below require a load, otherwise there's no output current, & no output power.

$$\text{current gain} = \frac{i_{out}}{i_{in}} = \frac{i_L}{i_{in}}$$
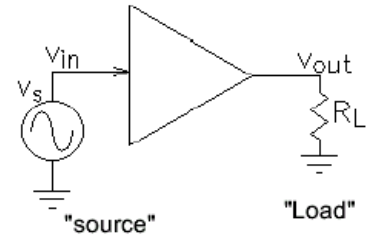
$$\text{power gain} = \frac{P_{out}}{P_{in}} = \frac{P_L}{P_{in}}$$




Gains are dimensionless numbers

Gain is just an idealized transfer function.

If only 1 input is shown, assume that other input is grounded.

Two stages

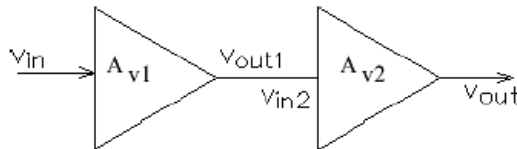


$$v_{out} = v_{in2} \cdot A_{v2} = v_{out1} \cdot A_{v2} = v_{in} \cdot A_{v1} \cdot A_{v2}$$

$$A_{vtotal} = A_{v1} \cdot A_{v2}$$

if $A_{v1} := 10$ & $A_{v2} := 4$ then $A_{vtotal} = A_{v1} \cdot A_{v2} = 40$ Same holds for multiple stages

Multiple Stages

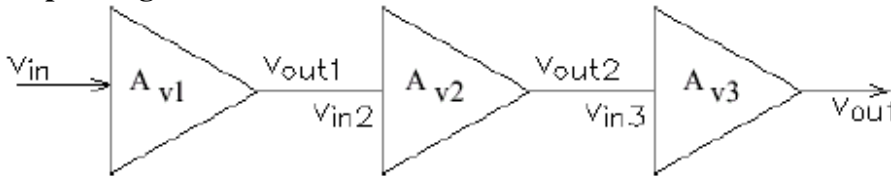

$$\text{Gain expressed as ratios: } A_{vtotal} = A_{v1} \cdot A_{v2} \cdot A_{v3}$$

$$\text{Gain expressed as dB: } A_{vtotal_dB} = A_{v1_dB} + A_{v2_dB} + A_{v3_dB}$$

If $A_{v1} := 20$, $A_{v2} := 8$ & $A_{v3} := 4$ then $A_{vtotal} = A_{v1} \cdot A_{v2} \cdot A_{v3} = 640$


$A_{v1_dB} := 20 \cdot \log(20)$ $A_{v2_dB} := 20 \cdot \log(8)$ $A_{v3_dB} := 20 \cdot \log(4)$ $20 \cdot \log(640) = 56.124 \cdot \text{dB}$

$A_{v1_dB} = 26.021 \cdot \text{dB}$ $A_{v2_dB} = 18.062 \cdot \text{dB}$ $A_{v3_dB} = 12.041 \cdot \text{dB}$

$A_{vtotal_dB} = A_{v1_dB} + A_{v2_dB} + A_{v3_dB} = 56.124 \cdot \text{dB}$

Amplifier Models

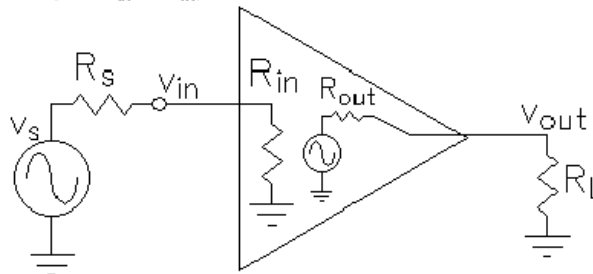Up until now we haven't worried about the currents into and out-of our amplifiers. In reality, any source, including the amplifier, will have a source resistance (R_s or Z_s for the source and R_{out} or Z_{out} for the amp). Also any amplifier will let a little signal current flow in (modeled by an R_{in} or Z_{in}).




At this point, the triangle symbol gets to be a little cumbersome and is dropped.

Procedure for solving ideal op-amp circuits:


1. If the noninverting terminal of the op-amp is at ground potential, then the inverting terminal is at virtual ground. Sum currents at this node, assuming zero current enters the op-amp itself.
2. If the noninverting terminal of the op-amp is not at ground potential, then the inverting terminal voltage is equal to that at the noninverting terminal. Sum currents at the inverting terminal node, assuming zero current enters the op-amp itself.
3. For the ideal op-amp circuit, the output voltage is determined from either step 1 or step 2 above and is independent of any load connected to the output terminal.

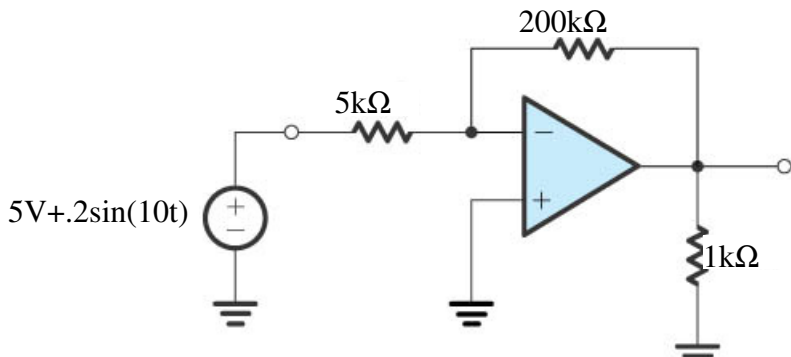Example 12:

For the circuit below, assume an ideal op-amp. Find the currents through all branches and the voltages at all nodes. Since the current supplied by the op amp is greater than the current drawn from the input signal source, where does the additional current come from?



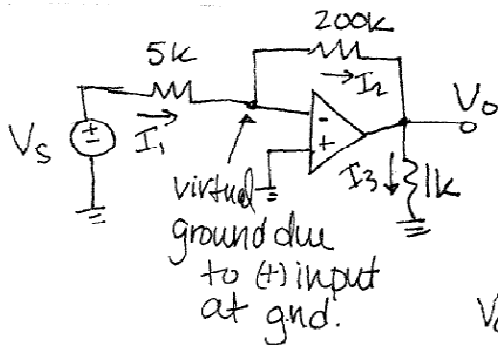The additional current is supplied from the supply power for the op amp.



$$I_1 = I_2$$

$$I_1 = \frac{V_s}{5k} = \frac{5V + 0.2\sin(10t)}{5k}$$

$$I_1 = I_2 = 1mA + 40\mu(\sin(10t))$$

$$V_o = -I_2 (200k)$$

$$\therefore V_o = -1m(200k) - 40\mu(200k)\sin(10t)$$


$$V_o = -200V - 8\sin(10t)$$

$$I_3 = \frac{V_o}{1k}$$

$$I_3 = -200mA - 8mA\sin(10t)$$

ECE2280 FUNDAMENTALS OF ELECTRICAL ENGINEERING


Example 13: Use the following circuit.

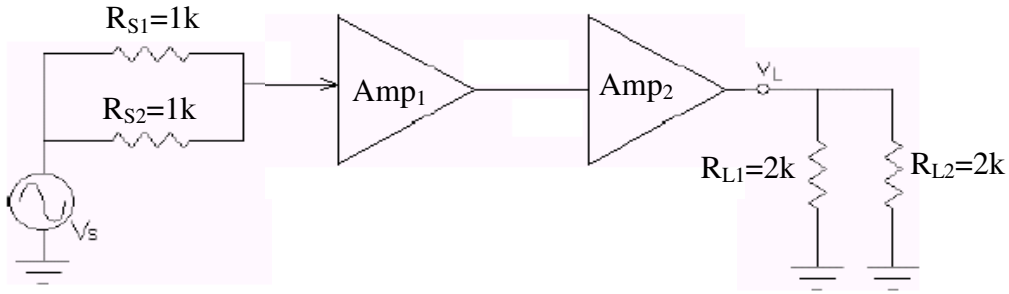

You are given: Amp₁ has an $A_{vo}=5$, $R_i=500$, $R_o=12k$

Amp₂ has an $A_{vo}=20$, $R_i=3k$, $R_o=4k$

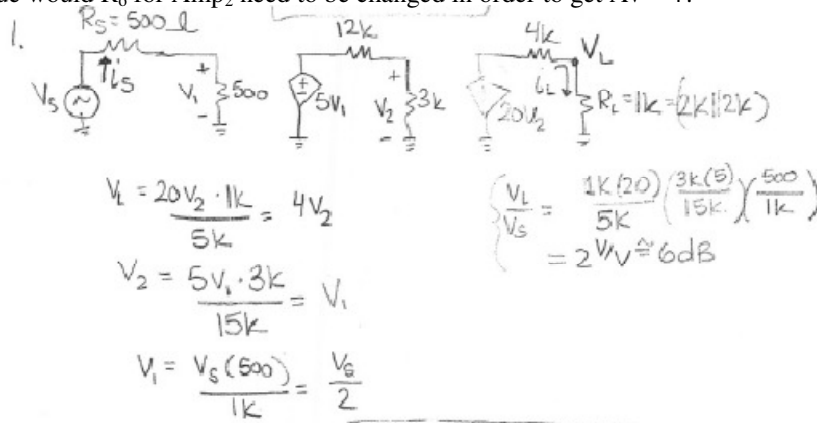- (a) Find $A_v = \frac{V_L}{V_s}$. Express your answer as a ratio in dB.
- (b) Evaluate the overall current gain $(\frac{i_L}{i_s})$. Express your answer as a ratio in dB form.
- (c) Evaluate the overall power gain $(\frac{P_L}{P_s})$. Express your answer as a ratio in dB form.
- (d) If $V_s=40mV_{pp}$. What is the output voltage (peak-to-peak) at V_L ?
- (e) What value would R_o for Amp₂ need to be changed in order to get $A_v = 4$?



(a) $V_L = 4(1)(\frac{V_s}{2}) \Rightarrow \frac{V_L}{V_s} = 2 \text{ } \approx 6 \text{ dB}$

Once one quantity is found, the others can be found by their relationship to V_2 and $V_s \Rightarrow$

(b) $\frac{V_L}{R_L} = i_L \Rightarrow V_L = (i_L \cdot R_L)$
 $V_s = i_s(1k)$
 $\frac{V_L}{V_s} = 2 = \frac{i_L(1k)}{i_s(1k)} \Rightarrow \frac{i_L}{i_s} = 2 \cdot \frac{A_v}{A} \approx 6 \text{ dB}$

(c) $P_L = i_L \cdot V_L$, $P_s = i_s \cdot V_s$
 $\frac{P_L}{P_s} = \frac{i_L \cdot V_L}{i_s \cdot V_s} = 2 \cdot 2 = 4 \text{ } \approx 12 \text{ dB}$

(d) $V_s = 40mV_{pp} \Rightarrow \frac{V_L}{V_s} = 2 \Rightarrow V_L = 2(40mV_{pp}) = 80mV_{pp}$

(e) $A_v = 4 = \frac{20 \cdot 1k}{R_o} (1)(1/2) \Rightarrow R_o = 1500 \Omega$

Operational Amplifier:

An operational amplifier is basically a complete high-gain voltage amplifier in a small package. Op-amps were originally developed to perform mathematical operations in analog computers, hence the odd name. With the proper external components, the operational amplifier can perform a wide variety of "operations" on the input voltage. It can multiply the input voltage by nearly any constant factor, positive or negative, it can add the input voltage to other input voltages, and it can integrate or differentiate the input voltage. The respective circuits are called amplifiers, summers, integrators, and differentiators. Op-amps are also used to make active frequency filters, current-to-voltage converters, voltage-to-current converters, current amplifiers, voltage comparators, etc. etc.. These little parts are so versatile, useful, handy, and cheap that they're kind of like electronic Lego blocks — although somewhat drably colored.

Op-amp characteristics

An op-amp has two inputs
 Amplifies the voltage *difference* between those two inputs.

$$v_o = G \cdot (v_a - v_b)$$

G = voltage gain of the op-amp

G is usually very big, $\geq 100,000$

The op-amp must be connected to external sources of power, V+ and V-.

The output voltage is limited by the power supply voltages.



$$V_- \leq v_o \leq V_+ \quad (\text{Usually even more limited than this})$$

$$\text{So: } V_- \leq G(v_a - v_b) \leq V_+$$

If the op amp is in its **active** region:



Since G is very big, $(v_a - v_b)$ must be very small, in fact the usual assumption is that
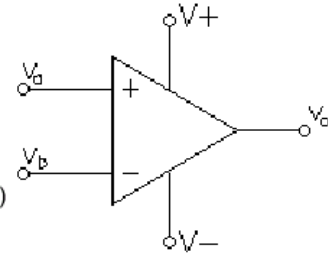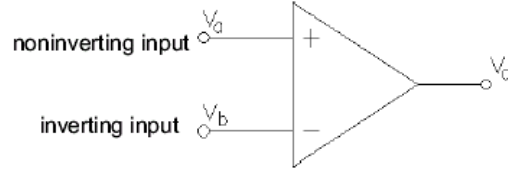
$$v_a \approx v_b \quad \text{Active region ONLY}$$



Clipping

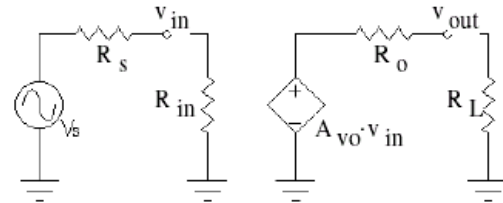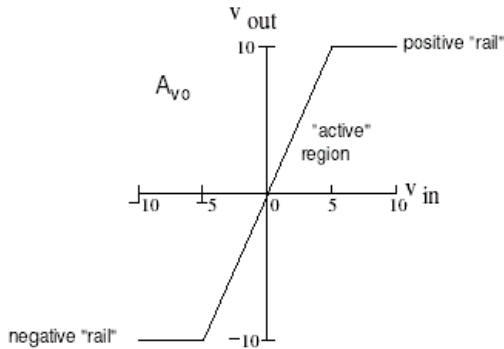All real amplifiers will clip the output signal if the input is too big.
 Only one part in the model can possibly account for the clipping-- a nonlinear A_{vo} .



Clipping level at the output (v_{out}) is less than that of A_{vo} ($\pm 10V$) because of the R_o, R_L voltage divider.


$$\text{The maximum allowable } v_{in} = \frac{10 \cdot V}{A_{vo}}$$

The maximum allowable v_s is greater than this because of the R_s, R_{in} voltage divider.

Op Amp Configurations:

1. Voltage Follower $\Rightarrow V_o = V_i$


Used as a current amplifier

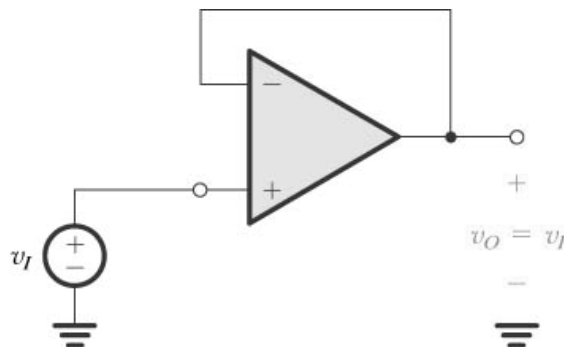

(a)

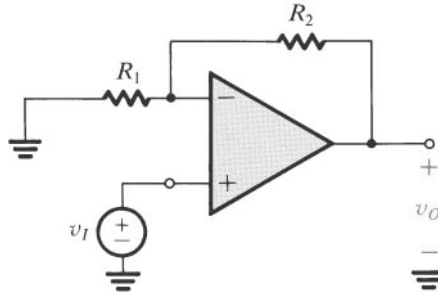
2. Noninverting amplifier =>

$$v_o = \left(\frac{R_2}{R_1} + 1 \right) \cdot v_i$$




3. Inverting amplifier =>

$$v_o = -\frac{R_2}{R_1} \cdot v_i$$

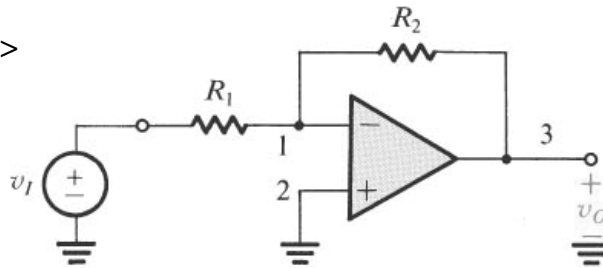

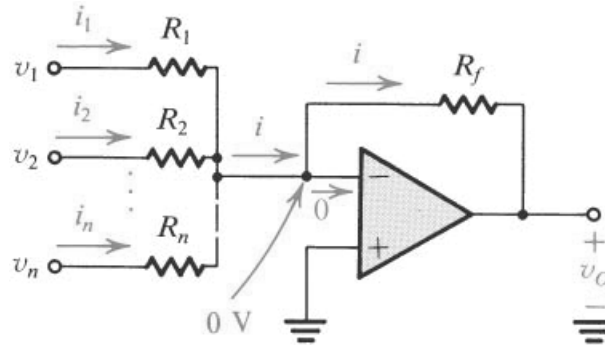
4. Summer =>

$$v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \frac{R_f}{R_3} v_3 + \dots + \frac{R_f}{R_n} v_n \right)$$



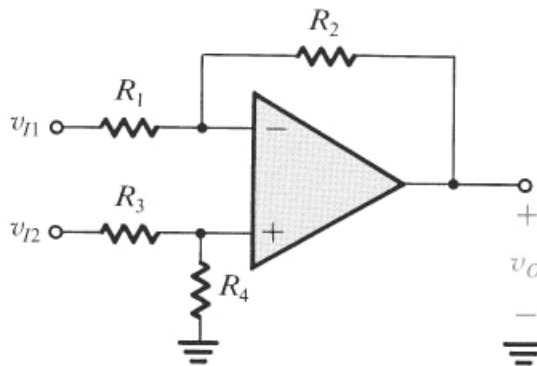5. Differential Amplifier =>

$$v_o = \left(\frac{R_2}{R_1} (v_2 - v_1) \right)$$



$$v_o = -\left(\frac{R_f}{R_1} v_1 + \frac{R_f}{R_2} v_2 + \dots + \frac{R_f}{R_n} v_n \right)$$

6. Instrumentation Amplifier =>

* This amplifier configuration can have large gain because of the two stages. Lower noise

$$v_o = \left(1 + \frac{2R_2}{R_1} \right) \left(\frac{R_4}{R_3} (v_2 - v_1) \right)$$

