

The material we have covered so far this semester is summarized (but NOT limited to) below:

Understand the basic operation of a MosFet:

- 3 regions of operation: cutoff, triode, saturation and know all current equations associated with each region and what their cross sections look like
- the I_D versus V_{DS} graph

Understand the bias point concept for linear amplification.

Be able to separate the DC and AC analysis for a circuit containing a MosFet.

Be able to analyze a circuit (with or without cap in it) containing a MosFet for DC operation.

Be able to draw a small-signal model of a MosFet circuit.

Be able to analyze a small-signal circuit to find overall gain, midband gain, input resistance, and output resistance.


Determine ω_L and ω_H or f_L and f_H .

$V_t=1V,$
 $k_n'(W/L)=2A/V^2,$
 $\lambda=0$

The 0.25A current source is not ideal and may have a voltage drop across it. All caps are large.

Solve the circuit for the DC values of:

- V_{D2}
- V_{s1}
- I_s

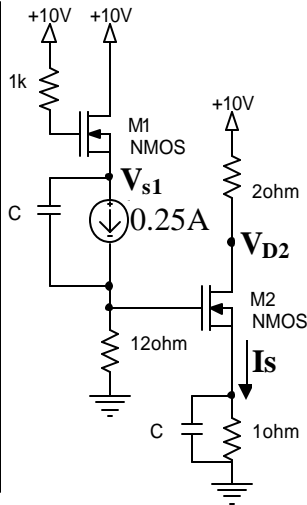


$V_t=1V, k_n'(W/L)=1mA/V^2,$ v_{sig} is an AC source
 Transistor 1 has DC values: $V_{GS}=5V, I_D=8mA$
 Transistor 2 has DC values: $V_{GS}=5V, I_D=8mA$
 Transistor 3 has DC values: $V_{GS}=3V, I_D=2mA$
 $\lambda=0$ (for all transistors)


Find (a) R_i (input resistance – ignore the 50ohm and V_{sig})

(b) R_{out} (output resistance)

(c) midband gain, $\frac{V_o}{V_{sig}}$

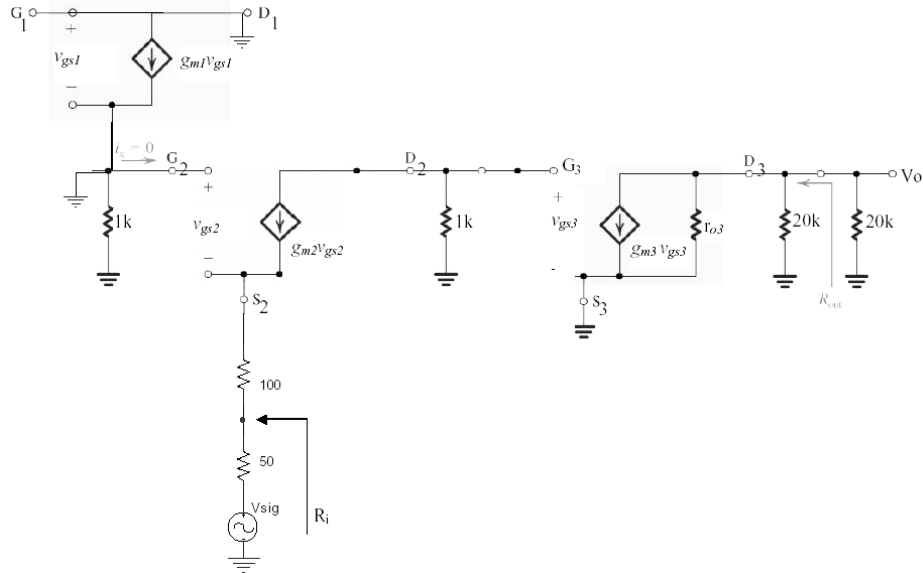

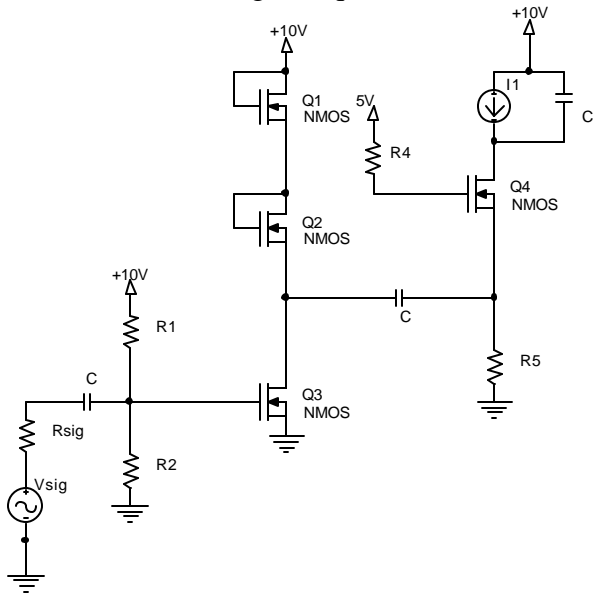Draw the small signal equivalent circuit.



at $V_t=1V$, $k_n'(W/L)=1mA/V^2$, and $\lambda=0$.

-) Draw the small-signal equivalent circuit
-) Analyze the circuit to find $A_v=V_o/V_{in}$, R_{in} and R_{out}
-) Find all low frequency pole values
-) Find ω_H given $C_{gs}=10pF$ and $C_{gd}=0.1pF$.

